THE FUTURE OF SHORTWAVE RADIO

SEPTEMBER 1996

Electronics NOW®

Build This Hobby Spectrum Analyzer For Under $100!

Removable Media Drives
Which one is right for you

Our Executive Decision Support System
takes the guesswork out of decision making

Using Lasers
in security applications

$3.50 U.S.
$3.95 CAN.

A GERNSBACK PUBLICATION

#BXNBQWF CAR-RT SORT ** C009
#LRI0424W098 2#751768 0AP25

MAR 97
JOE LORITZ 09EN
424 WILSON AVE
GREEN BAY WI 54303-4115

Before you get turned on by the front of a meter, make sure there's something behind it.

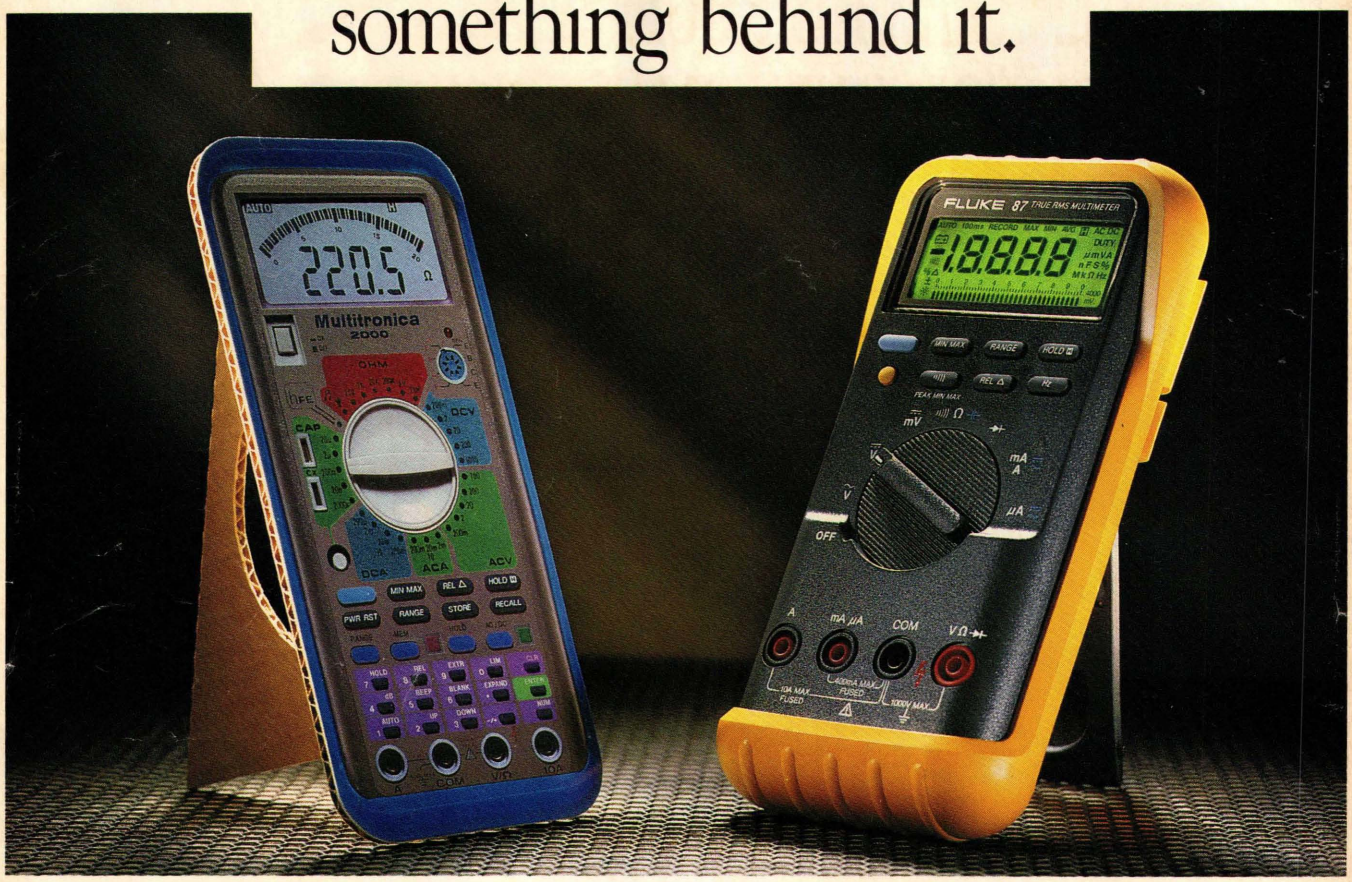

Fluke meters are designed for professionals who value function over frills.

There's nothing superficial about the Fluke family of versatile digital multimeters. Pick one up and you feel that it's a substantial tool. Designed to fit the application and the way you work. With features like our patented Touch Hold® function that freezes a reading on the display, and intelligently updates with each new reading. Automatically. Without requiring a third hand to push a button. Fluke meters attain stable, accurate readings in half the time of most imitations, making you more productive on the job.

Other meters are merely "designed to meet" certain guidelines; Fluke designs and builds a full line of meters that actually achieve UL, VDE and TÜV safety certification. Fluke's guarantee goes beyond manufacturing defects to include meter specifications for an entire year, so you can trust the readings. And Fluke backs you with toll-free customer assistance numbers, and a worldwide service organization. Discover why more professionals around the world say, "Hand me the Fluke." See your local distributor, or call **1-800-87-FLUKE** for a catalog and the name of the distributor nearest you.

SUPPLIER TO THE OLYMPIC GAMES
Atlanta 1996

Serious Tools for Serious Work

FLUKE®

© 1994 Fluke Corporation. P.O. Box 9090, M/S 250E, Everett, WA, USA 98206-9090. U.S. (206) 356-5400. Canada (905) 890-7600. Europe (31 40) 644200. Other Countries (206) 356-5500. All rights reserved. Ad No. 00567

CIRCLE 121 ON FREE INFORMATION CARD

Take this GIANT CIRCUIT LIBRARY FOR ONLY $14.95

when you join the

Electronics Engineers' Book Club®

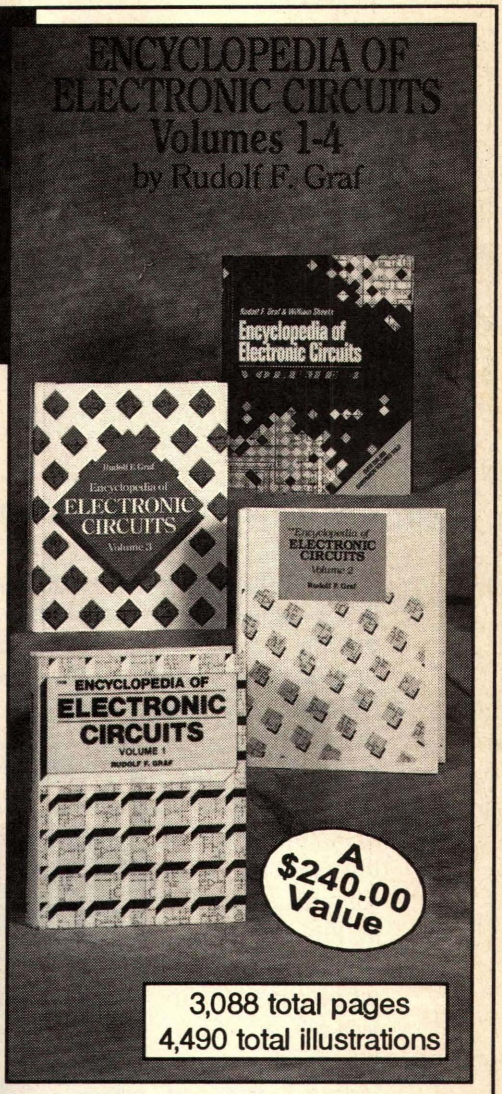

Hundreds of circuit ideas alphabetically arranged–from Alarm circuits to Zero crossing detector circuits!

Turn to this comprehensive circuit library for hundreds of project ideas...and concise pinout diagrams and schematics. In each volume you'll find more than 700 electronic and integrated circuits and 100+ circuit categories right at your fingertips to give you ideas you can use on the job or at your workbench.

As a member of the Electronics Engineers' Book Club®... you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off the regular publishers' prices. If you want the Main selection, do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. If you ever receive a book you don't want due to late delivery of the bulletin, you can return it at our expense. And you'll be eligible for FREE BOOKS through the Bonus Book Plan. Your only obligation is to purchase 3 more books during the next 2 years, after which you may cancel your membership at any time. Publishers' price shown. ©1996 EEBC

If coupon is missing, write to: **Electronics Engineers' Book Club,**
A Division of The McGraw-Hill Companies, P.O. Box 549, Blacklick, OH 43004-9918

MONEY-SAVING BONUS OFFER!

Take the *ENCYCLOPEDIA OF ELECTONIC CIRCUITS Vol. 5* at 50% off Publishers' price

Publisher's price-$60.00

ELECTRONICS ENGINEERS' BOOK CLUB®

A Division of The McGraw-Hill Companies,
P.O. Box 549, Blacklick, OH 43004-9918

YES! Rush me the *Encyclopedia of Electronic Circuits–Vols. 1-4* (5861488), billing me just $14.95 plus $12.00 shipping/handling & sales tax. Enroll me as a member of the **Electronics Engineers' Book Club** according to the terms outlined in this ad. If not satisfied, I may return the books within 10 days for a full refund and my membership will be cancelled. I agree to purchase just 3 more selections at regular Club prices during the next 2 years and may resign anytime thereafter.

☐ **BILL ME** (Bonus offer not available with this option.)

SPECIAL OFFER! Prepay your order by check, money order, or credit card and receive the *Encyclopedia of Electronic Circuits–Vol. 5* for $30.00 (That's 50% off the publisher's list price!)

☐ **50% MONEY-SAVING OPTION:** I also wish to order Vol. 5 (011076X) at 50% off the Publishers' price. I then need to purchase only 2 more books within the next 2 years. According to the terms outlined, my payment of $56.95, plus applicable sales tax is enclosed.

☐ Check or money order enclosed made payable to: The McGraw-Hill Companies

Please charge my: ☐ VISA ☐ MasterCard ☐ American Express ☐ Discover

Acct. No. _____ Exp. Date _____

Signature _____ Phone _____
(required on all orders)

Name _____

Address/Apt. # _____

City/State/Zip _____

Offer valid for new members only, subject to acceptance by EEBC. U.S. orders are shipped 4th Class Book Post. Canada must remit in U.S. funds drawn on U.S. banks. *Canadian orders are shipped International Book Post–add $16.00 shipping/handling. Applicants outside the U.S. and Canada will receive special ordering instructions. A shipping/handling charge & sales tax will be added to all orders.

RPIF 996

Electronics NOW

Vol. 67 No. 9

CONTENTS

SEPTEMBER 1996

ON THE COVER

29 BUILD THE HOBBY SPECTRUM ANALYZER

A spectrum analyzer is among the most useful pieces of test gear a radio hobbyist could own. For one thing, it allows the user to actually see the signals on a large portion of the spectrum at a glance. Unfortunately, its cost often puts it out of reach for many. That is, until now. This month, we show you a spectrum analyzer that can be built for less than $100! While not a lab-grade instrument, when mated with virtually any oscilloscope it will provide performance that will be more than adequate for most applications. *— Bob Kopski*

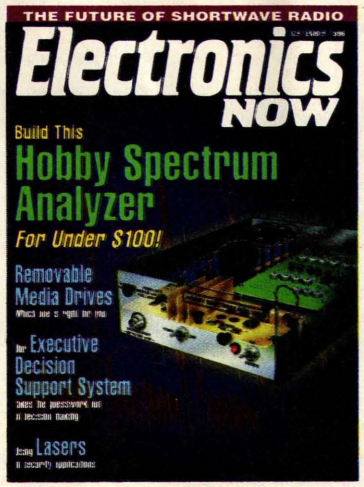

BUILD THIS

40 EXECUTIVE DECISION SUPPORT SYSTEM

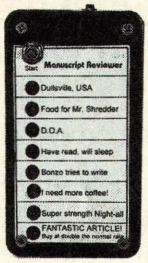

Use it just for fun, or to make your hard decisions just a little easier. *— James Edwards*

61 TONAL VOLTMETER

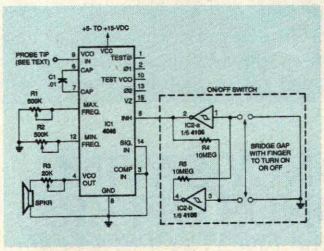

Put your ears to work for quick relative voltage checks. *— Mark O. Bender*

As a service to readers, ELECTRONICS NOW publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, ELECTRONICS NOW disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry in ELECTRONICS NOW may relate to or be covered by U.S. patents, ELECTRONICS NOW disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

ELECTRONICS NOW, (ISSN 1067-9294) September 1996. Published monthly by Gernsback Publications, Inc., 500 Bi-County Boulevard, Farmingdale, NY 11735-3931. Second-Class Postage paid at Farmingdale, NY and additional mailing offices. Canada Post IPM Agreement No. 334103, authorized at Mississauga, Canada. One-year subscription rate U.S.A. and possessions $19.97, Canada $27.79 (includes G.S.T. Canadian Goods and Services Tax, Registration No. R125166280), all other countries $28.97. All subscription orders payable in U.S.A. funds only, via international postal money order or check drawn on a U.S.A. bank. Single copies $3.50. © 1996 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

POSTMASTER: Please send address changes to ELECTRONICS NOW, Subscription Dept., Box 55115, Boulder, CO 80321-5115.

A stamped self-address envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

SEPTEMBER 1996

TECHNOLOGY

44 ALL ABOUT REMOVABLE MEDIA
Need a quick way to back-up your hard drive or to transport data from place to place? One of these technologies might be right for you. — *TJ Byers*

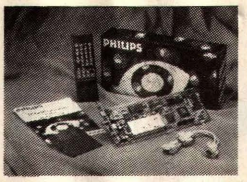

56 THE COMING REVOLUTION IN SHORTWAVE BROADCASTING
Learn how governments are cooperating to make the shortwave bands less cluttered for all. — *Stanley Leinwoll*

DEPARTMENTS

8 VIDEO NEWS
What's new in this fast-changing industry. — *Dave Lachenbruch*

16 EQUIPMENT REPORTS
Philips Professional Solutions PC TV-tuner card.

62 SERVICING
A glossary of DSO terms. — *Dick LaJeunesse*

65 TECH MUSINGS
Earth field magnetometry, flux-gate sensors and ICs, and more. — *Don Lancaster*

74 COMPUTER CONNECTIONS
Java and the "dumb little box". — *Jeff Holtzman*

77 LASER EXPERIMENTS
Lasers and security applications. — *Carl J. Bergquist*

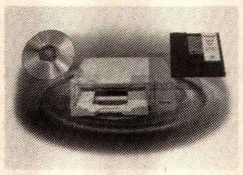

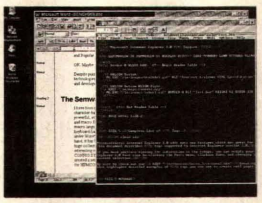

AND MORE

4 EDITORIAL
6 WHAT'S NEWS
10 Q&A
14 LETTERS
20 NEW PRODUCTS
24 NEW LITERATURE
136 ADVERTISING SALES OFFICE
136 ADVERTISING INDEX

Electronics NOW®

Hugo Gernsback (1884-1967) founder

LARRY STECKLER, EHF, CET, Editor-in-chief and publisher

EDITORIAL DEPARTMENT
CARL LARON, editor
JULIAN S. MARTIN, associate editor
TERI SCADUTO, assistant editor
JEFFREY K. HOLTZMAN computer editor
LARRY KLEIN, audio editor
DAVID LACHENBRUCH contributing editor
DON LANCASTER contributing editor
MICHAEL A. COVINGTON, N4TMI contributing editor
EVELYN ROSE, editorial assistant

ART DEPARTMENT
ANDRE DUZANT, art director
RUSSELL C. TRUELSON, illustrator

PRODUCTION DEPARTMENT
RUBY M. YEE, production director
KATHRYN R. CAMPBELL production assistant
KEN COREN desktop production

CIRCULATION DEPARTMENT
JACQUELINE P. CHEESEBORO circulation director
THERESA LOMBARDO circulation assistant

REPRINT DEPARTMENT
MICHELE TORRILLO reprint bookstore

Typography by Mates Graphics
Cover design by David Loewy

Electronics Now is indexed in *Applied Science & Technology Index*, and *Readers Guide to Periodical Literature, Academic Abstracts*, and *Magazine Article Summaries.*
Microfilm & Microfiche editions are available. Contact reprint bookstore for details.

Advertising Sales Offices listed on page 136.
Electronics Now Executive and Administrative Offices
1-516-293-3000.
Customer Service:
1-800-999-7139.
7:00 AM – 6:00 PM M-F MST

Audit Bureau of Circulations **Member**

EARN YOUR
B.S. DEGREE
IN
COMPUTERS
OR
ELECTRONICS

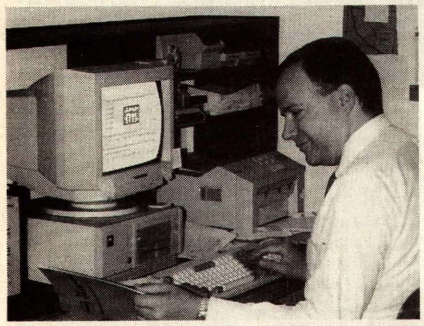

By Studying at Home

Grantham College of Engineering, now in our 46th year, is highly experienced in "distance education"—teaching by correspondence—through printed materials, computer materials, fax, modem, and phone.

No commuting to class. Study at your own pace, while continuing on your present job. Learn from easy-to-understand but complete and thorough lesson materials, with additional help from our instructors.

Grantham offers three separate distance-education programs, leading to the following accredited degrees;

(1) The B.S.E.T. with Major Emphasis in Electronics.

(2) The B.S.E.T. with Major Emphasis in Computers.

(3) The B.S.C.S. — the Bachelor of Science in Computer Science.

An important part of being prepared to *move up* is holding the right college degree, and the absolutely necessary part is knowing your field. Grantham can help you both ways—to learn more and to earn your degree in the process.

Write or phone for our free catalog. Toll free, 1-800-955-2527, or see mailing address below.

•

**Accredited by
the Accrediting Commission of the
Distance Education and
Training Council**

•

*GRANTHAM
College of Engineering*
Grantham College Road
Slidell, LA 70460

EDITORIAL

HELLO, AGAIN

Eagle-eyed readers might have noticed a few changes in the masthead for this month. First and foremost, Brian Fenton, the long-time editor of this magazine has left to pursue other interests. I have had the privilege of knowing Brian for many years, and his contributions to **Electronics Now**, and all of Gernsback Publications will be sorely missed. It is truly an honor to succeed him here.

For those not familiar with me, I have been Managing Editor and Editor for our sister publication, **Popular Electronics** since 1988. But prior to that (from 1980 to 1988) I had been Assistant Editor and Associate Editor for this magazine's predecessor, **Radio-Electronics**. While I really enjoyed my stint at **Popular Electronics**, it is great to be re-united with an old friend—and the magazine where I got my start.

Now that the introductions are out of the way, I am sure that there is one question that has occurred to most of you: How will this change affect me and **Electronics Now**? The answer is: That's up to you.

Electronics Now is at a bit of a crossroads, and there are some important decisions we need to make to keep serving you, our readers, in the best possible way. First of all, we have always been, and always will be, a technical magazine, but have we gotten too technical? Or, are we not technical enough? Would you prefer to see simpler projects? Or, would you prefer to see ones that are more complex?

What about computers? Do we spend enough space on computer-related articles and projects? Or should we spend less? And what do you think we should cover?

How about consumer electronics? Would you like to see expanded coverage—including, for instance, buyer's guides of consumer video and audio gear?

Or, would you prefer to see things stay pretty much as they are?

Drop us a note and tell us what you think. While we won't be able to respond to each of you individually, your thoughts are important to us, and we promise that each and every letter will be read and considered.

And while we are on the topic of change, there are a couple of things you should be made aware of. First, you may notice that some of the articles in this issue have a slightly different look to them. We are phasing in changes in type and style so that we can squeeze a little extra information into each article. The changes will be gradual and should be complete within a few months.

And last, but not least, I am pleased to announce the introduction of the Gernsback Web page. Readers have long asked when we will have a site on the World Wide Web. Well, the wait is over. Why the delay? We wanted to make sure that when we committed to the Internet, we did things right. The site will include things like current issue information, subscription information, an FTP site for recent story-related files, and more. The URL is http:\\www.gernsback.com\. It should be operational by the time you read this, so why not check it out today!

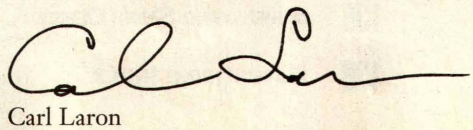

Carl Laron
Editor

CircuitMaker®

The Virtual Electronics Lab™

where you can launch today's electronics project
into tomorrow and beyond...

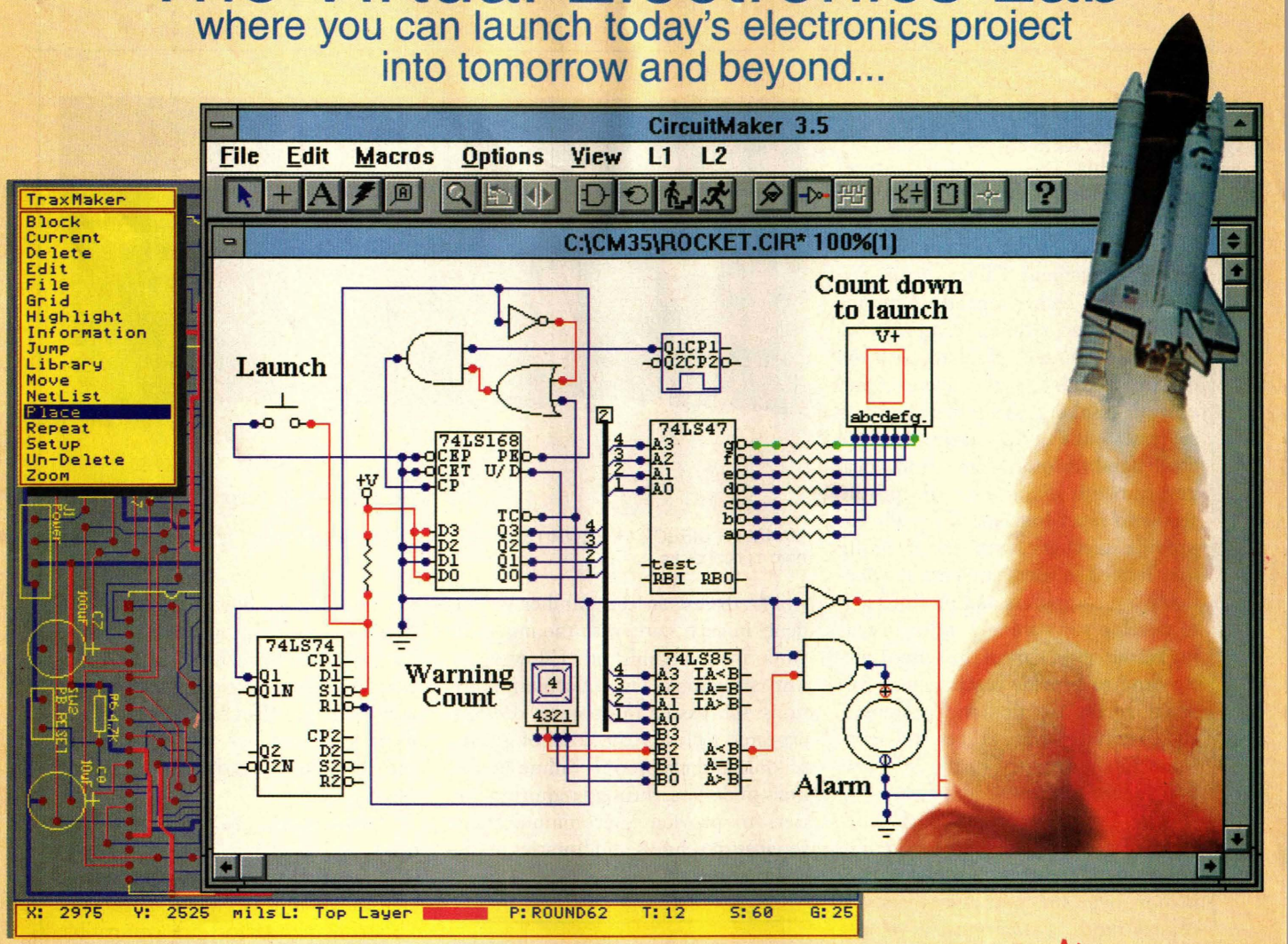

TraxMaker™

New Product

- DOS version only $299
- 30 day satisfaction guarantee
- user definable "Design Rules"
- imports CircuitMaker PCB netlist
- automatic or manual routing of tracks
- 8 layer, 32" x 32" maximum board size
- automatic or manual component placement

CircuitMaker®

New Windows 95/NT/3.1x Versions

- still only $299
- PCB netlist export
- includes 1500+ devices
- SPICE netlist import/export
- 30 day satisfaction guarantee
- professional schematic features
- digital, analog and mixed-mode simulation

Call now to order your complete circuit design system or request additional information:

800-419-4242

MicroCode Engineering
573 W. 1830 N. Suite 4
Orem, UT 84057 USA
Phone (801) 226-4470
FAX (801) 226-6532

FREE ON-LINE DEMO:
AOL; file search, CircuitMaker
CompuServe; GO MICROCODE
Internet; http://www.microcode.com

All trademarks are the property of their owners.

CIRCLE 128 ON FREE INFORMATION CARD

WHAT'S NEWS

A REVIEW OF THE LATEST HAPPENINGS IN ELECTRONICS

A PC in every class

Declaring, "We must make sure all of our children—every single one of them—has access to the education opportunities of the present and the future," President Clinton launched America's Technological Literacy Challenge, a national campaign to equip the country's children with the communication, math, science, and critical thinking skills required for success in the Information Age. He challenged federal, state, and local governments, along with the private sector to meet four specific goals: To provide teachers with the training they'll need to teach students to effectively use computers and the Internet; to develop software and online learning resources as part of the school curriculum; to provide teachers and students access to modern computers; and to connect every school and classroom in the country to the information superhighway.

The President proposed the creation of a $2-billion fund to catalyze government and private-sector participation over the next five years. To receive funds, a state must develop a strategy to ensure that *every* school meets those four goals. State strategies should include significant private-sector participation, at least matching the amount of federal support. Public progress reports are also required of each state.

Even if a state does not come up with a comprehensive strategy, communities can present local plans. And whether or not a state-wide plan exists, private companies and local communities can cooperate in a competition to receive part of the $50-million annual Innovation Challenge Fund.

The amount of funding per state will be based on the number of students in each state, with the money to come from slashing other, lower priority programs. The Telecommunications Act, passed in February 1996, is expected to lower the costs of getting schools and classrooms online by billions of dollars, through requiring carriers to provide telecommunications services to schools and libraries at discounted rates.

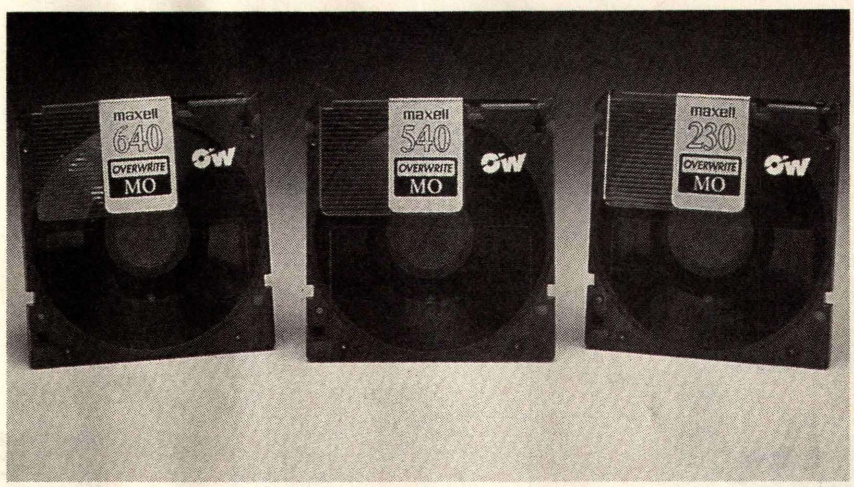

MAXELL'S DIRECT OVERWRITE DISKS double the rewrite speed of conventional magneto-optical disks.

Direct OverWrite magneto-optical disks

Using Light Intensity Modulated Direct OverWrite (LIM-DOW) technology, Maxell Corporation of America (Fair Lawn, NJ) has introduced the 3.5-inch magneto-optical (M-O) disks with rewrite speeds that are twice those of conventional M-O media.

Current technology requires an erase cycle before new data is written to the disk. The disk must rotate twice, once to erase and once more for writing. Direct OverWrite eliminates the erase cycle. New data is written directly over existing data, doubling the transfer rate. The disks also feature Mark-edge recording technology, which reduces the laser wavelength to form much smaller recording marks and provide much higher recording density.

Three models of Direct OverWrite disks are available. The RO-M640 (638 megabytes, 2048 bytes per sector) and the RO-M540 (534 megabytes, 512 bytes per sector) are compatible with ISO/IEC standard drives that have LIM-DOW function. The RO-M230 (320 megabytes, 512 bytes per sector) was created specially for the Fujitsu 17mm-height drive designed for notebook PCs.

Interactive application notes

Hewlett-Packard's Test and Measurement Organization (TMO) is now providing animation and interactive features to the application notes

continued on page 27

Radio distress calls answered daily.

You can rely on RadioShack parts to improve your station and help keep you on the air. Plus, we've got America's best-selling 2-meter HT, a value-packed 440MHz handheld, hot new mobile 2M rig, 2M mobile amplifier, and remote-sensing digital HF SWR meter. Now you can enjoy fast delivery of Ham gear from AEA™, Hy-Gain®, Glen Martin™ MobileAm™, Uniden® and Vectronics™, too. From replacement mic plugs and licensing software to packet TNCs, beam antennas and crank-up towers, see what's new for Hams today at RadioShack. We've got the products, the parts and the people to help you put it all together. For a store near you, call 1-800-THE-SHACK.

RadioShackSM
You've got questions. We've got answers.®

CIRCLE 78 ON FREE INFORMATION CARD

VIDEO NEWS

WHATS NEW IN THE FAST-CHANGING VIDEO INDUSTRY

BY DAVID LACHENBRUCH

Video game price war

The war between the three major video-game systems now includes prices as well as format and performance. The second annual Electronic Entertainment Expo, or E3, was supposed to serve as the launching pad for Nintendo's widely promoted (and oft-postponed) 64-bit N64 format. But Sony, whose PlayStation has been clobbering the competition, decided to take no chances and to rain on Nintendo's parade. Despite its best-selling status, Sony sent a thunderbolt into the game scene by reducing the price of its console by $100—to $199.

That put Sega into a strange position. Just six weeks after cutting the price of its Saturn game to $249 from $299, it was forced to chop off another $50 to equal the Sony tag. Nintendo, whose 64-bit game is priced at $249, cried foul and said that Sony's move was a sign of desperation and confirmation that N64 would "eat their lunch." Sony, of course, scoffed at that and claimed it has sold 5,000,000 PlayStation platforms worldwide, including 1,200,000 in the U.S. alone. Obviously, the money is in the software, and both Sony and Sega can afford to lose money on their consoles if they can sell large quantities of games. Sony says it will have 170 titles by year end, as opposed to N64's twelve.

Get ready for a big war of words (and TV commercials) among the video-game proponents. Sony and Nintendo each plan to spend more than $50 million to promote their platforms by year-end. Sega says that once consumers are in the stores and try out all three games, they will be convinced of Saturn's superiority, and that Saturn's lower software prices will give it an edge.

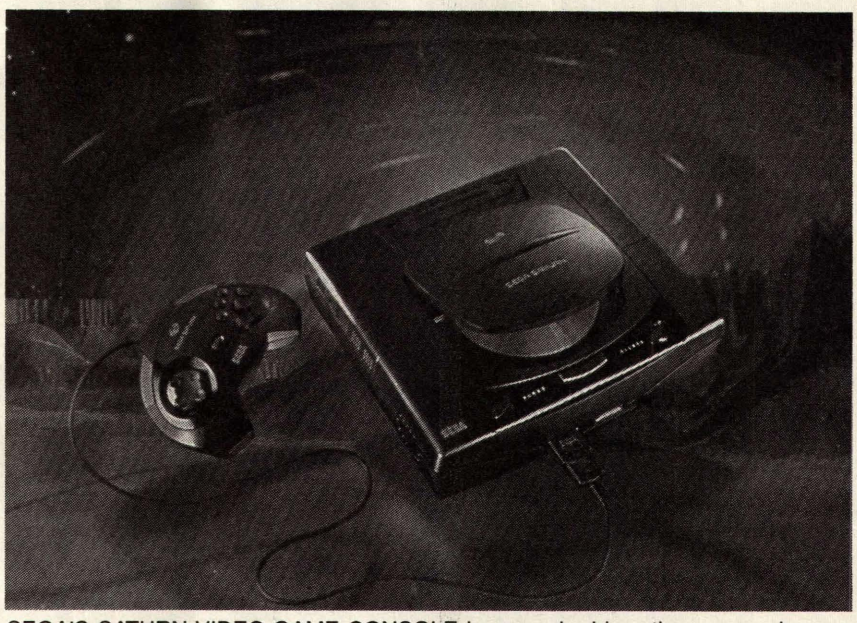

SEGA'S SATURN VIDEO-GAME CONSOLE is enmeshed in a three-way price war with Sony's PlayStation and Nintendo's N64.

Satellite prices plunge

Here's a tip if you're contemplating buying a Digital Satellite System (DSS) receiver: Shop around. You can spend as much as $800 on a receiver to get the multi-channel broadcasts, but if you're a good shopper, you might not have to put up more than $499—or even $399.

That is because the two main satellite programmers—DirecTV and United States Satellite Broadcasting (USSB)—are subsidizing retailers to sell their services. Some retailers are applying the subsidies to the price of the hardware. If you go DSS, you're going to have to subscribe to the program services anyway, so it might be a good idea to take advantage of the cuts in the price of the hardware. AT&T is direct-marketing its DSS hardware at $499.

Another way to save money on DSS gear is to install it yourself. Thomson Consumer Electronics, RCA's parent, says that more than half of DSS buyers do their own installations—not very difficult in view of the small dish and complete instructions package with every reciever. Meanwhile, EchoStar, a DSS competitor, is offering its Digital Sky Highway (DISH) receiver for just $199 in selected markets, with a one-year subscription to its program service priced at $300.

RCA teams with Compaq

As computer makers rush to add TV tuning, and TV makers pull out all the stops to add PC features, it's interesting to find two top manufacturers in both fields joining hands for the future. RCA, one of the top brands of TV, has joined with Compaq, which is a leader in PCs, to develop combination products that will be sold under both brand names. At our deadline,

continued on page 27

What's better than speed reading?
Speed Learning.

Speed Learning has replaced speed reading. It's a whole new way to read and learn. It's easy to learn...lasts a lifetime... applies to everything you read. It may be the most productive course you've ever taken.

Do you have too much to read and too little time to read it? Do you mentally pronounce each word as you read? Do you frequently have to go back and reread words, or whole paragraphs, you just finished reading? Do you have trouble concentrating? Do you quickly forget most of what you read?

If you answer "Yes" to any of these questions — then here at last is the practical help you've been waiting for. Whether you read for business or pleasure, school or college, you will build exceptional skills from this major breakthrough in effective reading, created by Dr. Russell Stauffer at the University of Delaware.

Not just "speed reading" — but speed reading — thinking — understanding — remembering — and — learning

The new *Speed Learning Program* shows you, step-by-proven step, how to increase your reading skill and speed, so you understand more, remember more and use more of everything you read. The typical remark from over one million people taking the Speed Learning program is, "Why didn't someone teach me this a long time ago." They were no longer held back by their lack of skills and poor reading habits. They could read almost as fast as they could think.

What makes Speed Learning so successful?

The new *Speed Learning Program* does not offer you a rehash of the usual eye-exercises, timing devices, and costly gadgets you've probably heard about in connection with speed reading courses, or even tried and found ineffective.

In just a few spare minutes a day of easy reading and exciting listening, you discover an entirely new way to read and think — a radical departure from anything you have ever seen or heard about. Speed Learning is the largest selling self-study reading program in the world. Successful with Fortune 500 corporations, colleges, government agencies and accredited by 18 professional societies. Research shows that reading is 95% *thinking* and only 5% eye movement. Yet most of today's speed reading programs spend their time teaching you rapid eye movement (5% of the problem), and ignore the most important part, (95%) *thinking.* In brief, *Speed Learning gives you what speed reading can't.*

Imagine the new freedom you'll have when you learn how to dash through all types of reading material at least twice as fast as you do now, and with greater comprehension. Think of being able to get on top of the avalanche of newspapers, magazines and correspondence you have to read...finishing a stimulating book and retaining facts and details more clearly, and with greater accuracy, than ever before.

SPEED LEARNING
SPEED LEARNING
Goes Beyond Speed Reading To Develop Advanced Learning Skills
High Efficiency Reading BOOK 2
HEMINGWAY
THE OLD MAN AND THE SEA

FOR FASTER SHIPMENT CALL 1-800-729-7323 OR FAX 1-609-273-7766

Listen — and learn — at your own pace

This is a practical, easy-to-learn program that will work for you — no matter how slow a reader you think you are now. The *Speed Learning Program* is scientifically planned to get you started quickly...to help you in spare minutes a day. It brings you a "teacher-on-cassettes" who guides you, instructs, and encourages, explaining material as you read. Interesting items taken from *Time* Magazine, *Business Week, Wall Street Journal, Money, Reader's Digest, N.Y. Times* and many others, make the program stimulating, easy and fun...and so much more effective.

Executives, students, professional people, men and women in all walks of life from 15 to 70 have benefitted from this program. Speed Learning is a fully accredited course...costing only 1/4 the price of less effective speed reading classroom courses. Now you can examine the same easy, practical and proven methods at home...in your spare time...without risking a penny.

Examine Speed Learning RISK FREE for 15 days

You will be thrilled at how quickly this program will begin to develop new thinking and reading skills. After listening to just one cassette and reading the preface, you will quickly see how you can achieve increases in both the speed at which you read, and in the amount you understand and remember.

You must be delighted with what you see, or you pay nothing. Examine this remarkable program for 15 days. If, at the end of that time you are not convinced that you would like to master Speed Learning, simply return the program for a prompt refund. (See the coupon for low price and convenient credit terms.)

RISK-FREE ORDER FORM

☐ **YES!** I want to try Speed Learning for 15 days without risk. Enclosed is the first of 4 monthly payments of $32.25*. If I'm not completely satisfied, I may return it for a prompt refund.

☐ **SAVE 8.00!** I prefer to pay the $129.00 now, and save the $8.00 shipping & handling charge. I may still return the program for a full refund.

Method of payment: (Federal Tax Deductible)
☐ Check or money order payable to Learn Incorporated

☐ Charge to: ☐ Visa ☐ MC ☐ Am Ex ☐ Discover

Card # _____ Exp. _____

Signature _____

Phone (_____) _____

Name _____

Address _____

City _____ State ____ Zip _____

*Plus $8.00 shipping and handling. U.S. funds only. For New Jersey residents, sales tax will be added.

learn INCORPORATED Dept. LEC-01, 113 Gaither Drive, Mt. Laurel, NJ 08054-9987

Q & A

READERS QUESTIONS, EDITORS ANSWERS

Wanted: 700 Volts

Q *I would like to build a regulated 700-volt, 0.25-mA power supply for a Geiger counter, powered by batteries.—A. H., Petaluma, CA.*

A Figure 1 shows a circuit you can use as a starting point for experimentation. Powered by a 9-volt battery, it delivers 700 volts at 0 to 0.3 mA. Although not regulated, it's stable enough for a Geiger counter and has less than 1% ripple. To add regulation, modify the circuit as shown in Figure 2.

The basic circuit consists of an oscillator to chop the DC into AC, a step-up transformer, a voltage doubler, and a load resistance to keep the voltage from going too high. The step-up transformer is actually a split-primary power transformer used backward. It has two 8-volt windings, which we connect in parallel, and two 120-volt windings, which we connect in series. The transformer (note its unusual pinout, as indicated in the diagram.) is available from Signal Transformer Company, 500 Bayview Avenue, Inwood, NY 11096, as part number LP-16-700 for $14.30 plus shipping. The smaller and lighter LP-16-150, priced at $10.50, will probably work just as well, as will similar transformers from other manufacturers. Signal Transformer is a good company to know about; they make rugged, reliable power transformers and sell them in single quantities. You can phone them at 516-239-5777.

The diodes and capacitors in the voltage doubler are not critical as long as all of them are rated for at least 1 kilovolt (1000 volts). Radio Shack's 276-1114 diodes are ideal.

The regulated version of the circuit (see Fig. 2) uses a tripler instead of a doubler in order to ensure that the voltage is well above 700 volts. The actual regulation is done by a string of neon lamps. We used fourteen NE-2s, but each batch of bulbs is different and you may need a different number of them.

You may also want to look at the Geiger counter parts available from Electronic Goldmine, PO Box 5408, Scottsdale, AZ 85261, including special transformers, high-voltage capacitors, and kits.

Hard Disk Vs. CD-ROM

Q *The designers of the IBM PC seem to have made a bad mistake when the CD-ROM came around. Why is it necessary to load the contents of the CD-ROM onto the hard disk in order to run the software? On a Commodore computer, every program can be loaded from its own disk without taking up room on the hard drive.—C. E. S., Anacortes, WA.*

A The same is true of PCs; the CD-ROM has a file system just like that of any other disk, and you can run programs from the CD-ROM without copying them elsewhere. In fact, the contents of the CD-ROM are usually too large to copy onto the hard disk even if you wanted to.

So why does CD-ROM software have to be "installed"? For several reasons. First, even if running it from the CD-ROM, the user generally wants to have a Windows icon to launch the program. That requires a small amount of information to be recorded on the hard disk, but it certainly doesn't require copying the entire contents of the CD-ROM.

Second, it's impossible to write on a conventional CD-ROM, so if the program or its installation are customized in any way, that information has to go on the hard disk. That's why, even when running software from the CD-ROM, you'll often need to install some configuration files.

Third, CD-ROMs are considerably slower than hard disks; large programs load slowly when you try to run them from the CD-ROM. With many large software packages, the speed when executing from the CD-ROM is not acceptable. Accordingly, it's common for software to be delivered on CD-ROM but run from the hard disk. The CD-ROM takes the place of the box of diskettes on which the software would otherwise be delivered. In that situation, there is often a "runimage" directory on the CD that contains a ready-to-run copy of the software, so

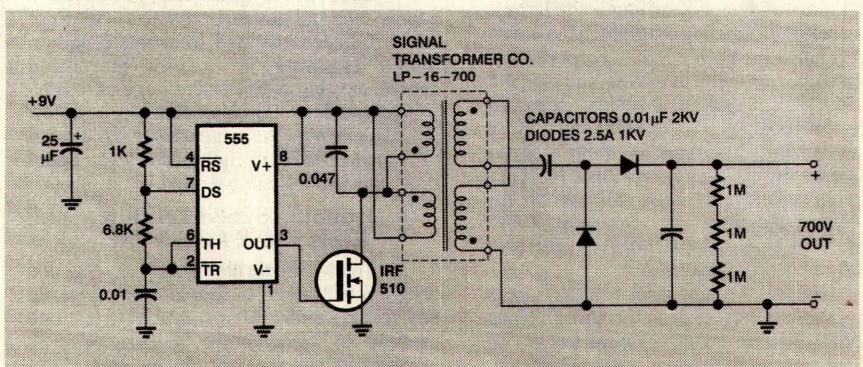

FIG. 1—THIS 700-VOLT, 0.25-mA power supply converts a +9-volt DC input to 10-kHz AC, then uses the step-up transformer and the voltage doubler circuit to produce the required output.

Two ways to fit a 100 MHz benchtop scope in your hand.

Bigger hands.

TekScope™

Got huge hands? Then you can probably lug a benchtop scope around the field. For the rest of us, there's TekScope,™ the first hand-held with true 100 MHz bandwidth and 500MS/s sample rate on both channels. It's got the familiar Tek interface, a bright, backlit display and is priced at just $2195 MSRP. Call 1-800-479-4490, action code 709, or visit our Web site at http://www.tek.com.

TEKTOOLS

Tektronix

© 1995 Tektronix, Inc. All rights reserved. Tektronix is a registered trademark and TekScope is a trademark of Tektronix, Inc. 3MW-500662-2

that you can run it from the CD if you don't have the disk space to do a full installation.

Mystery Diode

Q *I'm repairing a Sanyo Plus 55 AM-FM stereo receiver and am having trouble locating a replacement for a Zener diode #W-I35. I wrote to Sanyo and have not received a reply. Can you help?—G. O., Monte Lake, B.C., Canada.*

A We didn't find "W-I35" or "W-135" in the ECG replacement directory. But Sanyo parts are distributed by Diversified Parts, 2114 SE 9th Avenue, Portland, OR 97214; Tel: 800-338-6342; they can probably help you. You can get a service manual for your receiver from Howard W. Sams and Company at 800-528-7267. Both companies will probably need an exact chassis number or model number from the back of the unit (more than just "Plus 55," which might cover several variations of the design).

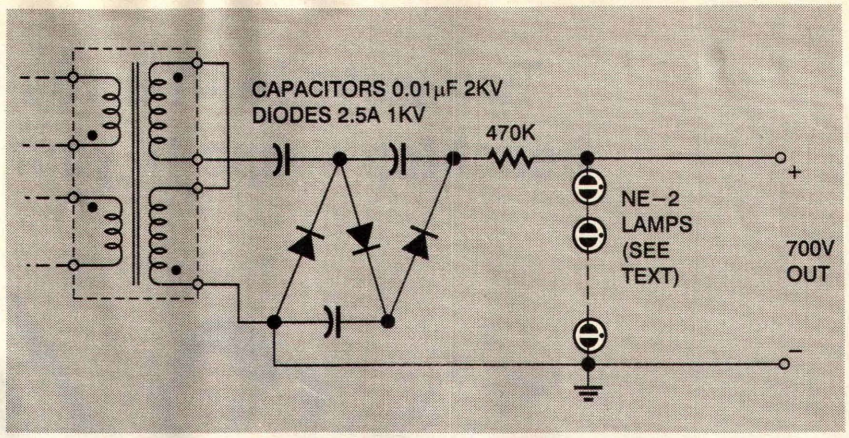

FIG. 2—IF YOU NEED A REGULATED OUTPUT, change the voltage doubler to a tripler, and use neon lamps as a regulator. The number of lamps you will need will depend on the characteristics of the lamps used, and will have to be found by experimentation.

Scoreboard Puzzle

Q *I'm trying to find out how a computerized scoreboard works. I don't want to buy one and take it apart. I know that it contains some counters and clocks, but how does the controller turn the message that is going to the scoreboard into a one-wire data stream and then decode it to drive the numbers on the scoreboard? Could you give me a schematic of a small version of one?—S. W. R., Verona, VA.*

A It's done with microprocessors, and a schematic wouldn't tell you much. The control unit and the scoreboard each contain at least one CPU with memory and input-output circuitry. The control unit scans its keyboard and responds to the switches that are

HAMEG® Instruments

HM1004

High-Tech for low Budgets

Made in Germany

2 Probes Included 3 Year Warranty

☑ 2 x DC to 100 MHz; 1mV – 20V/div.
☑ AUTOSET ☑ READOUT and CURSOR
☑ Dual Time Base ☑ SAVE/RECALL (9 setups)
☑ Delay-Line ☑ 14kV-CRT
☑ Triggering: DC to 200MHz, (<0.5div.)
☑ Remote Control via RS-232 built-in Interface

Call now: Toll-free (800) 247-1241 $ 1380.00

HAMEG Inc.
266 East Meadow Ave.
East Meadow, NY11554
(516) 794-4080
(516) 794-1855
1939 Plaza Real
Oceanside, CA 92056
(619) 630-4080
(619) 630-6507

CIRCLE 129 ON FREE INFORMATION CARD

Buy One Get One 50% off!

Explore the Caribbean on a 6 or 13 day sailing adventure.

Call your travel agent or
1-800-327-2601
http://www.windjammer.com

Windjammer Barefoot Cruises LTD.
P.O. Box 190120, Dept.5569
Miami Beach, FL 33139-0120

June - mid Dec. sailings only. Restrictions apply.

A World With Trees...where the trees you plant create cool, quiet neighborhoods

Trees Make a World of Difference™

Trees Make a World of Difference. Between drab, barren yards, and cozy, sheltered homes. Between hot, sunbaked streets, and cool, shaded neighborhoods where bird songs fill the air.

By planting trees, you can increase the value of your property up to 15% or more. At the same time, you'll make a personal, positive contribution to a better environment.

A World Without Trees

The trees you plant will remove carbon dioxide from the air, produce oxygen, and give wildlife a home. And trees help conserve energy. They can lower your heating bills 10-20%, and cut cooling costs 15-35%.

Find out how trees can make a world of difference for you, and your neighborhood. For your free brochure write: Trees For America, The National Arbor Day Foundation, Nebraska City, NE 68410.

The National Arbor Day Foundation

closed; the scoreboard unit scans the screen and turns each light on or off as required. They are connected by a serial data stream whose format might be anything the manufacturer dreamed up. Several microcontroller families, such as the 8051, have built-in UARTs (universal asynchronous receiver-transmitters) built right into the CPU; that device enables CPUs to transmit or receive data over a single wire.

We know of no books specifically dealing with scoreboards, but the chapter on microprocessors in Horowitz and Hill's *The Art of Electronics* (published by Cambridge University Press) should help you understand how they work.

DC Converter Needed

Q *I need a DC-DC converter. The input will be 11.5 to 12.5 volts DC and the output will be 14.5 volts at up to 10 amps.—W. S., Jacksonville, FL.*

A That's a lot of amps, certainly well beyond the capacity of standard DC converter modules. The most economical solution is probably to convert the incoming DC to 120-volt AC with an inverter such as Radio Shack's 22-138, and then convert the AC back to DC with a conventional power supply. Ham and CB radio dealers have 13.8-volt, 10-amp power supplies that will probably do the job; for information on building your own, see RadioShack's book, *Building Power Supplies*, and the ARRL's *Handbook for Radio Amateurs*. If 13.8 volts at 2.5 amps will do, you can use Radio Shack's 22-120 ($39.99); you may be able to convert it to 14.5 volts by changing one Zener diode.

Four Heads Better Than Two?

Q *What is the advantage of a four-head rather than two-head video cassette recorder?*

Also, how is 1/1000-second exposure accomplished in a camcorder, since it takes 1/30 second to scan a full frame?—F. J. B., Fallbrook, CA.

A A four-head VCR has a separate pair of heads for standard play and for extended play tapes. Thus, each pair of heads can be optimized for best performance at one speed rather than being a compromise between two different speeds. Camcorders that record at both speeds can equally well benefit from four heads.

As for the 1/1000 second, it's possible because the CCD sensor in a modern video camera does not do the exposure and the scanning at the same time. Instead, it exposes a frame all at once, then reads it out in a sequential scan. The exposure could be as long as 1/30 second (the duration of a whole scan), but it also could be shorter.

Measuring Loudness

Q *Please tell me if there is any way I can make a sound detector with a meter. Can I buy one?—J. M., Terre Haute, IN.*

A If all you need to do is compare two sounds, connect a microphone to a suitable amplifier, and then put an AC voltmeter across the output. Louder sounds produce higher voltages. An analog meter is best because the sound level is likely to be fluctuating.

To measure loudness in decibels is trickier because the meter must respond logarithmically, the frequency response must be flat over the relevant part of the audio range, and the instrument must be calibrated against a sound of known loudness. Fortunately, RadioShack sells two inexpensive decibel meters, the 33-2050 ($31.99) and the 33-2055 ($59.99).

Projection CRT

Q *Where can I buy used or rebuilt blue and green CRTs for an NEC projection TV?—N. M., Gloucester, Ont., Canada.*

A Start by contacting NEC's parts department at 1255 Michael Drive, Wood Dale, IL 60191; Tel: 708-860-0335. Also, replacement CRTs of all types are available from Video Display Corporation, 1868 Tucker Industrial Drive, Tucker, GA 30084; Tel: 770-938-2080. EN

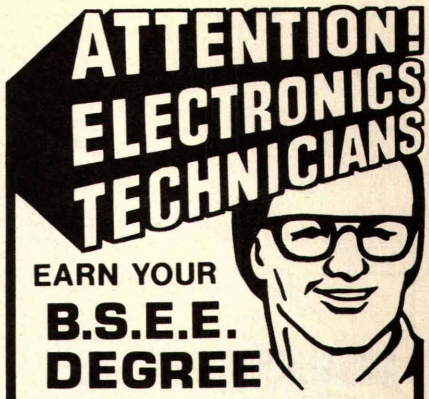

THROUGH HOME STUDY

Our Highly Effective Advanced-Placement Program for experienced Electronic Technicians grants credit for previous Schooling and Professional Experience, and can greatly reduce the time required to complete the program and reach graduation. No residence schooling required for qualified Electronic Technicians. Through our Special Program you can pull all of the loose ends of your electronics background together and earn your B.S.E.E. Degree. Upgrade your status and pay to the engineering level. Advance rapidly! Many finish in 12 months or less! Students and graduates in all 50 states and throughout the world! Established Over 50 Years! Write or call for free Descriptive Literature. (601) 371-1351

COOK'S INSTITUTE
OF ELECTRONICS ENGINEERING
CIE 4251 CYPRESS DRIVE
JACKSON, MISSISSIPPI 39212

CIRCLE 58 ON FREE INFORMATION CARD

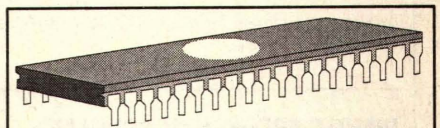

CABLE CONVERTER
DIAGNOSTIC TEST CHIP

LOAD FULL ACTIVATION OF CABLE CONVERTER

WE STOCK A COMPLETE LINE OF CHIPS,TOOLS, WIRELESS QUICK INSTALL TEST BOARDS AND DIAGNOSTIC CUBES FOR ALL CONVERTERS!

ANYONE IMPLYING ILLEGAL USE WILL BE DENIED SALE.WE SELL PRODUCTS ONLY!! TO TECHNICIANS OR CABLE REPAIR FACILITIES!!

#1 IN CUSTOMER SERVICE & TECH. SUPPORT!
*ALL ORDERS SHIP WITHIN 24HRS, UPS/ FED-X.
*PRIORITY NEXT DAY SHIPPING AVAILABLE!
*SALE= BUY 5 TEST BOARDS AND GET 1 FREE.
*LOWEST PRICE & SUPERIOR PRODUCT GUAR!!
*FRIENDLY COURTEOUS SERVICE. WE'RE PRO'S

VISA MasterCard VISUAL COMMUNICATIONS INC.
FOR ORDERS 1-800-GO-CABLE
CATALOG & TECH. SUPPORT 717-620-4363 EST. 1977

ANTIQUE RADIO CLASSIFIED
Free Sample!
Antique Radio's Largest Circulation Monthly. Articles, Ads & Classifieds.
6-Month Trial: $18.95. 1-Yr: $36.95 ($53.95-1st Class).
A.R.C., P.O. Box 802-L17, Carlisle, MA 01741
Phone:(508) 371-0512 VISA/MC Fax:(508) 371-7129

LETTERS

SEND YOUR COMMENTS TO THE EDITORS OF ELECTRONICS NOW MAGAZINE

AXIS GENERATOR SOURCES

I really appreciated the June 1996 installment of "Experiments with Laser Light." I read the article when I was on vacation at the beach, and it made the trip all the better. The article got me interested in controlling the X-Y modulators/axis generators. I was wondering if you would be so kind as to give me a few good places to look for axis generators, so that I might try to control them with a computer.

Thanks a lot, and, again, it was a very nice article!
ADAM RIXEY

Happy to hear that you liked the article, Adam. Hope you continue to enjoy the rest of the series.

I don't have the answer to your question. However, I will send it on to the author, who may be able to help.—Editor

SIMPLE FREQUENCY DOUBLER

I recently got involved in a project that required a frequency doubler without a lower frequency limit and was unable to locate one in any reference books or magazine articles. Left to my own ingenuity, Fig. 1 is a design that I came up with. It works quite well, and I thought that it might be of some use to your readers.

The circuit is really quite simple. The 74LS393 (dual counter) is used to keep down the parts count, but any counter with a reset input should work equally well. The 74LS393 is designed to advance one count on the positive to negative transition of the pulse at the clock input (pins 1 and 13). An inverter in front of the B section of the counter causes the B section to advance one count on the negative to positive transition of the input pulse.

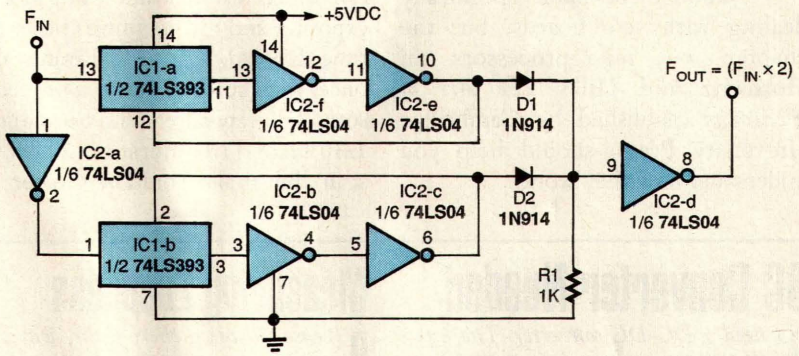

FIG. 1—A SIMPLE FREQUENCY DOUBLER. IC1 is a 74LS393 dual counter; IC2 is a 74LS04 hex inverter.

Each section of the counter is cleared with a positive-going pulse on the master reset input (pins 2 and 12). By connecting the Q0 output of each counter (pins 3 and 11) to its respective master clear pin, through two inverter sections, we end up with positive-going output pulses from pins 6 and 10 of IC2, which resets the respective counters.

The duration of the pulses depends upon the propagation delay of the inverters. With the 74LS04 hex inverter, that delay will probably be in the vicinity of 20 to 25 nanoseconds. The output pulses are also connected to the remaining inverter gate through switching diodes and a pull-down resistor, which configures the remaining inverter as a NOR gate. The output at pin 8 of IC2 represents the input frequency multiplied by two.

Because the output pulse lengths are about 25 nanoseconds, they are difficult to see on the typical hobby oscilloscope. But if you have a logic probe with a pulse mode, you can put in an input frequency of just a few hertz and see it quite well. If you would like to experiment, you can connect the output of the doubler to a divide-by-two circuit. That will allow you to confirm that the circuit is working because the frequency at the output of the divide-by-two circuit will be the same as the input frequency to the frequency doubler. If you have a dual-trace scope to connect to those two points, you will notice that the waveforms are identical. Keep in mind that the only way to get evenly spaced output pulses from the doubler is to feed it with a 50% duty-cycle squarewave.

There you have it. I hope others can find a good use for this circuit. Keep up the good work. I always look forward to the next issue of **Electronics Now.**
BOBBY SMITH
Eddy, TX

EN

Write To:
Letters
Electronics Now
500 Bi-County Blvd.
Farmingdale, NY 11735

Due to the volume of mail we receive, not all letters can be answered personally. All letters are subject to editing for clarity and length.

Where Do I Go When It Doesn't Work?

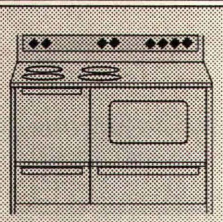
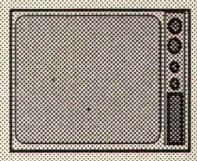
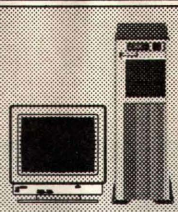

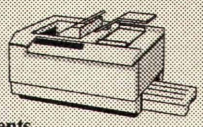

- Answering Machines
- Appliances
- Audio Equipment
- Camcorders
- Cellular Telephones
- Computers
- Computer Monitors
- Copy Machines
- Clothes Dryers
- Electronic Musical Instruments
- Fax Machines
- Home Automation
- Home Theatre
- Microphones
- Microwave Ovens
- Printers
- Radar Detectors
- Radios
- Satellite Receivers
- Security Systems
- Speakers
- Telephones
- Televisions Sets
- Vehicular Electronics
- Video Games
- Washing Machines

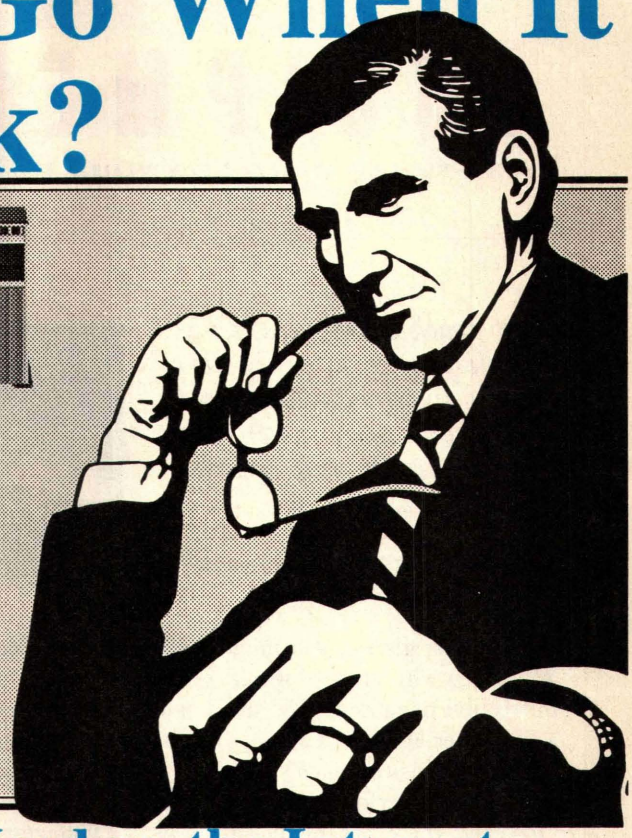

Guaranteed Quality Service for All Your Computers, Office Machines, Appliances, and Consumer Electronics Products.

Find the Service You Need on the Internet at http://www.nesda.com

You deserve to have your equipment serviced by professionals in product service. National Electronics Service Dealers Association (NESDA) and National Independent Appliance Dealers (NIAS) presents a worldwide listing of competent, professional independent appliance, computer, consumer electronics, and home-office product service centers. All are pledged to provide quality service and adhere to a comprehensive code of business ethics. at NESDA.com on the worldwide seb, you will:

- ☑ Find out how to get good service — every time
- ☑ Find a nearby quality, ethical, professional service center by zip code now
- ☑ Get advice on service contracts and extended warranties
- ☑ Learn how to file a complaint
- ☑ Arrange a service appointment to meet your schedule
- ☑ Phone, fax, or send an e-mail message to a participating service center or visit their worldwide web site
- ☑ Get more useful information

Soon to Come:

- ☐ Select by your product type
- ☐ Select by the product's brand-name
- ☐ Select the factory-authorized service centers for your product and brand
- ☐ Get product pruchasing advice

Have Your Equipment Repaired and Maintained by the Ethical Professionals in Product Service

National Electronics Service Dealers Association (NESDA)
and National Independent Appliance Dealers (NIAS)

A worldwide listing of competent, professional independent appliance, computer, consumer electronics, and home-office product service centers. Pledged to provide quality, service, and adhering to a comprehensive code of business ethics.

http://www.nesda.com

NESDA .com

2708 W. Berry St., Fort Worth TX 76109; Phone 817-921-9061; Fax 817.921.3741

EQUIPMENT REPORTS

A TV-TUNER CARD FOR YOUR PC FROM PHILIPS PROFESSIONAL SOLUTIONS

Keep track of important news while you work, easily store video images on your hard disk, and more, when you turn your PC into a cable-ready TV set.

CIRCLE 15 ON FREE INFORMATION CARD

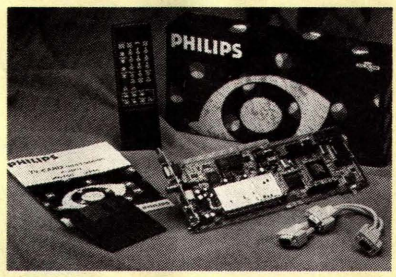

At first glance, you might wonder why anyone would go to the trouble of adding a TV function to a PC. After all, the "TV" that results is more expensive than a standard TV and doesn't perform quite as well. However, there are many situations that are ideal for just such a PC/TV combo. For instance, if your job entails keeping tabs on news or financial data, a small TV window can help you do just that without cluttering up your work area with another large device (a TV receiver). Also, if you need to move video images from tape, or to capture them off the air, and store them on disk, such a setup might be the easiest way to go about it.

So how do you go about adding a TV function to your PC? Easy! You purchase and install the new *PCA 20 TV* television-tuner card from *Philips Professional Solutions* (2099 Gateway Place, Suite 100, San Jose, CA 95110; Tel: 800-235-7373).

The PCA 20 TV is a $329 cable-ready television tuner with stereo sound on an ISA expansion card. The card installs in an empty ISA slot in a 386 or better PC, comes complete with an infrared remote control, and is available in NTSC and PAL versions.

Hardware hurdles

Installing the PCA 20 TV card is quite simple, although there was one obstacle along the way—one that was more of a problem with the PC being used rather than with the TV card. The ¾-length card (10½ inches) would only fit in one expansion slot in the computer. The CPU heat sink and a voltage-regulator heat sink blocked long cards from most of the slots in the system. We had to juggle the positions of all the ISA cards that were already installed to fit the TV card.

Another inconvenience is that you need two slots to install the TV card. The card really needs just one slot, but an accessory bracket must be installed in another slot. The slot itself is actually not used, just the bracket space. The extra bracket is necessary for the IR sensor jack, because the bracket on the TV card is all filled up with a D connector, an F-type cable-TV input jack, an S-video input, a composite-video input, and an audio-output jack. The wired IR sensor plugs into the extra bracket and sticks onto your monitor bezel (or wherever you like). The sensor then receives IR commands from the remote control.

You don't have to use the sensor or install its jack in an extra slot, but since they are included with the package, it's a shame not to use them—and less convenient as well. One alternative is to drill out one of the vent holes on the back of your computer, large enough to fit the sensor jack when it's removed from the bracket. And that's only if there isn't a large enough hole to begin with. Then the TV card needs only one slot with the sensor installed. The only requirements for making this modification is that you must have the nerve to put a drill to your PC, and the common sense to keep metal shavings from falling into the system or from putting a drill bit through one of your expansion cards.

An included "Y" adapter cable connects the TV card to your graphics card and monitor. The TV card does not affect your graphics card in any way, and the adapter cable eliminates the need for a feature connector on your graphics card—something found on most, but not all, graphics cards. This is also much easier than having to deal with internal connectors. A line-level audio output on the TV card connects to amplified speakers or to an external input on your sound card. Alternatively, you can make an internal connection between the TV card and your sound card.

TV on PC

The software for the TV card, contained on a single diskette, couldn't be easier to install. The installation configures the card to work in DOS and Windows 3.1x and higher. We tested the card under Windows 95 with no problems at all. The TV card defaults to seldom-used settings (IRQ10 and I/O port address 510h) so that there's less of a chance of encountering hardware conflicts. If necessary, the default settings can be changed, although they worked fine for us. We had the card working in minutes. We then set it to scan for all received channels and store them in memory.

The TV card's picture quality is nearly as good as a standard, good-

quality TV receiver; however there are some artifacts due to the conversion from NTSC to VGA video. To minimize those, settings within the TV software let you adjust various parameters for the best picture. For example, you can set the X and Y position relative to the TV window, and set the VGA clock delay for the best picture within a particular system. In our setup, we got the best picture with an inverted delay for the VGA clock. You will have to experiment with the VGA clock settings to see what works best for you. After selecting the best type of delay, you can set the rising and falling portions of it for an even better picture.

You can control the TV card with the IR remote if you've installed the sensor, or with an on-screen set of controls. Either way, you'll see TV-like on-screen displays for channel, volume, color, brightness, and so on.

As we alluded to earlier, perhaps the most valuable feature of the TV card is its ability to freeze and capture video, and then store it on your hard disk. The video can be from any standard source—over-the air TV, videotape, laserdisc, or camcorder.

The remote control lets you change video sources (RF, S-video, composite video), switch between full-screen and window modes, adjust sound and picture quality, change channels and volume, and do everything else you would expect from a TV remote. Pressing a picture-in-picture (PIP) button first decreases the size of the TV window, and subsequent presses move the downsized TV window to different corners of the screen. This way you can see different parts of the screen depending on what's there. We tested the TV while working in Microsoft Word, and found no compatibility or operational problems—both worked flawlessly at the same time.

If you need (or like) to watch TV while you work on your computer, the Philips PCA 20 TV television-tuner card can't be beat! It doesn't take up any extra space in your office or work area, and if you need to capture and store video images of almost any type, it is hard to find anything that can do the job better. EN

Wavetek. The Way Value Is Measured.

For the best values in digital multimeters everyone is turning to the Wavetek XT Series. Each of these full-function DMMs measures voltage, current, resistance, and also a set of additional electrical or electronic properties you work with every day. Inductance. Capacitance. Frequency. Temperature. There is an XT Series DMM right for you.

With oversized character displays, these DMMs are as easy to read as they are to use. All have fully-fused current inputs and input warning beepers to protect you and the meter. Each comes with safety test leads and are approved to IEC1010-1 safety standards.

27XT
A unique combination of DMM and component checking in a single meter.
- *Inductance*
- *Capacitance*
- *Logic*
- *Frequency*

Accessories include current clamps, RF & HV probes, temperature converters, holsters, boots and carrying cases.

23XT
Electronic and electrical test functions for general duty and HVAC/R.
- *VAC Safety Tester™*
- *Temperature*
- *Capacitance*
- *Logic*

25XT
A full C-meter in a DMM, and more! Ideal for A/V, cell-phone & antenna matching, component inspection.
- *Full Capacitance 0.1pF to 20mF*
- *Capacitance Zeroing & Test Slots*

28XT
A thermometer + DMM for HVAC/R, building or plant maintenance.
- *Temperature*
- *Capacitance*
- *Frequency*
- *Max-Hold*

85XT
A precision True-RMS reading DMM, ideal for equipment like copiers.
- *4 1/2 digit*
- *0.05% Accuracy*
- *True-RMS*
- *Frequency*
- *Duty Cycle*

LCR55
Full-function LCR, extra test features for "best-buy" in a component checker.
- *Inductance*
- *Capacitance*
- *Resistance*
- *Transistor*
- *Dual Diode*

Our commitment to reliability and high-quality is backed by the industry's only "No Hassle" warranty program. If your XT Series meter requires warranty service, your local dealer replaces it immediately. Call today for full details and the names of your local Wavetek distributors. You'll find that when it comes to Wavetek performance and price, nothing else measures up.

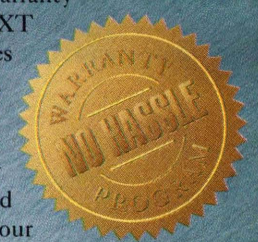

Wavetek Corporation
9145 Balboa Avenue, San Diego, CA 92123
(800) 854 2708

WAVETEK

CIRCLE 98 ON FREE INFORMATION CARD

NEW PRODUCTS

USE THE FREE INFORMATION CARD FOR FAST RESPONSE

High-Resolution Digital Multimeters

THE FOUR MODELS IN Metrix's ASYC IIB Series are among the first handheld digital multimeters to offer backlit displays and the ability to print hard copy of either test results or calibration results. All models have a 50,000-count digital-display resolution and offer true-rms (AC, and DC plus AC) measurements for accuracy in handling non-sinusoidal, or irregular, waveforms. The digital multimeters feature basic DC accuracy to 0.025%; bandwidths to 100 kHz; provide facilities for automatic storage of the last reading; and hold, fast, peak-capture, and relative-reading modes. The DMMs also perform comprehensive autoranging voltage, current, capacitance, and frequency (to 500 kHz) measurements. Duty-cycle percentage, positive or negative pulse width, and pulse-counting functions are provided as well. The top-of-the-line model adds a resistive power function that offers a choice of reference resistances.

An optional calibration kit allows you to recalibrate the ASYC IIB meters without opening them. Calibration results are printed on a personal computer; an optional adapter is provided for a serial printer connection. LabWindows drivers and calibration software are provided with the calibration kit. Recalibrating the ASYC IIB meters is done by removing the fuse/battery-compartment cover, temporarily replacing it with a faceplate, and then following software prompts to recalibrate and print the results. The meter need not be opened during the procedure.

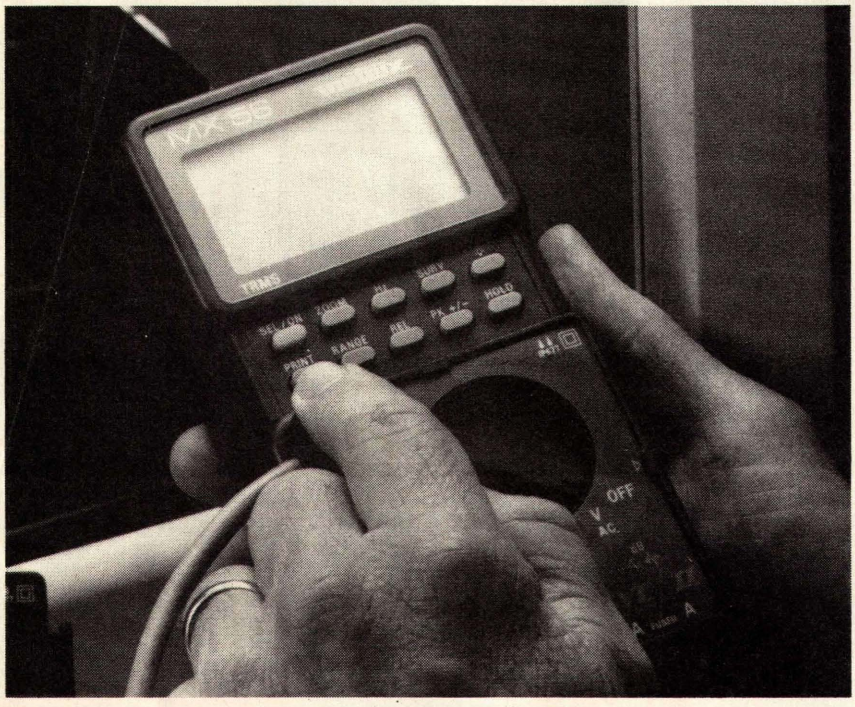

CIRCLE 20 ON FREE INFORMATION CARD

The ASYC (Advanced Safety Concept) meters offer a host of safety features including full water and dust sealing to IP677 standards. A separate compartment allows the battery or fuses to be replaced without using metal tools and without breaking the calibration label. Test lead retainers keep leads from being accidentally disconnected.

Prices for the four models in the ASYC IIB Series of digital multimeters range from $259 to $399. The SX-ASYC IIC calibration kit costs $199.

METRIX
P. O. Box 332
Brea, CA 92622-0332
Tel: 714-992-1239

TRIPLE-OUTPUT POWER SUPPLY

THE MODEL 1670 TRIPLE-output power supply from B+K Precision is designed for applications in the servicing, educational, and hobbyist markets where a low-cost solution to multiple outputs is desired. The power supply features a variable DC supply—0 to 30 volts at 0 to 2.5 amps—with variable current limiting, constant current or constant voltage operation, tight regulation, low ripple, and separate digital LCD current and voltage meters. Another fixed 5-volt, half-amp supply is provided for TTL projects, and a fixed 12-volt, half-amp supply is included for mobile electron-

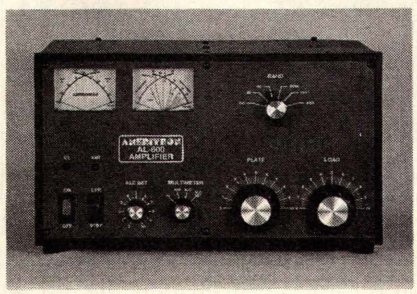

CIRCLE 21 0 ON FREE INFORMATION CARD

ics and digital CMOS projects.

The Model 1670 costs $199.

B+K PRECISION
6740 West Cortland Street
Chicago, IL 60635
Tel: 1-800-462-9832
Fax: 312-794-9740

Helping Hand For Soldering

WHEN YOU'RE TRYING TO hold the soldering iron, solder, wire, and connectors, sometimes you could use an extra hand. Ironwood Pacific's Free Hand provides just that.

The Free Hand cuff fits around your wrist. Attached to the cuff is an arm with a holding clip mounted at its end. The clip can be opened to hold a wire or electrical component, freeing both of your hands to hold the soldering iron (or gun), wire, or solder.

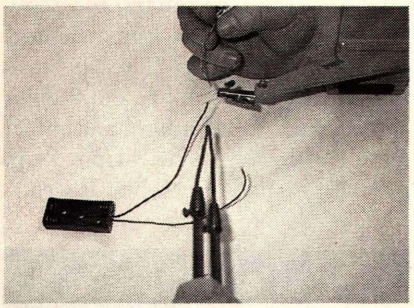

CIRCLE 22 ON FREE INFORMATION CARD

The Free Hand is equipped with a built-in cutter and six-inch ruler for cutting fine wire and measuring distances. Its two-piece design allows it to be easily stored or to be adapted for mounting directly to the table or work surface. Molded from high-impact plastic, the cuff is adjustable to fit most wrist sizes.

The Free Hand costs $8.95 plus $3 shipping and handling.

IRONWOOD PACIFIC INC.
P. O. Box 1568
Lake Oswego, OR 79035
Tel: 800-261-1330

Desktop Personal Theater

ONE CONSUMER-ELECTRONICS buzzword that you'll be hearing a lot in coming months is "PC/TV," which refers to any single unit that combines computer and television functions. Core Dynamics presents an inexpensive add-on solution with its DynaMax Hi-Rez Plus interactive video/television card. Compatible with all VGA cards without the need for internal cables, the 8-inch ISA bus card supports up to 1280×1024 resolution and displays 16.7 million colors at full frame and full motion.

The interactive video and television card allows you to use your PC to watch broadcast, cable, or direct-access TV, as well as videotapes from your VCR or camcorder. A built-in video snapshot captures images that you can use for personal home pages,

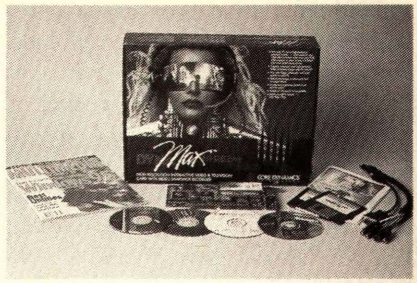

CIRCLE 23 ON FREE INFORMATION CARD

AT $299.95, NO OTHER DESIGN WORKSTATION GIVES YOU SO MUCH FOR SO LITTLE.

PROTO BOARD BRAND

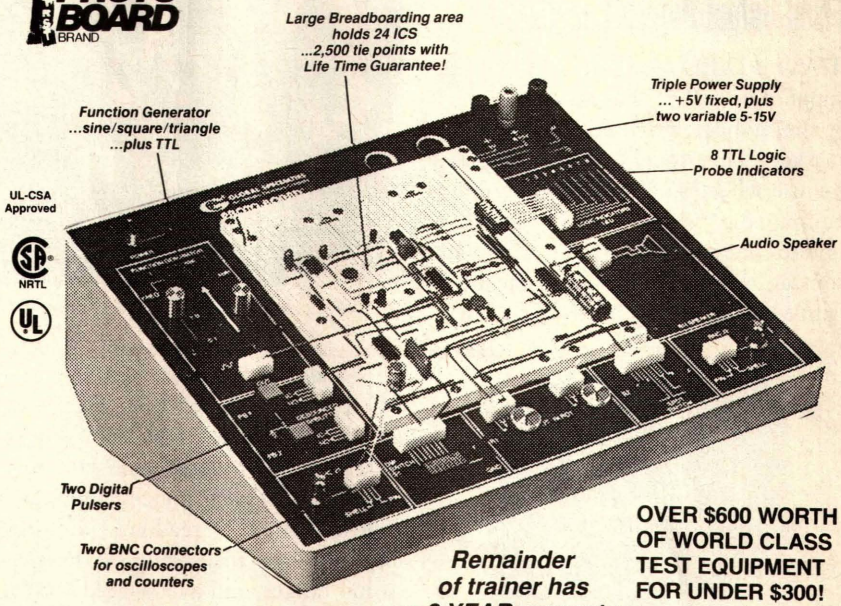
Large Breadboarding area holds 24 ICS ...2,500 tie points with Life Time Guarantee!
Triple Power Supply ... +5V fixed, plus two variable 5-15V
Function Generator ...sine/square/triangle ...plus TTL
8 TTL Logic Probe Indicators
UL-CSA Approved
NRTL
Audio Speaker
Two Digital Pulsers
Two BNC Connectors for oscilloscopes and counters

Remainder of trainer has a 2 YEAR warranty

OVER $600 WORTH OF WORLD CLASS TEST EQUIPMENT FOR UNDER $300!

Here's PB-503, the total design workstation. It has everything! **Instrumentation,** including a function generator with continuously variable sine/square/triangle wave forms—plus TTL pulses. **Breadboards** with 8 logic probe circuits.

And a **Triple Power Supply** with fixed 5VDC, plus two variable outputs (+5 to 15VDC and −5 to 15VDC). Throw-in 8 TTL compatible LED indicators, switches, pulsers, potentiometers, audio experimentation speaker...plus a lifetime guarantee on all breadboarding sockets! You have everything you need right there in front of you! PB-503—one super test station for under $300! Order yours today!!

GLOBAL® SPECIALTIES

Can't Wait! Call Toll-Free
1-800-572-1028

70 Fulton Terrace, New Haven, CT 06512
(203) 466-6103 • Fax: (203) 468-0060

an Interplex Industries company

CIRCLE 122 ON FREE INFORMATION CARD

add to school projects or business presentations, or store in video albums. You can also use the Hi-Rez Plus as the basis for a video-conferencing or security system. On board spatial stereo sound enhances the video.

Three CD-ROM titles—A Guided Tour of Multimedia, Second Edition; ESPN's Baseball Tonight; and CNN's Time Capsule—are included, as is Corel's PhotoPaint 5 Special Edition. The video/TV card also comes with a VCR input cable, loopback cable, software drivers for Windows 3.1x and Windows 95, an installation manual, and a trial subscription to Multimedia World magazine.

The Dynamax Hi-Rez Plus card costs $299.

CORE DYNAMICS
8 Thomas Street
Suite 100
Irvine, CA 92718
Tel: 800-611-CORE
Web site: http://www.core-dynamics.com

Fixed-Output Power Supplies

TWO FIXED-OUTPUT POWER supplies from B+K Precision are aimed at the mobile-electronics and hobbyist markets. The Model 1680 is well-suited for use when bench testing autosound equipment, two-way radios, cellular phones, and amateur-radio gear. Its standard binding posts are augmented with a convenient cigarette-lighter jack.

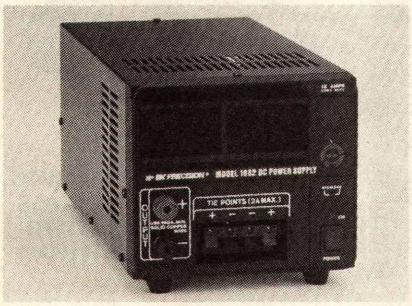

CIRCLE 24 ON FREE INFORMATION CARD

The Model 1680 features a 13.8-volt output with an intermittent-current capability of up to 6 amps. Ripple voltage is a low 5mV rms. Overload protection is provided via current foldback with air-convection cooling.

Designed for higher current applications, the Model 1682 features up to 15 amps intermittent duty at 13.8 volts. Ripple voltage is 6 mV rms. The Model 1682 offers convection cooling and foldback overload protection with a built-in overload indicator.

The Models 1680 and 1682 fixed-output power supplies cost $50 and $90, respectively.

B+K PRECISION
6470 West Cortland Street
Chicago, IL 60635
Tel: 1-800-462-9832
Fax: 312-794-9740

Clamp-On Digital Multimeters

THREE ADDITIONS TO Wavetek's line of clamp-on digital multimeters are designed for the installation, testing, verification, servicing, and troubleshooting of modern electrical systems. The clamp-on method is non-invasive, allowing for quicker and safer current measuring without disrupting the circuitry.

CIRCLE 25 ON FREE INFORMATION CARD

Models AC60 and AC65 feature AC transformers, while the Hall-Effect transducer of the Model AD105 allows both AC and DC measuring. All three meters include a 4000-count LCD readout, autoranging, true-rms measuring, wide measuring ranges, and a data-hold button. The compact meters' "hand-guard" design meets new international standards, and their rugged construction allows them to withstand drops of up to four feet without damage.

The AC60 and AC65 DMMs measure AC current to 600 amps, AC voltage to 600 volts, resistance to 40K ohms, and they offer a quick continuity-check function. The AD105 is a high-range ammeter that measures both AC and DC to 1000 amps and frequency to 10 kHz. A peak-hold button captures and holds peak measurements, which comes in handy in many real-world situations.

The AC60, AC65, and AC105 clamp-on DMMs have list prices of $109.95, $149.95, and $249.95, respectively.

WAVETEK CORPORATION
9045 Balboa Avenue
San Diego, CA 92123
Tel: 619-279-2200
Fax: 619-565-9558

DIMM Module Tester

THE DIMMCHECK 168P IS AN add-on option for Aristo Computers' SIMCHECK PLUS SIMM/SIP memory module and DRAM tester. With the addition of the DIMMCHECK 168P, you can test the popular 168-pin Dual In-Line Memory Modules, or DIMMs. The unit tests the DIMMs with 64, 72, and 80 bits, as required by Pentium and other RISC processors. The adapter supports ECC and Parity types, as well as some non-standard wiring.

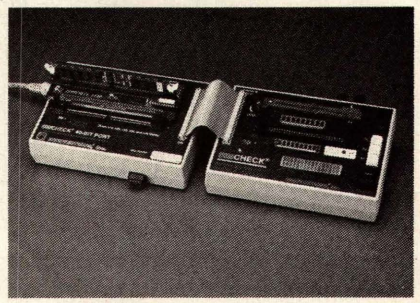

CIRCLE 26 ON FREE INFORMATION CARD

The adapter connects to the SIMCHECK PLUS base unit. The test identifies the size, speed, type, and structure of the DIMM and provides a reading of the DIMMs presence detect (PRD) code. When a fault is encountered, explicit error information is provided.

The DIMMCHECK 168P has a retail price of $295. The SIMCHECK PLUS base unit costs $1490.

ARISTO COMPUTERS INC.
6700 SW 105th Avenue
Beaverton, OR 97008
Tel: 800-3ARISTO or
503-626-6333
Fax: 503-626-6492

EN

MCM ELECTRONICS®

FOR VALUED READERS ONLY!
Save up to 20% on select items!
Take advantage of this tremendous offer.
Call today, time is limited!

To take advantage of these offers, you must supply this special price code:

CODE: ENS26

20th Anniversary 1996

Value And Selection From One Source...

- Test Equipment from Tenma, Fluke, Hitachi, Leader, B+K
- Name Brand and Low Cost Generic Technician's Tools
- OEM and Generic TV/VCR repair parts
- Over 10,000 American and Original Japanese Semiconductors

MCM offers a comprehensive line of tools and test equipment engineered for the repair of computers, TVs, VCRs and more. In addition, you will find a wide variety of OEM and low cost generic TV/VCR parts, passive components and semiconductors, over 25,000 items in all, stocked and ready to ship.

SAVE 15%

TENMA®

3½ Digit DMM

Ideal for general testing and hobby applications. Accurately measures AC/DC voltage, DC current, resistance and tests transistors.

#72-2055 Reg. ~~$31.95~~

Sale **$27.00**

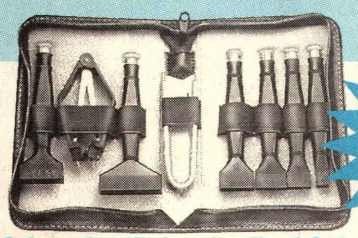

SAVE 20%

IC Inserter/Extractor Tool Set

Eight piece kit contains specific insertion tools for 8 pin DIP, 14/16 pin DIP, 18/20 pin DIP, 22 pin DIP, 24/28 pin DIP, and 36/40 pin DIP packages. ALso includes IC extractor tweezer and square IC extractor. Housed in vinyl zipper case.

#21-3605 Reg. ~~$24.95~~ Sale **$19.95**

SAVE 20%

CLARKE

Heavy-Duty Aluminum Tool Case

Constructed of lightweight durable aluminum, this case is designed to take rough field use. Attractive black finish holds up after years of use. Measures approximately 19" x 14" x 6".

#21-3460 Reg. ~~$49.95~~ Sale **$39.95**

Prices effective August 1 through September 30, 1996

FREE Catalog

To order the items listed, or for a FREE catalog, Call...

1-800-543-4330

MCM ELECTRONICS®
650 CONGRESS PARK DR.
CENTERVILLE, OH 45459-4072
A PREMIER Company

RCA/GE Premier Distributor

Authorized Panasonic Quasar/Technics Original Parts Distributor

Hours: M~F 7 a.m.~9 p.m., Sat. 9 a.m.~6 p.m.,EST.

CODE: ENS26

CIRCLE 314 ON FREE INFORMATION CARD

NEW LITERATURE

USE THE FREE INFORMATION CARD FOR FAST RESPONSE

ISDN: How to Get a High-Speed Connection to the Internet

by Charles Summers and Bryant Dunetz
John Wiley & Sons, Inc.
605 Third Avenue
New York, NY 10158-0012
Tel: 800-CALL-WILEY
Web site: http://www.wiley.com/compbooks
$22.95

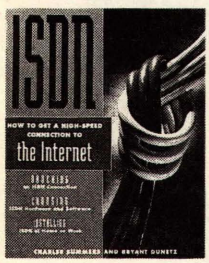

CIRCLE 337 ON FREE INFORMATION CARD

Downloading graphics and sound from the Internet and World Wide Web can be excruciatingly slow. Although today's 28.8-baud modems work fairly well over traditional phone lines, the bandwidth of those lines can hardly manage the massive amounts of data moving onto and off the Internet.

ISDN, or Integrated Services Digital Network, is a technology that allows people to use existing phone lines to access data at much higher speeds. Although it has existed in conceptual form since 1988, its actual availability has been very limited until recently. Internet access is the "killer application" that could put ISDN on the map. ISDN telephone service is becoming available throughout the country, and Internet service providers have begun offering ISDN connections.

This book is a complete guide to getting and using an ISDN connection to the Internet. It shows individual dial-up and small-business users how to analyze their needs and select the best type of ISDN connection, obtain the necessary telephone service, secure an ISDN connection from an Internet service provider, and install ISDN hardware and modify Internet software to work with ISDN. The book helps readers get the most out of their ISDN connection to the Internet and World Wide Web, and provides extensive lists of ISDN resources, including ISDN carriers, service providers, and capability requirements.

Electronic Components and Computer Products Catalog

Jameco
1355 Shoreway Road
Belmont, CA 94002-4100
Tel: 800-831-4242
Fax: 800-237-6948
Web site: http://www.jameco.com
Free

CIRCLE 338 ON FREE INFORMATION CARD

Jameco's complete product line includes more than 5000 electronic and computer products, such as ICs, discrete components, power components, prototyping equipment, tools and test equipment, sockets and connectors, books, consumer electronic products, and cellular phones. This catalog features more than 250 new products, including Gentron relays, cellular-phone accessories, networking products, ADAM remote data-acquisition and control modules, and high-capacity Seagate hard drives. It also offers hundreds of sale items and closeouts. A free gift is shipped with each order; the gifts range from a mousepad to a 16-bit IDE disk-drive adapter, depending on the amount of your order.

Visual Basic Algorithms: A Developer's Sourcebook ofReady-to-Run Code

by Rod Stephens
John Wiley & Sons, Inc.
605 Third Avenue
New York, NY 10158-0012
Tel: 800-CALL-WILEY
Web site: http://www.wiley.com/compbooks/
$39.95, with companion diskette

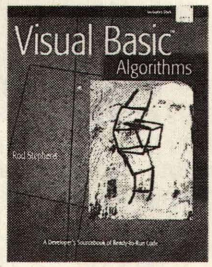

CIRCLE 339 ON FREE INFORMATION CARD

Visual Basic's popularity stems from its point-and-click programming interface—but that falls short of the task when a programmer needs to implement more sophisticated code into a Windows program. This book give Visual Basic programmers everything they need to create complex applications and put more muscle into their everyday programs.

The book provides a solid working introduction to the world of algorithms, and serves as a sourcebook packed with valuable, ready-to-run code. Readers learn the basics of how algorithms work, how to analyze the usefulness of any algorithm, and how to incorporate algorithms into Visual Basic programs. Dozens useful algorithms are presented, implemented in Visual Basic and clearly explained in plain English. Those algorithms can be used for a wide variety of common programming tasks, including memory allocation, sorting, searching, hashing, trees, networking, assignment, shortest path, and queue simulation.

The book also provides an array of implemented algorithms for user-interface design and graphics programs.

The companion disk includes a wealth of Visual Basic source code, including practical algorithms that can be modified to fit each programmer's specific needs. The disk also contains working examples of applications that demonstrate the uses of every algorithm covered.

Digital Techniques in Frequency Synthesis

by Bar-Giora Goldberg
McGraw-Hill, Inc.
11 West 19th Street
New York, NY 10011
Tel: 800-2-MCGRAW
$60

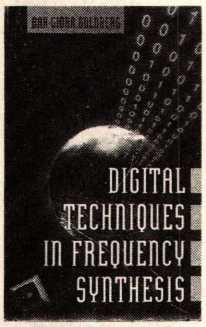

CIRCLE 340 ON FREE INFORMATION CARD

Technological progress and the ability to integrate complex circuitry in a single chip makes possible low-power, low-cost frequency synthesis. As a consequence, digital and analog technologies are now used synergistically in the implementation of complex signal generation and modulation.

This comprehensive guide to frequency synthesis technology focuses specifically on the modernization and digitization of signal generation. Digital frequency synthesis is used in a wide variety of modern electronics and communications technologies ranging from radar, satellite communications, medical imaging, and spectroscopy to cellular, wireless, and PCS/PCN systems.

The book is filled with design examples and hands-on approaches, helping readers analyze and manipulate the methods described in the text. It provides detailed coverage of direct digital synthesizers (DDSs), phase-locked loops (PLLs), and fractional-N PLLs used to generate and modulate signals accurately and effectively.

Speakers for Your Home and Automobile: How to Build and Enjoy a Quality Audio System

by Gordon McComb, Alvis J. Evans, and Eric J. Evans
Prompt Publications
2647 Waterfront Parkway East Drive
Indianapolis, IN 46214-2041
Tel: 800-428-7267
$14.95

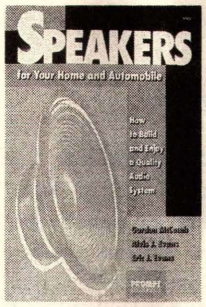

CIRCLE 341 ON FREE INFORMATION CARD

High-quality speakers are an integral part of any fine audio system. This book shows you how to build quality speakers for use in your home and car. Directions for four home speaker systems and automotive installations are presented with easy-to-follow instructions and clear illustrations. The book also covers enclosures and finishing touches, construction techniques, and wiring speakers.

Soldering Irons Catalog

M.M. Newman Corporation
24 Tioga Way
P. O. Box 615
Marblehead, MA 01945
Tel: 617-631-7100
Fax: 617-631-8887
Free

CIRCLE 342 ON FREE INFORMATION CARD

This eight-page catalog features the full line of Antex precision miniature and standard-size soldering irons, iron stands, temperature control stations, and a wide variety of slide-on tips.

Photo-graphs and specifications for each product, and a fully illustrated chart of available tips in different shapes and sizes, are included. Highlights include the new 600 Series of static-dissipative, temperature-controlled soldering stations; a 60-watt electric hot knife; and a portable soldering iron that operates from any automotive-type 12-volt battery.

1996 Equipment, Tools & Supplies Catalog

Print Products International
8931 Brookville Road
Silver Spring, MD 20910
Tel: 1-800-638-2020 (in Maryland, 301-587-7824)
Fax: 1-800-545-0058 (in Maryland, 301-585-5402
E-mail: smprodintl@aol.com
Free

CIRCLE 343 ON FREE INFORMATION CARD

The 84 pages of this catalog are packed with electronic test gear for anyone who builds, maintains, services, or purchases today's advanced electronics. Products range from simple scopes, power supplies, and soldering stations to the most advanced spectrum analyzers, digital storage oscilloscopes, surface mount rework and repair equipment, arbitrary waveform generators, and analog/digital cellular test sets.

Law on the Net: Easy Access to Online Legal Resources

by James Evans
Nolo Press
950 Parker Street
Berkeley, CA 94710-9867
Tel: 510-549-1976
$39.95

Lawyers might compare self-help law to do-it-yourself brain surgery. You might not want to defend yourself in a court of law, but it is possible to find the answers to some of your legal questions without consulting an attorney. The resources are right at your fingertips if you are connected to the Internet—and if you

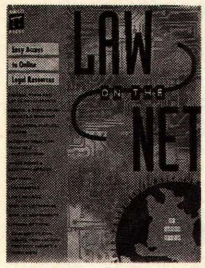

CIRCLE 344 ON FREE INFORMATION CARD

know where to look.

This book points you directly to the locations of hundreds of online legal resources. It tells you all you need to know about what sites are available, what information they offer, and exactly how to get to them. The book's comprehensive index—which includes such topics as biotechnology, divorce and custody, immigration, tax law, privacy, intellectual property, environmental law, computer regulation and crime, health care, and bankruptcy—takes you straight to the information you need.

The book shows you how to tap into federal and state statutes and regulations, White House and executive offices, the U.S. Congress, federal and state courts, law firms, law schools, bar associations, and even international treaties and constitutions. More than 150 law-related "listservers"—automated mailing lists that will keep you informed on issues in your field are listed. You'll also find more than 100 law-related newsgroups, where you can exchange information and discuss legal issues with experts.

Radio/Tech Modifications & Alignment Controls

Artsci
P. O. Box 1428
Burbank, CA 91057
Tel: 818-843-4080
Fax: 818-846-2298
E-mail: artsci@artscipub.com
Web site: http://www.earthlink.net/~artsci
$19.95 each, plus $4 shipping

This two-volume set is aimed at radio repair technicians and amateur-radio hobbyists who are serious about enhancing their radio transceivers and scanners. The typical modifications presented in the books increase the radios' transmit and reception frequency coverage. Many of the modifications will allow a radio or scanner to monitor "illegal" frequencies.

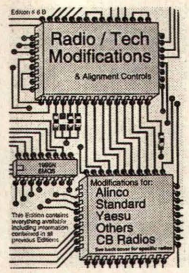

CIRCLE 345 ON FREE INFORMATION CARD

The new editions (8A and 8B) cover radios that were introduced in 1995, as well as all the radios presented in previous editions. A new page format simplifies the modifications. Illustrations are detailed and easy to follow.

The "A" edition contains modification information for Kenwood and Icom amateur radios and Uniden, Regency, and RadioShack scanners. The "B" edition (pictured here), completes the set with all the modifications for Alinco, Yaesu, Standard, Azden, RCI, and other amateur radios, as well as modifications for citizen band (CB) radios. EN

THE SALVATION ARMY
Volunteers Welcome

FACTCARDS

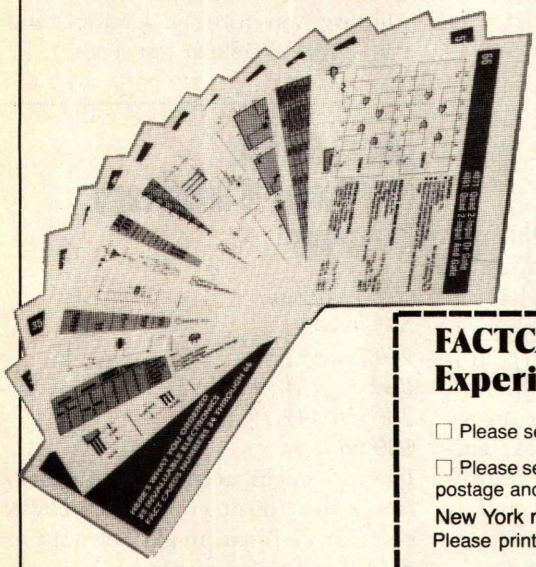

■ ALL YOU NEED to know about electronics from transistor packaging to substitution and replacement guides. FACTCARDS numbers 34 through 66 are now available. These beautifully-printed cards measure a full three-by-five inches and are printed in two colors. They cover a wide range of subjects from Triac circuit/replacement guides to flip-flops, Schmitt triggers, Thyristor circuits, Opto-Isolator/Coupler selection and replacement. All are clearly explained with typical circuit applications.

■ WANT TO EXPAND your knowledge of electronics? Do it the easy way by studying the Electronics Fact Cards. Do you travel to and from your job each day? Drop a handful of cards in your pocket before you leave, and the bus becomes a schoolroom! At home, you can build some of the projects and not only have fun building and using them, but learn how they work at the same time.

■ YOU'LL BE AMAZED both at how rapidly you learn with these cards, and how easy it is to understand. These new cards are available right now. Don't miss out. Send your check or money order today.

Jampacked with information at your fingertips

FACTCARDS—Facts at your fingertips for Experimenters and Project Builders!

☐ Please send one copy of FACTCARDS at $3.50. Shipping $1.00 (U.S. and Canada only).

☐ Please send _____ copies of FACTCARDS. Total cost is sum of copy price and First Class postage and handling cost multiplied by number of card sets ordered.

New York residents add sales tax to total cost of each order.

Please print — Allow 6-8 weeks for the material to arrive.

_____ (Name)

_____ (Street Address)

_____ (City) (State) (Zip)

Detach and mail today:
CLAGGK Inc.
P.O. Box 4099
Farmingdale, NY 11735

All Payment must be in U.S. Funds!

BS168

WHAT'S NEWS

continued from page 6

available on its Web site (http://www.hp.com/go/tmdir), giving a cutting-edge means of viewing highly technical information.

"We are continuing to evolve the [Web] site from a place that is simply a passive repository for information to one that will ultimately allow interactive, two-way communication on many levels with customers," said Jeff Gruszynski, TMO's web master.

Customers can download the full text of many popular application notes. The animations that have been added to the downloadable notes illustrate technical product information such as wave frequency and amplitude. Viewers can stop the animations at any point and zoom in to see intricate details in even the most complex graphs. Key portions of the notes can be viewed online along with interactive mathematical models whose parameters can be adjusted in real time.

To access the interactive notes, users must be working in the Windows 95, Windows NT, Power Macintosh, or UNIX operating environment and must be running a JAVA-enabled Web browser such as Netscape. Adobe Acrobat Reader 2.0 and Quicktime, both of which can be downloaded free from the Internet, are also required to download the full electronic text of the notes and to view the animated graphics.

The TMO Web site also provides a complete list and descriptions of service and support programs, descriptions of course offerings covering a wide range of instrument and computer solutions, and online product selection.

HDTV host station announced

The Model HDTV Station Project, jointly sponsored by U.S. broadcast television stations and the professional- and consumer-electronics industries, has selected WRC-TV as the host station for the HDTV Project. WRC-TV is located in Washington, D.C., and is owned and operated by NBC. The Model HDTV Station Project also contracted with the David Sarnoff Research Center (Princeton, NJ) to implement the construction of the HDTV station. Funds for the three year project are being collected and provided by the Association for Maximum Service Television (MSTV) and the Consumer Electronics Manufacturers Association (CEMA). MSTV invites all U.S. television stations to contribute to the funding.

"With Sarnoff, NBC, and WRC-TV, we have a team in place that will turn the dream of the Grand Alliance into a reality for broadcasters and consumers," enthused Gary Shapiro, president of CEMA.

For the duration of the project, WRC-TV will serve as a source of encoded digital television signals to aid equipment manufacturers in the development of professional- and consumer-electronic equipment. It will also provide public demonstrations of HDTV, as well as HDTV training for broadcast-station technical personnel. EN

VIDEO NEWS

continued from page 8

details hadn't been announced, but it's understood that the products of the collaboration are likely to use RCA's 36-inch fine-pitch picture tube and incorporate Web browsing and perhaps a wireless keyboard. According to Compaq, the requirements for the first products will include Internet access and compatibility with direct satellite broadcasting systems. The two companies have discussed software requirements with Microsoft and Intel. The resulting product will be sold by both companies under a joint trade name.

70 firms back net computer

Oracle announced a "reference profile" for its own idea for a network computer—a low-cost net browser, using the TV screen for display—for people who don't want to buy computers. Although the "profile" was a bit short of actual specifications, Oracle was able to give the names of 70 companies that it said endorse the system. In addition to the usual computer suspects, the list includes such consumer-electronic heavyweights as LG (Goldstar), Matsushita (Panasonic), Mitsubishi, Nokia, and Toshiba. Oracle chairman Larry Ellison had touted the $500 netcruiser as an inexpensive, simpler successor to the computer for home use. However, there were some estimates that the cost would escalate from the proposed $500 to $1000, bringing it into the same price category as low-end PCs.

A major defector from Oracle is Farzad Dibachi, formerly senior vice president, who complained that Oracle's price was escalating. He and his brother Farid formed a company called Diba, which developed a platform called "IDEAS" (for "interactive digital electronic appliances") to push a system of single-function, low-priced "information appliances," such as a telephone with a small screen and keypad for fax and e-mail, priced at less than $300. That caught the fancy of Zenith, which introduced 27- and 35-inch "NetVision" TVs using Diba technology at $1099 and $3499, designed for net browsing and telephony as well as ordinary TV viewing.

Cable modems hot

Virtually all major cable-TV operators are now experimenting with high-speed cable modems. CableLabs, the industry-supported testing organization, says that "thousands" of cable systems are currently using them, and that trials have been successful. Modems being testing vary from 4 to 40 Mbps and will provide the latest service that cable systems can charge their viewers for. The cable modems are hooked not to the customer's TV, but to his or her PC. Telephone companies are responding by testing different methods to develop higher speed modems to work with their existing or planned lines. The result: Much faster modems are in the works, one way or the other—or both. EN

SKYVISION®

1046 Frontier Drive Fergus Falls, MN 56537 Fax: 218-739-4879

DIGITAL *is the Future*

Introducing. . .

"The New Kid on The Block"

18" DIGITAL DISH

We've been hearing a lot lately about the new little dishes. The DISH℠ Network System is the latest, and he arrived as a shining star. He is small, attractive and the latest in technology, but what really sets him apart is the programming he delivers to your Television screen. The DISH℠ Network is chock full of the most popular programming at prices much lower than the competiton. Call us now for more information. Digital just may be in your future.

dish NETWORK

The Dish is Small The Programming BIG

Beat The Rush Call Now

800-500-9264

Special Digital Hotline

30%-60% $avings! Compare to Other 18" Dish Programming!

If you have one of these. . .

"Keep it Running Strong" With a Discount Buyer's Guide

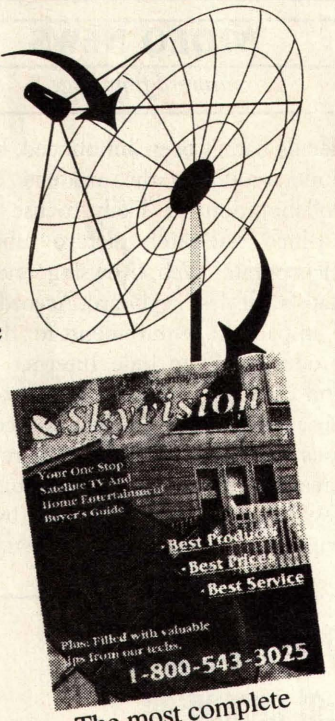
Skyvision
Your One Stop Satellite TV And Home Entertainment Buyer's Guide
Best Service
Plus: Filled with valuable tips from our techs.
1-800-543-3025

If you are the owner of a C/Ku-band Full View Satellite System, we know you'll want to keep it up and running strong. The Skyvision Discount Buyer's Guide will give you advice and products to get the job done right.

You Will Find a Wide Selection of:

- **Complete Systems**
- **Advanced Upgrades**
- **Parts & Accessories**
- **Tune-Up Tools & Advice**
- **Technical Tips Galore**
- **Discount *Skypac*℠ Programming**

For Your Free Issue Call Now

800-334-6455

Need a repair item Fast??

"We'll Get It Out Today"

The most complete Big Dish Satellite Discount Buyer's Guide! Get your FREE copy now

CIRCLE 270 ON FREE INFORMATION CARD

BUILD THIS

Hobby Spectrum Analyzer

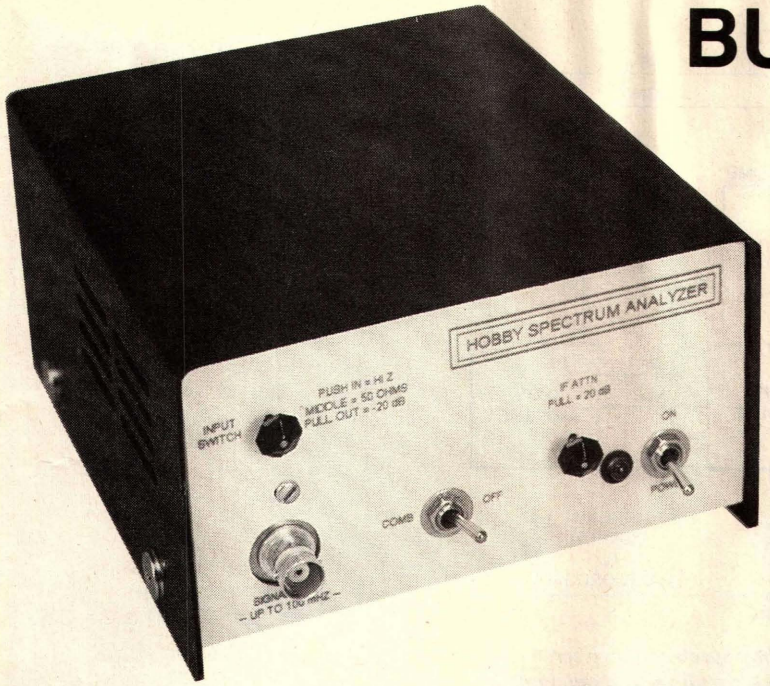

At less than $100 to build, this spectrum analyzer is a must for every hobbyist!

BOB KOPSKI

The project described in this article was inspired by a need to analyze the radio-frequency spectrum for hobby applications related to radio-controlled (R/C) model planes. The author suspected that some microprocessor-controlled R/C accessories were causing interference with the onboard guidance radio. Those problems were tracked down by using a borrowed Smith Design "Spectrum Probe" and very expensive HP spectrum analyzer. (Smith Design is located in North Wales, PA.) That experienced prompted the author to design and build this inexpensive, yet effective, Hobby Spectrum Analyzer (HSA).

What is it? A spectrum analyzer might be perceived as an automatically-tuned visual radio. To envision this, connect the audio output from a radio to an oscilloscope's vertical input. Spin the tuning dial slowly; every time you tune through a station the output will show up as a random vertical blip on the oscilloscope. Now imagine you are able to tune the radio and synchronize the oscilloscope's horizontal sweep in step with it. The horizontal axis on the oscilloscope would simulate a radio tuning dial. Radio signals would show up on the display at their frequency locations. In addition, the size of the blip could be an indication of the radio signal's relative strength.

The HSA can do all of the above and be built for less than $100 using commonly available parts. The HSA tunes from low MHz frequencies to 100 MHz. With a few inches of antenna wire connected to the input terminal, the HSA routinely displays RF signals within its operating range on an inexpensive oscilloscope. Those detected signals include CB and amateur-radio activity, wireless phone, RC signals, local TV stations, and a significant portion of the FM band; plus any local EMI, all *at the same time and on one display*!

The HSA is actually a double-conversion superhetrodyne radio. The tuning sweep is electronically and repeatedly generated by an internal sweep circuit that linearly tunes the frequency range in a 10-mS time period. If the oscilloscope time base is set to 1 mS per-major-division, then each division represents a 10-MHz segment of the tuning range. This is the "frequency dial" analogy and the blips on it are received radio-frequency signals. The HSA outputs a trigger pulse to initiate the internal sweep of the oscilloscope coincident with the beginning of the frequency sweep. This assures solid synchronization between the HSA's frequency tuning and the oscilloscope display.

The HSA is an excellent relative RF voltmeter or power meter. It has a sensitivity of better than −80 dBm which is about 22 microvolts rms on a 50-ohm line. It has an amplitude dynamic range exceeding 50 dB, which can be further increased with built-in RF and IF attenuators. A built-in comb generator allows accurate calibration of both frequency and amplitude performance. When the HSA is aligned, it has a frequency accuracy within ±1 MHz, and the prototype has an amplitude flatness/accuracy better than ±2 dB across the entire range. The HSA is battery powered with eight alkaline AA cells in an internal battery pack.

Almost any inexpensive, one-channel oscilloscope with a triggered-sweep feature can serve as the HSA's companion unit. A two-channel oscilloscope, or one with a time-base magnifier adds versatility, but is not necessary. The HSA is easy to align and use. What is needed to align the HSA is the companion oscilloscope, plus a DVM, an adjustable DC power supply, an audio or function generator producing a 10-kHz (or so) sine-wave signal, and a source of 145 MHz for IF alignment.

While the HSA will be more than adequate for hobbyist or other "less demanding" applications, remember that it is not intended to be a "lab-grade" instrument. For example, the HSA has no input filter, so signals beyond 100 MHz may sneak in as im-

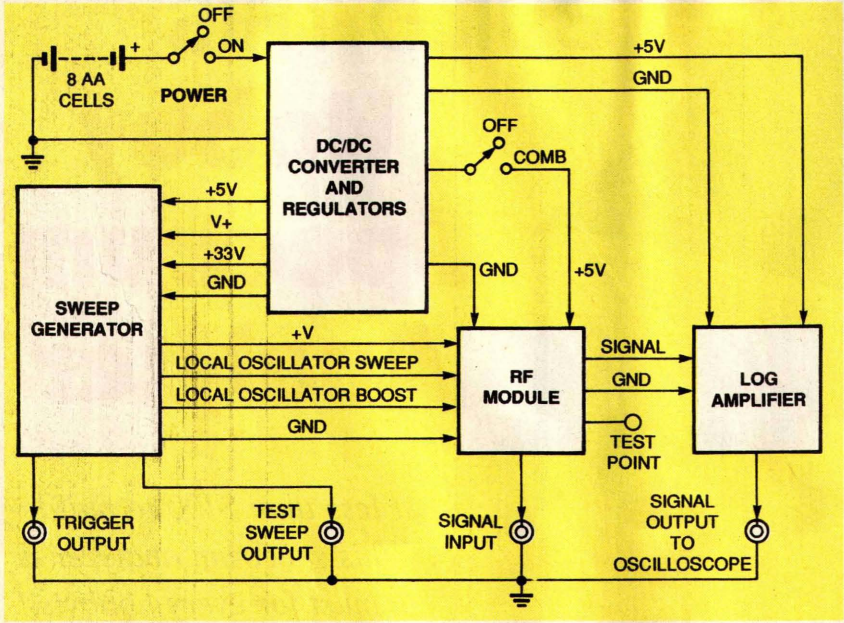

FIG. 1—SIMPLIFIED BLOCK DIAGRAM for the Hobby Spectrum Analyzer. Functional blocks are actual circuit boards which make circuit understanding and construction easier for the hobbyist.

ages and appear on the display. Also, the HSA uses a simple heterodyne detector technique and the resulting spectral lines are actually swept-through zero beats. This results in some amplitude display jitter. You just have to look a bit more carefully at the oscilloscope display for more accurate readings.

How it works. The Hobby Spectrum Analyzer's four main functional blocks (see Fig. 1) are the sweep generator, RF module, log amplifier, and DC/DC converter and regulators. All four blocks are constructed as individual assemblies. They are tested individually for basic operation, then interconnected with short cables, and housed in a metal case.

RF circuit module. The RF circuit module schematic diagram is shown in Fig. 2. The RF input signal first reaches the INPUT SWITCH S1, which is a three-pole, three-throw slide switch. It selects either a HIGH Z input, a 50 OHM input, or a –20-DB input for the first mixer/converter. The HI Z input is very useful with a short-wire antenna connected to the SIGNAL INPUT jack while the latter two options are useful for more accurate amplitude measurements in 50-ohm cable systems. (The same basic idea can be extended to 75-ohm systems if that is your preference.) The comb generator block is the built-in calibrator function mentioned earlier and will be discussed in detail in the alignment section.

The signal from S1 flows to the first converter IC1, a Signetics NE602 oscillator-mixer. The local oscillator is a varactor-tuned Colpitts configuration. A sweep voltage of about 4 to 30 volts is applied to varactor D1 and that causes the local oscillator to vary from about 145 MHz to about 245 MHz. Thus, the first converter is an "up converter". For example, when an incoming signal is at 50 MHz, it is mixed with the swept local oscillator signal. At some point in the timed local-oscillator sweep signal, the 195-MHz point of the sweep mixes with the 50-MHz signal to produce the mixer output signal at 145 MHz, which is the first IF frequency. This spot frequency signal is then processed by the remainder of the HSA functions. The LO (local oscillator) boost input shown in Fig. 2 is a finer detail and will be discussed later.

The first converter is followed by a simple double-tuned, 145-MHz bandpass filter and then the IF ATTN switch. The latter uses a double-pole, double-throw slide switch and permits the filtered 145-MHz signal to flow either directly into the second converter or to first experience 20 dB of attenuation. Since the second converter is the first circuit to overload with high input levels, the IF attenuator is aptly located.

PARTS LIST FOR THE RF CIRCUIT MODULE (Fig. 2)

SEMICONDUCTORS

D1—MV209 varactor diode
IC1, IC2—NE602A oscillator-mixer, integrated circuit (Signetics)

RESISTORS

(All resistors are ¼-watt, 5% units.)
R1, R3—60.4-ohm, 1%, metal film
R2—249-ohm, 1%, metal film
R4—49.9-ohm, 1%, metal film
R5—100-ohm
R6—22,000-ohm
R7—10,000-ohm
R8—1300-ohm
R9—150-ohm

CAPACITORS

(All capacitors are ceramic discs unless otherwise noted.)
C1, C2, C4, C5, C8–C11, C20, C21, C25, C28—0.001-µF
C3, C22—0.1-µF
C6, C13, C17, C18, C27—2.5–7.5-pF trimmer, 6 millimeter
C7—4-pF
C12—15-pF
C14, C16—7-pF
C15—1-pF
C19—100-pF
C23—5-pF
C24—2-pF
C26—12-pF

ADDITIONAL PARTS AND MATERIALS

L1, L5—Ferrite bead (Panasonic EXC-L351390)
L2, L6—5 turns of #30, solid, enameled wire, 3/32-in. i.d., air-core, spread turns as required (see text)
L3, L4—5 turns of #20, solid, tinned wire, ¼-in. i.d., air-core, spread turns as required (see text); L4 is tapped (tack soldered) at 1 turn above ground to lead from C15
S1—Three-pole, three-throw, slide switch (Digi-Key SW336, or equiv.)
S2—Two pole, two-throw slide switch (Digi-Key SW335, or equiv.)
Double-sided PC board material (unetched) plus scrap pieces from PC universal prototyping board (RadioShack 276- 168); BNC male connector, flange mount; 6-pin, straight, male plug with 0.1-in. centers; metal and plastic spacers; screws; nuts; washers; copper foil; etc.

The second converter has a fixed local oscillator frequency of 145 MHz. Thus, its input signal from the at-

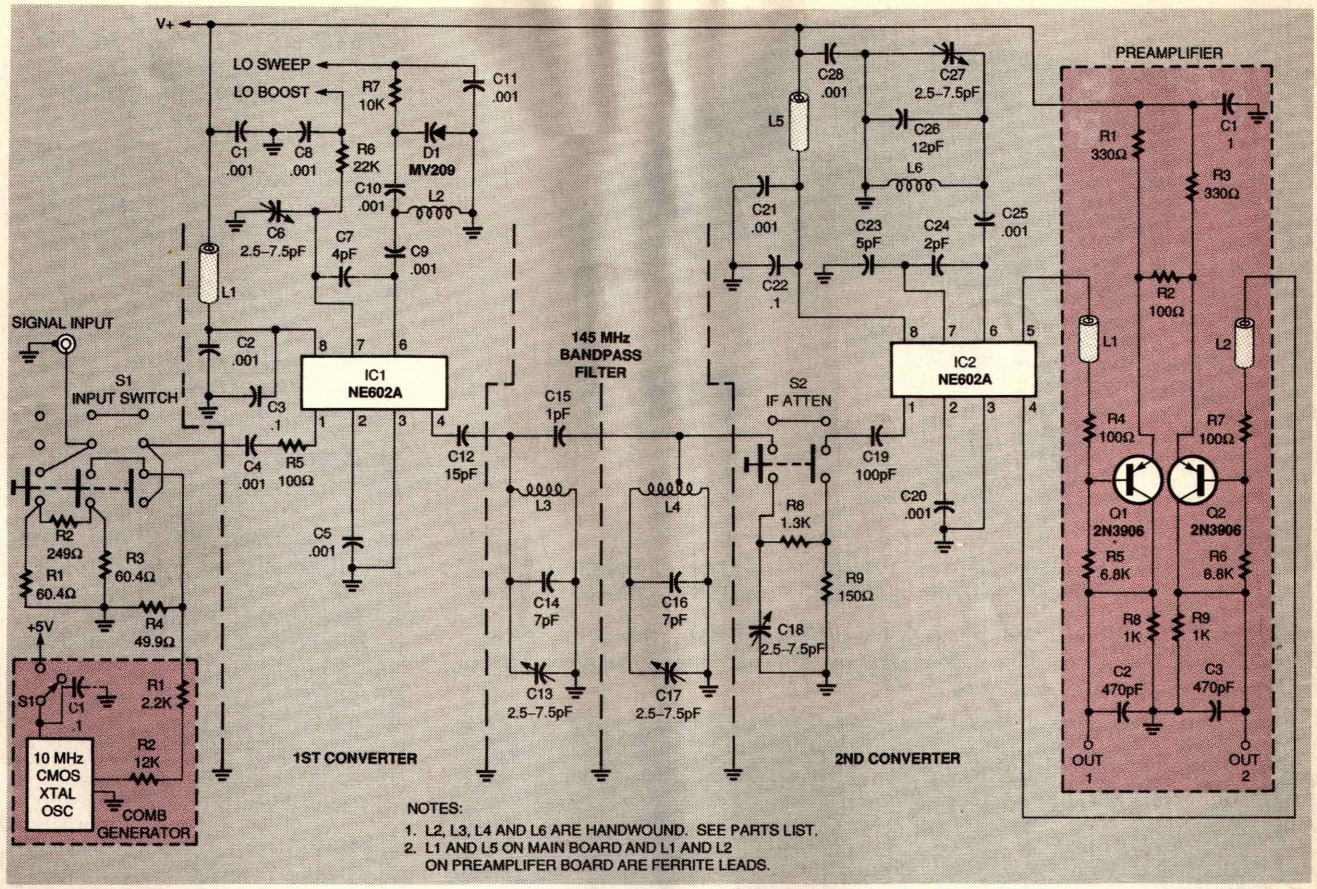

FIG. 2—SCHEMATIC DIAGRAM for the RF circuit module. Note that the circuit includes two subassemblies—comb generator and preamplifier—each of which is assembled on its own board. Since the parts symbol for each assembly section begins with "1," there are three R1s, etc., in the diagram. The text clearly separates discussion on each section so there is no confusion.

tenuator and its own oscillator signal heterodyne (mix) to produce swept zero-beat signals with incoming signals.

The second converter also uses a Signetics NE602, and its balanced output drives a preamplifier. The heterodyne output signals are low frequencies that range from zero at "beat" upwards to low 100s of kHz during the heterodyne sweep. The preamplifier and the log amplifier need only be low-frequency circuits. A bandwidth of 100 kHz for the second IF is adequate.

PARTS LIST FOR THE COMB GENERATOR SUBASSEMBLY (Fig. 2)

C1—0.1-μF, disc, ceramic capacitor
R1—2200-ohm, ¼-watt, 5% resistor
R2—12,000-ohm, ¼-watt, 5% resistor
S1—Single-pole, single-throw, toggle switch
10.0-MHz crystal-controlled, CMOS oscillator integrated circuit (Digi-Key CTX114); piece of PC universal prototyping board (Radio Shack 276-168); wire, etc.

DC/DC converter and regulators module. The DC/DC converter and regulators module (See Fig. 3) receives 12-volt DC from the eight AA dry-cell pack and provides three regulated output voltages to operate the HSA. What are those outputs and why are they needed? A separate +5 volt regulated supply powers the sweep generator, log amplifier, and comb generator boards. There is also a V+ output which only powers the RF and preamplifier circuits. The V+ output is adjusted during alignment to between 5 and 7 volts to optimize HSA performance. Finally, there is a +33-volt DC output. This high voltage powers the sweep generator output system for varactor tuning. The voltage is obtained from a simple, regulated voltage multiplier powered directly from the 12-volt battery. While the +5 volts and the V+ voltages are obtained from common-type 78L05 three-terminal regulators, the +33-volt generator deserves some expanded explanation.

The DC/DC converter and regulators module uses a classic diode

PARTS LIST FOR THE PREAMPLIFIER SUBASSEMBLY (Fig. 2)

SEMICONDUCTORS
Q1, Q2—2N3906, PNP, RF amplifier transistor

RESISTORS
(All resistors are ¼-watt, 5% units.)
R1, R3—330-ohm
R2, R4, R7—100-ohm
R5, R6—6800-ohm
R8, R9—1000-ohm

CAPACITORS
C1—1.0-μF, 16-WVDC, tantalum
C2, C3—470-pF, ceramic disc

ADDITIONAL PARTS AND MATERIALS
L1, L2— Ferrite bead (Panasonic EXC-L351390)
PC universal prototyping board (RadioShack 276-168), wire, hardware, etc.

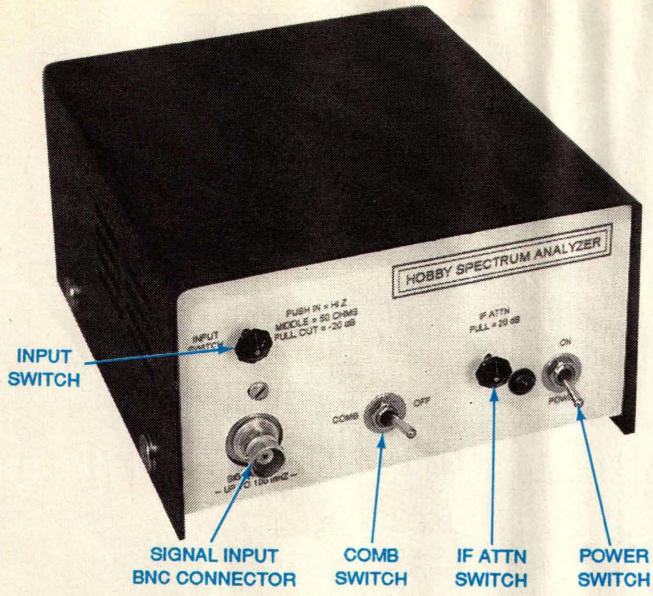

FRONT PANEL OF THE HSA mounts four switches and a BNC connector for the input signal. The rear panel (not shown) has four RCA phono jacks that provide three output signals and a battery test point.

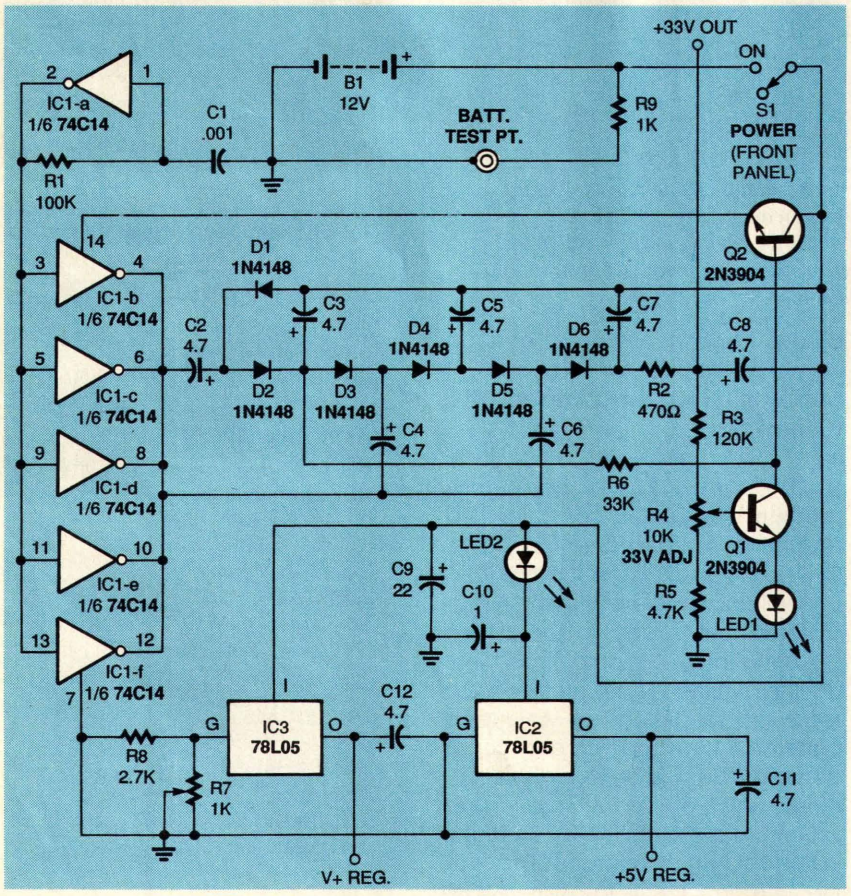

FIG. 3—SCHEMATIC DIAGRAM for the DC/DC converter and regulators module. The V+-volt DC supply is used in the RF module where the final voltage setting of R7 is made for optimum performance. The +33-volt DC output is used in the sweep circuit module to generate the output log sweep.

PARTS LIST FOR THE DC/DC CONVERTER AND REGULATORS MODULE (Fig. 3)

SEMICONDUCTORS

D1–D6—1N4148 diode, or equiv.
LED1, LED2—Light-emitting diode, red
Q1, Q2—2N3904, NPN, RF amplifier transistor
IC1—74C14 CMOS hex Schmitt inverter, integrated circuit
IC2, IC3—78L05 +5-volt regulator, integrated circuit

RESISTORS

(All fixed resistors are ¼-watt, 5% units.)
R1—100,000-ohm
R2—470-ohm
R3—120,000-ohm
R4—10,000-ohm, PC-mount, potentiometer
R5—4700-ohm
R6—33,000-ohm
R7–1000-ohm, PC-mount, potentiometer
R8—2700-ohm
R9—1000-ohm

CAPACITORS

C1—0.001-µF, Mylar
C2–C8—4.7-µF, 35-WVDC, aluminum electrolytic
C9—22-µF, 16-WVDC, tantalum
C10—1.0-µF, 16-WVDC, tantalum
C11, C12—4.7-µF, 10-WVDC, tantalum

ADDITIONAL PARTS AND MATERIALS

B1—+12-volt battery (see text)
S1—Single-pole, single-throw, toggle switch
PC universal prototyping board (RadioShack 276-168), 8 AA-cell holder (RadioShack 270-387, or equiv.), battery snap (RadioShack 270-324, or equiv.) phono jack, copper foil, etc.

and capacitor voltage multiplier chain with some *tricks* added in. Integrated circuit IC1 contains six CMOS Schmitt inverters with IC1-a wired as an astable squarewave oscillator. The oscillation frequency is set by R1 and C1 to about 65 kHz. The remaining five Schmitt inverter sections are wired in parallel to form a power amplifier. This combination of Schmitt triggers delivers squarewave current to the diode-capacitor multiplier string (D1-D6 and C2-C7).

The DC/DC voltage-multiplier converter would output about 45 volts were it not for transistors Q1 and Q2. Those semiconductors and their associated circuitry form an adjustable DC-voltage regulator wherein Q1 serves as an error amplifier. Transistor Q1 compares the voltage at wiper of

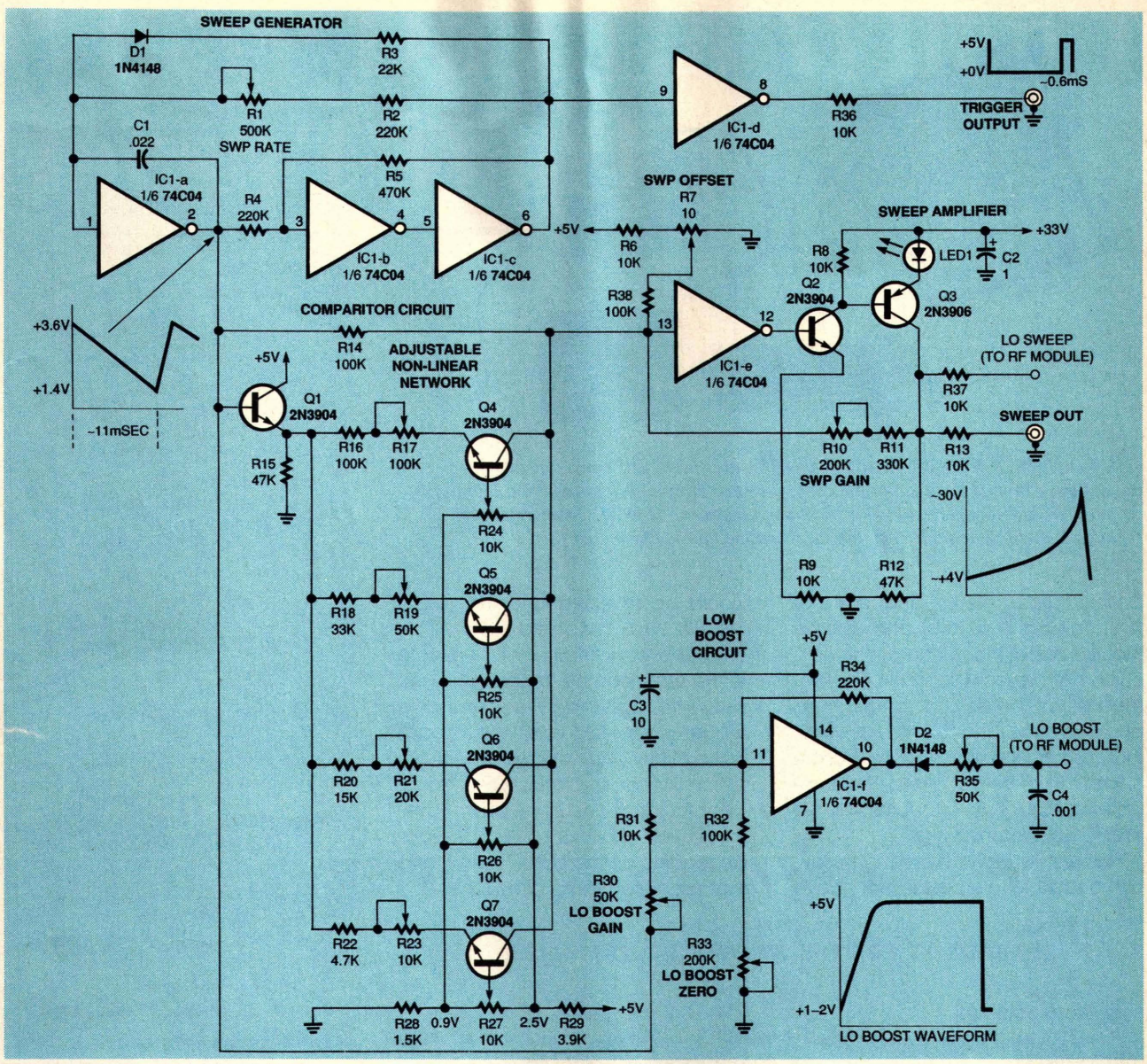

FIG. 4—SCHEMATIC DIAGRAM for the sweep-circuit module. This module provides the "curvy" sweep voltage for the first-converter local oscillator to make the frequency sweep (radio dial) linear, and also provides the oscilloscope's trigger signal.

R4 to the reference pedestal of its own base-emitter junction and LED1 in the emitter circuit (which is about 2.4-volts DC equivalent).

In operation, an error signal is amplified by Q1 which controls series-pass transistor Q2 (Fig. 3). Thus, a variable voltage is supplied to power IC1 as needed to control the squarewave amplitude that drives the voltage multiplier in the first place! For example, if for some reason the +33-volt level would tend to drop, Q1 would conduct less and its collector voltage would rise. This would increase the voltage powering IC1, which in turn would make the squarewave drive to the multiplier chain increase, preempting the precipitating voltage drop! Should the +33-volt level increase, the opposite occurs.

The nominal value of +33-volts DC is adjusted by trimmer R4 and that value holds over the useful range of the battery voltage (+13 when *fresh* to +10 volts when *dead*). Light-emitting diode LED1 will glow rather dimly, but light-emitting diode LED2, which is in the supply path to regulator IC2, glows brightly and serves as the HSA's POWER indicator.

The sweep circuit. The schematic diagram for the sweep circuit is shown in Fig. 4. A CMOS hex inverter, IC1, has four sections wired as operational amplifiers. Section IC1-a is configured as an integrator circuit. With capacitor C1 connecting from the inverter's output to input, a linear voltage ramp will appear at the output, pin 2, for a step change in the DC voltage (astable squarewave) applied to a resistor on input pin 1.

Inverters IC1-b and IC2-c are wired as a comparator circuit, which is not a linear system. The inverters here have outputs that are either high or low and *nothing* in-between. This is assured by the positive feedback connection via R4 and R5. Thus, a switched waveform at pin 6 of IC1-c will either be +5 volts or 0 volts.

To visualize operation of the com-

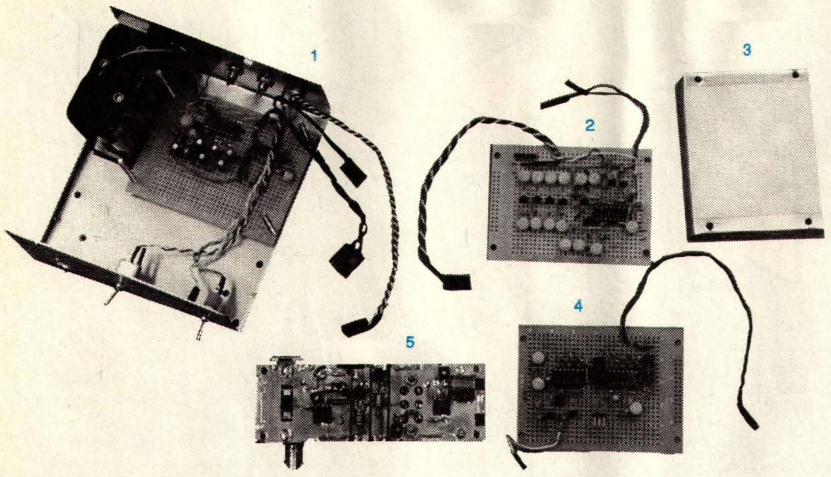

THE FOUR MAJOR ASSEMBLIES of the HSA are: 1–DC/DC converter and regulators, which is mounted in the case, 2–sweep circuit, 4–log amplifier, and 5–RF circuit. The aluminum shield (3) is positioned between the DC/DC converter and regulators and log amplifier assemblies when the unit is assembled.

parator circuit, assume that pin 6 of IC1-c is high (+5 volts) and assume that resistor R4 in the comparator circuit is not present (open circuit). That means that the input at pin 3 is high, and thus pins 4 and 5 are low (0 volts), thus assuring the high condition at pin 6, which is where we started. The comparator made up of sections IC1-b and IC1-c is *latched* high.

Had we started with pin 6, IC1-c low, all voltage levels described above would be reversed and the circuit would be latched low. The changeover from one latched state to the other can be forced by driving pin 3 to approach mid-voltage range, or about 2.5 volts. With R4 back in the circuit and ramp voltages from IC1-a pin 2 driving it, the 2.5-volt condition at pin 3 occurs at ramp waveform levels of about 1.3 and 3.7 volts, depending on the state of pin 8 and the associated ramp direction.

PARTS LIST FOR THE SWEEP CIRCUIT MODULE (Fig. 4)

SEMICONDUCTORS

IC1—74C04 or CD4069, CMOS hex inverter
Q1, Q2, Q4–Q7—2N3904, NPN, RF amplifier transistor
Q3—2N3906, PNP transistor
D1, D2—1N4148, fast-switching, silicon diode (or equiv.)
LED1—Light-emitting diode, red

RESISTORS

(All resistors are ¼-watt, 5% units unless otherwise noted.)
R1—500,000-ohm PC-mount trimmer potentiometer
R2, R4, R34—220,000-ohm
R3—22,000-ohm
R5—470,000-ohm
R6, R8, R9, R13, R31, R36, R37—10,000-ohm
R7, R23–R27—10,000-ohm PC-mount trimmer potentiometer
R10, R33—200,000-ohm PC-mount trimmer potentiometer
R11—330,000-ohm
R12, R15—47,000-ohm
R14, R16, R32, R38—100,000-ohm
R17-100,000-ohm PC-mount trimmer potentiometer
R18—33,000-ohm
R19, R30, R35—50,000-ohm PC-mount trimmer potentiometer
R20—15,000-ohm
R21—20,000-ohm PC-mount trimmer potentiometer
R22—4700-ohm
R28—1500-ohm
R29—3900-ohm

CAPACITORS

C1—0.022-µF, Mylar
C2—1.0-µF, 35-WVDC, tantalum
C3—10-µF, 10-WVDC, tantalum
C4—0.001-µF, ceramic disc

ADDITIONAL PARTS AND MATERIALS

PC universal prototyping board (RadioShack 276-168); phono jacks (2 required); 5-pin 0.1-in. centers, right-angle male connector; 6-pin 0.1-in. centers, female connector; wire, solder, etc.

PARTS LIST FOR THE LOG AMPLIFIER MODULE (Fig. 5)

SEMICONDUCTORS

IC1, IC2—74C04 or CD4069, CMOS hex inverter, integrated circuit
Q1, Q2—2N3904, NPN, RF amplifier transistor

RESISTORS

(All fixed resistors are ¼-watt, 5% units.)
R1—10,000-ohm
R2—20,000-ohm, PC-mount, potentiometer
R3—27,000-ohm
R4—68,000-ohm
R5, R8, R11, R14, R17, R20—39,000-ohm
R6, R9, R12, R15, R18, R22—150,000-ohm
R7, R10, R13, R16, R19, R23—100,000-ohm
R21, R25—5100-ohm
R24, R31—2200-ohm
R26—10,000-ohm, PC-mount, potentiometer
R27—3900-ohm
R28—5000-ohm, PC-mount, potentiometer
R29—2700-ohm
R30—1000-ohm

CAPACITORS

C1—4.7-µF, 10-WVDC, non-polarized, aluminum, electrolytic
C2—18-pF, ceramic disc
C3—2.2-µF, 10-WVDC, non-polarized, aluminum, electrolytic
C4—100-pF, ceramic disc
C5—0.01-µF, Mylar
C6—10-µF, 10-WVDC, tantalum

ADDITIONAL PARTS AND MATERIALS

PC universal prototyping board (Radio Shack 276-168), Connector, 3-pin, male, 0.1-in. centers, right angle, phono jack, wire, solder, etc.

The ramp motion is caused by pin 6 of IC1-c driving integrator inputs via R1 and R2 or D1 and R3. The ramp voltages corresponding to crossover are determined by the ratio of R5/R4. Thus, for the pin 6 high condition we began with, the integrator's pin 2 voltage is decreasing, and when it hits about 1.3 volts, the comparator pair of IC1-b and IC1-c changes state. This drives pin 6 low, and the integrator output ramps upwards. When it hits approximately 3.7 volts, the comparator pair again changes state, and the process begins over. The repetitive waveform

GET HERE.

FREE One Year Subscription of Electronics Now When You Enroll in Any CIE or World College Program!

LEARN A SKILL YOU ENJOY... ...THEN FIND A JOB THAT HAS A FUTURE.

Everyone has to start somewhere.

As 150,000 CIE graduates have discovered, independent-study from The Cleveland Institute of Electronics can get you were you want to be. *In a secure, financially rewarding, exciting career field of your choice.*

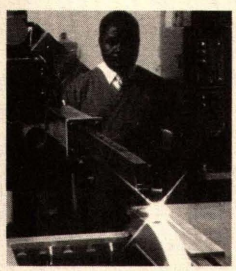

Industrial Robotics

Since 1934, CIE has been on the forefront of an ever expanding technological revolution.

ment. CIE's curriculum is unique from other independent-study schools in the respect that we not only provide hands-on training utilizing today's technology we also instill the knowledge and understanding of why technology works the way it does. This is the foundation upon which every CIE graduate can trace their success back to and in which CIE's reputation as a quality learning facility is based on.

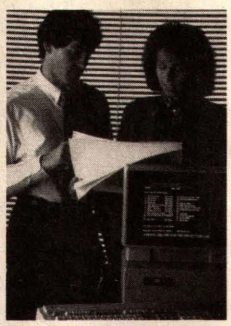

Project Engineer

Independent study is not for everyone. But, if you have the desire, the basic intellect and the motivation to succeed, CIE can make it happen. Our learning program is patented and each lesson is designed for independent study while our instructors are available to assist you whenever you feel you need help. In fact, CIE's curriculum is so well respected many Fortune 1000 companies utilize it for their own employees.

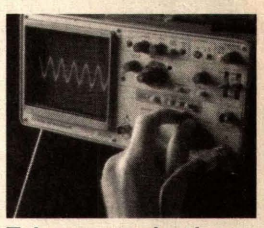

Telecommunications

CIE offers personalized training to match your background with over ten career courses, an Associate Degree Program and a Bachelor Degree Program through our affiliation with World College. And every CIE graduate got started in a successful career the same way you can...by sending for your free CIE course catalog and judging for yourself if CIE's for you.

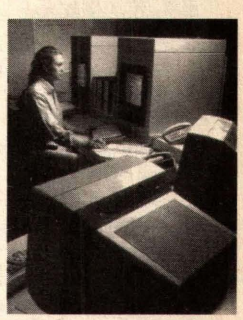

Computer Programming

START HERE...

Electronics

Back then it was radio and TV, today it's computer technology, programming and the electronics that make it all possible. Today and yesterday's similarities are uncanny... *Employers are looking for qualified applicants to hire and having a hard time finding them.*

Students at CIE receive the training and the education needed to get hired and to succeed in challenging fields such as computer programming, robotics, broadcast engineering, and information systems manage-

YES! Please send me more information on:

- ☐ CIE's Associate Degree Program
- ☐ CIE's Computer Programming Course
- ☐ CIE's 12 Career Courses
- ☐ World College's Bachelor Degree Program

AE 90

Name _____

Address _____

City _____

State _____ Zip _____

Phone: _____

Check for G.I. Bill Details
☐ Active Duty ☐ Veteran

CIE

It's More Than Just Training... ...It's an Education

1776 East 17th Street
Cleveland, OH 44114
(216) 781-9400 • 1-800-243-64

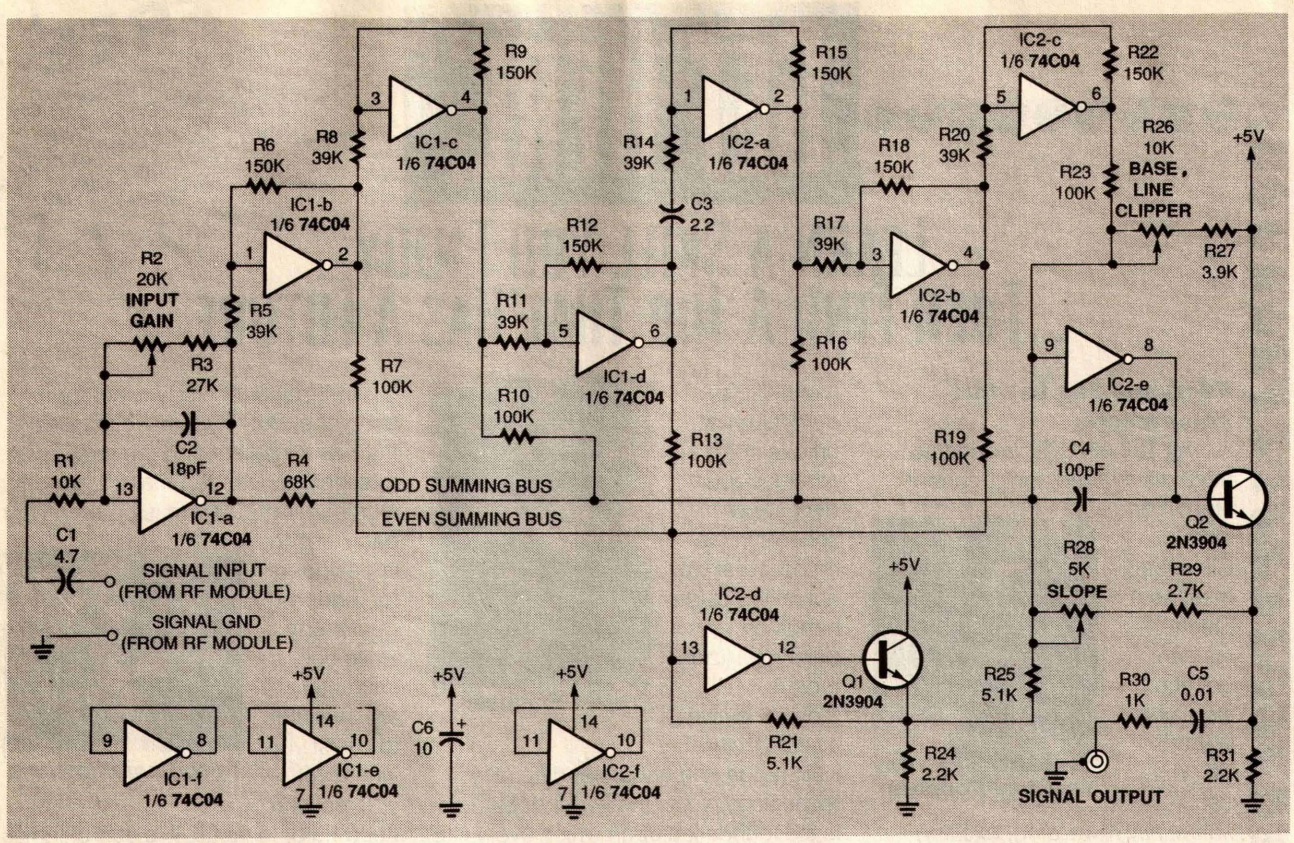

FIG. 5—SCHEMATIC DIAGRAM for the log amplifier module. The log amplifier provides the accurate non-linear transfer function needed to make the oscilloscope's graticule read out in dB instead of linear voltage.

MATERIALS LIST FOR THE HSA CASE ASSEMBLY

1—3 × 5 × 5⅞ metal cabinet (RadioShack 270-253)
4—6-32 × 2-in. machine screws
23—6-32 × ¼-in. hex nuts
4—Plastic or metal spacers (see text)
4—#6 outside star washers
4—¼-in. × 1¾-in. plastic or metal standoffs, 4-40 thread
12—4-40 × ¼-in. cap head screws
1—Sheet of 0.010 to 0.020-in. aluminum for formed shield cover (see text)
1—Sheet of copper tooling foil, 36 gauge (craft store)
1—5-in. brass (or comparable) 1/16-in dia. rod stock (hobby shop)
4—1/16-in. metal wheel collars w/set screws (hobby shop)
2—Decorative beads, 1/16-in. bore for pull knobs (craft store)
2—6-32 × ¼-in. machine screws (to mount slide switch)
2—6-32 × ⅝-in. machine screws (to mount slide switch)
2—4-40 × ⅜-in. threaded spacers
1—¼-in. × ¾ × 2¼-in. wood or foam spacer block
1—¾-in. × 2½-in. double-stick Velcro (to mount battery holder)

at pin 2 is depicted in Fig. 4 as an asymetrical triangular wave. It's a fast positive ramp followed by a slower negative going ramp. The latter is what's ultimately used to sweep the local oscillator's first converter.

In all the above, the waveform at pin 8 is a rectangular waveform which is buffered by inverter IC1-d. This waveform is the trigger output used to initiate oscilloscope sweep on the negative going slope of the pulse. This sweep is time coincident with the beginning of the slow negative ramp at pin 2 of IC1-a.

The triangle waveform voltage at IC1-a, pin 2 is about 2.4 volts peak-to-peak. Varactor D1 in the first converter local oscillator (Fig. 2) requires about a 28-volt swing to effect a local oscillator frequency change of about 100 MHz. Thus, the limited ramp levels at pin 2 of IC1-a (Fig. 4) must be amplified to much higher levels. Not only that, but the change in frequency of the first converter is non-linear with respect to varactor D1's bias drive, so the drive shape must be "bent" into shape. Those dual requirements are met with the sweep amplifier and adjustable nonlinear network in Fig. 4.

The sweep amplifier assembly consists of IC1-e, Q2, and Q3, which are configured as an operational inverter whose basic gain is established by the ratio of three resistors: (R10 + R11) ÷ R14. Gain is adjustable by adjusting trimmer R10. The output transistor, Q3, is powered from the +33-volt line, so it is capable of swinging the high voltage needed by varactor D1 (Fig. 2). The sweep voltage at Q3's collector and SWEEP OUT jack is shown in Fig. 4. Remember, the first converter local oscillator needs a "curvy" sweep voltage to make the frequency sweep ("radio dial") linear.

Sweep voltage shaping is obtained by "piecewise linear waveform shaping" as brought about by the circuitry of Q1, Q4 through Q7, and their related components. Given that the ultimate output voltage at Q3 collector is governed by the sweep drive to IC1-e's input, all that's needed is to vary the sweep drive dynamically in a nonlinear manner. In effect, what's needed is to equivalently "lower" the value of R14 during the driving ramp time. However, there is no resistive val-

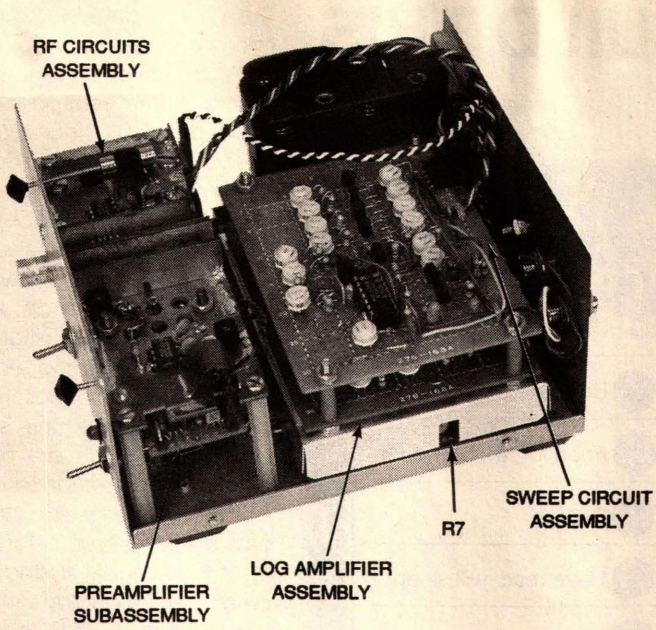

RIGHT-SIDE VIEW OF THE HSA shows part of the preamplifier subassembly under the RF circuits assembly. The small slot cut in the shield that covers the DC/DC converter and regulators permits adjustment of potentiometer R7, which sets the V+ voltage.

ue change. Rather, transistors Q4 through Q7 sink more and more current from the IC1-e input node as a sweep progresses, simulating what appears to be lowered resistance in R14.

Transistor Q1 buffers the ramp waveform at IC1-a, pin 2, and drives the four resistive networks shown in Fig. 4. Transistors Q4 through Q7 have base biases adjusted by their individual base-voltage-divider potentiometers, R24 through R27. Emitter currents (and collector currents) in those transistors can only flow for Q1 emitter voltage levels falling lower than the emitter voltages of Q4 through Q7. The magnitude of those currents is then controlled by resistors R16 through R23. As Q1's emitter ramp voltage sweep moves in a negative going direction, and with the transistor base biases properly adjusted, transistors Q4 through Q7 sequentially come into conduction and progressively sink more current from the IC1-e input node. As that sequence takes place the sweep output voltage at Q3's emitter increases nonlinearly. The exact shape of the resulting waveform is easily adjusted (tuned) during the HSA alignment.

LO boost. Now for that elusive LO-boost function mentioned earlier. During the development of the HSA, several RF modules were built and tested. In each, the amplitude response rolled off about 5 dB from about 30 MHz to zero. The output display suffered response flatness at the lower third of the frequency sweep. This problem was fixed by time-varying the local oscillator power level in the first converter. Thus, from sweep initiation to about one-third the frequency range, the local oscillator power of the first converter is adjusted "on the fly" to yield an overall flat frequency response. The circuitry of IC1-f and associated adjustment trimmers perform that mission, and those tuneup details are discussed later.

The log amplifier module. A log amplifier module output is the mathematical logarithm of the input signal. The log amplifier displays a diminishing gain as its input signal increases. A good log amplifier has an accurate "log transfer characteristic". The log amplifier function in the HSA is accomplished with 74C04 CMOS hex inverter logic circuits operating in linear/limiting fashion (See Fig. 5).

The HSA transfer function will be set to 100 mV per 10 dB during alignment. Then a 10 dB increase in input signal will cause a 100 mV output increase. So does the next 10 dB. And the next. And so on. The HSA has a nominal 60 dB log amplifier. This means that the output changes only about 0.6 volt for an input signal range of 1000:1 (60 dB).

The log amplifier module schematic diagram shown in Fig. 5 is a configuration known as a "piecewise linear synthesized log amplifier". This means that the overall 60-dB transfer is "constructed" of individual short quasi-linear transfer segments strung end to end to look like a smooth log function. While that may sound like a "bumpy-curve" technique, the resulting circuit behavior is actually very smooth. In fact, the log linearity of the HSA circuit is better than ±1 dB over the entire range.

Seven sections from two hex inverter ICs are connected as amplifiers in series. Except for the first stage (IC1-a), all stages have a fixed voltage gain of about 10 dB. This is primarily established by the 150,000-ohm and 39,000-ohm resistors around each stage. The 7-stage amplifier has over 70 dB of gain. A very small input signal causes a large output signal at the last stage (IC2-c). This last stage quickly saturates with increasing input. More input causes the next-to-the-last stage to similarly saturate. Eventually all the preceding stages saturate.

Each interim amplifier stage drives two loads. One load is the next amplifier stage. The other load is a 100,000-ohm resistor connected to a summing

(Continued on page 80)

PARTS SUPPLIERS

DC Electronics
PO Box 3203
Scottsdale, AZ 85257-3293
Tel: 800-467-7736

Digi-Key Corp.
701 Brooks Ave So.
Thief River Falls, MN 56701-0677
Tel: 800-344-4539

Electronix Express
365 Blair Road
Avenel, NJ 07001
Tel: 800-972-2225

Hosfelt Electronics Inc.
2700 Sunset Blvd.
Steubenville, OH 43952-1158
Tel: 800-524-6464

Ocean State Electronics
PO Box 1458
6 Industrial Drive
Westerly, RI 02891
Tel: 401-596-3080

BUILD THIS

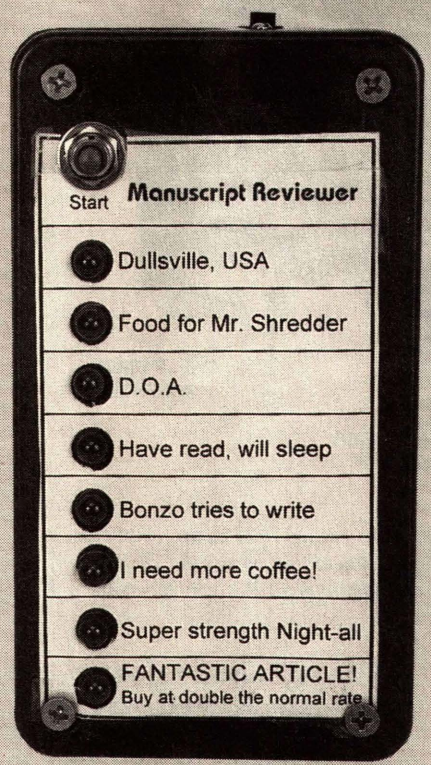

Executive Decision Support System

Here's a great gift for anyone who makes major decisions.

JAMES EDWARDS

Let's face it—the world is getting more and more complicated every day. At the grocery store, it's aisles of breakfast cereals. For investors, there are more mutual funds than stocks to choose from. And don't even think about trying to select a computer without considering a mind-numbing range of configurations!

If you feel that this is all too much to deal with, we agree. And we want to help. *Ergo*, the Executive Decision Support System (or EDSS). Based on little known but indisputable scientific principles, the device can quickly and easily help you resolve all the troubling issues of your life. Can't decide what to eat for lunch? EDSS can help. Can't decide where to go to college? No sweat for EDSS. Can't decide whether to pop the question to your significant other? Easy. Just ask EDSS beforehand what the answer will be.

As useful as such a device can be in your own life, it also makes a great gift—one that's both inexpensive and easy to build. Not only that, but the device can be easily configured to cover a wide range of different types of decisions. So you might want to build several to have on hand, and customize them as the need arises.

For example, suppose your company is opening a branch office and your buddy John is being promoted to a management position in the new office. As you bid John farewell, you explain that in his new position he'll need to make a lot of important decisions. And, because you want the new office to do well, you certainly don't want to leave those decisions entirely in his hands! Therefore you give him an EDSS labeled as shown in Fig. 1. Now whenever John needs to make an important decision, he'll have all the help he needs.

The technology behind this wizardry is Motorola's popular 68HC705K1 microcontroller, a favorite of **Electronics Now** readers. We've purposely kept the cost low, used easy-to-find parts, and have made arrangements to supply circuit boards and preprogrammed microcontrollers. So you've got no excuse! (By the way—the scientific principle we referred to above is known as *random-number generation*.)

How to make important decisions.

The project centers around a small microcontroller (a 68HC705K1), eight LEDs, a power switch, and a start switch. On the front panel of the unit, beside each LED, is a word or phrase describing a potential decision outcome. When you apply power to the circuit, the microcontroller initializes. That process involves reading the states of two jumpers, which determine operating mode. After determining mode, the microcontroller blinks out a test sequence on the eight LEDs, and sounds the buzzer to let you know the unit is operating properly. All lights are extinguished after the test sequence completes.

To begin the decision-making process, quickly press the start button. The lights then blink in a random pattern. Eventually the display settles down so that a single LED is lit; that LED represents the outcome of the decision-making process. Repeat the process as often as you like by pressing start.

To increase flexibility, EDSS has three modes of operation that are set using a pair of jumpers; those jumpers are implemented using a pair of 0.1-inch header blocks. Mode 0 provides truly random output; any of the eight LEDs may light up. Mode 1 *always* ends on LED8. Mode 2 *never* lights LED8.

The mode is determined on power-

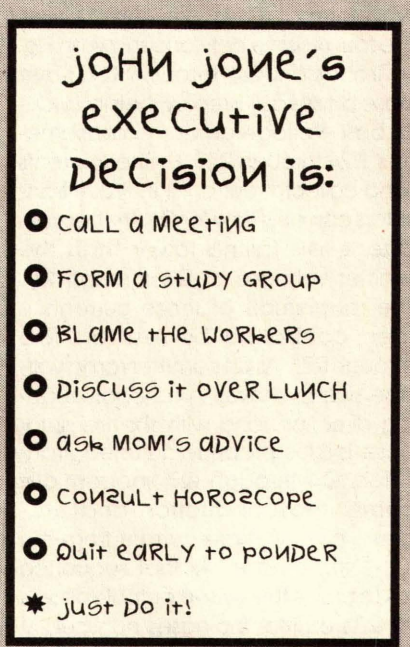

Fig. 1. The Executive Decision Support System can be easily customized by changing the front-panel label. One possible example is shown here; others can be found as part of the EDSS.ZIP file on the Gernsback BBS.

up. If you set jumpers for Mode 1, but hold the start button when turning on the power, it actually comes up in Mode 0. Now give the EDSS to someone. That person quickly figures out that the answer is always the same. Of course, you insist that it's not, cycle the power with your finger on the Start button, and prove that it's not. Then you power down, return the unit to the "victim," and let him or her try again. It's positively devious!

Note that the trick only works when you start in Mode 1. If you start in Mode 2, the LED is physically disconnected from the circuit, so the EDSS cannot revert to either of the other modes.

The circuit. As shown in Fig. 2, the EDSS consists of a single microcontroller, a Motorola 68HC705K1. The microcontroller contains 32 bytes of RAM (for variable storage), 504 bytes of ROM (for code storage), and ten digital I/O ports, all in a 16-pin package. Although compact in size, it has plenty of resources for this application.

The 68HC705K1 drives nine outputs and reads three inputs. The outputs are the eight LEDs and a low-current buzzer, which emits a short beep whenever a new LED turns on. The three inputs are start switch S1 and two mode-select jumpers.

Careful readers may note that the circuit contains two more I/O devices (12) than the microcontroller has I/O lines (10). Close examination of the circuit yields the cause of the apparent discrepancy.

Pin 4 of the microcontroller is the interrupt request (IRQ) line. IRQ is a dedicated input line that, when temporarily shorted to ground via S1, tells the microcontroller to execute a special section of code known as an *interrupt service routine,* or ISR. In our application, the ISR starts the LED blinking sequence. By using that pin, one of the "regular" I/O lines is spared for other uses.

Microcontroller port PA3 (pin 8) does double duty. In Mode 2, LED8 never lights. We set Mode 2 by connecting JU2 to ground (position B). That in turn grounds PA3, which would otherwise be high. During power-up initialization, one of the first things the firmware in the microcontroller does is examine the state of PA3. It can only be high if the LED is connected via the

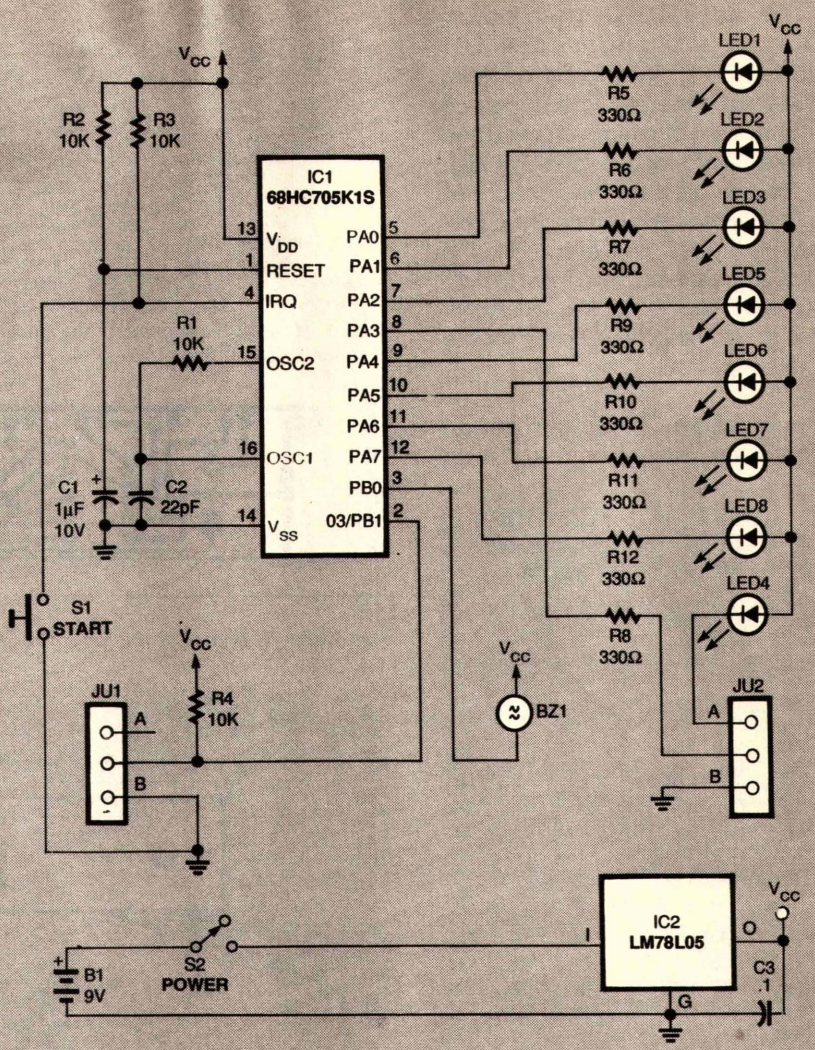

Fig. 2. The circuit centers around Motorola's popular 68HC705K1 microcontroller. Although fairly simple, it has power to spare for our application.

appropriate pins of JU2 (position A). If it is high, the EDSS enters Mode 0 or Mode 1, depending on the state of JU1 and S1, as described above. On the other hand, if the microcontroller sees a low, it puts the unit in Mode 2, and that's that. The appropriate jumper settings for each mode are summarized in Table 1.

The microcontroller has five other pins used for "housekeeping." Pins 13 and 14 supply the device with power and ground, respectively, and pin 1 is the reset line. Whenever reset goes low, the microcontroller restarts itself in an organized manner. For our purposes, the only reset required is on power-up.

The lines labeled OSC1 and OSC2, in conjunction with resistor R1 and capacitor C2, generate a clock signal that sequences events inside the microcontroller. The RC clock is not as accurate as a crystal clock, but it is significantly cheaper and more than accurate enough for our application.

Circuit power is supplied by a 9-volt battery. The battery drives a standard LM78L05 voltage regulator, which provides 5-volt circuit power. Capacitor C3 filters the regulator's output.

TABLE 1—JUMPER SETTINGS

Mode	JU1	JU2
Mode 0: Random Output	B	A
Mode 1: Always the last LED	A	A
Mode 2: Never the last LED	A or B	B

Software. The software that controls the EDSS must be "burned" into the microcontroller. If you have the appropriate hardware, you can burn the IC yourself. The object code is stored

in a file called EDSS.ZIP, which is available on the Gernsback BBS (516-293-2283). The Zip file contains an S-record file, a readme, and some sample labels and templates you can use (with Word for Windows 2 or later versions) to dress up the front panel. You can also simply purchase a preprogrammed IC, as explained in the Parts List. Even if you don't want to burn your own microcontroller, you might want to download the Zip file for the label templates.

Construction. The main design goals of this project were that it be inexpensive as well as quick and easy to build. Thus we used very common components, most of which are available at RadioShack.

Most components mount on a single PC board, as shown in Fig. 3 (the parts-placement diagram) and Fig. 4 (the assembly diagram). The PC board is designed to slide into containment rails molded into the sides of the recommended project enclosure. This slide-in design greatly reduces assembly time because no additional mounting hardware is required.

With that mounting scheme, the board stands perpendicular to the enclosure's display face. Consequently, the LEDs must be bent at a right angle relative to the surface of the PC board. Lead length both before and after the bend is critical; if the leads are too long the enclosure cover will not fit, but if they're too short the board will not mount securely. You'll want approximately ⅛-inch be-

(Continued on page 80)

PARTS LIST FOR THE EXECUTIVE DECISION SUPPORT SYSTEM

R1–R4—10,000-ohm, ¼-watt, 5% resistor
R5–R12—330-ohm, ¼-watt, 5% resistor
C1—1.0-µF, 10-volt, tantalum capacitor
C2—22-pF, polyester capacitor
C3—0.1-µF, ceramic-disc capacitor
IC1—68HC705K1S microcontroller, integrated circuit
IC2—LM78L05, +5-volt, 100-mA regulator, integrated circuit
LED1–LED8—Light-emitting diodes, red
BZ1—9-volt piezoelectric buzzer (Radio Shack 273-074 or equivalent)
B1—9-volt transistor battery
S1—Normally-open, momentary, pushbutton switch
S2—SPST toggle or slide switch, panel mount
JU1, JU2—0.1-inch male PCB mount 3-pin connectors
Enclosure (RadioShack 270-221 or equivalent), PC board, 0.1-inch female header blocks, 16-pin DIP socket, wire, solder, etc.

Note: The following are available for purchase from: Aurora Software, PO Box 080133, Rochester, MI 48309-0133: pre-programmed 68HC05K1CP microcontroller ($12.78); 360k (5.25-inch) or 1.44M (3.5-inch) PC disk containing S-record file of the software for IC1 ($6). Please add $2 shipping and handling for all orders and (sorry) no Michigan orders can be accepted. An etched, drilled, and tinned PC board for the project is available for $4.50 from Chelco Electronics, 61 Water Street, Mayville, NY 14757. NY residents must add 7% sales tax.

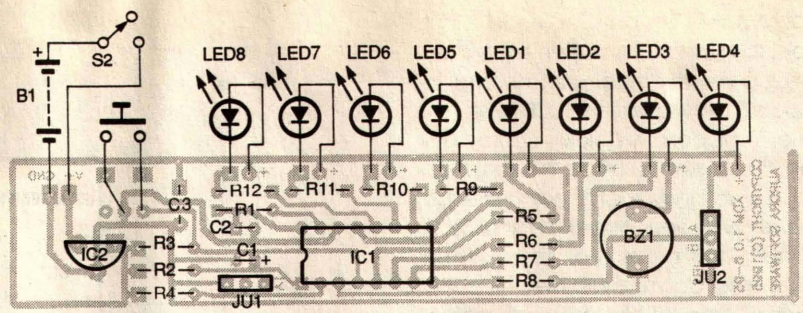

Fig. 3. Here's the component placement diagram. The LED lead length is critical, so test one LED before soldering the rest to the board.

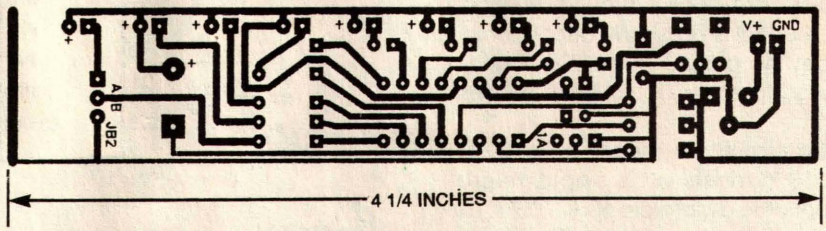

Here's the PC board for the Executive Decision Support System. It is shown full sized.

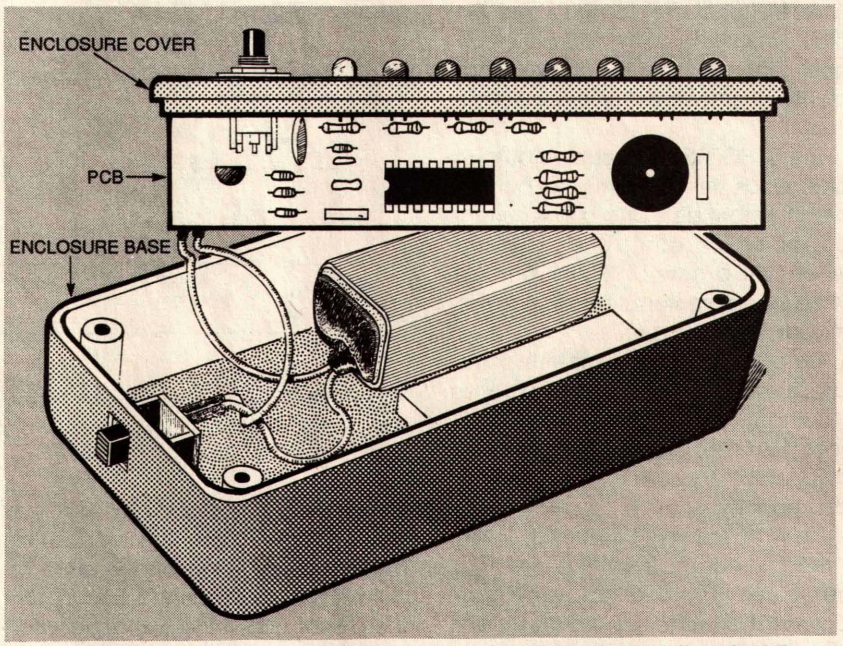

Fig. 4. The recommended case for the project has molded rails that allow the PC board to slide in to its permanent mounting spot. Use the left-most set of moldings to allow room for the 9V battery.

RETAILERS THAT SELL OUR MAGAZINE MONTHLY

Alaska

Frigid North Co.
1207 W. 36th Avenue
Anchorage, AK 99503

Arizona

Dalis Electronics
2829 E. McDowell Road
Phoenix, AZ 85008

California

California Electronics
221 N. Johnson Ave.
El Cajon, CA 90202

Signal Electronics
22307 Ocean Avenue
Torrance, CA 90505

Ford Electronics
8431 Commonwealth Avenue
Buena Park, CA 90621

All Electronics
14928 Oxnard Street
Van Nuys, CA 91411

Gateway Electronics of CA
9222 Chesapeake Drive
San Diego, CA 92123

Mac's Electronics
191 South "E" Street
San Bernardino, CA 92401

Electronics Warehouse
2691 Main Street
Riverside, CA 92501

Orvac Electronics
1645 E Orangethorpe Ave.
Fullerton, CA 92631

Sav-On Electronics
13225 Harbor Blvd.
Garden Grove, CA 92643

Marvac Dow Electronics
980 S. A Street
Oxnard, CA 93030

Kandarian Electronics
1101 19th Street
Bakersfield, CA 93301

Whitcomm Electronics
105 W. Dakota #106
Clovia, CA 93612

Marvac Dow Electronics
265-B Reservation Road
Marina, CA 93933

Minuteman Electronics
37111 Post St., Suite 1
Fremont, CA 94536

HCS Electronics
6819 S. Redwood Drive
Cotati, CA 94931

Halted Specialties Co.
3500 Ryder Street
Santa Clara, CA 95051

Metro Electronics
1831 J Street
Sacramento, CA 95814

The Radio Place, Inc.
5675-A Power Inn Road
Sacramento, CA 95824

HSC Electronics
4837 Amber Lane
Sacramento, CA 95841

Colorado

Gateway Electronics of CO
2525 Federal Blvd.
Denver, CO 80211

Centennial Electronics
2324 E. Bijou
Colorado Sps., CO 80909

Connecticut

Signal Electronics Supply
589 New Park Avenue
W. Hartford, CT 06110

Cables & Connectors
2198 Berlin Turnpike
Newington, CT 06111

Electronic Service Prod.
437 Washington Avenue
North Haven, CT 06473

Florida

Sanyca Electronics
596 NW 99th Ct.
Miami, FL 33172

Georgia

Norman's Electronics, Inc.
3653 Clairmont Road
Chamblee, GA 30341

Idaho

The Current Source
5159 Glenwood
Boise, ID 83714

Illinois

Tri State Elex
200 W. Northwest Hwy.
Mt. Prospect, IL 60056

Maryland

Mark Elec. Supply Inc.
5015 Herzel Place
Beltsville, MD 20705

Amateur Radio Center
1117 West 36th Street
Baltimore, MD 21211

Massachusetts

U-Do-It Electronics
40 Franklin Street
Needham, MA 02194

Michigan

Purchase Radio Supply
327 East Hoover Avenue
Ann Arbor, MI 48104

Norwest Electronics
33760 Plymouth Road
Livonia, MI 48150

The Elec. Connection
37387 Ford Road
Westland, MI 48185

Elec. Parts Specialists
711 Kelso Street
Flint, MI 48506

Minnesota

Acme Electronics
224 Washington Avenue N.
Minneapolis, MN 55401

Missouri

Gateway Electronics Of MO
8123-25 Page Blvd.
St. Louis, MO 63130

William Elec & Ind Supply
803 Davis Blvd.
Sikeston, MO 63801

New Jersey

Lashen Electronics Inc.
21 Broadway
Denville, NJ 07834

New York

Sylvan Wellington Co.
269 Canal Street
New York, NY 10013

R&E Electronics
4991 Rt. 209
Accord, NY 12404

Unicorn Electronics
Valley Plaza
Johnson City, NY 13790

Ohio

Philcap Electronic Suppliers
275 E. Market Street
Akron, OH 44308

Oregon

Norvac Electronics
7940 SW Nimbus Avenue
Beaverton, OR 97005

Pennsylvania

Business & Computer Bookstore
213 N. Easton Road
Willow Grove, PA 19090

Texas

Mouser Electronics
2401 Hwy. 287 N
Mansfield, TX 76063

Electronic Parts Outlet
17318 Highway 3
Webster, TX 77598

Washington

Amateur Radio Supply Co.
5963 Corson Ave., Ste 140
Seattle, WA 98108

Wyoming

Chris Supply
2007 S. Douglas Hwy., Ste. C
Gillette, WY 82716

If you'd like to sell our magazine in your store, please circle 210 on Free Information Card.

ALL ABOUT
Removable Media Drives

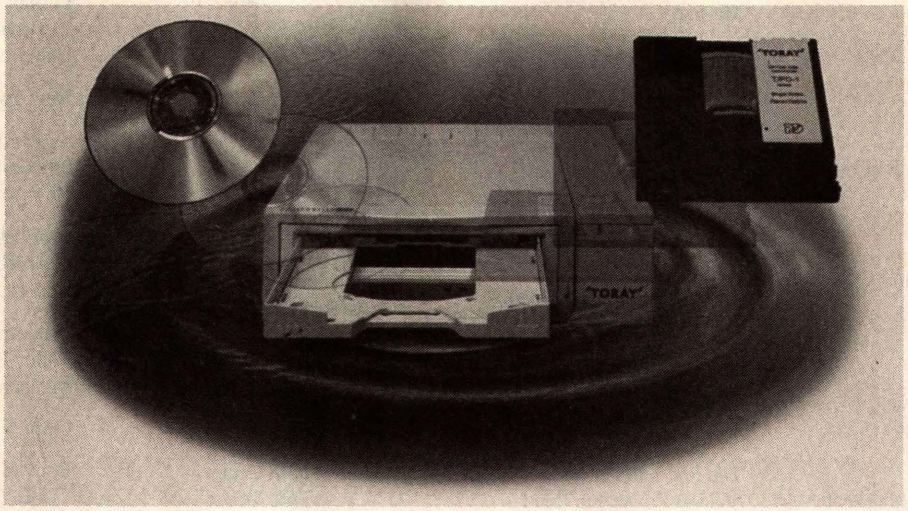

Whether for data backup or exchange, removable-media-drive technology is evolving to meet the needs of today's—and tomorrow's—user.

TJ BYERS

Like a good entree, each ingredient of a computer has to blend with the others if it's to work properly. If even one component is out of balance, the flavor will be off.

Now consider the following recipe: Stir together an Intel Zappa Tritron motherboard with a Pentium 133-MHz CPU, 256K cache, and 16MB EDO RAM; Matrox 1.6GB EIDE hard-disk drive; Teac 1.44MB floppy drive; Diamond Stealth 64 with 2MB RAM; 17-inch ViewSonic monitor with 0.26mm dot pitch; Sound Blaster 16 sound card; Toshiba 6X CD-ROM; Zoltrix 28.8 kbps fax/modem; Logitech Mouseman; Microsoft Windows 95 keyboard; Labtec 100W amplified speakers; and an Epson ink-jet color printer.

From all appearances, this is a gourmet system made with only the finest ingredients. That is, except for one: Check out the 1.44MB floppy drive. Is that supposed to be your backup device? If so, it's going to leave a bad taste in your mouth.

Well, you might ask, what's the alternative? The answer is that there are plenty of them. In fact, presently there are four technologies vying for the title of *de facto* removable-media standard: floppy disk, hard (rigid) disk, streaming tape, and optical storage. This article looks at the most popular removable-media products on the market today, and how they might fit your needs and your lifestyle.

Back it up! The main use for removable storage is backup. For that application it probably won't matter whether or not the particular format you choose is common in other computers. As long as you can store lots of data and reliably retrieve it, you should be happy.

The ideal candidate for this job should be reliable, inexpensive, and durable. While speedy access to the data is desirable, it's not a high priority. Above all, though, the storage system must be easy to use. No matter what else the backup system has going for it, if you have to do more than insert a blank cartridge and click an icon, chances are you won't back up as often as you should. The two competing media for the "ease-of-use championship" are recordable CD-ROMs and streaming tape.

On the road again. Another use for removable storage is data exchange. While the use of local- and wide-area networks (specifically the Internet) has largely reduced the need to exchange data using a portable media, there's still a place for it. That is particularly true of large files, generally those in excess of 5MB, that would tie up network resources for long periods of time (typically an hour or more).

The solution is to use the tried and proven "sneakernet" method of exchanging files. That method requires a transportable media, like a 1.44MB floppy, that you can easily slip in your pocket or a diskette mailer. It also requires the same hardware and software standards at both ends. Physical size, durability, and speedy data access are the desired traits here. Competing in this arena are flexible disk, hard disk, and optical disk.

Although it's not stated anywhere in the job description, the removable media should be rewritable. That is, you should be able to write over or erase the old data. Some devices, like the recordable CD-ROM, can't be erased or recycled.

Magnetic drives. Storage devices

based on magnetic-recording technology are the least expensive. With a track record that spans more than three decades, magnetic recordings have proven to be cost effective for all types of data storage, including long-term archival. Basically, you have three choices in this area: floppy media, like the 3.5-inch, 1.44MB floppy; the removable hard disk, which is popularly called the Winchester drive; and streaming tape, most notably the QIC-80 cartridge variety.

Flexible flyer. The market leader, by a good margin, of new floppy technologies is Iomega's Zip drive (see Fig. 1). Each Zip diskette holds 100MB of data (200MB if you use compression software). Taking a cue from the successful 1.44MB floppy, Iomega designed the Zip diskette to be a rugged, small cartridge that easily slips into your shirt pocket or a diskette mailer. In fact, the Zip cartridge is exactly the same size as a 1.44M floppy, but a little bit fatter, and slides in and out of the Zip drive exactly like a 1.44M diskette. And there's a combo Zip with a built-in 1.44MB drive that fits into a standard 5.25-inch bay.

Zip is a hybrid between the 1.44MB floppy and the hard disk. Like the 1.44MB diskette, the rotating media is flexible, not solid. To condition the platter to the properties needed for hard-disk recording, the drive spins the disk at a dizzying 2945 rpm. (That is slightly slower than the 3600 rpm of a real hard disk, and eight times faster than the floppy.) At that speed, centrifugal force stretches the flexible plastic as tight as a drum skin, making it rigid and dimensionally stable.

Now that we have a solid platform to work on, all we have to do is lay down the tracks (see Fig. 2). Because the Zip disk has to hold 70 times more data than its floppy counterpart, the tracks are narrower and closer together. Consequently, the low-level formatting is done at the factory using a precision servo positioner.

The no-frills construction of Zip should allow for drastic price cuts as the production lines crank up to full speed, perhaps leveling off at $100 from its present street price of $200. That, plus the fact that the drive and cartridge are so similar to existing 1.44MB technology, makes Zip a logical replacement for the floppy.

Fig. 1. Iomega's Zip floppy-based drive is today's market leader. This 1.44MB look-alike provides 100MB at low cost, and is the most likely replacement for the venerable floppy.

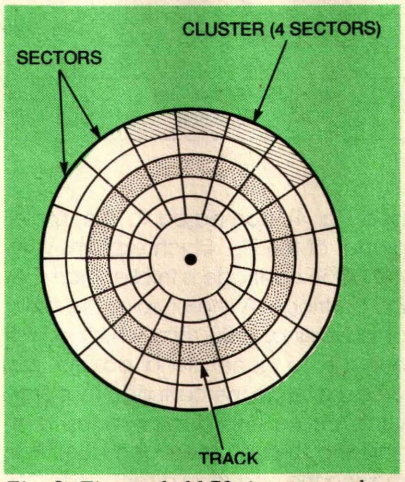

Fig. 2. Zip can hold 70 times more data than its floppy counterpart, which makes the tracks narrower and closer together. As a result, you can't do low-level formatting; that's done at the factory using a precision servo positioner.

Although 100MB isn't big enough to back up your gigabyte hard disk, it's just the right size for many projects. In fact, 100MB is large enough to hold both the application software and data files in many cases, which lets you quickly switch from one project to another by simply swapping diskettes.

The hard choices. Hot on the heels of Zip is SyQuest's EZ135 removable hard-disk drive (see Fig. 3). It, too, is built along the lines of the 1.44MB-floppy form factor and sells for $200. Unlike Zip, though, EZ135 is a true Winchester-drive design. As such, it offers hard-disk-like performance. For example, the EZ135's average access time is 13.5 ms, compared to 29 ms for Zip and 10 msec for an Enhanced IDE (EIDE) hard disk.

In fact, the only difference between your internal hard disk and the EZ135 is that the platters in your hard disk are permanently sealed inside the drive's case, whereas the EZ135's platters are contained in a removable cartridge. Access to the platters are through a trap door that works in much the same way as the protective cover of a VHS videotape cartridge works. When you insert the EZ135 cartridge into the drive, the door flips open and the read/write heads slide through the opening and into place, ready for work. Altogether there are eleven platters stacked inside the cartridge

TABLE 1—TECHNOLOGIES AT A GLANCE

Technology	Capacity	Initial Investment	Drive Cost ($ per megabyte)	Media Cost ($ per megabyte)
Flexible				
3.5" floppy	1.44 MB	$40	27.78	0.34
Zip	100 MB	$200	2.00	0.20
Hard disk				
EIDE	1,000 MB	$250	0.25	0.25
SQ327	270 MB	$400	1.48	0.22
EZ135	135 MB	$200	1.48	0.15
Jaz	1,000 MB	$600	0.60	0.10
Tape				
QIC-80	250 MB	$150	0.60	0.07
Travan TR-1	800 MB	$200	0.25	0.03
Travan TR-2	1,600 MB	$400	0.25	0.03
Travan TR-3	3,200 MB	$450	0.14	0.01
Optical disk				
Magneto-optical	230 MB	$600	2.60	0.17
MiniDisk DATA	140 MB	$400	2.86	0.21
HyperStorage	650 MB	tba	tba	tba
Phase Change Dual	2,300 MB	$599	0.26	0.07

TABLE 2—TRAVAN MINICARTRIDGE SPECIFICATIONS

	TR-1 Minicartridge	TR-2 Minicartridge	TR-3 Minicartridge	TR-4 Minicartridge
Capacity				
Uncompressed	400MB	800MB	1.6G	4G
Compressed	800MB	1.6G	3.2G	8G
Data Transfer Rate				
Minimum	62.5K/s	62.5K/s	125K/s	567K/s
Maximum	62.5K/s	125K/s	250K/s	567K/s
Tape				
Length	750 ft.	750 ft.	750 ft.	750 ft.
Width	.315 in.	.315 in.	.315 in.	.315 in.
Coercivity	550 Oe	900 Oe	900 Oe	900 Oe
Recording				
Number of tracks	36	50	50	72
Data density	14,700 ftpi	22,125 ftpi	44,250 ftpi	50,800 ftpi
Drive Interface	floppy	floppy	floppy	SCSI/EIDE
Backward compatibility	QIC-80 (read/write) QIC-40 (read only)	QIC-3010 (read/write) QIC-80 (read only)	QIC-3020 (read/write) QIC-3010 (read only)	QIC-3080/3095 (read/write) QIC-3020 (read only)

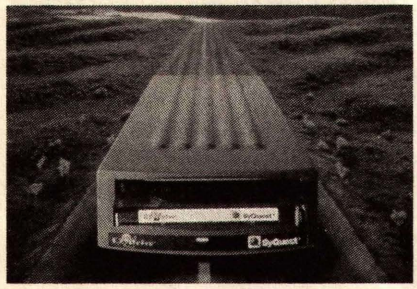

Fig. 3. With an average access time of just 13.5 seconds, Syquest's EZ135 demonstrates the very fast speeds typical of removable hard disk media.

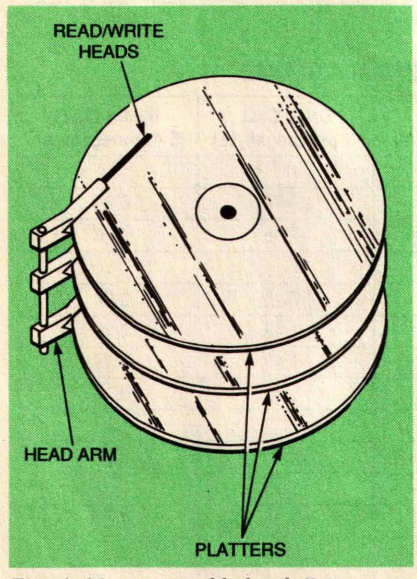

Fig. 4. Most removable hard-disk cartridges have several platters attached to a common spindle. The read/write heads often read only one side of the platter, instead of both top and bottom as is done in sealed hard disks.

(see Fig. 4), compared to the single platter of the Zip, which explains why the EZ135 cartridge is thicker than the Zip cartridge. A motor spins the disks at a whirling 3600 rpm, which is fast enough to generate a positive air pressure inside the cartridge that prevents smoke and dust particles from entering through the open door. Removing the cartridge disengages the motor, retracts the heads, then closes and seals the door to protect the disks from contamination.

Unfortunately, the EZ135 cartridge suffers from the same affliction as the Zip cartridge: Its 135MB capacity is too small for serious backup. It takes way too many cartridges to backup a 1.6GB drive. The cartridge is also bigger and more expensive to manufacturer than the Zip diskette.

Another choice in this area is Jaz from Iomega. Like the EZ135, Jaz is based on removable hard-disk technology, and the two drives have a lot in common. For example, both have multiple platters and the typical sliding dust-cover door.

But there are important differences, too. For one, the Jaz cartridge has a 1GB capacity, which is much better suited to backing up today's larger drives. Also, the cartridge is physically larger than the EZ135's, but that's to be expected given the bigger capacity. Jaz also has a unique disk-capture system that secures the disk platters when not installed in the drive; that system reduces the possibility of losing valuable data during transportation and storage. It has a motorized, cartridge-ejection mechanism, and a data-transfer rate of 10MB/sec in the burst mode.

While Jaz will cost you the most bucks up front, its per-byte cost is among the cheapest. Jaz comes in two configurations: an internal drive that fits in a 3.5-inch bay ($499), and an external parallel-port version ($629). A 1GB cartridge is included; extra cartridges come in 540MB and 1GB capacities, and sell for $69 and $99, respectively. Both drives need a SCSI interface, but there's talk of an EIDE version which should bring the price down below $400.

Streaming along. One of the major drawbacks of the systems we've discussed so far is that none is capable of backing up your new 1.6G hard disk in one pass. In every case you need a bevy of cartridges—and deep pockets—to even come close. For example, it takes 16 Zip cartridges ($320), a dozen EZ135 cartridges ($240), or two Jaz cartridges ($198). And you don't even want to know how many floppy diskettes it'll take or how much they cost. (Hint: 1111 disks at $0.50 each = $555).

Instead, for one-pass backups, the reel-to-reel minicartridge reigns supreme. Data minicartridges come in a wide variety of capacities, ranging in size from 80MB to 4GB. For years, savvy users turned to QIC-80 tape drives, which have a capacity of 250MB, as the affordable answer to

Fig. 5. Using Travan technology, Segate's (formerly Conner) Tape-Stor 800 tape drive can boost the compressed capacity from the 250MB level of the QIC-80 minicartridge to 800MB.

archival data storage. Over the years, the QIC-80 standard expanded to its present day format—the Travan drive. Developed in the laboratories of 3M (the inventors of data-cartridge technology), the Travan platform allows minicartridge technology to keep pace with rapidly increasing hard-disk capacities, while providing backward compatibility with previous QIC formats.

The amount of data storage available depends on the length and width of the tape. For example, the DC2120 QIC-80 minicartridge contains 307 feet of quarter-inch tape for 250MB of storage space, while the QIC-3010 minicartridge has 400 feet of quarter-inch tape with a 750MB capacity. The larger TR-1 Travan cartridge holds 750 feet of ⅜-inch tape, which can store up to 800MB.

The compressed capacity of the Travan minicartridge is really an estimate rather than a specification that's based on a 2:1 compression ratio. The actual compressed capacity depends on the type of the data file. Files that compress a lot will yield a greater capacity, while those that compress little or not at all result in storage capacities that are closer to the native (uncompressed) capacity of the tape. For example, a TR-1 Travan minicartridge filled with GIF graphics images can hold only 400MB worth of data because the GIF files are already in compressed format. By comparison, the same TR-1 minicartridge can hold 950MB of ASCII text files, which are highly compressible.

To make the Travan drive compati-

How To Shop For A Removable Media Drive

There are several factors to consider when buying a removable media drive, not the least of which is speed. Even if you only use the drive for archival backup, you don't want to be kept waiting while the drive endlessly grinds away. If it takes too long to backup your work, you're less likely to do it. Here are the parameters you should consider when comparing the speed of one drive to another.

Average Access Time is the most commonly-used measure of a drive's speed. That is the average time it takes to find and read the selected data on the media. Generally, the smaller the number, the faster the drive.

Data Transfer Rate is another popular measure of drive speed that tells you how fast data moves from the drive to your PC's memory. Those numbers typically range from 500KB/sec to 5MB/sec. A related measurement, the **Burst Transfer Rate**, measures the transfer rate for a small block of data in a single burst. Those figures typically range from 4MB to 10MB per second. In theory, larger numbers should mean faster throughput. However, that isn't always the case, especially when comparing rotating-drive media.

Rotational Speed is a better measure of data throughput when considering a rotating disk drive, like Zip, EZ135, and MO drives. That measurement is important because part of the data-transfer latency is caused by the head-positioning mechanism that locates the head over the track containing the requested data. Just placing the read/write head on the right track doesn't guarantee instant data access. It still has to wait for the sector that contains the data to pass under the head. The faster the platter rotates, the more often that sector passes under the head, thus reducing wait time.

Cache Size often plays a large role in determining how fast data can be retrieved from a drive. In many cases, the requested data has already been asked for one or more times. So it's really a waste of time and effort to locate the data and read it again when the data can be stored in a cache for quicker access. In fact, that is generally the case with disk drives. The on-board cache usually ranges in size from 64KB to 256KB. Generally, the larger the cache, the more likely the data you're looking for is in the cache, and the faster it can be retrieved. Ω

TABLE 3—ROTATING MEDIA BACKUP DRIVES

	APS 230 MO	Fujitsu M2512A	Iomega Jaz	Iomega Zip	Olympus MOS 320E	Panasonic PD/CD-ROM
Capacity (MB)	128MB/230MB	128MB/230MB	540MB/1GB	100MB	230MB	650MB
Technology	Optical Disk	Optical Disk	Hard Disk	Floppy Disk	Optical Disk	Optical Disk
Recording method	MO	MO	DOS	DOS	MO	PD
Price	$449	$599	$599	$199	$699	$599
Cartridge						
Disk size	3.5"	3.5"	5.25"	3.5"	3.5"	5.25"
Price	$40	$40	$69/$99	$20	$40	$50
Interface	SCSI	SCSI	SCSI	EPP/SCSI	SCSI	SCSI
Average access time	27 msec	35 msec	12 msec	29 msec	35 msec	180 msec
Sustained transfer rate						
Maximum	1.3M/s	5M/s	5M/s	1.4M/s	5M/s	1M/s
Minimum	500K/s	3.3M/s	3.3M/s	800K/s	3.3M/s	500K/s
Burst transfer rate	4M/s	10M/s	10M/s	5M/s	10M/s	n/a
Rotational speed	4500	3600	5400	2945	4200	2026
Buffer size	256K	237K	256K	32K	1MB	256K
Start time	n/a	n/a	10 sec	3 sec	n/a	6 sec
Stop time	n/a	n/a	5 sec	3 sec	n/a	3 sec

TABLE 3 (cont)

	Pinnacle Apex 4.6GB	Pinnacle Tahoe 230	Sharp MD	Sony MDH-10	Syquest EZ135	Toray Phasewriter
Capacity (MB)	4.6GB	128MB/230MB	140MB	140MB	135MB	650MB
Technology	Optical Disk	Optical Disk	Optical Disk	Optical Disk	Hard Disk	Optical Disk
Recording method	LIMM	MO	MiniDisk	MiniDisk	DOS	PD
Price	$1695	$699	$200	$470	$199	$599
Cartridge						
Disk size	5.25"	3.5"	2.5"	2.5"	3.5"	5.25"
Price	$199	$25/$35	$6.50	$29	$20	$50
Interface	SCSI	EPP/SCSI	AT floppy	SCSI	IDE/SCSI	SCSI
Average access time	17 msec	28 msec	500 msec	300 msec	13.5 msec	165 msec
Sustained transfer rate						
Maximum	6M/s	1.47M/s	n/a	150K/s	2.4M/s / 5M/s	512K/s
Minimum	2.5M/s	490K/s	n/a	150K/s	1.4M/s / 2M/s	1.14M/s
Burst transfer rate	10M/s	5M/s	n/a	2.5M/s	4M/s / 10M/s	n/a
Rotational speed	3755	3600	n/a	990	3600	n/a
Buffer size	1M	256K	n/a	320K	64K	256K
Start time	n/a	5 sec	n/a	n/a	8 sec	n/a
Stop time	n/a	3.5 sec	n/a	n/a	10 sec	n/a

ble with quarter-inch data cartridges, the drive has a notch at the top two corners that allows it to distinguish between the smaller QIC-80 minicartridge and the larger Travan cartridge. To date, only the TR-1 minicartridge has been widely used, but greater capacities are evolving even as we speak. 3M expects the Travan minicartridge to have capacities that exceed 15GB by 1997.

Among the vendors participating in the Travan program are 3M, Aiwa, Colorado Memory Systems, Seagate (formerly Conner Peripherals), and Iomega (see Fig. 5). In addition, Rexon, Sony, and Pertec Memories have announced plans to develop products incorporating Travan technology.

Optical storage. While floppy-disk, hard-disk, and tape-stream technologies are all widely used and well established, a fourth technology—optical—holds the greatest long-term solution for low-cost, high-capacity, removable-media data storage. An optical recording is small, lightweight, robust, and durable. Because it's a non-contact medium, the disk isn't susceptible to wear or head crashes, as is common with floppy- and hard-disk drives. Moreover, optical disks are immune to erasure from stray magnetic fields.

Magneto-optical drives. Magneto-optical technology, abbreviated MO, combines the ease of use and transportability of a floppy disk with the capacity and speed of a hard disk. Magneto-optical disks come in two sizes, 3.5 inches and 5.25 inches, and four capacities: 128MB and 230MB for the 3.5-inch format, and 650MB and 1.3GB for the 5.25-inch format.

As the name implies, magneto-optical drives perform their magic using both magnetic and optical technology. An MO drive writes to the disk using a read/write head assisted by a laser. The laser heats up the disk surface to its Curie point—the temperature at which the magnetic alignment of the recording media is unfrozen. You can now realign the magnetic particles on the disk surface using the magnetic field of the read/write head. Presently, there are three different methods used to record data on the magneto-optical disk: optical

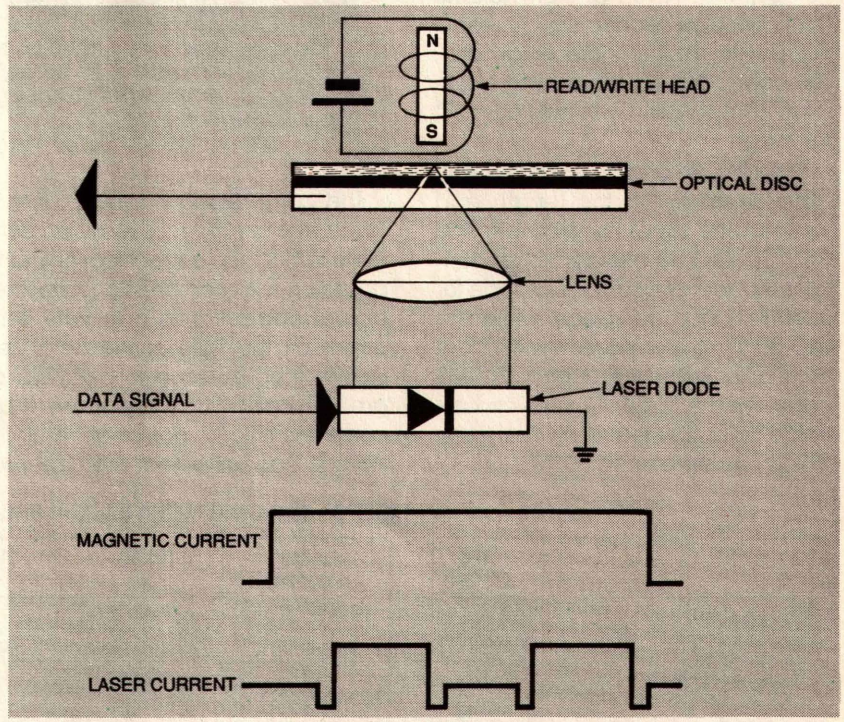

Fig. 6. The standard recording format for 640MB magneto-optical disks is optical modulation, where data is stored on the disk by applying a constant external magnetic field while using a pulsed laser to write the bits.

TABLE 4—TRAVAN TAPE DRIVE BACKUP

	Segate Tape-Stor 800	Segate Tape-Stor 3200	Exabyte Eagle TR-3	Iomega Ditto Easy 800	Iomega Ditto 3200	HP Colorado T-1000
Price						
Internal	$170	n/a	$279	$150	$325	n/a
External	n/a	n/a	n/a	$300	$425	$224
Media type	TR-1	TR-3	TR-3	TR-1	TR-3	TR-1
Capacity						
Native	400MB	1.6G	2.2G	400MB	1.6G	400MB
Compressed	800MB	3.2G	4.4G	800MB	3.2G	800MB
Interface	floppy/EPP	floppy/EPP	floppy	floppy/EPP	floppy/EPP	EPP
Data transfer rate	500K/s / 1M/s	1M/s / 2M/s	5M/s	500k/s / 1M/s	1M/s / 2M/s	500K/s / 1M/s
Effective backup rate	9.5M/min.	19M/min.	20M/min.	9.5M/min.	19M/min.	9.5M/min.
Recording tracks	36	50	50	36	50	36
Recording density	14,7000 bpi	44,250 bpi	44,250 bpi	14,700 bpi	44,250 bpi	14,700 bpi
Recording method	MFM	MFM	MFM	MFM	MFM	MFM
Read/write tape speed	34 ips/68 ips	45.3 ips	45.3 ips	34 ips/68 ips	45.3 ips	34 ips/68 ips

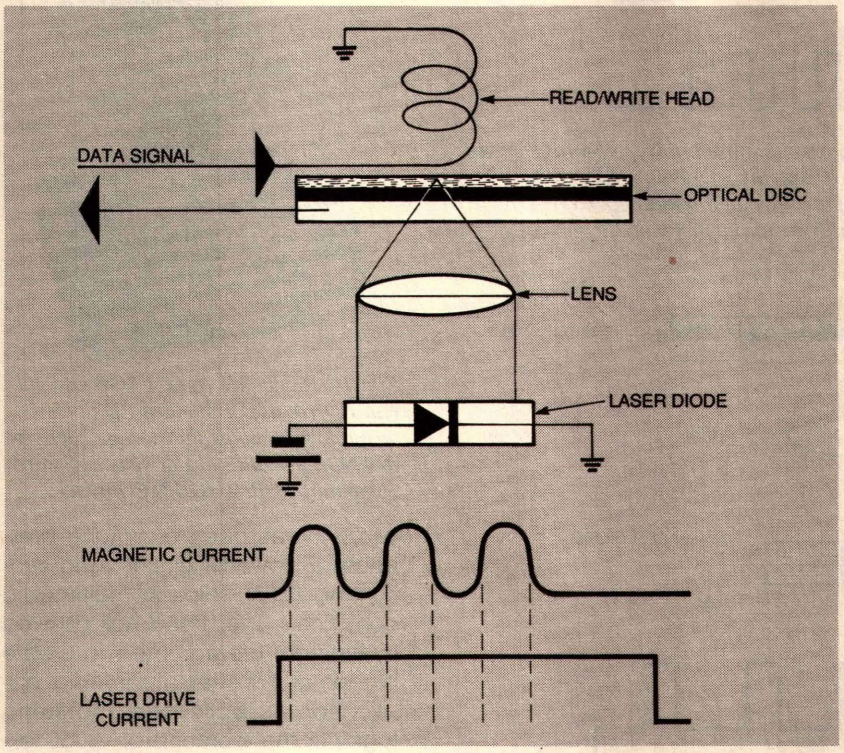

Fig. 7. Magnetically-modulated optical drives, like Sony's MiniDisk Data, store data by shining a DC-powered laser on the disk and modulating the magnetic field.

modulation, magnetic-field modulation, and laser-strobed magnetic-field modulation.

The standard for the 230MB and 650MB MO disks is optical modulation, where an external magnetic field is held constant while a pulse-modulated laser beam writes the data on the disk (see Fig. 6). It takes two rotations of the disk to write a bit. In the first rotation, all the bits are set to the same orientation, effectively erasing the data; in the second pass, select bits are reoriented to the opposite pole to establish the 0 and 1 data-bit pattern.

MiniDisk format. In the magnetic-field modulation method, the laser current is held constant and the magnetic field is modulated (see Fig. 7) using the read/write head. That is the method used by Sony for its MiniDisk (MD) Data format. Sony has sold more than a million audio players using that 2.5-inch technology, and plans to extend the technology to other consumer products, like cameras.

While the technology is well suited for PC data storage, especially in notebook and palmtop computers where its small size and low power requirements are a real plus, Sony hasn't aggressively pursued that market. As a result, production volumes of Sony's MD optical drive are quite low and the cost is a hefty $470—way too expensive for a drive of just 140MB with a very slow 500-ms average access time.

Sharp and National Semiconductor have jointly taken a different tack on the MD technology. Using an interface chip created by National Semiconductor, Sharp links its MD DATA drive to the PC through the floppy-drive port built into all PCs. That approach saves money on two fronts. First, it makes use

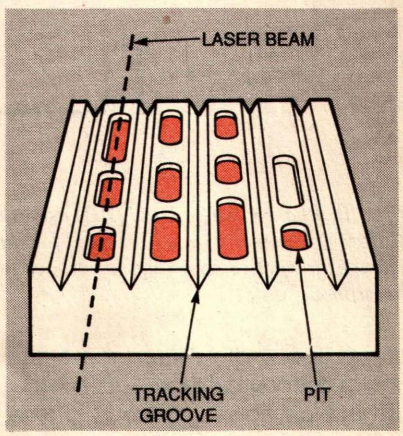

Fig. 8. When writing to an optical disk, pits are etched into the surface to represent data. The areas surrounding the pits are called lands. The closer together the pits are, the more data the disk can store.

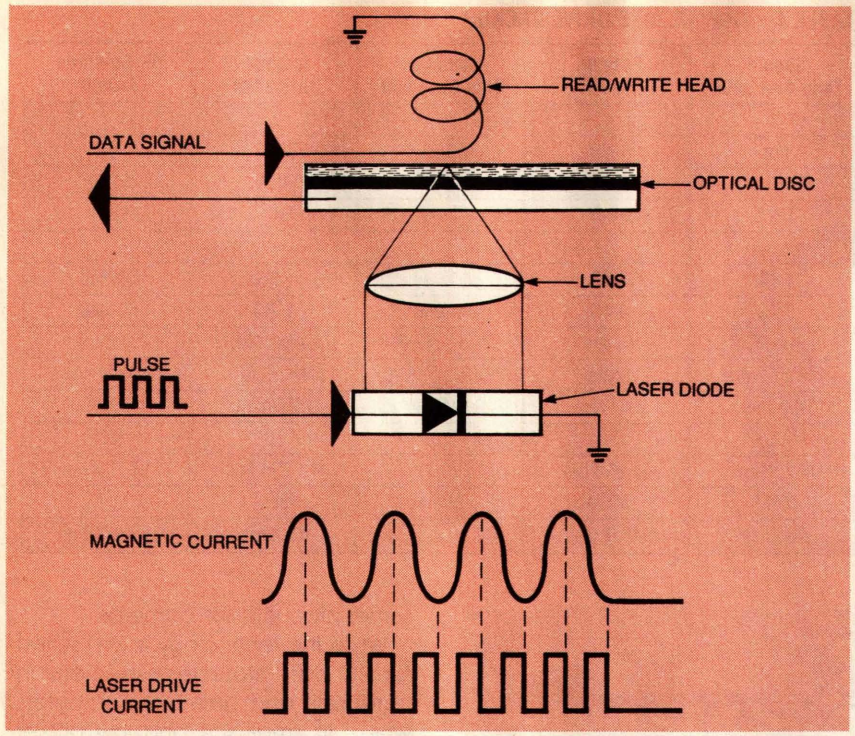

Fig. 9. Laser-strobe magnetic field modulation, like that used in HyperStorage drives, provides increased storage capacity by synchronizing the magnetic field's modulation with the laser pulse. That produces a sharper pit edge that doesn't depend on the magnetic field's reversal speed, a problem that limits the capacity of magnetically-modulated drives.

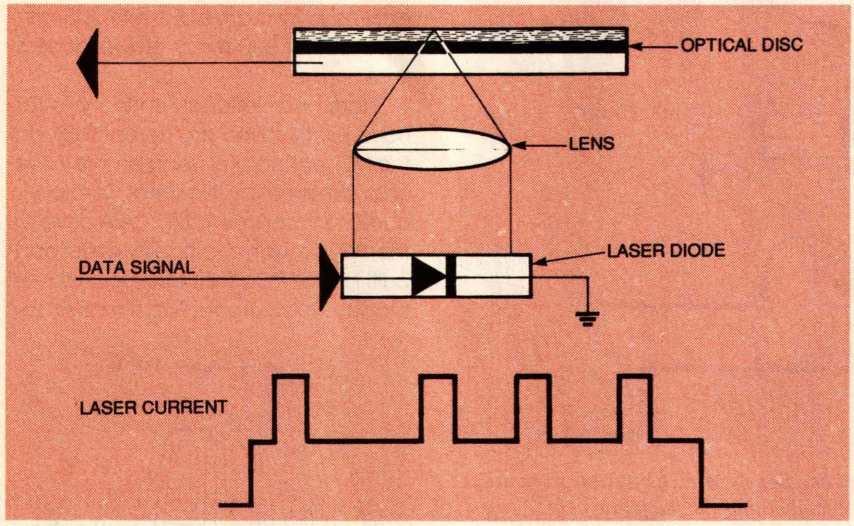

Fig. 10. Phase Change Dual (PD) drives use the Light Intensity Modulation Method (LIMM), which eliminates the need for a magnetic field. Instead, a laser beam changes the active recording layer back and forth between a crystalline and amorphous state.

of the floppy-drive-interface electronics already in place. Second, the use of National's interface chip renders what few drive electronics are left into a single package, which results in lower production costs. The result is an MD drive that sells for $200 in OEM quantities. To further reduce the cost, rather than create a specialized data cartridge, Sharp uses standard, blank audio MDs for storage. That is a smart move, because a blank MD audio cartridge, which works equally well in data drives, sells for as little as $6.50. By comparison, Sony MD Data cartridges sell for $29.

HyperStorage. In the last couple of years, there's been a growing presence of powerful digital signal-processing (DSP) chips in multimedia computers. That trend has allowed multimedia programmers to create bigger and better multimedia applications—applications that bring together the elements of visual, textual, and audio data. As multimedia applications grew in size, so did the need for a new type of storage medium that's inexpensive, compact, fast, and has enough capacity to handle this new breed of software. In August 1994, Sony, Hitachi and 3M announced the release of the HyperStorage (HS) optical drive, a new 3.5-inch magneto-optical drive that intends to fill the needs of that new discipline.

HyperStorage is based on the principle of laser-strobe magnetic-field modulation, where both the magnetic field and laser beam are modu-

Ditto Easy 800 Has 1-Step Backup

While everyone knows how important it is to back up your hard drive, it's easy to put it off when it takes more than a few seconds to set the gears in motion. Iomega's Ditto Easy 800 drive takes a lot of the pain out of doing backups with its "1-Step" software. Simply click on the Ditto Easy's icon and that's it. You can also have Ditto Easy do the backup for you using its "no-brainer" day and time scheduler.

The Ditto Easy 800 is but one in a family of Travan drives from Iomega. It has a street price of $150, and uses the TR-1 minicartridge. Other Ditto products include the Easy 450 ($99) and the Easy 3.2GB ($300). Ω

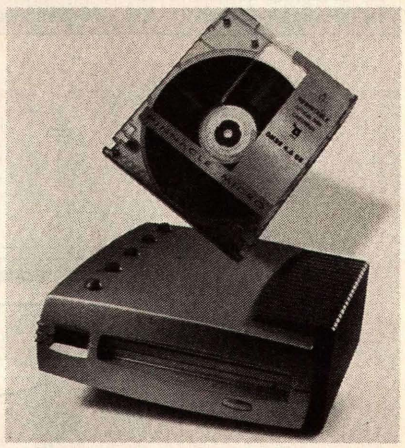

Fig. 11. Pinnacle's Apex 4.6GB Optical Hard Drive uses enhanced PD technology to boost the storage capacity to 4.6GB per disk. The drive is backward compatible with 2.3GB MO disks.

lated. In conventional magnetic-field modulation, the formation of edges between pits depends upon the speed with which the field can change polarity (see Fig. 8). Because the field is fairly intense, switching times are relatively slow, which leads to jitters that limit the density of the data on the disk. Laser-strobe magnetic field modulation (see Fig. 9) eliminates that problem by synchronizing the magnetic field's modulation with the laser pulse. The pit edge no longer depends on the magnetic field's reversal speed, but rather on the laser beam's timing, which reduces the likelihood of jitters and, in turn, opens up more area for data.

In current MO-disk technology, a sector must be erased before data can be written to it. That normally takes two spins of the platter, which takes extra time and limits the disk's usefulness as a back-up or file-transfer medium. Laser-strobed magnetic-field modulation, on the other hand, doesn't have that limitation. It can directly overwrite old data, resulting in faster write operations—about the same speed as read operations. In tests done by Sony where MPEG2 moving-picture data was written to a HS drive over a SCSI-2 interface, the HS drive was able to maintain a sustained data rate of better than 4 MB/sec—good enough for real-time recording.

In addition, the HS disk can be partitioned into two areas: a read-only boot sector, and a read/write data sector. That makes it possible for a HS drive to serve as the primary storage medium for a personal computer. Booting up the system or launching an application from the HS drive feels no different than it would from a hard drive.

Although HyperStorage technology has been around for a while, it's taken a long time to reach the market. The wait might soon be over, however; as of this writing, Sony is predicting delivery sometime this fall. The first drives will be targeted at high-end multimedia applications where complex graphics must run in real time, like fast-action games and virtual-reality applications. As the technology matures, look for prices to drop to the level where they will be affordable in the more traditional desktop setting.

NAMES AND ADRESSES

Exabyte Corporation
Eagle Division
4665 Nautilus Court South
Boulder, CO 80301

Fujitsu Computer Products of America Inc.
3055 Orchard Dr.
San Jose, CA 95134-2022
http://www.fujitsu.com/FCPA/

Iomega Corp.
1821 W. Iomega Way
Roy, UT 84067
http://www.iomega.com/

Olympus Image Systems Inc.
2 Corporate Drive
Melville, NY 11747

Panasonic Communications & Systems Co.
One Panasonic Way
Secaucus, NJ 97094
http://www.panasonic.com/

Pinnacle Micro Inc.
19 Technology
Irvine, CA 92718
http://www.pinnaclemicro.com/

Quantum
500 McCarthy Blvd.
Milpitas, CA 95035
http://www.quantum.com/welcome.html

Segate
1650 Sunflower Ave.
Costa Mesa, CA 92626

Sharp Electronics Corporation
Sharp Plaza
Mahwah, NJ 07430
http://www.sharp-usa.com/

Sony Electronics Inc.
3300 Zanker Rd.
San Jose, CA 95134-1901
http://www.sel.sony.com/

SyQuest Technology, Inc.
47071 Bayside Pkwy.
Fremont, CA 94538-6517
http://www.SyQuest.com/default.htm

Toray Optical Storage Solutions
1875 S. Grant St. #720
San Mateo, CA 94402

Toshiba America, Inc.
9740 Irvine Blvd.
Irvine, CA 92718
http://www.toshiba.com/text/

Phase Change Dual. Another way to achieve one-pass writing is via Phase-Change Dual (PD) technology. Unlike MO-disk technology, Phase-Change technology doesn't need a magnetic field. Both the reading and the writing operations are done using laser light alone.

Also called the Light Intensity Modulated method (LIMM), PD uses the intensity of a laser beam to change the active layer (a thin coating of wavelength-sensitive resins) of an optical disk back and forth between a crystalline and amorphous state (see Fig. 10). Because the method relies on light intensity, not heat, there is no heat build up like there is with the magneto-optical methods. A cooler laser reduces heat leakage on the disk surface, which means the laser can pack the data tracks much closer together yielding higher storage capacities.

Sometimes the PD drive is combined with a CD-ROM, as is the case with Panasonic's PD/CD-ROM and Toray's Phasewriter Dual. Both drives have the ability to read and write 650MB optical cartridges and to play CD-ROMs at 4× speed. That is a marriage of convenience, not of necessity. Because LIMM technology is relatively expensive, combining the two often justifies a sale that might otherwise be lost. However, the combination results in some tradeoffs. PDs typically have an average seek time of around 45 msec and a data transfer rate of 1.5MB per second, whereas a 4X CD-ROM has a 180-msec access time and a 870K data-transfer rate. When the two technologies share the same mechanics and electronics, the PD is doomed to run at the slower speeds of the CD-ROM.

When LIMM technology is freed from its CD-ROM constraints, it can do amazing things. Take Pinnacle's Apex 4.6GB Optical Hard Drive, for example (see Fig. 11). By fine tuning the LIMM technology, Apex is able to cram 4.6GB of data on a single 5.25-inch disk (2.3GB per side), and move that data back and forth (read and write) between the drive and the PC at speeds up to 6MB per second while keeping it compatible with the emerging 2.3GB standard still in committee. At the time of this writing, no less than four other vendors are poised and waiting to announce their versions of a LIMM drive.

Summary. There you have it: four technologies competing for your back-up buck. All of the technologies have their strengths and weaknesses. Which, if any, will eventually become a *de facto* standard will be determined by the marketplace—a marketplace that, of course, includes users like you! Ω

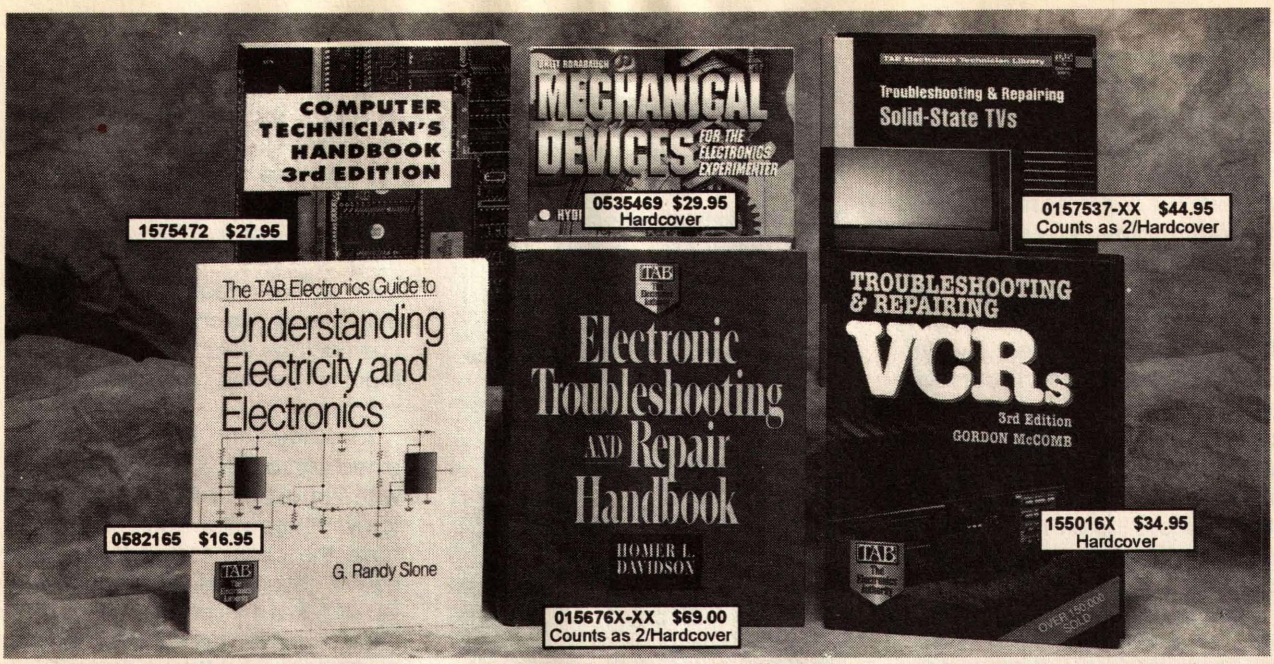
COMPUTER TECHNICIAN'S HANDBOOK 3rd EDITION
1575472 $27.95
MECHANICAL DEVICES FOR THE ELECTRONICS EXPERIMENTER
0535469 $29.95 Hardcover
Troubleshooting & Repairing Solid-State TVs
0157537-XX $44.95 Counts as 2/Hardcover
The TAB Electronics Guide to Understanding Electricity and Electronics
G. Randy Slone
0582165 $16.95
Electronic Troubleshooting AND Repair Handbook
HOMER L. DAVIDSON
015676X-XX $69.00 Counts as 2/Hardcover
TROUBLESHOOTING & REPAIRING VCRs 3rd Edition GORDON McCOMB
155016X $34.95 Hardcover

The leading source of information for electronics hobbyists for over 30 years!

5870606 $12.95

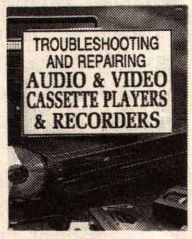

1577564 $22.95

5869179 $12.95

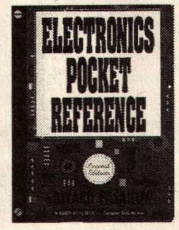

0487375 $24.95

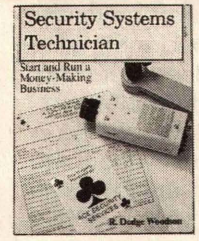

0717753 $19.95

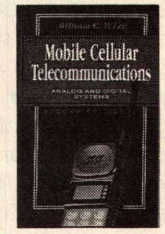

0380899-XX $60.00 Counts as 2/Hardcover

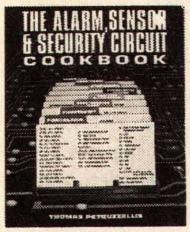

0497060 $29.95 Hardcover

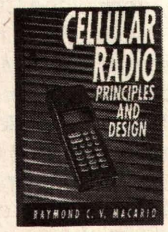

0443017 $50.00 Hardcover

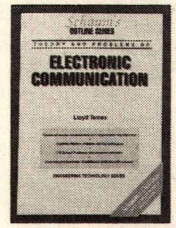

0634955 $11.95

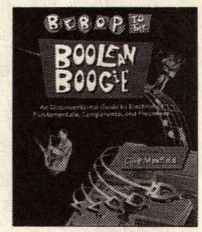

5871513-XX $35.00 Counts as 2

0304084-XX $24.95 Counts as 2

5869195 $12.95

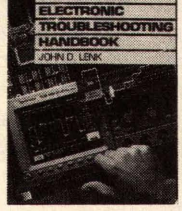

0376581-XX $39.50 Counts as 2/Hardcover

9122264-XX $39.95 Counts as 2

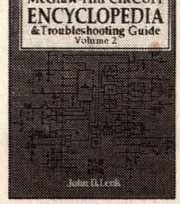

0376115 $36.00

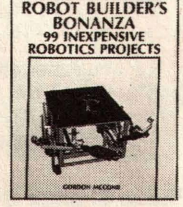

1571469 $18.95

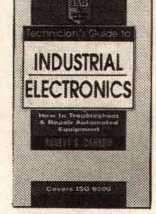

0112738-XX $45.00 Counts as 2/Hardcover

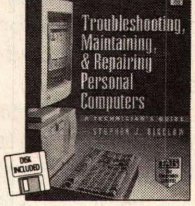

9120989-XX $70.00 Counts as 2/Hardcover

As a member of the ELECTRONICS BOOK CLUB® . . . you'll enjoy receiving Club bulletins every 3-4 weeks containing exciting offers on the latest books in the field at savings of up to 50% off the regular publishers' prices. If you want the Main selection, do nothing and it will be shipped automatically. If you want another book, or no book at all, simply return the reply form to us by the date specified. You'll have at least 10 days to decide. If you ever receive a book you don't want due to late delivery of the bulletin, you can return it at our expense. Your only obligation is to purchase 3 more books during the next 12 months, after which you may cancel your membership at any time. And you'll be eligible for FREE BOOKS through our Bonus Book Program.

A shipping/handling charge and sales tax will be added to all orders. All books are softcover unless otherwise noted. If you select a book that counts as 2 choices, write the book number in one box and XX in the next. (Publishers' Prices Shown) ©1996 EBC

PHONE ☎ 1(614)759-3666 • FAX 1(614)759-3749

(8:30 a.m. - 5:00 p.m. EST Monday-Friday) (24 hours a day, 7 days a week)

5 BOOKS FOR ONLY $4.95

VALUES TO $212.85

1570519 $17.95

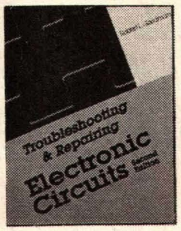

1573119 $19.95

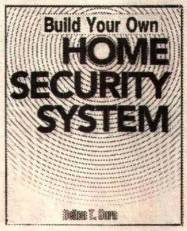

0303932 $17.95

1561579 $17.95

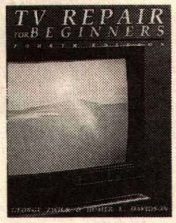

073092X $19.95

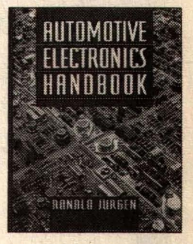

0331898-XX $89.50
Counts as 2/Hardcover

8820901-XX $27.95
Counts as 2

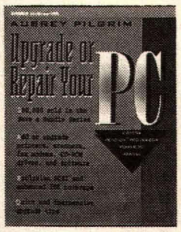

0501149 $26.95

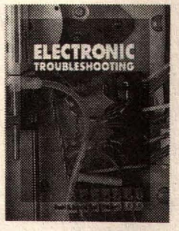

0650780 $24.95

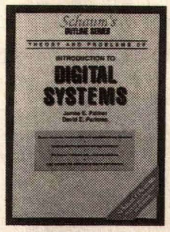

0484392 $13.95

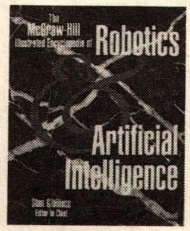

0236135-XX $40.00
Counts as 2/Hardcover

0156417 $19.95

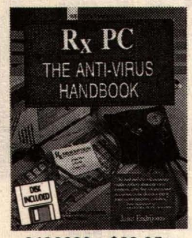

0196230 $39.95
Hardcover

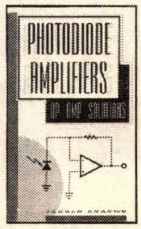

024247X $49.00
Hardcover

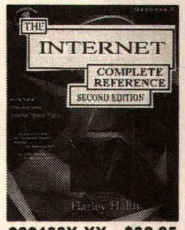

882138X-XX $32.95
Counts as 2

0707618 $19.95

0156786 $24.95

0052395 $17.95

0350787-XX $44.95
Counts as 2/Hardcover

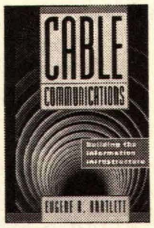

0053553-XX $50.00
Counts as 2/Hardcover

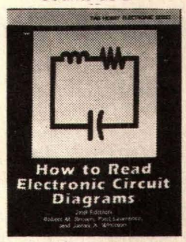

1554637 $16.95

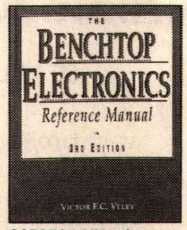

0673764-XX $54.95
Counts as 2/Hardcover

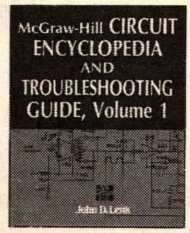

0380767 $36.95

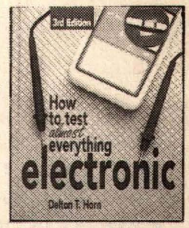

0304068 $15.95

If coupon is missing, write to: Electronics Book Club®, *A Division of The McGraw-Hill Companies*, P.O. Box 549, Blacklick, OH 43004-9918

Electronics Book Club™

A Division of The McGraw-Hill Companies
P.O. Box 549, Blacklick, OH 43004-9918

YES! Send me the 5 books listed below, for just $4.95 plus shipping/handling & tax, and enroll me as a member of the **Electronics Book Club®** according to the terms outlined in this ad. If not satisfied, I may return the books within ten days without obligation and have my membership cancelled.

If you select a book that counts as 2 choices, write the book number in one box and XX in the next box.

NAME _____

SIGNATURE _____
(required on all orders)

ADDRESS/APT. # _____

CITY _____ STATE _____ ZIP _____ PHONE _____

Valid for new members only, subject to acceptance by EBC. U.S. orders are shipped 4th Class Book Post. Applicants outside the U.S. and Canada will receive special ordering instructions. Canada *must* remit in U.S. funds drawn on U.S. banks. A shipping/handling charge and sales tax will be added to all orders.

RE996C

The Coming Revolution In Shortwave Broadcasting

Planning and common-sense scheduling unchoke the shortwave broadcast bands.

STANLEY LEINWOLL

IF YOU'VE NOTICED THAT SHORTwave radio reception is better than it has been for recent years, it is probably due to the work of a group of broadcasting experts who meet semi-annually to reduce interference by coordinating their shortwave broadcasting schedules. This work is all the more noteworthy because it comes at a time of minimum sunspot activity, when reception conditions are ordinarily at their worst.

Known as the High Frequency Coordinating Committee (HFCC), the group consists of some 70 delegates from 27 countries, representing approximately 50 shortwave broadcasting organizations. The HFCC coordinates more than 17,000 frequency hours, which amounts to more than 70 percent of the world's total shortwave broadcasting effort. Table I lists the countries attending the HFCC Conference held in Bern, Switzerland, from February 5th through the 9th, 1996.

The HFCC first met in April, 1991. There were 14 countries in attendance. The cold war had ended, radio jamming had ended, and telecommunication authorities from East and West were discussing methods of eliminating, or at least alleviating, unintentional harmful interference which permeated the shortwave bands.

Committee membership has grown with time. Admission to the HFCC is open to all broadcasters; any administration wishing to attend is first invited to attend a semiannual conference as an observer. Membership is extended to them at the conclusion of that meeting.

HFCC meetings last a full week, and they have been increasingly successful in their efforts to resolve co-channel and adjacent-channel frequency conflicts, termed "collisions."

The HFCC coordinates a winter schedule [W], and a summer schedule [Z], the periods of each are now determined by European clock time-shifts. For example, the current Z schedule commenced March 31, 1996, when European Daylight Time started, and will end on October 27, 1996, when European Standard Time is resumed. Most broadcasters now conform to these two-per-year schedule formats. Meetings are convened about six weeks before the commencement of a new schedule, and the participants have been taking turns hosting conferences.

TABLE 1—COUNTRIES ATTENDING FIRST 1996 HFCC CONFERENCE

Austria	Monaco
Belgium	Netherlands
Bulgaria	Norway
Canada	Poland
Czech Republic	Romania
Denmark	Russia
Finland	Slovakia
France	Sweden
Germany	Switzerland
Greece	Turkey
Hungary	Ukraine
Iran	United Kingdom
Israel	USA
Italy	Vatican City

Note: The United States was represented by delegates from the International Bureau of Broadcasting (IBB) on behalf of Radio Free Europe, Radio Liberty and The Voice of America. The Federal Communications Commission (FCC) was present on behalf of 23 privately owned shortwave broadcast stations licensed by the FCC. Monaco was represented by TransWorld Radio.

Participating broadcasters submitted their requirements on diskette, and the data is inserted into a data bank; a computer compiles it in useful form and a book is published by a host country. A typical schedule is more than 200 pages long. At the beginning of a conference, schedules are distributed to each participant. A representative Z-96 (Summer, 1996) schedule page at the begining of the conference is shown at the top of Fig. 1. The technical characteristics of each requirement include the frequency, hours of operation, transmitter power, type of antenna being used, beam heading of the antenna, location of the transmitter site, and the target area. Target areas are depicted and described in Fig. 2.

The software, which has been developed by J.W. Drexhage of Radio Nederland, and H. Scholz and T. Feustel of Deutsche Welle [Radio Germany] is being constantly refined to handle data inputs and readable outputs. The software can now analyze conflicts among two or more entries, defining these as co-channel (two stations beamed to the same target areas on the same frequency), or adjacent channel (±5 kHz conflicts beamed to the same target area). In Fig. 1, a co-channel collision between Ukraine (RRT) and Israel (ISL) on 11,590 kHz is indicated by the dark shading. Adjacent-channel collisions are shown by light shading.

Resolving conflicts

The software is now at the stage where each organization participating in an HFCC conference receives a list of collisions between their requirements and those of other broadcasters, and a list of all the requirements as they appear in the HFCC book on the first day of the conference. Each broadcaster can then check to be certain that requirements have been correctly posted; incompatibilities with other broadcasters are then examined and possible solutions can be suggested. At that point, the informal coordination process of the HFCC begins.

Collisions are dealt with during bilateral consultations; these are conducted in English, with Russian to English, and English to Russian translation, where appropriate. The languages used are only limited by the number of participants. The discussions are generally amicable, because those taking part in the HFCC meeting are interested in resolving as many problems as possible. The bottom of Fig. 1 is a page from the most recent version of the Z-96 schedule; it shows that the collision at the top of Fig. 1 was solved by Israel, which moved its requirement from 11,590 kHz to another frequency.

There are several unwritten rules which guide the conference members in their efforts to resolve collisions. Among these are:

- If a broadcaster has been operating on a frequency-time slot in previous schedules, and a conflict is created by another broadcaster who is new on the same frequency, the newcomer is generally expected to move to another frequency, or delete the requirement.
- If a broadcaster has a transmission on a frequency for a long period, and another broadcaster is on the same frequency for a shorter period and they have a collision, it is generally easier for the shorter transmission period to find another frequency. Usually the broadcaster with the shorter collision period vacates the frequency.
- A problem can sometimes be resolved if one of the broadcasters in conflict can move its transmission to another useful band where the propagation features are not compromised.

About the Author

Stanley Leinwoll has worked as a hands-on shortwave broadcaster for almost half a century. He started working for the Voice of America as a Propagation Specialist in 1950. In 1957 he joined Radio Free Europe as its Radio Frequency and Propagation Manager. He was the Director of Engineering for Radio Free Europe/Radio Liberty from 1975 until his retirement in 1994. He is currently working as a Technical Consultant to three private sector US shortwave broadcasters, WYFR, WEWN, and WVHA, and he attended the February 1996 HFCC in Bern on behalf of his clients.

Mr. Leinwoll has served on five United States Delegations to International World Administrative Radio Conferences, and has also written extensively; of his ten books, titles include, *From Spark to Satellite*, *A History of Wireless Communication*, *Shortwave Propagation*, and *Space Communications*.

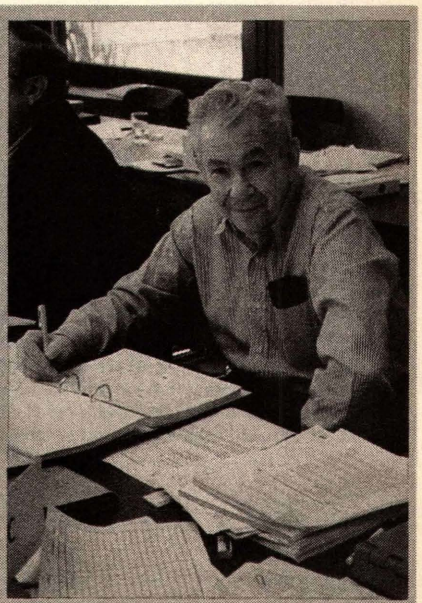

STANLEY LEINWOLL at work at the HFCC in Bern.

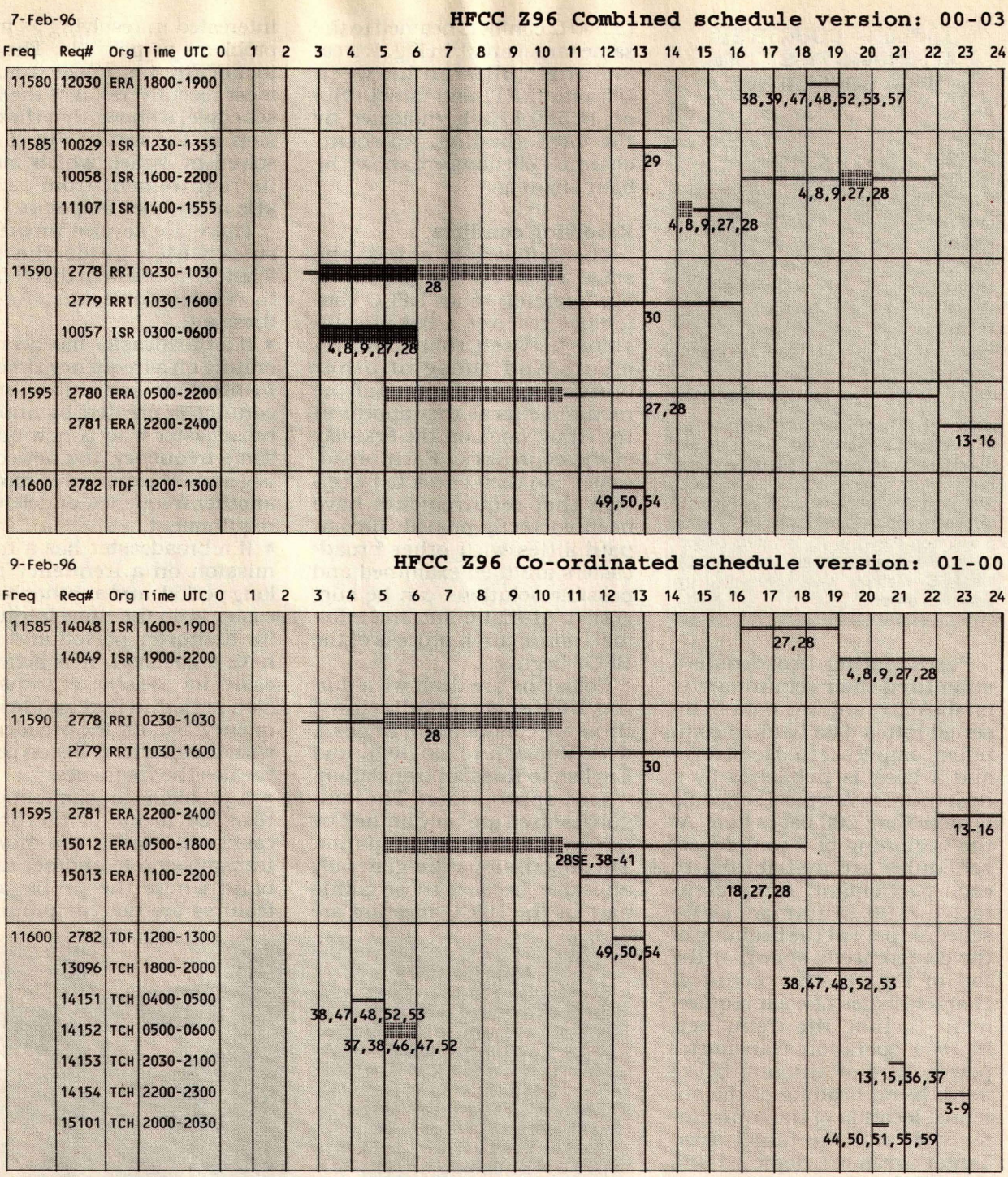

FIG. 1—TWO VIEWS OF A PAGE from the Summer 1996 HFCC working schedule. The top view printed at the beginning of the conference shows a co-channel collision (darkly shaded area) on 15,590 kHz between Ukraine (RRT) and Israel (ISL). Adjacent channel collisions (±5 kHz) are shown lightly shaded. The bottom view is the result of the conference's final version, indicating that the colision between Ukraine and Israel was solved by Israel vacating the frequency. An adjacent channel problem betwen Ukraine on 15,590 kHz and Greece (ERA), on 11,595 kHz, could not be resolved. Note the the 11,600 kHz frequency has many new schedules added, obviously taken from many other frequencies to avoid collisions.

It is common to switch from the 9-MHz band to either 7-MHz or 11-Mhz band.

The general practice has been that the larger broadcasters have been helpful in trying to assist the smaller ones. Some of the smaller participating broadcasters have as few as one or two transmitters, while some of the larger ones may have more than 100 transmitters at many sites hundreds of miles apart. It is a typical result for a broadcasting giant to switch from his original requirement to another on a different frequency, at another transmitting site and still enjoy favorable propagation results for his transmission. Small broadcasters with one or two

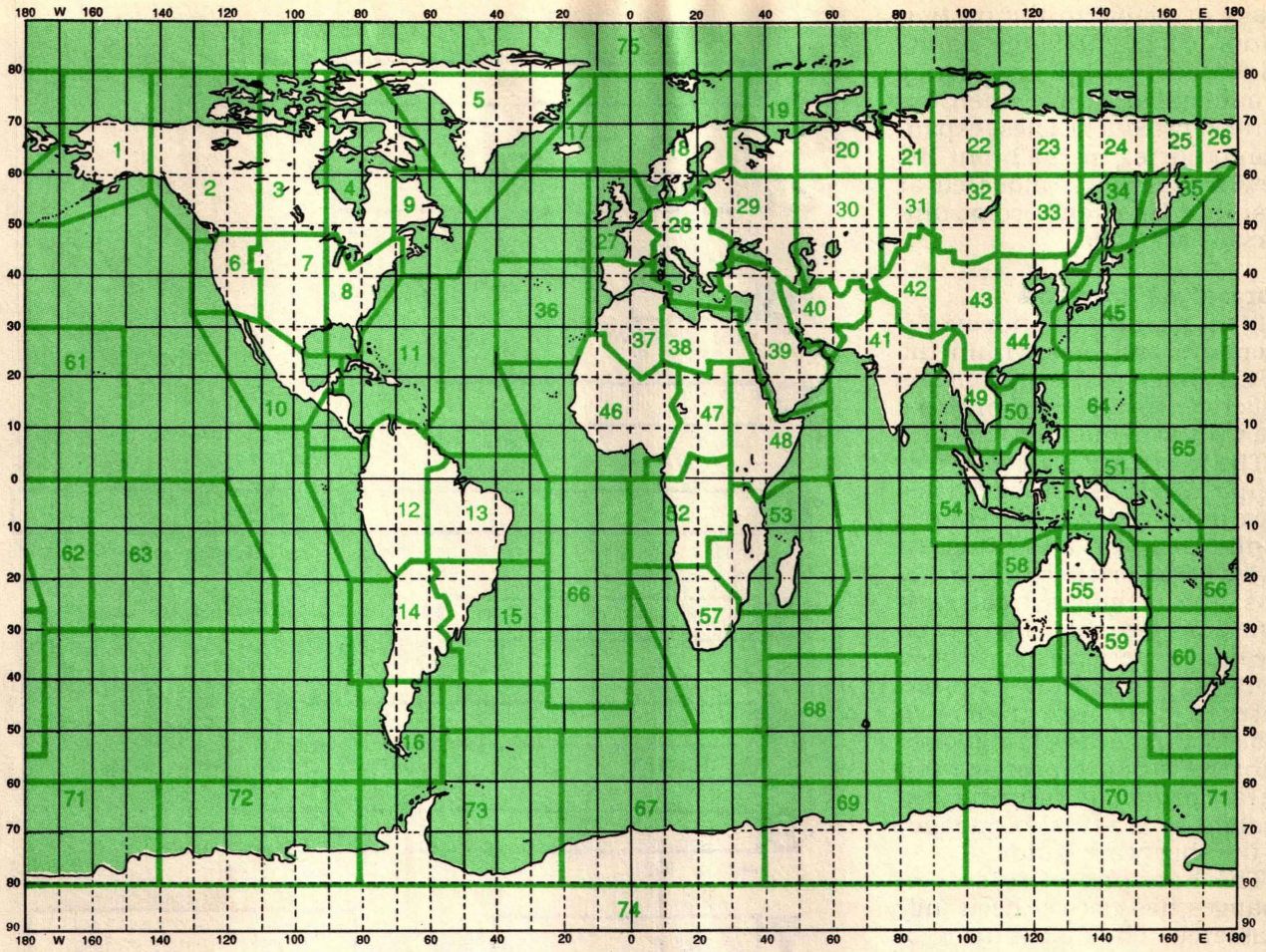

FIG. 2—THE TARGET AREA MAP of the world used to define collisions. The numbered areas are target areas often referred to as "CIRAF" zones, a Spanish acronym referring to the International High Frequency Radio Conference held in Mexico City in 1947 where they were first defined. Collisions are said to occur when two or more broadcasters target the same CIRAF zone on the same frequency, or on adjacent frequencies.

sites usually do not enjoy this flexibility of choice.

Russian conflicts

The Russians are the world's largest shortwave broadcaster, and their broadcasting requirements are generally about five thousand frequency hours per schedule, or about 30 percent of all submitted requirements. Consequently, the Russians have the greatest number of collisions with other participants. The HFCC has found the most efficient way of dealing with collisions involving the Russians has been to divide the collisions and to set them up at two separate tables at the conference. The six member Russian delegation generally divides into two groups, one of which handles the lower frequencies (6-11 MHz), and a second group with handles collisions involving 13 MHz and higher.

Broadcasters who have problems involving the Russians make an appointment to speak to them. The Russian delegates have been extremely cooperative in the HFCC, and have contributed toward the solution of numerous conflicts.

The evolution of HFCC

Since the formation of the HFCC its membership has doubled; as a natural consequence of this growth the number of collisions and the number of solutions has increased significantly. At a recent conference, there were 507 co-channel collisions at the start of the conference. By noon of the fifth and final day the number had been reduced to 299, an impressive 41 percent reduction in the most serious conflicts. This may not sound like much improvement; however, consider this: Each collision involves at least two broadcasters. When 208 collisions are rectified, that means at least 416 additional uninterfered daily and weekly broadcasts are transmitted for the world to hear.

Rapid resolution of conflicts has been brought about, in part, by the application of dedicated software, which has enabled the HFCC to provide the conferees with daily, completely up-to-date, usage books, requirements lists, and lists of collisions. In order to produce timely lists, changes made on a given day are collected at 4 P.M. and inserted into the data base. The computer processes the requirement changes and prints new lists that are available at the start of the next day's proceedings.

Figure 3 indicates the shortwave bands that have been gen-

erally available to the participants. Since 1979 the bands allocated to high-frequency broadcasting have been expanded twice. The latest expansion occurred in 1992, but the new frequencies allocated at that time have not become universally available.

Unresolved problems

Like all human endeavors, there are problems within the HFCC which currently limit its effectiveness. Several of these are worthy of mention.

The frequency managers participating in HFCC activities have differing levels of technical sophistication, and different levels of experience. Nevertheless, the members treat each other as co-equals. Those who are more experienced have been working with their counterparts in other organizations to assist with the dissemination of shortwave radio propagation data, and with information dealing with actual occupancy of the shortwave bands.

The handling of in-season changes has not yet been fully mastered. The distribution of information involving some 50 broadcast organizations is sometimes cumbersome. Methods of distributing schedule changes are constantly improving. They are not yet perfect.

The HFCC has evolved into a highly productive group dedicated to the solutions of problems in the high-frequency bands being used for broadcasting. Progress in the last five years has been significant and should continue as the software continues to be improved, and as participating broadcasters become more aware of the realities in specifying their requirements and the responsibilities of coordination.

The future–more planning

Over the past fifty years there have been numerous unsuccessful attempts to plan the bands used for shortwave broadcasting. Such planning attempts have failed because the number of requirements submitted by the broadcasters has always far exceeded the amount of available radio spectrum. To fit all the requirements into a master plan would necessitate either mandatory reduction of some of these requirements, or the massive expansion of the bands allocated to high-frequency broadcasting.

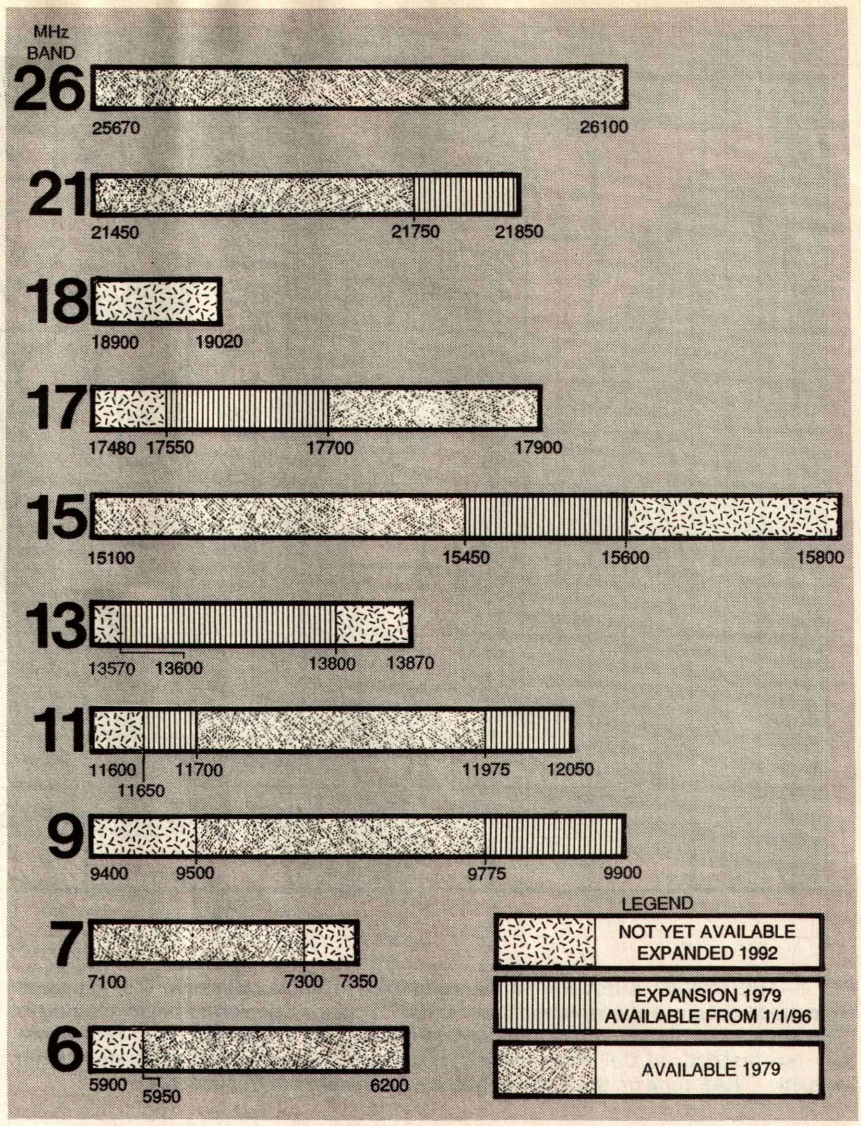

FIG. 3—THESE ARE THE SHORTWAVE bands that are available to participants. They have been expanded twice since 1979.

The most recent efforts to plan the high-frequency bands at high-frequency broadcasting planning conferences in 1984 and 1987 left much to be desired. The HFCC conferences, which are, in essence, short-term planning exercises, have provided the most viable means of establishing a world-wide planning model. The informal approach taken by the HFCC participants has provided a relaxed forum for solving many problems, and suggests a world-wide planning procedure.

By establishing regional committees like the HFCC for Asia and the Far East, Africa and the Middle East, Europe and the Americas, a procedure exists for coordinating up to 100 percent of the world's shortwave broadcasting allocations. Such informal regional conferences could provide the world with the framework for a revolutionary planning procedure, offering a degree of success never before achieved in the arena of world high-frequency broadcast planning. Such a revolution appears to be a distinct possibility for the future. Ω

MARK O. BENDER

TONAL VOLTMETER

This circuit gives an audible indication of voltage levels.

MOST VOLTMETERS HAVE A DIGITAL or analog moving-needle display to indicate the voltage being measured. However, the tonal voltmeter, or TVM presented here emits a tone that changes in pitch according to changes in the voltage being measured. While this is no substitute for the accuracy of a digital display, it can give a quick, relative indication of a voltage value without the user having to stop and look at a display.

The TVM is a great time-saver when performing quick voltage-level checks as normally done with a logic probe. If one regularly repairs or tests many of the same circuits, a tonal pattern of the various test points will soon be recognized. Then, any voltage reading that generates an unfamiliar tone will immediately be suspected as an indication of a possible problem that can then be investigated in greater detail with more sophisticated test equipment. The TVM is also a great way to find voltage peaks or nulls when making circuit adjustments. The simple circuit's main limitation is that the input voltage to be measured cannot be greater than the TVM circuit's supply voltage.

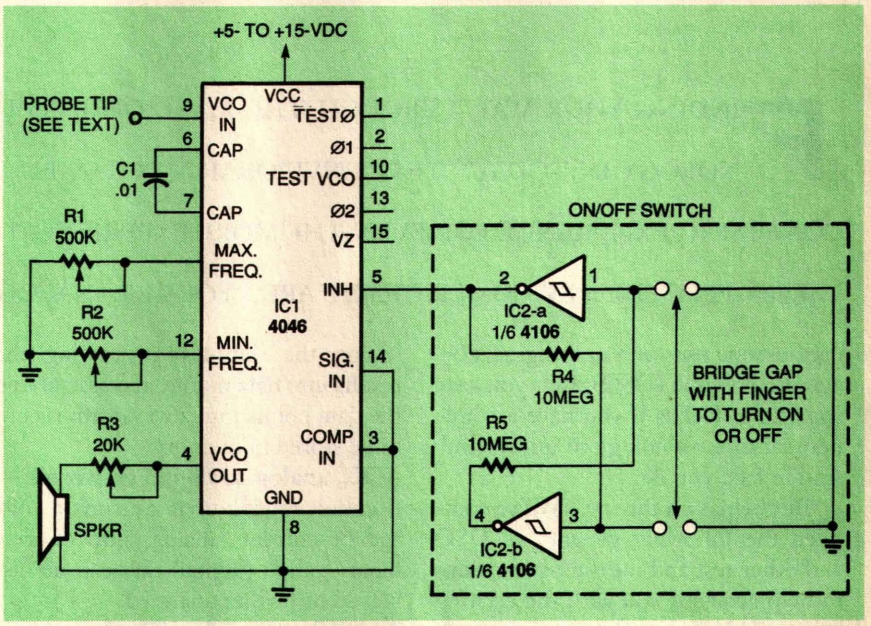

FIG. 1—TVM SCHEMATIC. The frequency of the VCO contained within IC1 is determined by the voltage at pin 9, C1, R1, and R2.

Circuitry

A schematic of the TVM circuit is shown in Fig. 1. The circuit is based on a CD4046B phase-locked loop (PLL) IC with a built-in voltage-controlled oscillator (VCO). The frequency of the VCO is determined by the voltage at pin 9, capacitor C1 between pins 6 and 7, potentiometer R1 at pin 11, which sets the maximum frequency, and potentiometer R2 at pin 12, which sets the TVM's minimum frequency.

The VCO output, which appears at pin 4, is normally fed back into the comparator input at pin 3. However, in this circuit, the VCO output drives a speaker directly. The VCO operates while the inhibit line (INH) at pin 5 is held logic low, and it turns off when INH is logic high.

A touch switch consisting of two Schmitt-trigger inverters (IC2-a and -b) turns the circuit on and off to conserve power when the TVM is not being used. The touch switch can be replaced with a standard SPST switch, if so desired. This is recommended if you don't have a Schmitt-trigger inverter and don't want to purchase one.

The TVM emits a low tone when reading a logic low. As voltage input increases, the tone pitch increases until the input voltage reaches a logic high. As the voltage input decreases, the pitch decreases.

Construction

The circuit is simple enough for point-to-point wiring on perforated construction board; no foil pattern is available. As mentioned before, a standard switch can replace the touch switch. If you use the touch switch, bring the two touch points shown in Fig. 1 (IC2 pins 1 and 6) to the outside of the enclosure you use and connect them to any pair of conductive pads. Leave a gap between the pads that you can bridge with your finger.

A probe for the VCO input can be made from a ball-point pen

Continued on page 79

PARTS LIST

R1, R2—500,000 ohms, potentiometer
R3—20,000 ohms, potentiometer
R4, R5—10 megohms
C1—0.01 µF, ceramic disc
IC1—CD4046B CMOS phase-locked loop, Harris or equiv.
IC2—CD4106B CMOS hex Schmitt trigger, Harris or equiv.
8-ohm speaker, probe body and tip (see text), shielded cable, 5-volt power supply, enclosure, solder

A Glossary of DSO test terms

FINDING YOUR WAY THROUGH THE MAZE OF TERMINOLOGY IN TODAY'S TEST ENVIRONMENTS CAN BE A CONFUSING EXPERIENCE FOR EVEN THE MORE EXPERIENCED USERS—PITY THE NEWCOMER. IF YOU ARE A FORMER ANALOG oscilloscope user or a new digital storage oscilloscope (DSO) user, you may sometimes feel as if you have a whole new set of terminology to understand. And in fact, you do.

But help is on the way. We've compiled the following glossary of DSO and other test and measurement terms to help acquaint you with the exciting new world of digital test equipment, and to ease the transition from an analog world to the digital storage realm. Keep in mind, however, that there will always be some overlap between the two environments, and thus between their respective terminologies.

To facilitate understanding all of the terms, we've organized the glossary around four general categories. Each one describes a specific class of activities that you will be performing with your DSO. They are:

- acquisition
- viewing the signal
- interpreting the waveform
- storage

We hope you will find this a helpful guide to understanding DSO terminology and some of the new capabilities of your digital storage oscilloscope.

ACQUISITION

Acquisition — The process of sampling signals from input channels, digitizing the samples, processing the results into data points, and assembling the data points into a waveform record to be stored in memory.

ADC, analog to digital converter — A circuit module that converts a voltage or current (analog) into discrete binary values (digital) that can be displayed or further analyzed.

Auto trigger mode — A trigger mode that causes the oscilloscope to automatically acquire a signal if it doesn't detect a triggerable event.

Average acquisition mode — A mode in which the oscilloscope acquires and displays a waveform that is the averaged result of several acquisitions. This reduces the apparent noise.

Digital-to-analog converter — A device that converts an input binary code (digital) into a continuous variable voltage (analog).

Digital Real-Time (DRT) digitizing — A digitizing technique that samples the input signal with a sample frequency of four to five times the oscilloscope bandwidth. This technique is ideal for capturing transient or single-shot events.

Digitize — The process of converting a continuous analog signal, such as a waveform, to a set of discrete numbers representing amplitude of the signal at specific points in time.

ET, equivalent-time sampling — A sampling mode in which the oscilloscope constructs a picture of a repetitive signal by capturing some information from each repetition.

GS/s, gigasamples per second — One billion samples per second.

Normal trigger mode — A mode where the oscilloscope only acquires a waveform if a valid trigger event occurs.

Peak detect — An acquisition mode for digital oscilloscopes that captures and displays the extreme peaks of a signal.

Real-time — The actual time during which a physical event takes place.

Real-time sampling — A sampling mode in which the oscilloscope collects as many samples as it can as the signal occurs.

Sample acquisition mode — A mode in which the oscilloscope creates a record point by saving the first sample during each acquisition interval. This is the default mode of the acquisition system.

Sweep — One horizontal pass of an oscilloscope's electron beam, from left to right across the CRT. In digitizing scopes, this spec has evolved into time/division range.

Transient or single-shot event — An oscilloscope-measured signal that only occurs once. DSOs, especially, digitizing real-time DSOs, excel at capturing these kinds of elusive events.

Trigger — The circuit that initiates a horizontal sweep on an oscilloscope and determines the beginning point of the waveform.

Trigger level — The voltage level that a trigger source signal must reach

*Tektronix, Inc.

before the trigger circuit initiates a sweep.

VIEWING THE SIGNAL

Active cursor — The cursor that moves when you adjust the +/− rocker. The @ readout on the display shows the position of the active cursor.

Cursors — Reference lines or markers on an oscilloscope display that can be aligned with a waveform to make accurate measurements, expressed in voltage or time values.

Delayed sweep — An oscilloscope function that permits delaying the start of waveform display for a specified time after a trigger event.

Envelope — The outline of a signal's highest and lowest values acquired over many repetitions.

Horizontal bar cursors — The two horizontal bars that you position to measure the voltage parameters of a waveform. The oscilloscope displays the active cursor value with respect to ground and the voltage value between the bars.

LCD, liquid crystal display — A type of display used on many handheld oscilloscopes because of its easy readability and low power use.

LED, light emitting diode — The bright digital display used on many bench test oscilloscopes.

Paired cursors — Two cross-shaped cursors that automatically track the vertical values of a waveform when you adjust its horizontal position. The oscilloscope displays the voltage and time values between the paired cursors.

Pixel — The smallest image-forming unit on a video display. The TekScope display is 320 pixels wide by 240 pixels high.

Pop-up menu — A submenu that temporarily occupies part of the waveform display and presents you with choices associated with the main menu item selected.

Pulse — A common waveform shape that has a fast-rising edge, a width and a fast-falling edge.

Record length — The number of waveform points used to create a record of a signal.

Resolution — The smallest unit that can be detected and displayed by an oscilloscope or other measurement device.

Roll mode — The ability of a DSO to continuously update its display memory as new data points are captured, permitting continuous observation of signal changes. Used with very slow time base speeds.

Sawtooth wave — A waveform containing a ramp and an abrupt return to its initial value; its graphic plot has the shape of sawteeth.

Selected waveform — The waveform on which all measurements are performed and which is affected by vertical position and scale adjustments of the oscilloscope.

Sinewave — The most common waveform (and normal AC waveform) whose graphic plot of voltage against time has the shape of a sine curve.

Spike — A short duration pulse superimposed on an otherwise regular or desired waveform.

Symmetry — A way of changing the shape of the output signal waveform without changing the signal frequency, so the waveforms are not symmetrical with respect to their longitudinal axis.

Vertical bar cursors — The two vertical bars positioned to measure the time parameter of a waveform record. The oscilloscope displays the value of the active cursor with respect to trigger and the time value between the bars.

Vertical resolution — In a DSO, this value indicates how precisely the ADC can turn input voltages into digital values.

Waveform — A graphic representation of a voltage varying over time.

Waveform point — A digital value representing the voltage of a signal at a specific point in time. Waveform points are calculated from sample points and stored in memory.

XY format — A display format that compares the voltage level of two waveform records point for point, useful for studying phase relationships between two waveforms.

YT format — The conventional oscilloscope display format showing the waveform voltage (on the vertical axis) as it varies over time (horizontal axis).

Zoom — The ability to expand a particular segment of a waveform to see details more clearly and to limit measurements within a given region of data. This capability is found only in DSOs.

INTERPRETING WAVEFORMS

Analog — Data in the form of continuously variable physical qualities such as voltage.

Automatic measurements — The broad range of measurements performed by the digital signal processors in DSOs, including such measurements as add, subtract, divide, multiply, as well as more complex measurements including averaging, FFT functions, histograms and pass/fail testing.

Autoranging — Automatically selects the appropriate range for making a measurement.

Continuity — A test to verify electrical conductivity from one point to another.

Delay time — The time by which a signal is retarded.

Diode test — A test to verify polarity and to measure the forward voltage drop of a semiconductor junction.

Distortion — An undesirable change in the waveform of a signal.

Floating measurements — Voltage measurements where the reference voltage is not earth ground.

Frequency — The number of events per unit of time for a periodic function. Measured in hertz (Hz).

Gain — The increase in signal amplitude as it passes through an amplifier or other circuit, expressed as a ratio.

Glitch — An intermittent error in a circuit.

Ground loop — Current flow between two or more ground connections, where each connection is at a slightly different potential due to the resistance of the common connection.

Harmonic — A sinusoidal component of a periodic wave with a frequency that is an integral multiple of the fundamental frequency.

Impedance — The total opposition to current in a circuit, composed of resistance and reactance (inductive or capacitive).

Linearity — The closeness with which a quantity represents a straight line when plotted against a variable.

Lissajous figure — A special case of x-y plot in which the signals applied to both axes are sinusoidal functions. Useful for determining phase and harmonic relationships. For a stable display, the signals must be harmonics.

Load — The impedance that a circuit

TIPS FOR MAIL ORDER PURCHASE

It is impossible for us to verify the claims of advertisers, including but not limited to product availability, credibility, reliability and existence of warranties. The following information is provided as a service for your protection. It is not intended to constitute legal advice and readers are advised to obtain independent advice on how to best protect their own interests based upon their individual circumstances and jurisdictions.

1. Confirm price and merchandise information with the seller, including brand, model, color or finish, accessories and rebates included in the price.

2. Understand the seller's return and/or refund policy, including the allowable return period, who pays the postage for returned merchandise and whether there is any "restocking" or "return" charge.

3. Understand the product's warranty. Is there a manufacturer's warranty, and if so, is it for a U.S. or foreign manufacturer? Note that many manufacturers assert that, even if the product comes with a U.S. manufacturer's warranty, if you purchase from an unauthorized dealer, you are not covered by the manufacturer's warranty. If in doubt, contact the manufacturer directly. In addition to, or instead of the manufacturer's warranty, the seller may offer its own warranty. In either case, what is covered by warranty, how long is the warranty period, where will the product be serviced, is there a charge for service, what do you have to do to obtain service and will the product be repaired or replaced? You may want to receive a copy of the written warranty before placing your order.

4. Keep a copy of all transactions, including but not limited to cancelled check, receipt and correspondence. For phone orders, make a note of the order including merchandise ordered, price, order date, expected delivery date and salesperson's name.

5. If the merchandise is not shipped within the promised time, or if no time was promised, within 30 days of receipt of the order, you generally have the right to cancel the order and get a refund.

6. Merchandise substitution without your express prior consent is generally not allowed.

7. If you have a problem with your order or the merchandise, write a letter to the seller with all the pertinent information and keep a copy.

8. If you are unable to obtain satisfaction from the seller, contact the consumer protection agency in the seller's state and your local Post Office.

If, after following the guidelines, you experience a problem with a mail order advertiser that you are unable to resolve, please let us know. Write to Advertising Department, Gernsback Publications Inc., 500B Bi-County Blvd. Farmingdale, NY 11735.

Be sure to include copies of all correspondence.

presents to the output of the reference instrument.

Loss — Power expended without accomplishing useful work, typically expressed in watts.

Modulation — A process by which the amplitude, phase or frequency of a sine wave is altered in accordance with information to be transmitted.

Noise — Unwanted disturbances superimposed on a useful signal that tend to obscure its information content.

Output frequency — The frequency of the signal produced by an instrument.

Overrange — Signal amplitudes or frequencies above the specified limits of the instrument.

Peak-to-peak voltage (Vp-p) — The voltage between the positive and negative peaks of a sine wave.

Phase — A relative quantity — expressed in degrees of phase — that describes the time relationship between or among waves of identical frequency; the frequency of the signal determines the length of time corresponding to one degree of phase.

Peak — The highest or lowest point of a signal wave, referred to as the maximum voltage level measured for a zero reference point.

Polarity — The positive or negative direction of voltage or current.

Pulse amplitude — The difference between the two states in a pulse, usually measured in volts.

Pulse fall time — The time interval for the falling edge of a pulse to go from 90% to 10% of the amplitude.

Pulse rise time — The time it takes for the rising edge of a pulse to go from 10% to 90% of pulse amplitude.

Pulse width — The time interval between the 50% amplitude points of the rising and falling edges of a pulse.

Ramp — The transition between voltage levels of a waveform where that transition occurs at a constant rate of change.

Response time — The time required for a resulting condition to reach steady state after variation of an input quantity.

Ringing — A distortion, in the form of circulating currents in the inductance and capacitance, which usually follows a major transition.

RMS — Root Mean Square—an expression of the effective value of an AC waveform.

Sensitivity — The smallest input signal to which an instrument can respond.

Shunt — A conductor of known resistance used to measure current flow between two points in a circuit.

Signal path compensation (SPC) — The ability of the oscilloscope to minimize the electrical offsets in the vertical, horizontal and trigger amplifiers caused by ambient temperature changes and component aging.

Slew rate — The maximum limit, under linear operating conditions, that the speed of output voltage can change with respect to change in input voltage. Measured in volts per second.

Totalize — A measurement mode that counts signal events at one-count-per-event increments.

Vertical resolution — In a DSO, this value indicates how precisely the ADC can turn input voltages into digital values.

Vertical sensitivity — A value indicating how much an oscilloscope's vertical amplifier can increase a weak signal voltage.

Wavelength — The distance between two points of corresponding phase in consecutive cycles of a periodic wave.

Readers can contact Tektronix by calling 800-479-4490, Action Code 300. Additionally, Tektronix maintains a home page at:
http://www.tek.com/Measurement

STORAGE

Memory store/recall — Stores a setup, waveform or series of waveforms in memory that can be recalled at a later time.

Min/max store — The min/max function captures and stores minimum and maximum readings in memory and can be used to monitor a signal for seconds or days.

Reference waveform — A saved waveform selected for display. Some DSOs can display two reference waveforms simultaneously.

Relative reference — Stores a reading in memory and shows the difference between it and any future readings. EN

BY DON LANCASTER

An introduction to vectors, Earth-field magnetometry, new flux-gate sensors and ICs, and more

WE HAVE A NEW MAGNETIC SENSOR THIS MONTH THAT SURE APPEARS REASONABLY PRICED AND EXTREMELY EASY TO USE, ESPECIALLY FOR COMPASS AND NAVIGATION APPLICATIONS. BUT FIRST, I THOUGHT WE MIGHT GO over a fundamental or two, so let's get right to it.

Vectors

A *scalar* quantity has *one* simple value, such as three quarts of milk. A *vector*, on the other hand, quantity relates *two or more* values. A car may travel at a scalar *speed* of 35 miles per hour, or travel at a vector *velocity* of 35 miles per hour to the northwest.

As Fig. 1 shows, any two dimensional vector can be drawn as an arrow. The *length* of the arrow tells us how strong the vector is and the *direction* of the arrow can tell us exactly where it is heading.

If you plot any vector graphically, you have a choice of many different *coordinate systems*. The *rectangular* coordinate system will go "so many steps over" and "so many steps up" to define a vector.

For instance, in electronics you often will plot real power left to right and the reactive power up and down. Real power is power that is actually generated or consumed in resistors or generators. Reactive power is power that gets swapped back and forth as energy storage between inductors and capacitors in your circuit.

The convention is to put resistors to the right, inductors up, generators (or "negative resistors") left, and the capacitors down. "East" is defined as the zero axis, such as you'd get when routing current into a resistor.

A *phase angle* is usually defined *counterclockwise* from 0 on up to 360 degrees, with zero degrees heading east. Some phase angles can also be separately defined as 0 to 90 degrees *lagging* as you go more inductive. Or as 0 to 90 degrees *leading* as you go more capacitive.

In other times and places, you pick other schemes for your rectangular coordinates. Most geographic maps place north as "up" or to your "top", and then express the *bearing* as so many degrees *clockwise*. Southwest is a bearing of 225 degrees. Needless to say, it is important to use the same origin, notation, and angle direction conventions as everyone else.

Sometimes it is best to use a vector as an arrow pointing in a direction. For example, an impedance of 5 ohms at a phase angle of 53.13 degrees lagging. When you do this, you are said to be in *polar coordinates*. Other times, it is better to *resolve* a vector into its rectangular *component parts*; 4 ohms resistive and 3 ohms inductive, for example.

Simple high school trigonometry can get you between rectangular and polar coordinates. Say you have an electronic vector in polar coordinates that has a strength r and a direction of q degrees. The resolved x and y rectangular components will be

$$x = r \cos\Theta$$
$$y = r \sin\Theta$$

To get to polar from rectangular coordinates, just remember the Indian chief who was running those fertility experiments: *The sum of the squaw on the hippopotamus hide equals the sum of the squaws on the other two hides.* Or, more conventionally:

$$r = \sqrt{x^2 + y^2}$$

And the phase angle

$$\Theta = \tan^{-1}(y/x)$$

tan^{-1} is math shorthand for *arctan* or *"the tangent whose angle is"*.

Details end up somewhat different with geographic maps. You substitute *north* for your x component and *east* for the y component to get the correct bearing using the above equations.

Earth field magnetometry

Bunches of helpline calls lately on measuring the Earth's magnetic field: for the solid state compasses used in orienteering, surveying, or caving; for vehicle and robotics navigation; for old archaeological mapping; for virtual reality headgear; or for research into earthquake detection.

The earth is a giant magnet most likely created by its spinning liquid nickel iron core. At any point on the earth surface, you'll find a *three* dimensional magnetic vector having x, y, and z components. The up and down part is known as *magnetic inclination* and can be measured with a *dipping needle*. The inclination varies with latitude; it ends up as horizontal near the equator and as vertical near the

new from
DON LANCASTER

ACTIVE FILTER COOKBOOK
The sixteenth (!) printing of Don's bible on analog op-amp lowpass, bandpass, and highpass active filters. De-mystified instant designs. **$28.50**

CMOS AND TTL COOKBOOKS
Millions of copies in print worldwide. **THE** two books for digital integrated circuit fundamentals. About as hands-on as you can get. **$24.50** each.

INCREDIBLE SECRET MONEY MACHINE II
Updated 2nd edition of Don's classic on setting up your own technical or craft venture. **$18.50**

LANCASTER CLASSICS LIBRARY
Don's best early stuff at a bargain price. Includes the CMOS Cookbook, The TTL Cookbook, Active Filter Cookbook, PostScript video, Case Against Patents, Incredible Secret Money Machine II, and Hardware Hacker II reprints. **$119.50**

LOTS OF OTHER GOODIES

Ask the Guru I or II or III	$24.50
Hardware Hacker II or III	$24.50
Micro Cookbook I	$19.50
PostScript Beginner Stuff	$29.50
PostScript Show and Tell	$29.50
Intro to PostScript Video	$29.50
PostScript Reference II	$31.50
PostScript Tutorial/Cookbook	$19.50
PostScript by Example	$31.50
Understanding PS Programming	$29.50
PostScript: A Visual Approach	$22.50
PostScript Program Design	$24.50
Thinking in PostScript	$22.50
LaserWriter Reference	$19.50
Type 1 Font Format	$15.50
Acrobat Reference	$24.50
Whole works (all PostScript)	$380.00
Synergetics Surplus Catalog	FREE
Technical Insider Secrets	FREE

POSTSCRIPT SECRETS
A Book/Disk combination crammed full of free fonts, insider resources, utilities, publications, workarounds, fontgrabbing, more. For most any PostScript printer. Mac or PC format. **$29.50**

BOOK-ON-DEMAND PUB KIT
Ongoing details on Book-on-demand publishing, a new method of producing books only when and as ordered. Reprints, sources, samples. **$39.50**

THE CASE AGAINST PATENTS
For most individuals, patents are virtually certain to result in a net loss of sanity, energy, time, and money. This reprint set reveals to you tested and proven real-world alternatives. **$28.50**

BLATANT OPPORTUNIST I
The reprints from all Don's Midnight Engineering columns. Includes a broad range of real world, proven coverage on small scale technical startup ventures. Stuff you can use right now. **$24.50**

RESOURCE BIN I
A complete collection of all Don's Nuts & Volts columns to date, including a new index and his master names and numbers list. **$24.50**

FREE SAMPLES
Visit The Guru's Lair at http://www.tinaja.com for interactive catalogs and online samples of Don's unique products. Searchable reprints and reference resources, too. Tech help, hot links to cool sites, consultants. email: don@tinaja.com
FREE VOICE HELPLINE VISA/MC

SYNERGETICS
Box 809-EN
Thatcher, AZ 85552
(520) 428-4073

 CIRCLE 205 ON FREE INFORMATION CARD

A vector can be shown in its **polar coordinate** form as an arrow. The length of the arrow *r* conveys the vector's **magnitude** and the positioning θ of the arrow will convey the vector's **direction**...

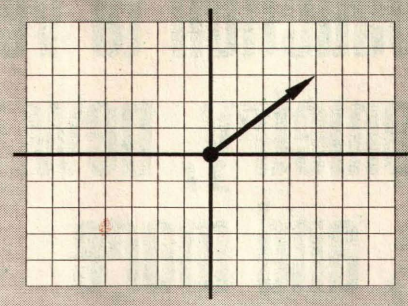

In this example, we have a vector that is five units long. Made up of whatever four blocks stand for on the horizontal *x* axis and whatever three blocks stand for on the vertical *y* axis. These blocks are in **rectangular coordinate** form.

If you are using "math" or "electronic" coordinates, real power relates along the *x* axis and reactive power along the *y* axis. Phase angles are measured **counterclockwise** from due **east**. In this case, we might be showing a 5 Ohm impedance with a 4 Ohm real component and a 3 Ohm reactive component. The phase angle of our vector is easily found to be 36.9 degrees.

On the other hand, if you are using "map" or "geographic" coordinates, north is to the top and east is to the right. Bearings are measured **clockwise** from **north**. The bearing of the very same vector is now 53.1 degrees!

Thus, when in Rome... It is extremely important to use both the axis and the angle direction conventions that are consistent with the intended use.

If you are using electronic coordinates, these trig relationships get you from polar to rectangular coordinates and back again...

$$x = r\cos\theta$$

$$y = r\sin\theta$$

$$r = \sqrt{x^2 + y^2}$$

$$\theta = \tan^{-1}(y/x)$$

FIG. 1—A VECTOR GETS USED to represent a relationship between two or more independent quantities. Here's some of the fundamentals.

poles. The back and forth part is known as a *magnetic declination* and is what gets measured with a *compass*. The difference between where a compass points and where you are heading is called a *bearing*.

For accuracy, the declination and inclination *must* be kept separate. For reliable readings *a compass must be held absolutely level!* Some precision boat compass mountings are known as *binnacles*. They are either floated on some liquid or are gravity-gimbal mounted to keep them level.

Note that a compass does *not* point true north. It points somewhere near true north to an eternally wandering *magnetic pole*. Thus, it is *very* important for you to distinguish between *true north* and a *magnetic north*. Here in Arizona, the declination is some 13 degrees easterly. Which says that a compass points badly to the east of where it is supposed to. Premium compasses and survey gear will have a provision that lets you automatically subtract out this error. If you use this feature, be sure it is correct for where you are.

In Kansas, there is very little error between true north and magnetic north. This is along *the line of zero declination*. But, when you are not in Kansas anymore, the rule is *the error*

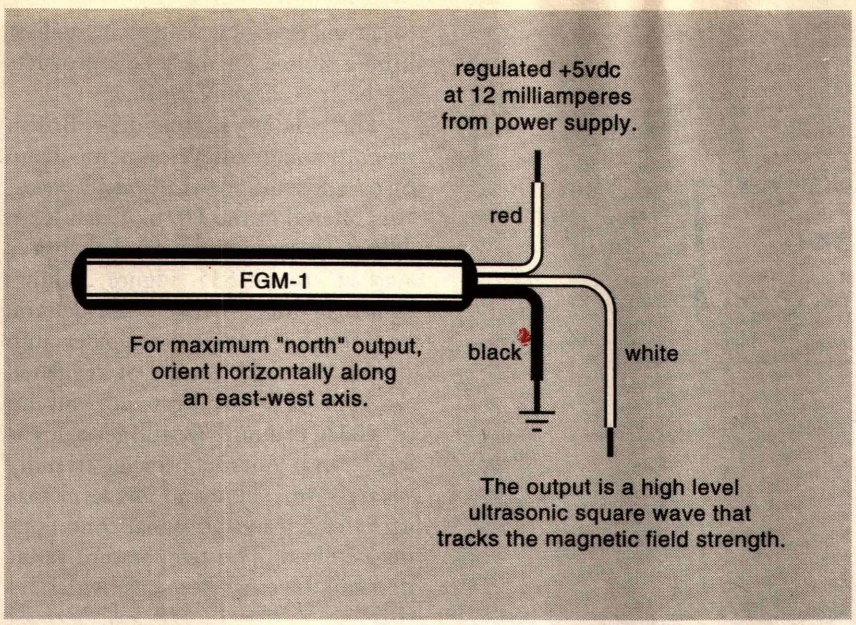

FIG. 2—THE FGM-1 MAGNETIC FIELD SENSOR is extremely easy to interface to microcontrollers. Obvious uses include vehicle detectors, solid state compasses, navigation aides, and virtual reality apps.

points to Kansas. In California, the compass points to the *right* of where you'd expect it to. In Vermont, it will point to the *left*.

Despite its humongous size, the earth's field at any locale is rather weak. One gauss is the nominal field strength. At mid-latitudes, 0.6 gauss is much more typical. An older field measure is the *gamma*. You will find 100,000 gammas in a gauss.

It is extremely difficult to build an electronic solid-state compass having an accuracy that is better than a few degrees. A minimum of twelve bits of resolution is an absolute must, but fourteen to sixteen bits are preferred. Temperature and calibration effects cut into this margin. A level scheme of one sort or another is mandatory.

Also required is some method to compensate for nearby metal. Parts of an automobile exude *ten times* or higher fields than the one you want to measure. A well designed digital car compass offers some calibration procedure you have to go through, such as driving around the block exactly one time. One classic paper on all this is called *Earth's Field Magnetometry* by W. F. Stuart, in the *Reports on Progress in Physics*, 1972, vol 35, on pages 803-881.

Some approaches

The classic approach to a compass is to magnetize something and float it. Another is to mount it on leveled low friction bearings. It will continuously try to point to the north. Obvious problems here include damping, "stiction," and vibration. It is also real tricky to get a digital data conversion.

There are quite a few *Hall Effect* devices cheaply available. These are usually transistor sized devices that produce a digital or analog output when any magnet gets placed nearby. *Allegro* and *MicroSwitch* are typical sources for these. Unfortunately, today's Hall Effect devices aren't nearly sensitive enough for earth magnetometry uses. They will usually miss by a factor of *one hundred* or more. You'll also find *magnetoresistor* components: resistors whose value changes with magnetic field strength. Unfortunately, every magnetoresistor I have seen has such incredibly bad habits as to make it *totally useless* for earth field magnetometry. Today's magnetoresistors aren't all that accurate or linear, have a strong temperature dependence, need bias magnets, and offer poor cross-axis sensitivity. They also have the nasty habit of suddenly turning themselves inside out without warning—literally flipping out!

A *proton precession magnetometer* is a bottle of pure water that has a coil around it. The heavy current through the coil can suddenly cease, causing wobbling of certain spinning water molecules. This precession in turn can induce a noisy and sub-microvolt audio signal around 1500 hertz back into the coil for a tiny fraction of a second. Accurately measuring that frequency indicates the strength of the magnetic field. Sensitivity can be exceptionally high.

The proton precession devices are

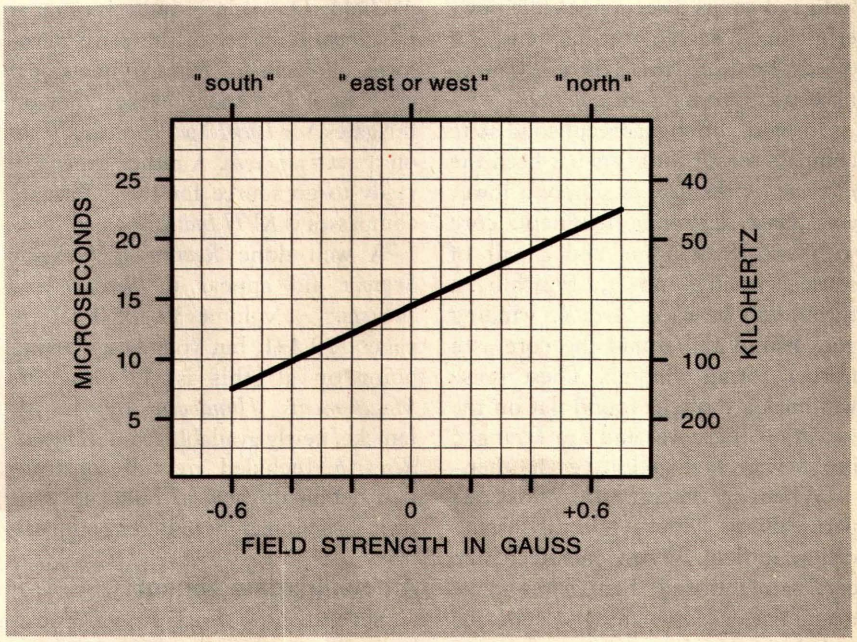

FIG. 3—THE TIME PERIOD OF THE FGM-1 increases or decreases with changing magnetic field strength and polarity. The initial 6% linearity can be significantly improved by table lookup or by using field nulling techniques.

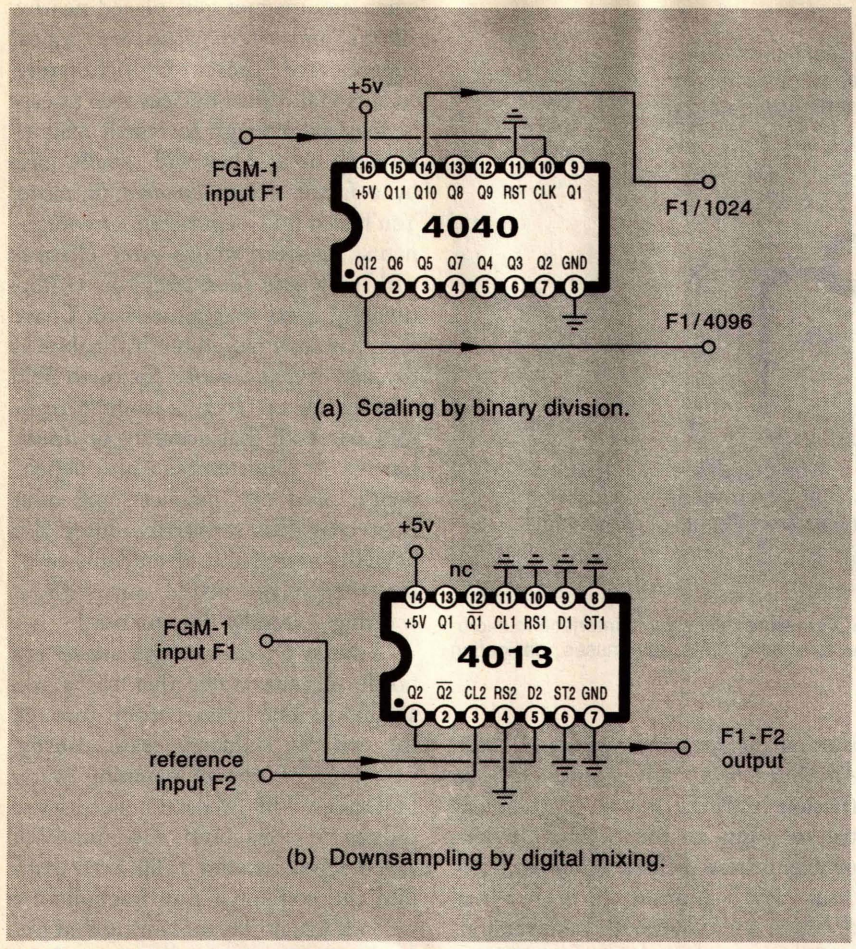

FIG. 4—THE FGM-1's OUTPUT SIGNAL can be reduced in frequency for accurate conversions in certain low end microcomputers.

scalar sensors that measure *only* a total field and *not* its direction. While powerful for archaeological mapping and oil exploration, there is no way to make a compass out of one.

Instead, the mainstream solid state compass sensor for years has been the *fluxgate*. A fluxgate is simply a lower cost *hard saturating* magnetic core with a drive winding and a pair of sense windings on it. Typically, a toroid will be used. A drive winding goes round and round the core as a normal toroid winding. These sense windings are often wound flat on the *outside* of the core, and are arranged precisely at 90 degrees to each other.

When *not* energized, a fluxgate's permeability "draws in" the earth's magnetic field. When energized, the core saturates and then ceases to be magnetic. As a switching occurs, the earth's field is drawn into or released from the core, resulting in a small induced voltage that is proportional to the strength and direction of the external field. This voltage pulse is often at the *second harmonic* of the drive waveform, allowing for fairly simple signal extraction. For more background on fluxgates, see *hack12.pdf* and *hack70.pdf* on *www.tinaja.com*. A rather expensive ready-to-go source for these fluxgate compasses is *KVH Industries*.

A well done *Review of Fluxgate Sensors* did appear in *Sensors and Actuators A*, volume 33 for 1992 on pages 129-141, but your best starting point on all this is the *Magnetic Mesurements Handbook* by J. M. Janicke, newly available from *Magnetic Research*. Included are full construction details on how to build up your own fluxgate magnetometer compass.

A new fluxgate sensor

Several new fluxgate variations have recently emerged. They still are driven and cored small coils, but are potentially a lot cheaper and allow lower operating currents. The highest profile source for these new products has been *Precision Navigation*.

There is an exciting new British magnetometer development from *SCL* called the *self-oscillating fluxgate*. It is offered in the US by Erich Kern at *Fat Quarters Software*. The prices start at around $35. Figure 2 shows details on their FGM-3 sensor. You basically have a small cylinder into which you send 12 mA of regulated +5 volts of DC and ground, and out of which you *directly* will get a high-level and microcontroller-friendly squarewave. There's no low level analog circuitry and no signal conditioning involved! The temperature variation and the cross-axis sensitivities are also low.

The squarewave's *time period* is pretty much proportional to the field strength. As Fig. 3 shows us, the time period ranges from around 7 microseconds at −0.6 gauss (south), to 14 microseconds at 0.0 gauss (east or west), and up to 25 microseconds at +0.6 gauss (north). The initial linearity is around 5 percent or so, but it can be corrected down into the 0.3-percent range for fractional degree accuracy.

These time periods are a tad fast for certain older microprocessors to accurately resolve. Figure 4 shows us two methods of making the outputs more micro friendly. A simple CMOS 4040 binary divider can be used to directly lower the output frequencies and thus lengthen the measurement period. Or half of a CMOS 4013 D-flop can be used to serve as a digital mixer or downconverter. Downconverting can give you a greater difference between minimum and maximum values. Note that creative PIC machine-language programming can eliminate the need for either of these circuits by doing the same job in high-speed internal firmware.

To build a compass, you can place one FGM-3 on some spinnable level surface. Or you might use a pair of these at right angles to each other. There is also a new dual unit called the FGM-2. This one is disk shaped, being a tad over an inch in diameter and a quarter inch thick. The free *SCL* ap notes show you simple *octant* algorithms that get rid of any fancy math.

NAMES AND NUMBERS

Andrews Decal
6559 N. Avondale Avenue
Chicago, IL 60631
Tel: 312-775-1000

Bertonee
184 High Street
7th Fl.
Boston, MA 02110
Tel: 800-510-5400

Clegg
19220 S. Normandie Avenue
Torrance, CA 90502
Tel: 310-542-1600

Instant & SC Printer
425 Huehl Rd., Bldg. 11
Northbrook, IL 60065
Tel: 708-564-5940

National Semiconductor
2900 Semiconductor Rd.
Santa Clara, CA 95052
Tel: 800-272-9959

Paper Plus
300 Oceangate #800
Long Beach, CA 90802
Tel: 213-436-8291

Pericom
2380 Bering Drive
San Jose, CA 95131
Tel: 408-435-0800

Philips Semiconductor
811 E. Arques Avenue
Sunnyvale, CA 94088
Tel: 800-234-7381

Power Integrations
477 N. Mathilda Avenue
Sunnyvale, CA 94086
Tel: 408-523-9265

Quick Printing
1680 S.W. Bayshore Blvd
Port St. Lucie, FL 34984
Tel: 407-879-6666

Raychem
300 Constitution Drive
Menlo Park, CA 94025
Tel: 800-227-7040

Synergetics
Box 809
Thatcher, AZ 85552
Tel: 520-428-4073

3M
3M Center Bldg.
St. Paul, MN 55144
Tel: 800-826-4886

Velcro Systems
406 Brown Avenue
Manchester, NH 03108
Tel: 603-669-4892

Web Master
492 Old Connecticut Path
Framingham, MA 01701
Tel: 508-872-0080

WEB Trac/LDS
571 Central Avenue
Murray Hill, NJ 07974
Tel: 800-ASK-LDSI

Specialized support chips are also available. For example, their SCL001 is for field nulling gauss meters, the SCL002 is for vehicle detectors, and the SCL006A for single-axis earth magnetometry. The *Basic Stamp* or another PIC is your obvious choice for interface and display. Stay tuned for more.

Magnetometry resources

For this month's resource sidebar, I've gathered together a few places to go for more compass info. *Dinsmore* is big on low-cost and low-resolution devices based on moving magnets and Hall sensors. *Honeywell* is into over-priced magnetoresistors. Your useful tech journals include *Sensors*, *Measurement & Control*, the *ITS World* (*Integrated Transportion Systems*), or GPS World. Books on all this are available from the *Navtech Bookstore*. I have also got some key navigation and GPS web site links up for you on my Web site, *www.tinaja.com*.

Web hits and misses

You don't have to be on the web all that long to discover that *www* means *world wide wait* and *url* stands for *utterly rancid location*. You will also see lots of people ranting and raving over the number of *hits* their site gets. Just what is a hit? Well, a *hit* is an obscenely bloated and utterly misleading measure of the supposed popularity of a web site. So much so that *hits are a totally useless index of your site's popularity!*

Unlike any book reader or a store customer, web site access gets done in bits and pieces. One web page or one file at a time. As these bits and pieces are sent, they get recorded in a pair of very important files, called the *log* file and the *error* file. Your access provider should tell you how to get at these crucial files. They are ordinary text files that can easily be copied to host. Each access is noted as a one line record of characters in the log file.

So is an access a hit? Uh, not so fast. Typical access to your home page probably also grabs some wallpaper, some buttons, and some fancy rules. Which *also* will go into your log file. Is this one hit or four? If the same visitor comes back in a few minutes, is this the same hit or a new one? Or a few hours? Or a few days?

What if the visitor is really some *spider* from a search service? Is this a hit? How many? What if you have no foreign sales or support. Do foreign hits count? What if someone takes one look at your home page and then quickly leaves?

These log files tell you about each visitor. Which pages he requested in what order. Plus how he left and any site bugs they discovered along the way. These mistakes are summarized in the separate error file.

Your simplest and cheapest way to measure site "hits" is to note the *change of size* of your log file each day. Divide by 75 to get your total number of hits. The 75 comes about because there are around seventy-five characters in an average log line. What if you want to know exactly how many left-handed Brazilian cat fanciers visit your site at 2 a.m. on Tuesdays? You can snoop around inside your log file to extract all this info. This is especially easy to hack using the general purpose PostScript computing language. Just write the file to your printer's hard disk. But any old data word processor or database tool will work.

There are quite a few sources for *hit analysis* software. One shareware location is *www.lds.com* with their *Webtrac* product. This one generates all sorts of fancy printed reports and colorful graphs and charts. Your best overall measure of the performance of your web site is how many people actually get far enough to fully download a lengthy file that you really want them to, such as a catalog or some hot new content.

All of which leads to an "exchange rate" between hits and useful visitors. For one month, a while back, when it was just starting, my new *www.tinaja.com* received some 18,000 "any page" US hits, while actually sending out 285 catalogs. My web exchange

EARTH'S FIELD MAGNETOMETRY RESOURCES

Allegro Micro Systems
Box 15036
Worcester, MA 01605
Tel: 508-853-5000

F. W. Bell
6120 Hanging Moss Road
Orlando, FL 32807
Tel: 407-678-6900

Dinsmore Instrument
1814 Remell St.
Flint, MI 48503
Tel: 313-744-1330

Fat Quarters Software
24774 Shoshonee Drive
Murrieta, CA 92562
Tel: 909-698-7950

Ferroxcube
2001 W. Blue Heron Blvd.
Riviera Beach, FL 33404
Tel: 407-881-3200

GPS World
859 Willamette St.
Eugene, OR 97440
Tel: 503-343-1200

Honeywell
12001 State Hwy. 55
Plymouth, MN 55441
Tel: 800-323-8295

ITS World
859 Willamete St.
Eugene, OR 97401
Tel: 503-343-1200

KVH Instruments
110 Enterprise Center
Middletown, RI 02840
Tel: 401-847-3327

Magnetic Research
122 Bellevue Ave.
Butler, NJ 07405
Tel: 201-838-6348

Magnetics Inc
Box 391
Butler, PA 16003
Tel: 412-282-8282

Measurement & Control
2994 W. Liberty Ave.
Pittsburgh, PA 15216
Tel: 412-343-9666

Micro Switch
11 W. Spring St .
Freeport, IL 61032
Tel: 815-235-6600

Natl. Speleological Society
Cave Ave.
Huntsville, AL 35810
Tel: 205-852-1300

Navtech Books & Software
2775 S. Quincy St., #610
Arlington, VA 22206
Tel: 800-NAV-0885

Phillips Magnetics
1033 Kings Highway
Saugerties, NY 12477
Tel: 914-246-2811

Precision Navigation
1235 Pear Ave, Suite 111
Mountain View, CA 94043
Tel: 415-962-8777

Sensors
174 Concord St.
Peterborough, NH 03458
Tel: 603-924-9631

TDK
1600 Feehanville Dr.
Mount Prospect, IL 60056
Tel: 708-803-6100

Walker Scientific
Rockdale St.
Worcester, MA 01606
Tel: 800-962-4638

rate here would appear to be around 63:1.

Which leads to this rule: To find your *useful* web site visitors, divide your total hits by *sixty* or your log file characters by *4500*.

Post-it note opportunities

Making up custom ink jet or laser printed Post-it notes is an obvious local service opportunity. For higher quantities, several sources advertise in *Quick Printing* and *Instant Printer* magazines. Doing your own notes has certainly been possible, but this has been rather labor intensive.

The usual do-it-yourself ploy is to make up a carrier sheet with marked rectangles on it, stick a blank note on each one, print your sheet, and then manually stack the results into pads. Another technique is post-applying a gentle spray-on adhesive.

3M has come up with an interesting alternative that greatly reduces your custom post-it note labor and hassle, but at higher materials cost. What they have done is taken *two* sheets of paper and applied magic glue in exactly the right places. They then stuck these two sheets together with *the glue on the inside*.

You'll then print *both* sides of the sheet in some eight-up note pattern. Next, you peel each sheet pair apart, flip the bottom sheet and restick them together, which gives you a pad of 8-up note stock. Finally, you cut up the individual notepads using a paper cutter or shear. Since it is much easier to fuss with one big sheet than eight little ones, the hassles are greatly reduced.

The 3M product is called *Post-it On-Demand Notepaper*. These should be available at *Paper Plus* and other retail or direct-mail chains. Bunches of additional tech venture opportunities appear in my *Incredible Secret Money Machine II*.

New tech lit

From *National Semiconductor* comes a whole slew of fat resources. Included are databooks on *Power ICs*, *Data Acquisition*, *Operational Amplifiers*, *Analog Products*, and on *Application Specific Analog*. From *Philips Semiconductors*, a freebie—*Car Radio Designer's Guide*. From *Raychem* comes a *Circuit Protection Databook*. From *Pericom*, a new data book on high performance CMOS and BiCMOS integrated circuits is now available. Some free samples of line operated switchmode *TOPSwitch* circuits are obtainable from *Power Integrations*, along with ap notes.

Decal papers for your own custom decals are offered by *Andrews Decal*. Free samples of *One-Wrap Straps* are available from *Velcro Systems*.

An extensive line of very low cost sound systems for greeting cards and ad specialty items are made by *Clegg Industries*. Smaller replacements for neon animation transformers are now offered by *Bertonee*. *Webmaster* is yet another of those brand new internet magazines.

For most individuals and smaller scale startups, most of the time, involvement with patents is virtually certain to end up as a *totally useless* waste of time, energy, money, and sanity. Find out why in my *Case Against Patents* package, along with tested and proven alternatives that work in the real world. It is available per my nearby *Synergetics* ad.

And don't forget that I've got a hot new Web site up at *www.tinaja.com* Your quickest way to pick up my catalogs is as *syncat01.pdf* and *surpcat01.pdf* at this location.

Finally, contacts for most of the mentioned items appear in our *Names and Numbers* or *Earth's Field Magnetometry Resources* sidebars located elsewhere in this article. Be sure to check these first. As usual, a no-charge US technical helpline is available per the *Need Help* box. Let's hear from you! EN

NEED HELP?

Phone or write all your US Tech Musings questions to:

Don Lancaster
Synergetics
Box 809-EN
Thatcher AZ, 85552
Tel: 520-428-4073

US email: don@tinaja.com
Web page: http://www.tinaja.com

The Four-Year Electronics Degree Program That Really Hits Home!

Bring The Technology Home With A Bachelor Of Electronics Engineering Degree. No Hassles. No High Cost!

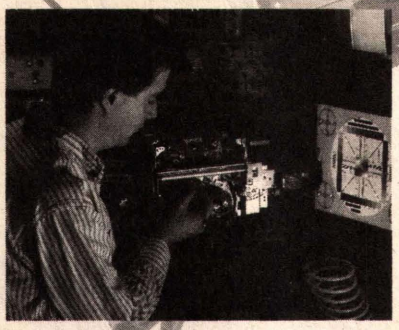

Now's the time to prepare for a profitable career.

We've lowered the cost of higher education.

It's true! You can earn a four-year Bachelor of Electronics Engineering Technology degree today ... and prepare yourself for a high-paying electronics career ... without quitting your job or ever leaving your home. Because World College, an affiliate of the Cleveland Institute of Electronics, offers you the total flexibility of independent study programs proven effective for people like you who truly want to succeed! World College independent study lessons help you build valuable skills step-by-step, and expert instructors are personally available to you with a toll-free call. What a way to earn an education!

Mail/Fax Today or Call 1-800-696-7532

A world of opportunity.

Where is your career headed? With a four-year bachelor's degree from World College, you call the shots, choosing from incredible, high-paying opportunities in electronics, telecommunications, computer, electrical power, and many other growing fields.

World College gives you the skills, the knowledge, the power to take advantage of your best opportunity in electronics. And you can do it all at your own pace!

Without leaving home.

World College continually works to provide its students with the most advanced education tools. From the latest equipment and reference books to breakthrough computer-simulated experiments, students are exposed to the latest technological advancements.

All the equipment, parts, and software you need are included in your affordable tuition, including more than 300 hands-on lab experiments you can complete in your home.

Choose your own pace.

Earn your bachelor's degree on your time — and at your pace — because you pay tuition to World College only as you complete the upper-level semesters close to graduation. The faster you make it through, the less you pay. So you have an incentive to make your future happen quickly — yet the freedom to choose your own pace!

Send today for your FREE course catalog — and give yourself that future you've always wanted — with an electronics degree education from World College.

Take charge of your future in electronics.

Four Powerful Reasons To Connect With World College Today:

1. **Earn your four-year degree!**
2. **Self-paced training!**
3. **Independent study in your home!**
4. **Expert instruction!**

Give Me The Power!

Send me a FREE World College course catalog today!

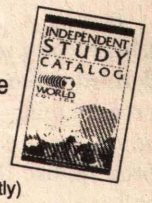

(Please Print Neatly)

Name _____

Address _____

City _____

State, Zip _____

Phone ( ) _____

Age _____

For faster service, call 1-800-696-7532, or call 1-804-464-4600.

Or fax this coupon to 1-804-464-3687.

WORLD COLLEGE

Lake Shores Plaza
5193 Drive, Suite 113
Virginia Beach, VA 23455-2500

CIE

Affiliated with
Cleveland Institute of Electronics

WAE36

BY JEFF HOLTZMAN

Java and the DLB

A FRIEND AND I WERE TALKING THE OTHER DAY ABOUT HOW JAVA, THE INTERNET, AND INTERNET TERMINALS ARE CHANGING THE WORLD. YOU MAY FIND PORTIONS OF OUR DISCUSSION INTERESTING. BUT I'M NOT GOING TO tell you which of us played the straight man, and which the wisecracker.

Java is a programming language. *(Another programming language!)* Java is derived from today's most popular programming language, C++. *(Big deal.)* Java is simpler than C++ because, like Basic, it has no pointers, and it does automatic memory management. *(Wow. A better Basic than Basic.)* It's also like Basic in that it is not compiled to machine language, but to an intermediate "p-code" that is subsequently executed on the run-time platform by a Java interpreter. *(Now there's a potential speed demon.)* It was created at Sun Microsystems—not Microsoft. *(Actually, that is interesting.)* As with Web-browsing technology, Java runs equally well on disparate platforms. *(Equally poorly, you mean.)*

Sun and other companies are designing Java CPU's that can execute Java p-code directly. *(Will it run on a 6502? Will there be an Amiga port?)* All the major software-tool vendors, including Microsoft, Borland, Symantec, and others, are rushing Java-development tools to market. *(So will it download nudie GIFs any faster?)*

Java was originally developed as a language to control programmable TV-set top boxes—like today's cable converters on steroids. *(50,000 channels and nothing's on.)* Even Microsoft is endorsing it—sort of. *(Deja vu all over again, Yogi?)* People are fed up with huge monolithic everything-including-the-kitchen-sink applications that gobble disk space, take forever to load, and 90% of which never gets used by 90% of the population. *(Hear, hear!)* Small Java-based programs *("applets")* will allow us to recover disk space, eliminate wait, and provide simplified centralized management and control over the apps. *(Who will police the Java police?)*

Then our conversation shifted to hardware, to the so-called internet terminal, *a.k.a.* network computer, *a.k.a.* simply interactive PC. The main idea is a $500 box with no disk drive and no monitor, but with built-in Internet connectivity.

Everybody knows that setting up, maintaining, and upgrading the average computer system is difficult, time-consuming, and expensive. *(Like walking and chewing gum, right?)* Corporations have difficulty showing how computers improve productivity at all, but their negative cost impact is

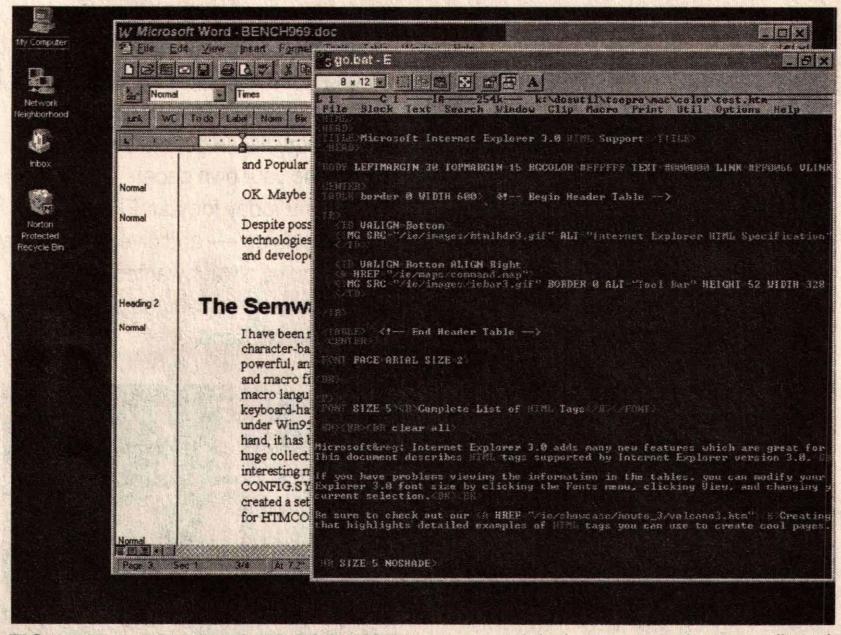

FIG.1—THE SEMWARE EDITOR (TSE) is a powerful character-mode text editor that works great for editing everything from system configuration files to HTML code to programs in C and Basic.

visible for all. *(I'm not going back to a typewriter.)*

Suppose that computers could be made truly appliance-like, even simpler than the Mac. *(And suppose we all decide to limit ourselves to whatever we managed to learn by third grade.)* Suppose they were truly plug-and-run, like toasters. No hardware upgrades or maintenance, and software that is self-healing, self-upgrading, self-maintaining. *(Because it doesn't do anything.)*

Suppose the paradigm represented by web browsers becomes the user interface—for everything. *(Suppose we stop eating protein.)* Telephones, TVs, microwaves, stereos—and computers. All have a simple point-and-click interface. People select things from lists. People accomplish tasks rather than getting mired down in how to do them. *(Gee, it's dumb and dumber.)* The focus shifts to tasks, not tools.

Anyway, that's enough dialog for now.

If Java wins

Seriously: Imagine a world with a different kind of computer infrastructure. Forget about terms like CPU, megabyte, megahertz, video adapter, serial port, network interface card, etc., etc., etc., *ad nauseam*. Think about things like screwdrivers, hammers, pliers. Dedicated tools for dedicated tasks.

By contrast, today's PC, and most of the software that runs on it, was designed from the ground up with the "Swiss Army Knife" philosophy. Everything was made as general-purpose as possible. And that was good. That's what fueled early growth of the PC industry. In fact, every attempt to decrease the general-purposeness of any part of the system was universally rejected. Early versions of OS/2 and IBM's MicroChannel-bus architecture are prime examples.

The PC also represented a sociological response to the then-centralized planning and control of computer resources. The early user said, "I don't need to wait for The Committee. I can do it myself." Now corporations are saying, "Yes, maybe you can do it yourself, but most can't, and for the sake of efficiency (read: better competitiveness in the global market—you'd rather have less control over your computer at work than no job because we're going out of business)—for the sake of efficiency, we're rescinding some of the computer freedoms you've enjoyed till now."

But now think about a Dumb Little Box (DLB), that is easily configured, maintained, and upgraded—all via remote control, *i.e.*, the network. If a box needs a new OS upgrade, it'll get it itself next the next time it logs on. Need an application upgrade? Likewise.

Some in the PC industry are threatened by the DLB. If universally adopted, it could put a lot of computer professionals out of work. It could also wreak havoc with both hardware vendors and software developers.

But let's be realistic. The DLB won't be universally adopted; it can't be. People who create—writers, engineers, analysts designers—will need general-purpose machines that can adapt to various tasks.

On the other hand, low-skill repetitive work situations would be prime targets for DLBs. For example, the DLB could displace dedicated hardware such as smart cash registers, credit-card validation systems, point-of-sale terminals, warehousing and inventory tracking, lookup devices in music and book stores, telemarketing systems, pay phones, vending-machine controls, keyless entry systems, stereo systems, TV sets, smart-home control systems, fax machines, automotive control systems, factory data-collection and monitoring systems, and on and on and on, to the point where anything that has a button or a wire becomes a target for a DLB running Java.

In this scenario, the DLB becomes truly ubiquitous, and costs plummet, unlike anything even we in the PC industry have seen so far. Gone will be all technically interesting but proprietary controllers, microcontrollers, and embedded languages like Basic, C, and Forth. Computer Science departments will stop teaching languages other than Java. Electrical Engineering departments will devise Ph.D. programs around DLB architectures.

All the major computer companies will die, as will Intel. The Far Eastern manufacturing giants (Matsushita, Hyundai, et al) will quickly settle on a few basic designs, and then shave profit margins down to nothing, in the process driving all other competition out of business.

The boxes themselves will be sealed throw-aways. They will be serviceable, but labor for doing so will be expensive, so the direction (as in all other consumer electronics the past thirty years) will be toward low-priced disposable units. Basic functionality will hardly evolve at all, but there will be thousands of packaging variations geared toward different market segments. Upgrades will be available, but ultimately more expensive than replacement systems.

The nature of all support industries will change radically. For example, all those magazines that begin with "PC" will either go out of business or imperceptibly morph into "DLB" mags.

Despite possible abuses, there is potential for evolving lots of overlapping, redundant technologies toward a single architecture with cost savings for all—consumers, manufacturers, and developers. This may be interesting. Or it may fizzle. Time will tell.

Product watch

I have been meaning for months to work in a mention of this little gem. The SemWare Editor is a character-based text editor that traces its heritage to the shareware product Qedit. It's small, fast, powerful, and configurable. The program consists of a run-time engine plus user-interface, help, and macro files, all of which can be combined and "burned in" to a single executable file. The macro language is like a forgiving version of Pascal, with lots of built-in screen-handling, keyboard-handling, and text-manipulation functions.

The program runs fine in a DOS session under Win95 and NT, except that the current version cannot handle long filenames. On the other hand, it has built-in support for cutting to and from the Windows clipboard. And on a 1024 × 768 monitor, running it in a 50-line DOS box is nice, nicer in fact

as a window than in full-screen DOS 50-line mode (better fonts).

TSE comes with a huge collection of macros, and more are available through various on-line sources. One interesting macro does color-coded syntax highlighting, with setup files for batch file commands, CONFIG.SYS commands, Basic, dBase, FORTRAN, Modula, Ada, Pascal, and other languages. I created a setup file for HTML commands, valid up through but not including HTML 3.2. Look for HTMCOLOR. TSE on the Gernsback BBS (516-293-2283), and elsewhere. In this color scheme, tags appear in magenta, attributes in gray, entities in green, and other text in cyan. I also implemented a news net browser that allows me to quickly scan news files, delete items I'm not interested in, and save the remainder. TSE comes with extensive documentation on the macro language, and has a well-done hypertext help system.

Another must-have shareware-derived gem is Paint Shop Pro. For capturing screens, converting among bitmap file formats, and general bitmap manipulation, it's extremely powerful, easy to use, and bargain priced. The latest version (3.12) is fully 32-bit. It includes an extensive collection of filters for creating special effects, and is also compatible with an even wilder set of special effects filters, Kai's Power Tools. (In fact, JASC provides a bundle of PSP and KPT for under $100.)

Kai's Power Tools takes advantage of the "plug-in" architecture devised by Adobe; this system allows tools to integrate seamlessly with bitmap editors to provide special effects. KPT is the leading special-effects generator, and Version 3 of the package will knock you out with some of the things it can do. It also has a very interesting and original user interface.

JASC also sells a multimedia cataloging utility called Media Center, and another program for creating stand-alone multimedia presentations called Illuminatus. All are low-priced, well-done utilities, and they're available in various bundles. Trial versions are also available on CompuServe and other on-line services.

PowerDesk is the name of a Win95 shell utility. It actually consists of two components: a pop-up toolbar, and an enhanced version of the Windows Explorer.

The toolbar component allows you to add your own icons for single-click launching of your favorite apps. It also includes a clock and various system-resource monitors. The whole thing is extremely configurable so you can run just the components you need.

The enhanced explorer provides built-in file viewing and ZIP file handling. In fact, it displays ZIP files just like ordinary directories, allowing you to drag and drop files in and out of ZIPs. It's slower than dedicated ZIP utilities like WinZip, but, for most uses, it's good enough. The viewer technology allows you to view most common file formats intact, and an enhanced version is available from a third-party organization. A 30-day trial version is available on CompuServe. EN

RESOURCES

PaintShop Pro ($69 or $99 with KPT), Media Center ($39), Illuminatus ($149)
JASC, Inc.
P.O. Box 44997
Eden Prairie, MN 55344
Tel: 612-930-9171
CIS: Go JASC

Kai's Power Tools 3 ($199)
MetaTools, Inc.
6303 Carpinteria Ave.
Carpinteria, CA 93113
Tel: 805-566-6200.

The SemWare Editor Professional v2.5 ($109)
SemWare Corporation
4343 Shallowford Road
Suite C3A,
Marietta, GA 30062-5022
Tel: 800-467-3692 or 770-641-9002
CIS: Go SEMWARE

PowerDesk ($49.95)
MicroHelp, Inc.
4211 J.V.L. Industrial Park Dr., NE
Marietta, GA 30066-2789.
Tel: 800-922-3383 or 770-516-0899
CIS: Go MICROHELP.

You can Build Gadgets!
Here are 3 reasons why!

☐ **BP345—GETTING STARTED IN PRACTICAL ELECTRONICS $5.95**
If you are looking into launching an exciting hobby activity, this text provides minimum essentials for the builder and 30 easy-to-build fun projects every experimenter should toy with. Printed-circuit board designs are included to give your project a professional appearance.

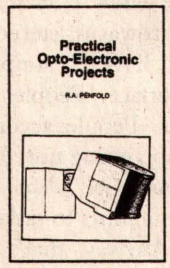

☐ **BP349—PRACTICAL OPTO-ELECTRONIC PROJECTS $5.95**
If you shun opto-electronic projects for lack of knowledge, this is the book for you. A bit of introductory theory comes first and then a number of practical projects which utilize a range of opto devices, from a filament bulb to modern infrared sensors and emitters—all are easy to build.

☐ **BP363—PRACTICAL ELECTRONIC MUSIC PROJECTS $5.95**
The text contains a goodly number of practical music projects most often requested by musicians. All the projects are relatively low-in-cost to build and all use standard, readily-available components that you can buy. The project categories are guitar, general music and MIDI.

Mail to:
Electronic Technology Today, Inc.
P.O. Box 240
Massapequa Park, NY 11762-0240

Shipping Charges in USA & Canada

$0.01 to $5.00.....$2.00	$30.01 to $40.00.....$6.00
$5.01 to $10.00.....$3.00	$40.01 to $50.00.....$7.00
$10.01 to $20.00.....$4.00	$50.01 and above.....$8.50
$20.01 to $30.00.....$5.00	

Sorry, no orders accepted outside of USA and Canada. All payments must be in U.S. funds only.

☐ Number of books ordered.

Total price of books..... $ _____
Shipping (see chart) ..... $ _____
Subtotal ..... $ _____
Sales Tax (NYS only)..... $ _____
Total enclosed ..... $ _____

Name _____
Address _____
City _____ State ___ ZIP _____
Please allow 6-8 weeks for delivery.

BY CARL J. BERGQUIST

Lasers in security systems

ONE AREA WHERE LASERS CAN BE EXTREMELY VALUABLE IS IN SECURITY. THERE ARE A VARIETY OF WAYS TO USE THEM TO MONITOR PROPERTY AND DELIVER SOME PEACE OF MIND TO THE PROPERTY OWNER.

WARNING! ! !

This article deals with and involves subject matter and the use of materials and substances that may be hazardous to health and life. Do not attempt to implement or use the information contained herein unless you are experienced and skilled with respect to such subject matter, materials and substances. Neither the publisher nor the author make any representations as for the completeness or the accuracy of the information contained herein and disclaim any liability for damages or injuries, whether caused by or arising from the lack of completeness, inaccuracies of the information, misinterpretations of the directions, misapplication of the information or otherwise.

But, before we can use lasers in such applications, we need some type of laser "sensor." Figure 1 shows a very simple, two-transistor relay circuit that does that job very well. The relay in that circuit activates whenever phototransistor Q1 is not illuminated; that is, whenever the laser beam projected on the sensor is broken by something moving through its path. Once assembled, the relay circuit could be used to trigger whatever alarm system you require.

What kinds of alarms can be triggered? Well, Fig. 2 presents some possibilities. For example, in addition to a standard audio alarm, the relay circuit can be used to trigger a camcorder or a closed-circuit-television surveillance system. The relay can also be used to turn on lights, activate solenoid-driven door or window locks, and more. The number and variety of possibilities are limited only by the user's needs and imagination. If you can come up with something a little on the unusual side, why not send them to Laser Editor, **Electronics Now,** 500 Bi-County Blvd., Farmingdale, NY 11735, or to the editor's e-mail address: Lartronics @aol.com.

Some security applications

Our first application uses a laser as a room-entry alarm. Arrange the laser so its beam crosses the entrance to the room and shines on the phototransistor. Whenever the beam is broken, either by the door opening or someone coming into the room, the relay closes and activates the attached warning device. Incidentally, that is the way that most of the security systems discussed in this month's installment function.

In the same fashion, the room can be protected by projecting the beam across it. Any movement within the room that breaks the beam sets off the alarm. To fully cover the entire room, add several small front-surface mirrors. Position them to bounce the beam back and forth until the room is filled with beams of laser light that are two to three feet apart. Also, vary the height of the beam. Remember, unless the beam contacts smoke, dust, or something similar, it is virtually invisible except where it reflects.

The next application is a perimeter alarm. Often used to monitor a fence or wall surrounding a business or house, such a system could also be used to protect an interior room. A typical outdoor application is shown in Fig. 3. As you can see, that example also uses the mirror-reflection technique. The laser and the relay circuit are placed approximately as shown and the beam is aimed at the first mir-

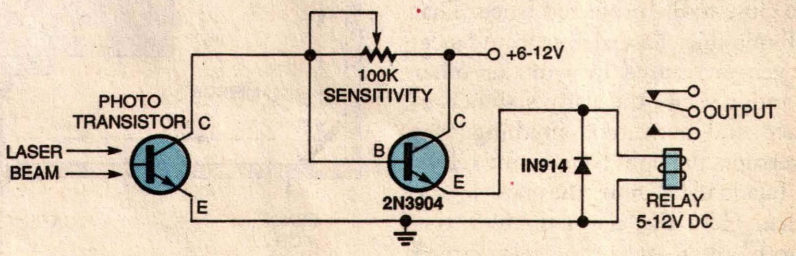

FIG. 1—TWO-TRANSISTOR RELAY CIRCUIT will activate whenever the phototransistor is illuminated by the laser beam.

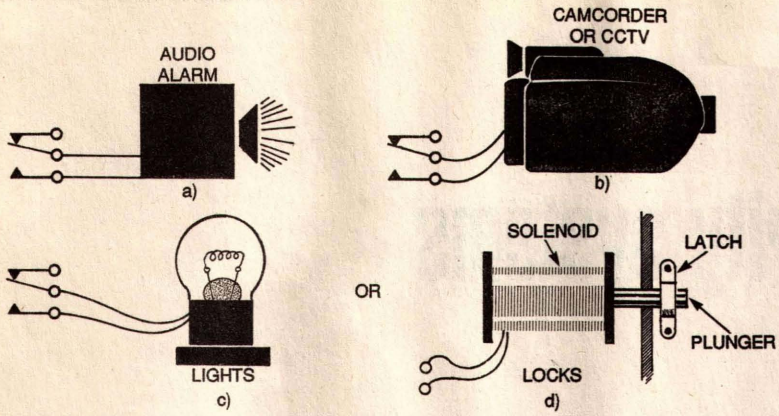

FIG. 2—FOUR DIFFERENT TYPES of alarms or devices: An audio alarm (a), a camcorder or CCTV camera (b), lights (c), and a solenoid operated lock (d).

ror. Additional mirrors are placed at each turn in the fence. The angle of each mirror is adjusted so that the reflected beam from one is aimed at the center of the next. In that way the laser beam travels the entire perimeter of the fence, and finally reflects back into the relay's phototransistor detector.

Since this is an outdoor assembly, the laser, relay circuit, and the mirrors must all be protected from the weather. If possible, locate the laser and the relay circuit inside the protected structure as shown. If that is not possible, keep it under some kind of cover to protect it from the weather. You also need to shelter the mirrors from the elements. Do that by placing them inside small housings that have openings for the beam. A spray coat of clear polyurethane can be applied to each front-surface mirror to provide additional protection.

The mirrors themselves can be either front- or rear-surface types, and should be about one inch square or larger. Mount them securely, but not too close to the protected fence. That will minimize false alarms from fence movement caused by wind or other vibration. Once the alarm system is in place and activated, anything that interrupts the light triggers the relay.

Incidentally, note the gate in the fence. Here the alarm doubles as a gate monitor. Again, the relay circuit can be interfaced to any number of alarms or devices depending upon your needs.

High sensitivity relay circuit

While the relay circuit shown back in Fig. 1 will be more than adequate in most cases, sometimes an application requires a sensor with a higher level of sensitivity. That can be done by adding an operational amplifier in series with the phototransistor detector. In the schematic of Fig. 4, an NE5534 low-noise op-amp is used to boost the gain.

The high-sensitivity relay circuit allows you to use lasers in even more security applications. For example, by reflecting the beam off the bumper of an automobile, then back into the relay, any vibration caused by entering or exiting the vehicle activates the relay. Select a fairly sharp curve on the bumper surface as the laser target; that will exaggerate any movement in the bumper, allowing the alarm to pick up even slight movements.

By using a piece of reflective Mylar mounted on a spring, you can monitor isolated areas for loud or inappropriate noise. Unattended rooms can also be "watched" for telltale smoke that might be a sign of fire. Aim the laser at the high-gain relay, either directly or by reflection, and adjust the sensitivity control, R1, to just activate the contacts. Back the control off just enough to reopen the relay. Now when smoke passes between the beam and the detector, the alarm will energize.

Another possible application is to detect flooding in a room or basement. Fashion a simple float by cementing a small piece of reflective Mylar to an ordinary cork that has a vertical hole drilled through the center. Place the hole in the cork on a spindle (the straight section of a metal coat hanger could serve for that) so it can move freely. Position the assembly in a low-lying area on the floor. Now reflect the laser beam off the Mylar back into the detector of the relay. If water floods the room, the cork will

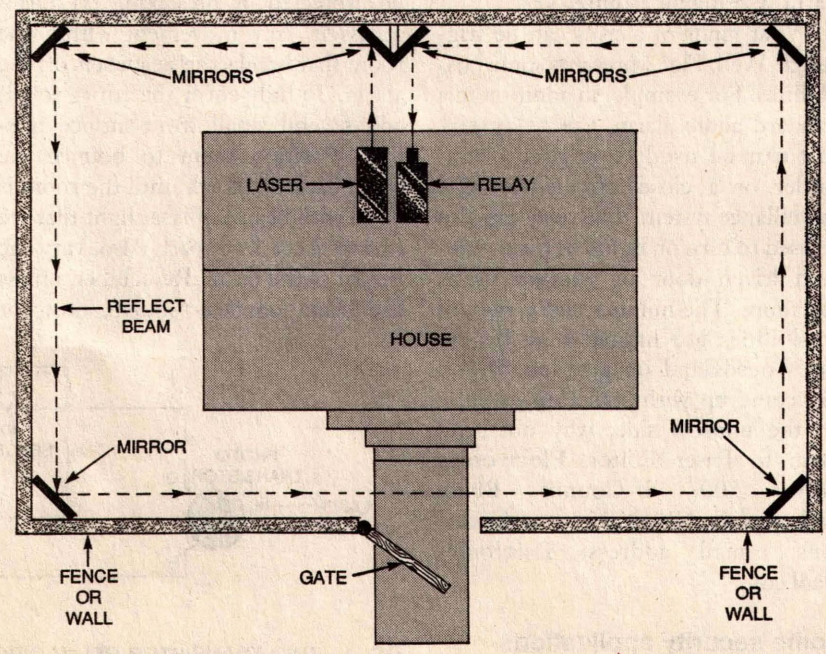

FIG. 3—IF YOU WANT TO USE THE LASER as a part of a perimeter alarm system, this is one way you can do it.

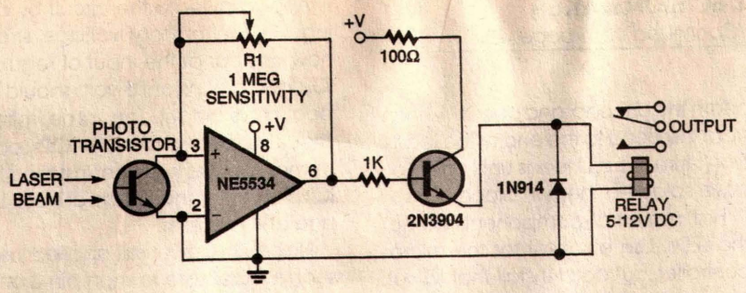

FIG. 4—FOR GREATER SENSITIVITY, add a low-noise op-amp to the relay circuit.

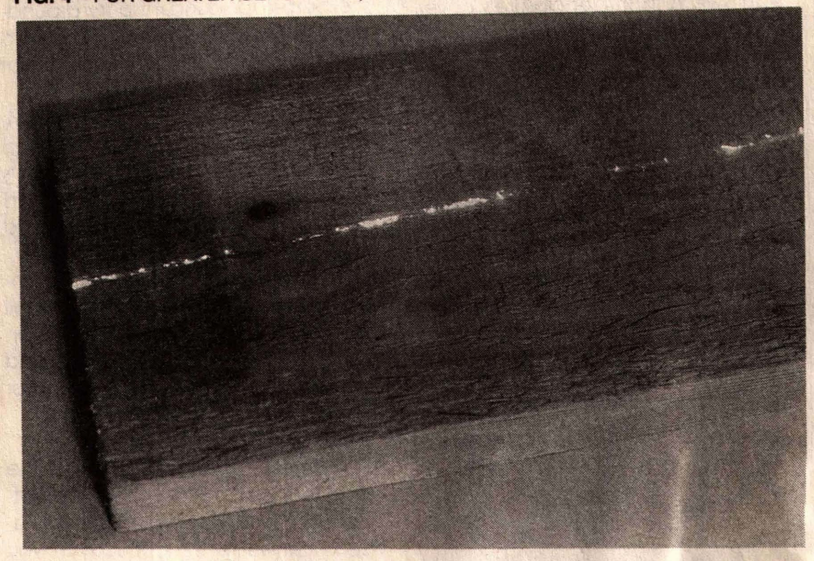

FIG. 5—USE A LASER BEAM TO DETECT high and low spots across a wood plank. The laser beam appears in this photo as a white streak across the board.

float, lifting the Mylar out of the laser beam, and activating the alarm.

These are just a few ideas along the lines of security. I am sure you could come up with even more.

Construction and surveying

One industry where lasers are used frequently is building construction and associated landscaping. The laser is an almost perfect straight edge, as the beam is extremely true even at long distances. Leveling soil beds or foundations, laying straight pipelines, keeping fences and/or walls in line, checking boundaries, and verifying angles on roofs and other structural details are all areas where construction crews use lasers to provide more accurate results. One experiment that illustrates the principle of using the laser in this way is to test the straightness of a piece of wood (see Fig. 5).

Align the wood so the edge of the beam barely illuminates the edge of the plank. A bright red line will appear wherever it encounters the same depth. That will indicate the "high" level of the surface. Now, introduce smoke, fog, or even a mist of fine powder (talc), and the full beam will become visible, pointing out the "low" level of the surface. A quick comparison will disclose how straight that piece of wood really is. Use the same technique to check walls, roofs, foundations, or any other section of a structure.

You can apply the same principle to ensure a correct angle across a wide section of wood that is to be cut. Measure the piece for the leading cut. Start the beam at that point and, with the help of a protractor, align the beam to the correct angle. On the far side, place a piece of cardboard against the edge of the wood and mark where the spot hits. By connecting the two markings, the guideline for the properly angled cut is also m[illegible]

TONAL VOLTMETER

continued from page 61

case with the ink cartridge removed. The probe tip can be any sharpened length of metal wire, such as a wire-wrap IC socket pin or small nail. Make the connection between the probe and pin 9 of IC1 with a length of shielded cable.

Any 5-volt DC supply is suitable for this project, either batteries or an AC adapter. Use whatever power supply is most convenient and least expensive for you. Mount the finished circuit in an enclosure that will protect it and you are done.

To adjust the two potentiometers in the circuit, first ground the probe tip and adjust R2 for the lowest tone desired. Then connect the probe tip to +5 volts and adjust R1 for highest tone desired. Adjust R3 to increase or decrease the speaker volume if necessary. Ω

"YOUR FREE CATALOG KNOCKED MY SOCKS OFF"

We get that sort of comment all the time. People are impressed that our free Consumer Information Catalog lists so many free and low-cost government booklets. There are more than 200 in all, containing a wealth of valuable information.

Our free Catalog will very likely impress you, too. But first you have to get it. Just send your name and address to:

Consumer Information Center
Department KO
Pueblo,
Colorado
81009

A public service of this publication and the Consumer Information Center of the U.S. General Services Administration

SPECTRUM ANALYZER

(Continued from page 39)

bus with other 100,000-ohm resistors (R7, R10, R13, R16, R19, and R23). Because each stage is an inverter, there are two summing buses; with one for the "evens" and one for the "odds" of the seven stages. Those buses sum signal samples from each of the series-strung stages described above. Once a stage saturates, its output is limited, and it contributes no more to the summation. Thus, as the stages progressively saturate with increasing signal input, the summing buses appear to have less and less gain in front of them.

Each stage within the chain comes into saturation (limiting) very smoothly; there is no sudden "corner" in the individual stage transfer functions. This smoothness is due to the way the CMOS inverters behave. The overall effect is a smooth logarithmic amplifier performance.

Because of the "even-odd" signal collection on the two buses, it is necessary to invert the signal on one so that both are in phase and ready to be totaled. This is done with IC2-d and emitter follower Q1. The signal at the emitter is now in phase with the signal on the other summing bus. The two bus contributions are finally summed in IC2-e and Q2, which form the final output stage of the log amplifier. The transfer function slope (mV/dB) constant is set with resistor R28.

The signal input to the log amplifier is a symmetrical heterodyne "bubble" of sinusoidal signal that consists of positive and negative swings around a baseline. Because spectrum analyzer displays are unipolar (one signal polarity), output stage IC2-e is bias-offset with resistors R26 and R27. This clips the negative going spectral line spikes and so only positive going ones are displayed on the oscilloscope. Finally, input gain trimmer R2 sets the smallest signal at which logging begins, so that logging does not occur on baseline noise but rather just above it.

This completes the theory discussion for the RSA and pretty much all the space we have for this month. Next time, we will get right to work on showing you how you can build your own under-$100 spectrum analyzer. Ω

DECISION MAKER

(Continued from page 42)

neath the LED cap, and about 3/16-inch from the bend to the end of the leads. Don't trim the LED leads until after you have soldered them in place.

First, mount all components except the LEDs. Use a socket for the microcontroller, but don't install that IC yet. Next drill the holes for the LEDs and the start switch in the enclosure's cover, using the template in Fig. 5 as a guide.

Now place the PCB in a pair of slots along the side of the enclosure and bend the leads of a single LED. Insert the LED into the board and tack-solder one lead. Temporarily place the cover on the enclosure to check lead length. If the cover fits properly, finish soldering the LED, then bend the remaining LEDs to fit, and solder them in. Otherwise, adjust the bend in the first LED and try again.

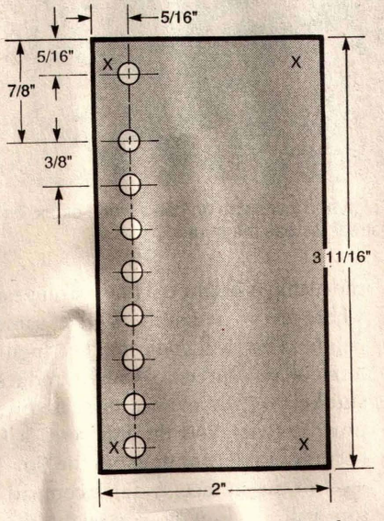

Fig. 5. Here's the hole template for the cover. Nine holes are required, eight for LEDs and one for the start switch. The power switch mounts on the upper end of the case.

To keep the front panel as clear as possible, we mounted power switch S2 in the side wall of the narrow end of the enclosure. We used a low-cost, low-profile slider for S2.

Test and disassembly. After completing construction, but before installing the microcontroller, let's do a few simple tests to ensure that everything is working properly.

Apply power to the circuit by closing S2. The battery voltage should now appear at the input of regulator IC2, and a constant 5-volts should appear at its output. The same voltage should appear at pin 13 of IC1's socket (remember, we have not installed that IC as of yet), at the anode of each LED, and at the buzzer.

Next, with power still applied, use a short jumper wire to short pin 3 of IC1 to ground (pin 14). That should cause the buzzer to sound. Also try grounding pins 5–12 of IC1. Each LED should light in turn. If LED4 does not light, put JU2 in the other position.

The last test verifies operation of S1. Connect your voltmeter between pin of IC1 and ground. When the switch is open, the meter should read + 5-volts DC, but when closed it should read zero.

After verifying operation of all components, remove power and install the 68HC705K1 into its socket. Then reapply power. You should see and hear the initialization sequence, after which the unit is ready for use.

The label. The most difficult (and the most fun) part of this project is creating the front panel label. Self-stick labels work well in this application; you can also use heavy stock and rubber cement.

The author created a template file in Word for Windows that allows you to format labels precisely. One is shown in Fig. 1, and another in the lead photo for this article.

Customization is the key to transforming this project from simple blinking lights into a memorable gift. When creating the label, it's best to focus on either the personality quirks of the recipient or on the general humor of the situation. Ask yourself questions like: What things does this person like and dislike? When is he or she the least decisive? Are there any stereotypes concerning the new situation he will soon be in? As soon as you start letting the creative juices flow, you can have a lot of fun. Ω

AMERICAN HEART ASSOCIATION
MEMORIALS & TRIBUTES
SM
1-800-AHA-USA1
American Heart Association

SUPPLEMENT TO ELECTRONICS NOW SEPTEMBER 1996

Electronic SHOPPER®

MICRO SIZE CCD VIDEO CAMERAS

- Wireless Models Available.
- Color Board Cameras "Y" / "C" SVHS signal.
- Models to 600 Line Res.
- 9V Battery Operation.
- Monitor in Darkness with IR Option.
- Can be plugged into any VCR or Monitor.
- Stealth/Covert Cameras.
- Low LUX/Low Noise.
- Low Power Consumption.
- Standard NTSC Output.
- Options: Lenses/Wireless/ Fiber Optics & More.

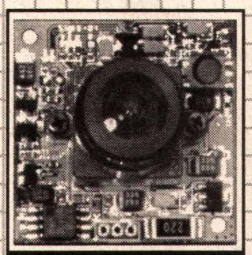

MB-750U (1.25" sq.)

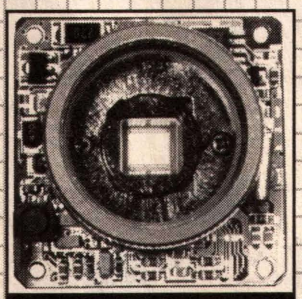

MB-750UX (1.5" sq.)

Visit Polaris Ind. Web Site at: http://www.polarisusa.com

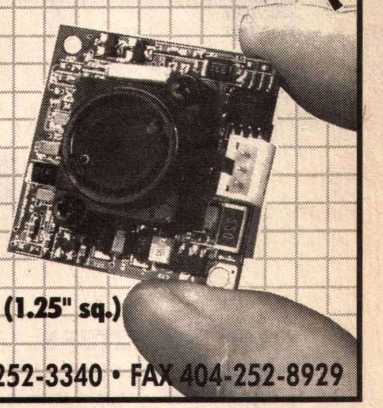

MB-750P (1.25" sq.)

Polaris Industries

1-800-752-3571

New Literature Available for All Models

Same Day Shipping from Stock!

MasterCard American Express VISA DISCOVER

141 West Wieuca Road • Suite 300 • Atlanta GA • 30342-3251 • Tech Info: 404-252-3340 • FAX 404-252-8929

ASSEMBLE YOUR OWN CNC

2.5, 3, & 4 AXIS

ROUTE PC BOARDS, MILL, DRILL, CARVE, & ENGRAVE WOOD, PLASTICS,& LT.METALS

STARTING AT $ 495.00

3,4, & 5 MOTOR GANTRY MILL CONFIGS.
OVER 20 DIFFERENT MODEL - OPTIONS
PC COMPUTER CONTROLLED CNC/DNC
IMPORT/EXPORT FILES TO OTHER CADS
AUTO-BACKLASH COMPENSATION
PRE-MACHINED HEAVY CASTINGS
SIMULTANEOUS 4 AXIS MOTION
OPTIONAL ALUM. WAY-COVERS
FREE 3D CAD/CAM SOFTWARE
AVAILABLE IN KITS OR ASSEMBLED
EXPEDITE SERVICE ALSO AVAILABLE
.0005" RESOLUTION / AMERICAN MADE

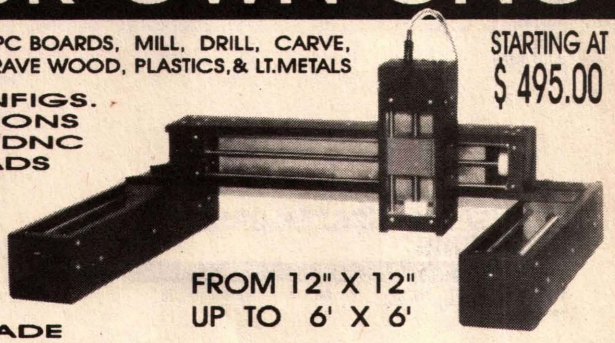

FROM 12" X 12" UP TO 6' X 6'

FOR INSTANT SPECS •24 HR. FAX-BACK• 501-839-8293

U.S. CYBERLAB, INC.
14786 SLATE GAP ROAD
WEST FORK, AR 72774

AND SAVE THOUSANDS.

CAPACITORS

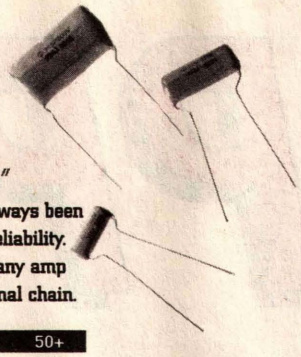

SPRAGUE "ORANGE DROPS"

Sprague polypropylene capacitors have always been famous for their great performance and reliability. Significantly improve the performance of any amp by upgrading to "Orange Drops" in the signal chain.

	1	10	25	50+
.001UF/600V	$.45	.36	.32	.29
.0015UF/600V	.46	.36	.32	.29
.0022UF/600V	.47	.37	.33	.30
.0033UF/600V	.48	.37	.34	.30
.0047UF/600V	.49	.38	.34	.31
.01UF/600V	.50	.45	.40	.35
.015UF/600V	.65	.50	.42	.38
.022UF/600V	.68	.55	.46	.39
.047UF/600V	.80	.65	.59	.52
.068UF/600V	.95	.80	.74	.69
.1UF/600V	1.05	.92	.83	.74
.15UF/600V	1.40	1.25	1.05	.95
.22UF/600V	1.90	1.55	1.35	1.24
.47UF/400V	1.85	1.50	1.30	1.20

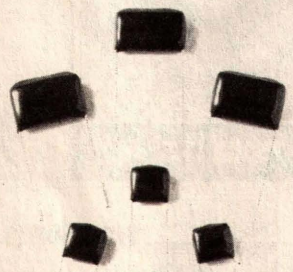

XICON CAPACITORS

Metalized Polypropylene. Made in JAPAN. A very high quality cost effective range of coupling capacitors. Great sound, small size.

	1	10	25	50+
.001UF/630V	$.30	.24	.20	.17
.0022UF/630V	.30	.24	.20	.17
.0047UF/630V	.30	.24	.20	.17
.01UF/630V	.30	.24	.20	.17
.022UF/630V	.35	.26	.22	.19
.047UF/630V	.42	.36	.30	.26
.1UF/630V	.46	.40	.34	.30
.22UF/630V	.63	.56	.45	.40
.47UF/630V	1.20	1.00	.88	.79

TRANSOHM - SCREEN GRID RESISTORS

	10	25	50	100+
470 OHM / 1 WATT	$.10	.08	.07	.06
1K OHM / 5 WATT	.32	.25	.22	.19

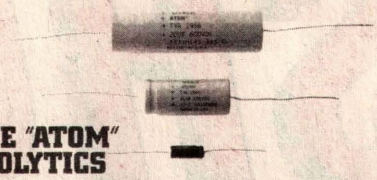

SPRAGUE "ATOM" ELECTROLYTICS

These electrolytics have been the standard in most vintage amps...and there's a good reason!

	1	10	25	50+
8UF/450V	$2.25	1.95	1.85	1.68
10UF/150V	1.20	1.05	.90	.82
10UF/500V	3.50	2.90	2.60	2.25
16UF/475V	3.60	2.95	2.65	2.35
20UF/500V	3.70	3.40	2.80	2.55
20UF/600V	6.70	6.20	5.90	5.65
25UF/25V	.80	.75	.70	.65
25UF/50V	.85	.79	.73	.69
40UF/500V	4.95	4.35	3.80	3.15
50UF/50V	.90	.83	.77	.73
80UF/450V	5.50	4.80	4.20	3.70
100UF/100V	1.75	1.55	1.35	1.30
100UF/350V	4.45	4.05	3.65	3.25
100UF/450V	6.90	6.10	5.50	4.70
250UF/25V	1.25	1.10	.95	.85

ILLINOIS ELECTROLYTICS

Excellent replacement electrolytic capacitors for general purpose applications requiring tight ripple control. Axial leads, made in Japan.

	1	10	25	50+
22UF/500V	$2.80	2.25	1.95	1.72
47UF/500V	4.75	3.80	3.35	3.20
80UF/450V	3.50	2.95	2.60	2.40
100UF/350V	2.80	2.30	2.10	1.95
100UF/450V	3.90	3.25	2.95	2.82
220UF/300V	4.00	3.65	3.35	3.10
5000UF/55V	1.90	1.80	1.70	1.65

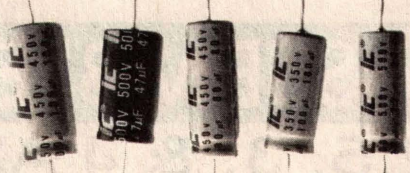

LCR CAPACITORS

Radial capacitors with solder lugs. Replacement for Marshall™, Hiwatt, Orange, Laney, Vox, Sound City & many others. Made in England.

	1	10	25+
32UF x 32UF @ 500 VOLTS	$7.20	6.75	6.45
50UF x 50UF @ 500 VOLTS	7.45	6.95	6.70
100UF x 100UF @ 500 VOLTS	8.95	8.20	7.75
Mounting bracket/clamp	1.40	.90	.65

NEW SENSOR CORPORATION
20 Cooper Square, New York City, NY 10003 • (212) 529-0466 • 1-800-633-5477 • Fax (212) 529-0486
5

CIRCLE 258 ON FREE INFORMATION CARD

Parts Express™

301 Standard PanaVise

Designed for the professional and hobbyist, the model 301 turns, tilts and rotates to achieve the desired position. Durable nylon jaws open 2-1/4". Net weight: 3 lbs.

PANAVISE

#EN-365-305 ..... **$39.95** EACH

Headband Magnifier

Features double lens for choice of 2.2x or 3.3x magnification and Velcro type headband. Net weight: 1/2 lb.

#EN-360-672 ..... **$19.95** EACH

GoldStar Oscilloscopes

GoldStar

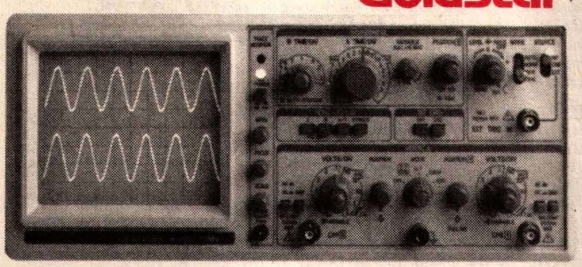

Part #	GoldStar #	Description	Price
EN-394-116	OS9100P	100MHz	$899.95
EN-394-115	OS9060D	60MHz	699.95
EN-394-110	OS9040D	40MHz	599.95
EN-394-105	OS9020G	20MHz w/generator	449.95
EN-394-100	OS9020A	20MHz	349.95

150 MHz Oscilloscope Probe Kit

Deluxe probe kit features a modular design for longer life, switchable 10:1 probe with 150 MHz bandwidth, 2.8 ns rise time, and adjustable capacitance from 10-35 pF. 60" in length. Kit includes 6" detachable ground lead, sprung hook, trimming tool, 2 channel identifier clips, and replacement tip. Includes plastic case.

#EN-390-100 ..... **$29.95** EACH

Sure Shot 18" Dish for DSS®

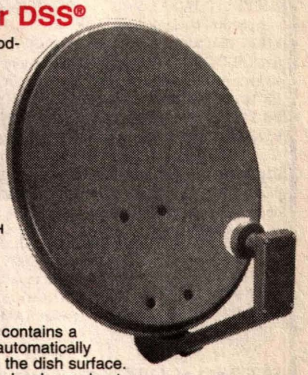

Built heavier and stronger than OEM models, able to withstand 120 MPH wind gusts! "Perfect Curve" manufacturing process allows for maximum signal reflectivity. Ideal for replacement of damaged OEM dishes or for additional viewing locations. Sure Shot comes complete with mounting hardware and instructions. Limited lifetime warranty. LNBF not included. Net weight: 13 lbs.

#EN-210-405 ..... **$49.95** EACH

Hot Shot 18" Dish for DSS®

The Hot Shot features the same quality construction as the Sure Shot, but also contains a safe low voltage, heating element that automatically eliminates ice, snow, and moisture from the dish surface. Hot Shot comes complete with mounting hardware, heater power supply and instructions. Note: 2 conductor, 18 gauge heater wire not included. Limited lifetime warranty. LNBF not included. Net weight: 27 lbs.

#EN-210-400 ..... **$139.95** EACH

Grundig LNBFs

Made in England quality! Designed to work in extreme real world conditions. Features "true circular polarization". For use with the Sure Shot and Hot Shot dishes or as a replacement for lightning damaged RCA DSS LNBFs. Available in single or dual feed. 18 month warranty. Net weight: 1 lb.

#EN-210-420 (Single feed) ..... **$79.95** EACH

#EN-210-425 (Dual feed) ..... **$99.95** EACH

Weller WLC100 Soldering Station

The Weller WLC100 solder station is adjustable from 5 to 40 watts. Includes 40 watt pencil iron. UL approved. Net weight: 1-3/4 lbs. One year manufacturer warranty.

Weller

#EN-372-120 ..... **$39.95** EACH

CAIG DeoxIT Deoxidizer

CAIG LABORATORIES, INC.

DeoxIT is a fast-acting deoxidizing solution that cleans, lubricates, and improves conductivity on all metal connectors and contacts. Seals and protects all electrical connections. Reduces intermittent failures, arcing, wear, and abrasion. Temperature range: -34 degrees C to 200 degrees C. Use as a general treatment for connectors, contacts, and other metal surfaces.

Part #	CAIG #/Description	Solution	Price (1-11)	Price (12-23)	Price (24-UP)
EN-341-200	DeoxIT D5, 5 oz. Spray	5%	$7.95	$7.15	$6.45
EN-341-202	DeoxIT Mini Spray, 15 g.	5%	4.95	4.50	3.95
EN-341-205	DeoxIT D100, 2 oz. Spray	100%	10.95	9.85	8.85
EN-341-210	DeoxIT Pen Applicator	100%	9.95	8.95	8.05
EN-341-215	DeoxIT Vial w/brush, 7.4 ml.	100%	6.95	6.25	5.65
EN-341-220	DeoxIT Precision Dispenser	100%	14.95	13.45	12.10

Phone FM Transmitter Kit

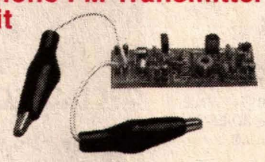

This small circuit, when connected to a phone line, transmits both sides of a telephone conversation into the FM radio band in the 90-95MHz area. The phone line itself is used as an antenna. Includes all components and instructions.

#EN-320-067 ..... **$9.95** EACH

2 Stage FM Transmitter Kit

Easy to build and tune in the upper part of the FM band. Reaches over 1/2 mile (depending on conditions). Uses RF transistor for its final stage. Requires a 9V battery (not included). High quality PCB and components. Circuit schematic provided.

#EN-320-066 ..... **$10.95** EACH

B & W CCD Board Cameras

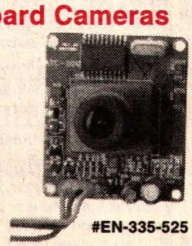

#EN-335-525

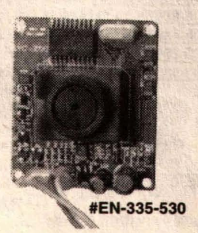

#EN-335-530

Ultra miniature, high performance 1/3" CCD single board cameras feature a built-in 3.6mm wide angle lens and 400 lines of resolution. Requires a 12 VDC power supply (our #120-1100). Dimensions: 1-1/2" W x 1-3/4" H x 1" D.

#EN-335-525 (Standard lens) ..... **$149.95** EACH

#EN-335-530 (Pin hole lens) ..... **$169.95** EACH

#EN-120-1100 (12VDC power supply) ..... **$7.15** EACH

FREE CATALOG

CALL TOLL FREE

1-800-338-0531

340 E. First St., Dayton, OH 45402-1257 ◆ Phone: 513-222-0173 ◆ Fax: 513-222-4644

◆30 day money back guarantee ◆$20.00 minimum order ◆We accept Mastercard, Visa, Discover, and company C.O.D. orders ◆24 hour shipping ◆Shipping charge = UPS chart rate + $1.90 ($5.00 minimum charge) ◆Hours 8:00 am - 8:00 pm ET, Monday - Friday ◆9:00 am - 5:00 pm Saturday. Mail order customers, please call for shipping estimate on orders exceeding 5 lbs. ◆Foreign destination customers please send $5.00 U.S. funds for catalog. ◆Quantity pricing available.

CIRCLE 262 ON FREE INFORMATION CARD

SEC Sun Equipment Corporation

3121-A Glen Royal Rd., Raleigh, NC 27612

Test Equipment for Cost-Minded People

LODESTAR Lodestar Electronics Corp. Since 1979

One Year Warranty. 15 Day Money Back Guarantee. OEM welcome.
School purchase order accepted. Bids accepted. VISA, DISCOVER
***SALES REP./DISTRIBUTORS/OEM WANTED.* MASTER, & AMER.**
1-800-870-1955/(919)870-1955 24-hr Fax:(919)870-5720

DC POWER SUPPLY

PS-303 $159.00 0-30VDC, 0-3A; 0.02%+2mV line regulation; 0.02%+3mV load regulation; 1mVrms noise & ripple; Short circuit/overload protection; constant current/voltage(CC/CV). **PS-303D $314.95** dual output, tracking **PS-305 $219.95**, 0-30VDC, 0-5A. **PS-305D $399.95**, dual, tracking.

8110 $289.95 0-60VDC, 0-3A. **8112 $399.95** 0-60VDC, 0-5A. **8108(8109) $549.95($699.95)** 0-60VDC, 0-3A(5A), dual, independent tracking. Low ripple. **8102(8103) $399.95($489.95)** dual 0-30VDC/0-3A(5A), fixed 5VDC/3A, indepedent tracking operation, constant voltage and current. Slave/Master, Serial/Parallel connection. **PS-1610S(8107) $289.00($399.95)** 0-16VDC(0-30VDC), 0-10A. **PS-2243(2245) $139.00($159.00)** 0-12/0-24VDC,3A(5A). **8200(8201) $179.95($239.95)** 0-30VDC(digital meter), 0-3A(5A). **8210(8211) $199.95($259.95)** two digital meters. **8202(8203) $499.95($549.95)** 3 outputs, digital display, dual 0-30VDC/0-3A(5A), a fixed 5VDC/3A, indepedent tracking operation, constant voltage and current.

AM/FM SWEEMAR SCOPE

SM-6225B/C $1999.95 *Freq Range:* (AM)490KHz; (FM) 10-11.4MHz; *Acuracy:* ± 0.1% *Marker:* (AM)455KHz, ±5KHz, ±10KHz; (FM)10.7MHz, ±7.5KHz, ±150KHz.

STEREO SCOPE OS-7505B $369.00 trigger, 0-10MHz.

ALIGMENT SCOPE OS-7001A $369.00 0-200KHz.

AM/FM STD SIGNAL GEN.

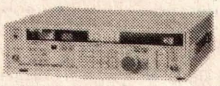

SG-4110A $1799.00 *Freq:* 100KHz-110MHz *Display:* 6-digit LED *Accuracy:* <±(5x10-E5 ±1 count) *Resolution:*100Hz (100-34.99MHz); 1KHz (35MHz-110MHz). *Output:* -19dBu, -99dBu, 1dB steps. *Impedence:* 50Ω VSWR 1.2.

NTSC TV COLOR BAR PAT. GEN.

CPG-1366A $159.95 VHF NTSC; *Freq.:* 45.75, 175.25, 187.25 MHz; *RF Output:* 10mV. *Impedence:* 75 Ohm; *Video Output:* BNC, 1Vp-p

SWR/RF POWER METER

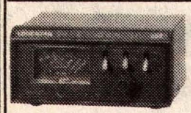

310 $89.95 *Freq.Range:* 1.8-150MHz. *RF Power:* 0-4W/20W/200W *SWR Measure.:* 1.0 - ∞, 4W min. Accurcy: 5%-10%; SO-239 plugs. *Insertion Loss:* O.3dB. *Input/Output Imp.:* 50Ω.

320 $89.95, 130-520MHz. **330 $119.95,** 1.8-520MHz. **SWR-3P $26.95** 1.7-150MHz; *RF Power:* 0.5-10W, 0.5W-100W. **SWR-2P $22.95,** 1.7-30MHz; *RF Power:* 0.5-10W. **mW RF Power Meter 340 $219.00**, 1.8-500MHz; 20mW ~ 2W.

RF SIGNAL GENERATOR

SG-4160B $124.95 100KHz-150MHz up to 450MHz on 3rd harmonics; 6 ranges; AM modulation. *RF Output:* 100mVrms to 3-5MHz. *Modulation:* Int. 1KHz AM, Ext. 50Hz-20KHz AM. *Audio Output:* 1KHz, 1Vrms. **SG-4162AD $229.95,** with Freq. Counter 1Hz-150MHz, 6 digits, for internal & external signals. Specification see SG-4160B above.

AUDIO GENERATOR

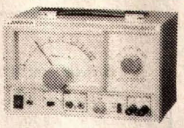

AG-2601A $124.95 10Hz-1MHz, 5 ranges; *Output Level:* sinewave 0-8Vrms, square 10Vp-p. *Output Impedence:* 600 Ohm. *Distortion:* <0.05% 500Hz-50KHz, <0.5% 50KHz-500KHz. **AG-2603AD $229.95,** with Freq. Counter 1Hz-150MHz, 6 digits, for internal & external signals. Specification see AG-2601A above

FUNCTION GENERATOR

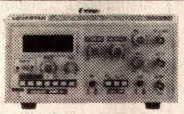

FG-2100A $169.95 0.2Hz-2MHz in 7 ranges; Sine, Square, Triangle, Pulse & Ramp *Output:* 5mVp-p-20Vp-p, 1% distortion. *VCF:* 0-10V control freq. to 1000:1. **FG-2102AD $229.95** generates signals same as FG-2100; 4-digit counter display, TTL & CMOS outputs, 30ppm ±1 count accuracy **FG-2020B $159.00** 0.5Hz-500KHz; Sine, Square, Triangle. **(FG)2103 $329.95,** Digital sweep generator, 0.5Hz-5MHz in 7 ranges. *Operating Mode:* sweep, AM, gated burst, VCG. *Freq. Counter:* Int. 0.5Hz-5MHz; Ext. 5HZ-10MHz

FM STEREO MODULATOR

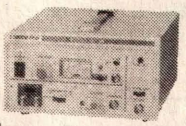

AG-2011A $549.00 **RF SECTION:** *Carrier:* 98MHz ±2MHz; *Output:* 10mV, 1mV & 0.1mV **COMPOSITE SIGNALS:** *Pilot:* 19KHz ±2Hz, 0.8Vrms **INT. MODULATION:** 400KHz, 1KHz ±1%, 1Vrms, distortion < .5%;*L-R Seperation:* >50dB. **EXT. MODULATION:** *Freq.:* 50Hz-15KHz *L-R Seperation:* >45dB 100Hz-3KHz; >35dB 50Hz-15KHz..

AC MILLIVOLT METER

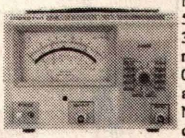

MV-3100A $159.95 wide band 5Hz~1MHz; 3 scales, mV, dB &dBm; 300μV~100V in 12 ranges, 10μV resolution; -70~40dB in 12 ranges, 0dB=1Vrms,0dBm=0.755V); ±3% accuracy; Input impedence 10MΩ; Noise <2%. **MV-3201B $309.95** dual channels, simultaneous measurement.. **OSCILLOSCOPE OS-7305B $249.00** DC~7MHz, *Vertical:* 10mV/Div; Horizontal: 250mV/Div; 10Hz~100KHz in 4 ranges; 3" CRT;Internal and External Sync.; Input: 1MΩ/35pF. **OS-7010A $369.00** DC~10MHz. 5" CRT, 10mV/Cm~10V/Cm, 1MΩ. **OS-622B $344.95** 20MHz/dual trace **OS-653 $699.95** 50MHz, dual, delay sweep, ALT trigger, TV syn. **OS-6100B $1329.95** 100MHz, 4ch. 8 traces, delay sweep,best buy

GRID DIP METER

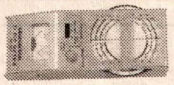

DM-4061 $89.95 1.5-250MHz, 6 bands;6 plug-in coils, 2 transistor, and 1 diode. *Modulation:*≈ 2KHz Sinewave. *Crystal Oscillator:* 1-15MHz. Wave absorption meter. Using 9VDCpower supply.

AUTO DISTORTION METER

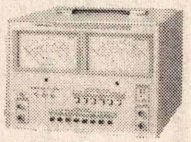

DM-3104A $799.95 *MEASUREMENT:* *Range:* 0.01%-30%, 0.1/0.3/1/3/10/30% full scale. *Freq.:* 400Hz±10%, 1000Hz±10%(HPF). *Input:* 3mV-100V, ratio measuring 20dB. *Auto. Switching Ranges:* Fundamental Freq. ≈ (fo)±10%; *Fund. Rejection:* >-80dB at (fo)±5%; >-70dB at (fo)±10%. *Harmonic Accuracy:* ±0.5dB, 1.8(fo)-20KHz. **DM-3204 $1,599.00** dual channels.

FREQUENCY COUNTER

FC-5250C $119.95 *Freq. Range:* 10Hz-220MHz (HF)10Hz-20MHz, (VHF)10MHz-200MHz *Gate Time:* 0.1 & 1sec. *Max. Input:* 10Vp-p. *Input Sensitivity:* 35mV 10Hz-200MHz. *Display:* 7-digit LEDs. *Input Imped.:* (HF) 1MOhm, (VHF) 50Ohm.

FC-5260A $146.00 10Hz-600MHz. 7-digit LEDs. **FC-5270 $149.95** 10Hz-1.2GHz. 8-digit LEDs. **FC-5600B $321.00** 10Hz-600MHz. 10-digit LEDs. **(FC)5700 $329.95** 10Hz ~ 1.3GHz. 10-digit LEDs.

SIGNAL TRACER/INJECTOR

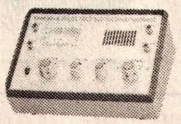

SE-6100 $134.95 **TRACER:** Gain Max. 60dB *Attenuation:* 0/20/40/60dB *Input Imped.:* 100KOhm *Output Imped.:* 600Ohm; *Speaker:* 8 Ohm. **INJECTOR:** *Freq.:* 1KHz Squarewave; *Output Level:* Continuously variable 0 - 4.5Vp-p.

AUTO. CAPACITANCE METER

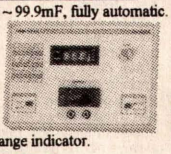

CM3300A $139.00 10 ranges, 99.9pF ~ 99.9mF, fully automatic. *Resolution:* 0.1pF lowest, 0.1% full scale. *Accuracy:* 0.5% of full scale±1digit to 99.9μF, 1% of full scale±1digit to 99.9μF. *Display:* 3 digit LED. *Unit indicator:* pF, nF, μF, mF. Overrange indicator.

WOW-FLUTTER METER

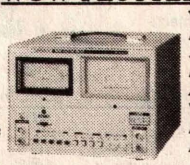

WF-3103A $699.95 *Freq. Range:* 3KHz±10% JIS/CCIR; 3.15KHz±10% DIN. *Range:* 0.03/.1/.3/3% full scale. *Accuracy:* ±5%. **WF-3105A $799.95,** digital; *Function:* LIN/WOW/Flutter/WTD. *Freq Cntr:* 10Hz-9.99MHz. *Indication:* CCIR/DIN/JIS.

MICROPROCESSOR/CONTROLLER TRAINER

Now, you can learn and apply Computer control on your PC with our low-cost trainers and lead yourself to the advanced 80386, 80486, etc.. Learn ASSEMBLY, C, and BASIC languages programming and debugging, and Microprocessor based system hardware design and troubleshooting. Experiment guide and example programs are included in each trainer. These trainers are widely adopted by technical colleges.

8088 Trainer $699.00 BGC-8088, teach yourself 8088 assembly language programming. **Features:** Assembly language coding, assembler, disassembler, single step and multi-breakpoint program debugger, display and rewrite registers, download/upload programs from/to external systems, I/O drivers, 56-key large size keyboard, LCD display, RS-232, UART, printer interface, two expansion slots, ±5V, ±12V switching power supply, 20 I/O applications available, e.g. servo& stepping motors, dot matrix display, D/A, A/D, sensors, ...

8051/8052 Embedded Microcontroller $979.00 BGC-8052, teach yourself Intel 8051/8052 Microcontroller controls. 8051/8052 is one of the most popular Microcontroller used in today's appliance controls and is compatible with the new powerful MCS 251.

8051/52 In-Circuit Emulator, APEX-IE assembly language programming and debugging.

CIC-100 $549.00 I/O control applications, learn Assembly, C, and BASIC programming languages, 800-pin solderless breadboard for circuit design and test, I/O drivers for controlling relay, step motor, LED, speaker, sensor, ..etc.. Application control modules available.

EDS-8804 $89.00 A/D and D/A converters. **EDS-8805 $239.00** Servo and stepper motors. **EDS-8806 $159.00** Basic I/O experiments. **EDS-8807N-16 $619.00** 16 Dot matrix LEDs. **EDS-8807N-8 $419.00** 8 Dot matrix LEDs. **EDS-8808 $269.00** Opto-couple controls. **EDS-8809-1 $589.00** stepper motor control , digital clock, speaker cntrl,dot-matrix LED, matrix keyboard, sign lights, electric piano, stop watch, ... 24 experiments, example programs included.

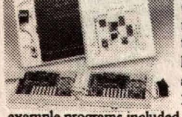

20% Off, DC POWER SUPPLIES

***DEMO UNITS:* 8102** triple outputs, 0-30V/0-3A, 5V/3A serial/parallel ~~$399.95~~ $319.95. **PS-303D** dual outputs, ~~$314.95~~ $252.95.

NEW PRODUCTS

mW RF Power Meter 340 $219.00 1.8-500MHz; RF power: 20mW/200mW/2W; Imp.: 50Ω; Accuracy: ±10% full scale; N-type connector;SWR <1.15

Digital DC Power Supply 8300 (8301) $199.95 (259.95) , 0-30V/3A(5A), CC/CV.

Electronic UHF Attenuator 085E (087E) $399.00, DC-950MHz, Imp: 50(75Ω), 1 dB step.

Computer Monitor Tester MT801 $175.00 Test MDA, CGA, EGA, VGA, SVGA, 8514A monitors; Video Patterns: color bars, cross hatch, dots, color raster and windows; Two video connectors: digital TTL 9-D & analog 15-HD; Power: 120VAC. **MT810 $129**: Hand held model, Power: 9VDC.

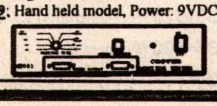

CIRCLE 308 ON FREE INFORMATION CARD

DALBANI

$20 MINIMUM ORDER
CALL NOW FOR YOUR
232 PAGE FREE CATALOG
1-800-325-2264

CODE EN96
PLEASE MENTION WHEN ORDERING

Items are subject to availability.
Prices are subject to change without any prior notice.

FLYBACK TRANSFORMERS

$12.50

Replaces GOLDSTAR 154-074R
ORDER Nº 63-0189

UNIQUE REALTIME OSCILLOSCOPE BUILT-IN FUNCTION GENERATOR

Order Nº 50-820

Manuf # OS-9020G
20MHz 2-CH DUAL TRACE

$498.00

1 MHZ FUNCTION GENERATOR

Features

• Wider than specified frequency response • High deflection factor of 1mV/div.• Wide dynamic range up to 30MHz without waveform distortion • Algebric sum of CH1 and CH2 • Low drift with compensation circuit • Superb trigger sensitivity • Maximum sweep rate of video signals with internal TV sync. separator • Jittless trigger circuitry • CH1 signal output terminal available • Variable trigger hold-off • High precision X-Y phase difference measurement up to 50kHz • Built-in function generator with BNC output of 50Ω and TTL • Three kinds of waveform are available with 50Ω output • Flat output waveform frequency up to 1MHz

Specifications:

Vertical deflection: • Bandwidth :DC coupled (DC to 20MHz normal), AC coupled :(10Hz to 20MHz normal) • Deflection factor: 5mV/div to 5V/div in 10 calibrated steps of 1-2-5 sequence • Rise time: 17.5nS or less
Horizantal deflection: • Time Base A: 0.2µs to 0.2S/div in 19 calibrated steps.1-2-5 sequence • Uncalibrated continuous control between steps of at least 1: 2.5.

HOT PRICES ON POPULAR SEMI'S

Order Nº	Brand	Min	Price
BU-208	TESLA	10	$1.49
BU-208/O	TOSHIBA	1	4.50
2N-3055	TESLA	10	0.60
2N-3773	TESLA	5	1.20
2SD1398	SANYO	10	1.49
2SD-1650	SANYO	5	1.69
STRD-1005	SANKEN	1	4.15
STR-30130	SANKEN	1	2.66
STRS-6301	SANKEN	1	8.50
TA-7777N	TOSHIBA	1	6.96
TDA-2005	SGS	5	1.49

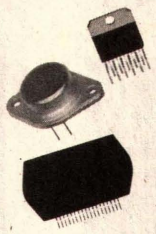

TUN-O-WASH®

Chemtronics

ORDER Nº 30-0100

$7.50 (CFC Free)

Fast drying electronics grade cleaner for tuners, controls and PC boards.

TUN-O-WASH is excellent cleaner and degreaser for tuners, controllers and PC boards.

• Designed for cleaning and degreasing consumer electronics • Cleans in one step, no rinsing required • Contains no ozone depleting compounds • CFC and HCFC free
• Not for use on energized equipment
• 12.5 Oz aerosol (12 cans per case)

DIGITAL MULTIMETERS

DALCO

NEW! *Digital*

• Overload protect 1000VDC or peak AC on all other ranges • Input impedance 10M Ohm on all ranges • Base accuracy range ± 0.5 % to ± 1.0 % • Resistance 200Ω, 2K, 20K, 200K, 2M, 20M • Audible continuity response lower than 50Ω • DC Voltage 200mV, 2V, 20V, 200V, 1000V AC Voltage 200mV, 2V, 20V, 200V, 700V

ORDER Nº 50-815

$19.95

COLOR CODED LEADS HEAVY DUTY

$2.82

ORDER Nº 56-500

• 11" Long Wire Lead
• Insulated 1 1/2" Alligator Clips
• 20 Gauge Wire Size • 10 Leads
• BLACK, GREEN, RED,YELLOW, WHITE

SOLDER WICK

• Solder Remover
• Length 5 Feet

85¢ Min. 2 pcs.

ORDER Nº 51-1050

VCR ALIGNMENTTOOL KIT

ORDER # 50-888

$24.99

The most popular

• VCR Head puller
• Retaining ring remover
• Spring hook
• Micro screwdriver
• Hex key set • Fitted vinyl • Soft zippered case
• Dimensions: 91/2"(W) X 121/4"(L)
• 7 Assorted head & guide aligners
• 3 Reverseable screwdrivers (Small-Flat-Philips)

LOGIC Probe

ORDER Nº 51-1015

$8.99

• Length: 8 inches
• Range: 4.5 To 15 VDC
• Includes Test Leads • Compatible With TTL,DTL,RTL,HTL,CMOS, NMOS Logic

SOLDER ROLL

• 1 LB Spool
• 370 deg F melting point
• Fastest solder
• Alloy 60/40, tin lead, non corrosive flux, Diam. 1.2mm

ORDER Nº 51-1005

$3.95

TEMPERATURE CONTROLLED SOLDERING STATION

$64.00

• Adjustable Temp.: 300°F - 790°F - 150°C - 480°C
• Grounded Tip for Soldering : Static Sensitive Devices, Heater Aid.
• Led Power Temperature Indicator
• Overheat Protection W/ Temperature Control
• Auxiliary Grounded Terminal
• Comes in digital LED display
• 48 Watts soldering iron

ORDER Nº 51-1035

Universal Audio/video Remote

ORDER Nº. 82-1055

• Controls basic functions of TV, VCR, cable box, and CD or laser player • Ergonomic design! Main buttons are in line with natural thumb motion • Two-minute memory allows time to replasce batteries without reprogramming • Programming reminder sticker inside battery compartment • Sleep time for 60, 30, or 15 minutes(according to your TV) • Set key recessed to prevent accidental deprogramming • Spanish instruction included. • Requires four AAA Batteries (not included)

MAGNAVOX

Smart. Very smart

$9.95

- **Cable (11 brands)**
- **VCR (68 brands)**
- **TV (77 brands)**
- **Compact disc and Laser Disc (94 brands)**

4225 N.W. 72nd AVE MIAMI, FLORIDA 33166 TEL : (305) 716-1016 FAX : (305) 594-6588

CIRCLE 234 ON FREE INFORMATION CARD

Books that work the way you work...

SPECIAL OFFER
No obligation

SAVE OVER 10%

NEW FROM JOHN LENK

1996, paperback
~~$29.95~~ $26.95
0-7506-9821-7

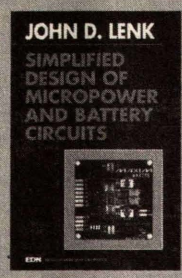

1996, paperback
~~$29.95~~ $26.95
0-7506-9510-2

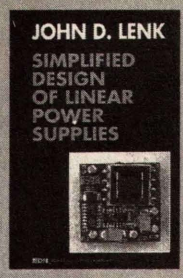

1996, paperback
~~$29.95~~ $26.95
0-7506-9820-9

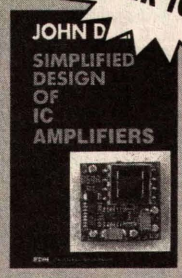

June 1996, paperback
~~$29.95~~ $26.95
0-7506-9508-0

Butterworth-Heinemann brings you something for everyone from John Lenk's Simplified Design Series. These books are all-inclusive, one-stop guides. Each has step-by-step instructions and diagrams that make it easy-to-use for the student, experimenter, and professional. All are available in paperback.

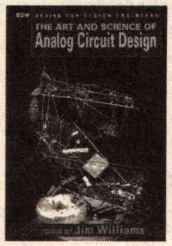

1995, hardcover
~~$49.95~~ $44.95
0-7506-9505-6

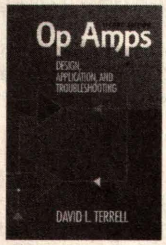

1996, hardcover
~~$49.95~~ $44.95
0-7506-9702-4

1995, paperback
~~$29.95~~ $26.95
0-7506-9694-X

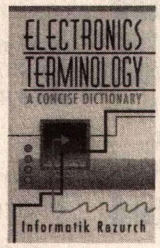

1996, paperback
~~$12.95~~ $10.95
0-7506-9751-2

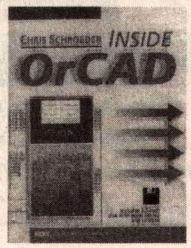

1996, paperback
includes disk
~~$39.95~~ $35.95
0-7506-9700-8

July 1996, hardcover
~~$49.95~~ $44.95
0-7506-9747-4

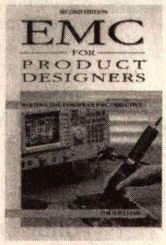

1996, paperback
~~$47.95~~ $42.95
0-7506-2466-3

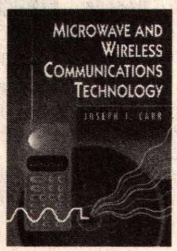

1996, paperback
~~$44.95~~ $39.95
0-7506-9707-5

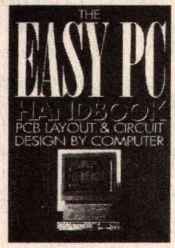

1995, paperback
~~$47.95~~ $42.95
0-7506-2281-4

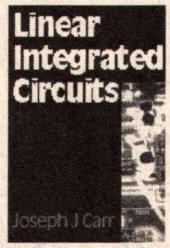

1996, paperback
~~$37.95~~ $33.95
0-7506-2591-0

❑ Please send me the book(s) listed below at 10% off! Phone: 1-800-366-BOOK FAX: 1-800-446-6520

Please add $4.00 for handling for the first item ordered and $1.50 for each additional item ordered to all check and credit card orders. Billed orders will be charged additional shipping based on weight and destination. All US orders must include your state sales tax. Prepayment or company purchase order is required for all orders. Canadian customers please pay by credit card or in US funds and include 7% GST on books and handling. Prices subject to change without notice.

Write book number(s) here

Charge my: ❑ VISA ❑ AMEX ❑ MC Card # _____ EXP Date _____

Name _____ Signature _____

Address _____ City/ State/ ZIP _____

Tel _____ E-mail _____

Visit us on the Internet @ http://www.bh.com/bh/el **❑ Send me a FREE catalog (item 642)**

BUTTERWORTH HEINEMANN **313 Washington Street, Newton, MA 02158**
from outside US and Canada, call 617-928-2500

TS123

CIRCLE 324 ON FREE INFORMATION CARD

Get the best, most accurate diagnostics for problem PCs...

Low-Level Formats IDE Drives!

the UNIVERSAL DIAGNOSTICS TOOLKIT™

Compatible with any PC & Operating System!

Call Now for Information on Special Pricing:

1-800-864-8008

or Fax (818) 547-0397

VISA MasterCard AMERICAN EXPRESS DISCOVER

1100 East Broadway, Suite 301, Glendale, California
Phone 818/547-0125 • Fax 818/547-0397
Web Page: http://www.micro2000.com
International Orders please call:
Micro 2000 Australia.....61-42-574-144
Micro 2000 UK.....44-462-483-483
Micro 2000 Amsterdam 31-206-384-433

CIRCLE 303 ON FREE INFORMATION CARD

New Releases:

Call about our Tutorial and TroubleShooting Series on video cassettes! A wealth of technical help at your fingertips.

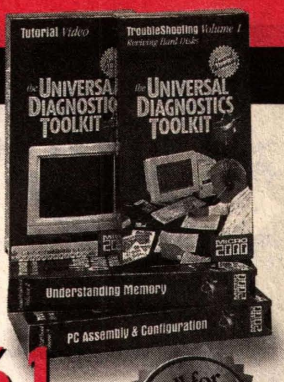

Micro-Scope™ 6.1

UNIVERSAL DIAGNOSTIC SOFTWARE

Call for Your 6.1 Upgrade

Fully O/S independent diagnostic software...

Call for upgrade pricing & complete new features list!

MICRO-SCOPE Universal Computer Diagnostics was developed to satisfy the expanding need for accurate system diagnosis in the rapidly growing desktop computer market. Patterned after super-mini and mainframe diagnostic routines, **MICRO-SCOPE** runs independently of any standard operating system, and is therefore at home on any machine in the Intel world. Speed, ease-of-use, and razor sharp **ACCURACY** are a few of the advantages that arise from this system independence. **Jerry Pournelle** awarded MICRO-SCOPE & POST-PROBE the User's Choice Award in the May 1994 issue of Byte Magazine, saying: **"You name it, this tests it. If you maintain PCs you'll love it."**

◆ **LOW-LEVEL FORMAT**—Performs Low-level format on all drive types including IDE drives. This function cannot hurt IDE drives. ◆ **TRUE HARDWARE DIAGNOSTICS**—Accurate testing of CPU, IRQ's, DMA's, memory, hard drives, floppy drives, video cards, etc. ◆ **IRQ CHECK**—Talks directly to hardware and shows I/O address and IRQ of devices that respond. ◆ **O/S INDEPENDENT**—Does not rely on O/S for diagnostics. Talks to PC on hardware level. All tests are full function regardless of O/S (i.e. Windows, Novell, UNIX, OS/2). ◆ **IRQ DISPLAY**—Show bits enabled in IRQ chip for finding cards that are software driven (Network, Tape Backup, etc.). ◆ **MEMORY EXAMINE**—Displays any physical bit of memory under 1 Meg. Very useful for determining memory conflicts and available memory space. ◆ **AND MUCH MORE...** We don't have enough space here for everything this software can do!

Post◆Probe™

First Ever Universal P.O.S.T. Card for All PCs!

Use this Power-On Self-Test card to debug any "dead" PC that won't boot...

"This is the only card that will function in every system on the market. The documentation is extensive, and not only covers the expected POST Codes for different BIOS versions, but also includes a detailed reference to the bus signals monitored by the card." **—Scott Mueller** from his globally recognized book, ***'Upgrading & Repairing PCs, Second Edition'***

◆ Includes pads for voltmeter to attach for actual voltage testing under load. ◆ 4 LEDs monitor +5vdc -5vdc +12vdc -12vdc. ◆ Monitors Hi & Lo clock and OSC cycles to distinguish between clock chip or crystal failure. ◆ Monitors I/O Write and I/O Read to distinguish between write and read errors. ◆ Accurately monitors progress of POST for computers *without* POST codes. ◆ Reads POST codes from any IBM or compatible that emits POST codes. ISA/EISA/MCA. ◆ Compatible with Micro Channel computers. ◆ Dip switch allows easy selection of I/O ports to read. ◆ Includes tri-state **LOGIC PROBE** to determine actual chip failures. ◆ Manual includes chip layouts and detailed POST procedures for all major BIOS's. ◆ **AND MUCH MORE...**call for more details.

Award Winning Diagnostics

1993 BYTE POURNELLE'S USER'S CHOICE AWARD

PCUPGRADE EDITOR'S CHOICE

SERVICE NEWS PRODUCT OF THE MONTH

Govt. Serv. #: GS-00K-94AGS-5396

MICRO 2000

Register Today!

Workshop Opportunities For Electronics Instructors and Technicians

For over seventy years, EIA has been the primary trade association representing all facets of electronics manufacturing. CEMA represents U.S. manufacturers of audio, video, home office and home automation, consumer information, accessories, mobile electronics, multimedia products, and assistive devices for people with disabilities. In addition to managing the International Winter Consumer Electronics Show, CEMA member manufacturers work to promote optimum servicing of consumer electronic products and foster interest in continuing education of electronics technicians through the Product Services Department.

EIA/CEMA Hands-On Technical Training Workshops

The Consumer Electronics Manufacturers Association (CEMA), a sector of the Electronic Industries Association (EIA) offers the following technical workshops listed below. These "hands-on" workshops are part of our continuing education program and are conducted nationally at various educational institutions that have integrated EIA's Electronics Curriculum and methodology. Attendees will cover the industry's newest technology and receive training to help them increase their troubleshooting abilities.

Considering the high quality and timeliness of these programs — combined with materials the attendees retain — we believe that the practical nature of these workshops will provide them with new skills of immediate benefit. Please refer to the concise workshop outlines below for selected course topics. Classes range from 3 to 5 day sessions and are designed to upgrade the skills of both technicians and educators with electronics backgrounds. The workshops are provided by EIA/CEMA for a nominal fee of $50. EIA/CEMA is also offering CEUs this year. To register, or for general questions pertaining to our educational programs, please contact our staff by writing or calling:

Product Services, EIA/CEMA, 2500 Wilson Boulevard,
Arlington, VA 22201-3834 (703) 907-7656
Web Site: http://www.eia.org/cema/ps

Video Laser Disc Technology & Servicing

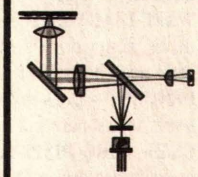

- VLD Servo Systems
- Video Signal Path
- Laser Optics
- Troubleshooting Techniques

3 days 2.0 CEUs

Computer Monitor Servicing

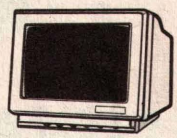

- Signal Formats
- Test Equipment
- Monitor Alignments
- Troubleshooting Techniques

3 days 2.0 CEUs

Color TV Technology & Servicing

- NTSC Signal Processing
- Test Equipment
- Receiver Alignments
- Troubleshooting Techniques

3 days 2.0 CEUs

VCR Technology & Servicing

- VCR Servo Systems
- VHS Signal Processing
- Tape Transport Alignment
- Troubleshooting Techniques

5 days 3.5 CEUs

1996 Technical Workshop Schedule

Workshop	Location	State/City		Date
VCR*	EIA - Headquarters	VA	Arlington	July 8-12, 1996
MON	EIA - Headquarters	VA	Arlington	Aug. 20-22, 1996
VLD	EIA - Headquarters	VA	Arlington	Sept. 11-13, 1996
CTV	EIA - Headquarters	VA	Arlington	Oct. 8-10, 1996
MON	EIA - Headquarters	VA	Arlington	Nov, 6-8, 1996
CTV*	Triton Community College	IL	River Grove	July 15-17, 1996
CTV	Triton Community College	IL	River Grove	Oct. 14-16, 1996
CTV*	Tampa Technical Institute	FL	Tampa	July 1-3, 1996
CTV	Tampa Technical Institute	FL	Tampa	Oct. 2-4, 1996
CTV	Mt. San Antonio Comm. College	CA	Walnut	Nov. 12-14, 1996

CEMA

* *Please call for possible openings due to cancellation.*

CTV = Color TV Technology & Servicing
MON = Computer Monitor Servicing
VLD = Video Laser Disc Technology & Servicing
VCR = Video Cassette Recorder Technology & Servicing

CIRCLE 312 ON FREE INFORMATION CARD

PumaD\eiregnow\596

TECH-SYSTEMS

1309 Hwy. 71 Belmar, NJ 07719
908-280-0007 FAX: 908-280-0111

800-435-1516

BUY - SELL - TRADE

VISA & MasterCard Accepted

90 Day Warranty / 10 Day Right of Return

N.I.S.T. Traceable Calibration Available on Most Items

SPECTRUM ANALYZERS

TEK 492/01/02 Spectrum Analyzer 50KHz to 21GHz	$6,995
Option 01 Adds Internal Preselection and 02 Adds Digital Storage	
TEK 492/02 Spectrum Analyzer 50KHz to 21GHz	6,650
Option 21 18GHz to 40GHz Waveguide Mixer Set	1,775
TEK 496 1kHz - 1800 MHz. Spectrum Analyzer	4,750.
TEK 7L12 100KHz to 1800MHz Spectrum Analyzer Plug-In	1,850
TEK 7L13 1KHz to 1800 MHz Spectrum Analyzer Plug-In	2,495
TEK TR503 Tracking Generator w/TM503 Power Supply	1,450
HP 141T/8552B/8555A 10 MHz to 18GHz Spectrum Analyzer	2,195
HP 141T Variable Persistence/Storage Display	595
HP 140T Non-Storage Display	425
HP 8553B 1KHz to 110MHz RF Section	450
HP 8554L 100KHz to 1250MHz RF Section	550
HP 8554B 100KHz to 1250MHz RF Section	795
HP 8555A 10MHz to 18GHz RF Section	995
HP 8556A 20Hz to 300 KHz LF Section	450
HP 8552B IF Section	650
HP 8552A Economy IF Section	295
HP 8443A 0.1 to 110MHz Tracking Generator	550
HP 8444A 0.1 to 1300MHz Tracking Generator	795
HP 8444A/059 0.5 to 1500MHz Tracking Generator	1,350
HP 8445B 1.8 to 18GHz Preselector	650
HP 182T Mainframe	495
HP 182T/8557A 10KHz to 350MHz Spectrum Analyzer	1,495
HP 182T/8558B 100KHz to 1500MHz Spectrum Analyzer	3,350
HP 8557A 10KHz to 350MHz Spectrum Analyzer Plug-In	1,250
HP 8558B 100KHz to 1500MHz Spectrum Analyzer Plug-In	2,395
HP 8559A 0.01 to 21GHz Spectrum Analyzer Plug-In	4,450

OSCILLOSCOPES

TEK 465 100MHz Portable Scope	$595
TEK 475 200MHz Portable Scope	795
TEK 485 300MHz Portable Scope	995
TEK 2465 300MHz Portable Scope	2,595
HP 1741A 100MHz Portable Scope	495
HP 1725A 275Hz Portable Scope	695
HP 54200A 50MHz/200Msa/s Digitizing Scope	2,250
HP 54200D 50MHz/200Msa/s Digitizing Scope	2,650
HP 54201D 300MHz/200Msa/s Digitizing Scope	2,995
HP 54110D 1GHz/40Msa/s Digitizing Scope	5,995
HP 54111D 500MHz/1Gsa/s Digitizing Scope	6,995
TEK 7603 w/7A18 (X2) & 7B53A Scope	695
TEK 7104 w/7A29 (X2), 7B10 & 7B15 Scope	5,995

Over 600 TEK 7000, 5000 & TM Series Mainframes and Plug-Ins
Call for pricing information

WAVE - DISTORTION - MODULATION

HP 331A Distortion Analyzer 5Hz - 600 kHz.	$195
HP 332A Distortion Analyzer with AM Detector	295
HP 333A Distortion Analyzer with Auto Nulling & High Pass Filter	395
HP 334A Distortion Analyzer with Auto Nulling/High Pass Filter/ AM Detector	495
HP 3581C Selective Level Meter	995
TEK AA501 Distortion Analyzer	1,295
BOONTON 82AD/01/03/04 Modulation Meter	995
Marconi 2305 2.32GHz Modulation Meter w/IEEE	4,995

OVER 3000 ITEMS IN STOCK !
Inventory Changes Daily!
OVER 500 DC & AC POWER SUPPLIES !
Any Voltage - Any Current ! CALL

CALL FOR FREE 40 PAGE CATALOG

COMPONENT TEST

HP 4342A Q Meter (22KHz to 70MHz)	$2,495
HP 4342A/001 Q Meter (10KHz to 32MHz)	1,650
BOONTON 5110 LCR Meter 100Hz, 120Hz & 1 KHz Test Frequency	1,450
includes 5110-1 Test Adapter & 5110-4 Kelvin Clip Adapter	
BOONTON 72BD Digital Capacitance Meter 1MHz Test Freq. 2pF to 2000pF	750
TEK 576 Curve Tracer	2,995
TEK 577/D2 Curve Tracer	1,695
HUNTRON TRACKER 5000 Computer Controlled Troubleshooting System	1,350
SAUNDERS 150C/09 Crystal Test Oscillator Microprocessor Controlled/IEEE/1 to 60MHz	1,695
GENRAD 1630AV Inductance Measuring System	2,995

STANDARDS & CALIBRATORS

FLUKE 5100B/03/05 Multifunction Calibrator	$5,750
FLUKE 3330B DC Calibrator	1,995
FLUKE 515A Portable Calibrator AC/DC/RES	1,695
FLUKE 332B DC Calibrator	595
FLUKE 5205A AC Amplifier	2,650
FLUKE 5450A Resistance Calibrator 1 OHM to 100 megohms/8ppm	1,995
FLUKE 730A DC Transfer Standard	450
FLUKE 750A Reference Divider	450
FLUKE 720A Kelvin Varley Divider	1,895
ESI RV722 DC Divider 1ppm Accuracy	1,295
DATRON 4200/30/80 Autocal AC Standard	2,495
BOONTON 25A Power Meter Calibrator	450
BOONTON 2500A Power Meter Calibrator	450
HP 8477A Power Meter Calibrator	495
HP 11683A Range Calibrator	775
TEK PG506 Calibration Generator	1,350
TEK TG501 Time Mark Generator	1,350
TEK SG503 Leveled Sine Wave Generator 250KHz to 250MHz	1,350
TEK SG504 Leveled Sine Wave Generator 245MHz to 1050MHz	2,650
RFL 829G Multi-Function Calibrator	1,495

FREQUENCY COUNTERS

HP 5314A 100MHz Universal Counter	$225
HP 5315B 100MHz Universal Counter	495
HP 5316A 100MHz Universal Counter	695
HP 5328A/011/030 512MHz/IEEE Universal Counter	695
HP 5328A/011/031 1.3GHz/IEEE Universal Counter	895
HP 5340A/011 18GHz/IEEE Microwave Counter	1,950
HP 5342A/011 18GHz/IEEE Microwave Counter	2,750
HP 5300B/5303B 525MHz Counter	450
HP 5257A Transfer Oscillator for HP 5245 Counters	175
HP 5255A 3 to 12.4GHz Frequency Convertor	175
HP 5359A Time Synthesizer	1,895
SYSTRON DONNER 6054B 20Hz to 26.5GHz IEEE Microwave Counter	2,295
TEK DC5009 Programmable 135MHz Universal Counter	695
TEK DC505A 225MHz Universal Counter Plug-In	295
TEK DC508 1.3GHz Universal Counter Plug-In	450

SIGNAL SOURCES

HP 8640B/003 512MHz Signal Generator w/Reverse Power	$1,895
HP 8640B/001/002 1024MHz Signal Generator w/Audio Oscillator	2,795
HP 8656A 100KHz to 990MHz Synthesized Signal Generator	2,995
HP 8660C/86603A/86632B 2600MHz Synthesized Signal Generator	3,995
HP 8660A/86602A/86632B 1300MHz Synthesized Signal Generator	2,350
HP 8620C Sweeper Mainframe	395
HP 86222A 0.01 to 2.4GHz RF Plug-In	1,495
HP 86222B/001 0.01 to 2.4GHz RF Plug-In w/Crystal Markers & 70dB ATTN	1,795
HP 86290C 2 to 18.6GHz RF Plug-In	2,395
HP 86260A 12.4 to 18GHz RF Plug-In	995
HP 8697A 26.5 to 40GHz RF Plug-In	1,450
HP 214B Pulse Generator	1,995
HP 8005B 20MHz Dual Pulse Generator	450
HP 8007B 100MHz Pulse Generator	695
HP 8013B 50MHz Dual Pulse Generator	695
HP 3312A 13MHz Function Generator	895
BOONTON 2000 20GHz Sweep Generator	2,450
TEK FG501 2Hz to 2MHz Function Generator	195
TEK FG502 1KHz to 11MHz Function Generator	295
TEK FG503 1 to 3MHz Function Generator	195
TEK PG501 50MHz Pulse Generator	250
TEK PG502 250MHz Pulse Generator	495
TEK PG508 50MHz Pulse Generator	795
APPLIED MICROWAVE/EPSCO PG5KB 5kW/575 to 925MHz RF Pulser	2,995
VELONEX 380 5kW High Power Pulser	2,995
COBER 605/P27 2kW/10Hz to 1MHz High Power Pulser	1,350

We Buy & Sell Service Manuals
Coax/Waveguide Components
WANTED !
Surplus Electronic Test Equipment
FAX US YOUR LIST
FAX: 908-280-0111

CIRCLE 329 ON FREE INFORMATION CARD

BRIGAR ELECTRONICS

7-9 ALICE ST.-BINGHAMTON, NY 13904

PHONE: (607) 723-3111
FAX: (607) 723-5202
E-MAIL: BRIGAR2@aol.com

WAREHOUSE SALE

SEND FOR FREE CATALOGUE

DISCOVER NOVUS · VISA · MasterCard

CREDIT CARD DISCOUNT

$ 0.00 - $ 99.99	NET
$100.00- $249.99	LESS 10%
$250.00- $499.99	LESS 15%
$500.00- $999.99	LESS 20%
$1000.00 AND UP	LESS 25%

WHY PAY MORE ?

SERVING: ■INDUSTRY ■SCHOOLS ■HOBBYISTS ■EXPERIMENTORS ■CONSUMERS

OPEN: MONDAY THRU FRIDAY 7:30AM TO 4:30 PM, SATURDAY 7:30AM TO NOON

MAC 24VDC PNEUMATIC SOLENOID VALVE
ALUMINUM MANIFOLD. THE VALVE IS A TWO-POSITION SINGLE SOLENOID TYPE. PRESSURE 20 TO 150 PSI WATTS 5.4 TO 6.7 - 10" WIRE LEADS SUITABLE FOR AIR AND INERT GASES. SIZE: 5-1/4"L X 2"H X 1"D (RFE Good Cond)
BRIGAR PRICE..... $6.95

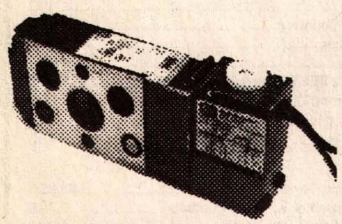

Modem Coupling TRANSFORMER
Midcom
PART # 671-8284
IMPEDANCE (OHM)

PRIM.	SEC.
600	**294**

INSERTION LOSS: **3.15 dB @ 1 kHz**

DC CURRENT: **0 MA**

RESISTANCE (ohm)

PRIM.	SEC.
156	**145**

DIELECTRIC RATING: **1000 VAC**

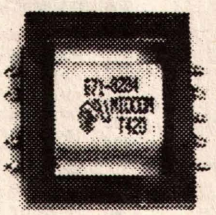

UL APPROVED.
PRICE $1.25 EA.

ROTRON - TARZAN FAN #TN3A2
■SIZE: 7" SQ X 4-11/32" DEEP
■WEIGHT 5 LB
■VOLTAGE 115VAC 50/60 HZ
■WATT 85 ■1.55AMP
■BALL BEARING
■ RPM 3300
■5 BLADE IMPELLER
Great for electronic cabinets & chassis.
BRAND NEW ...$49.95

ROHM # SLR47VR3F
RED LED T 1-3/4
5mm DIFFUSED LED
PRICE.....
100 PCS. FOR $10.00
1000 PCS. FOR $50.00

ROHM

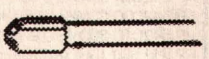

ULTRASONIC LIGHT SWITCH
Motion sensing sutomaticf switch replaces existing wall switcfh - operates from 120 vac power. 750 w. max load. Great for home alarm systems or controlling lights & small appliances.
Adjustable time & sensitivity, On-Off switch - LED Trip Indicator - color:white Size: 5"w x 5"h x 1-3/8"d
Energy Savings 30 to 60%
PRICE $12.95 EA.
5 FOR $60.00

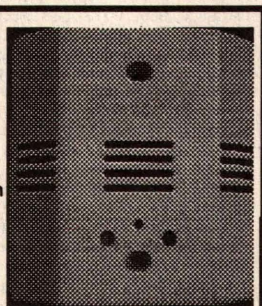

ISOLATED TOROID TRANSFORMER
BANNER MAGNETICS # 159249
INPUT: **120/240VAC**
ISOLATED OUTPUT **130VAC 10AMPS**
SIZE: 6.25" DIA. X 3.75"H
WEIGHT: 20 LB
PRICE.... $59.95

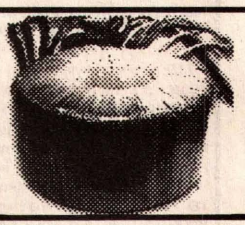

8000 SERIES MICROPROCESSOR
INTEL # P8051AH
8 BIT CMOS CPU, 256 BYTES RAM
12 MHz - 40 PIN
(Tie pin 31 low to bypass the internal ROM)
PRICE... $2.50 EA.
100 PCS & UP $1.75 EA.

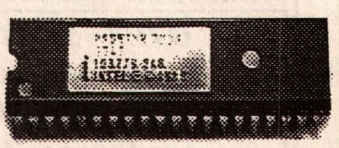

IBM 0S/2 STANDARD EDITION
VERSION 1.3 ON 3.5" DISKETTES
Supports large memory large files - Multiple applications and dos applications. Provides adobe type manager - High quality Typrographic fonts. Requirements: 2.0 MB of memory (min.) One 1.44 mb 3.5" Diskette drive - One fixed drive 12 MB free Space. **PRICE..... $49.95**

OPTREX #DMF50140NF-SEW
Intelligent graphic LCD Module "Supertwist" modules utilize surface mount tech. Displays blue pixels on white backround. Moudles have E-L backlighting - graphic-figure-character display. Built in drivers & 8 bit TTI Interface.
■Control LSI: T6963C Toshiba
■View angle: 6:00
■Dot Size .44(w) x .57(h)mm
■Dot pixels 143(w) x 98.4(h)mm
■View area 74.8(w) x 98.4(h)mm
■Dc Voltage 5vdc

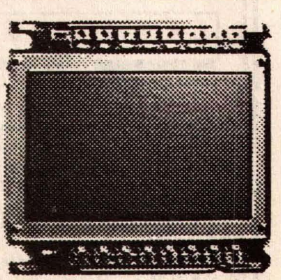

PRICE.... $14.95 EA.

SMITH CORONA #S-67181
WALL TRANSFORMER
INPUT: 120VAC 60 hz 12watt
OUTPUT: 9VDC 3.6 watt .4amp
6 ft. zip cord with 2.5mm Male plug
UL Listed - ***PRICE $2.25***

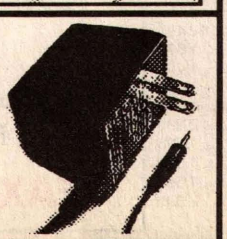

CIRCLE 325 ON FREE INFORMATION CARD

WORLD'S SMALLEST
UHF X-tal Controlled Video Transmitter

Full 100mW RF Output Power for realistic 500 foot+ range. Rugged epoxy encased Surface Mount Technology design. Optimized for High-Resolution Full Color and B&W Video. Transmits to any Cable-Ready TV or VCR (CATV Channel 59). Includes fully calibrated VidLink 50 module, cables and antenna

VidLink 50 Kit + B&W Micro Pinhole Camera *(Tiny! Only 1.2" x 1.2"):*
~~$599.00~~ **$399.00 +$5.50 S&H**

VidLink 50 Kit Only:
~~$399.00~~ **$199.00 +$5.50 S&H**

Payment by:
Check or MO, COD +$5.00

Manufacturer Direct! No Middlemen. Give us a call or visit us on the 'NET.

AEGIS RESEARCH

#671-1225 E. Sunset Dr.
Bellingham, WA
98226-3529 USA

1-604-224-0416

Visit our virtual catalog on the INTERNET at:
http://www.lynx.bc.ca/virtualspy

RF POWER
TRANSISTORS AND TUBES

In depth stocking of popular and hard-to-find Electronics Parts for Transmitters & Linear Amplifiers

Popular Transistors
2SC1969
2SC2166 • 2SC2290
2SC2312C • 2SC2879
MRF454 • MRF455
MRF455A • MRF477
MRF492 • MRF497
SRF3749 • SRF7000-90

Popular Tubes
6KD6 • 6LF6 • 6LQ6
M2057 • 6146B • 6146W
3-500Z • 3-500ZG
811A • 572B • 7199
7558 • 8417 • 8873
8874 • 8875 • 8877

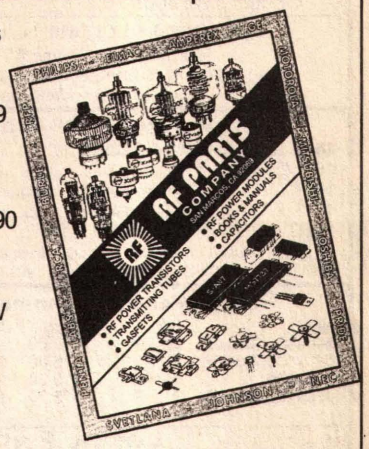

Order your FREE copy of our new Catalog by writing or calling us now.

Tel: (619) 744-0700 • Fax: (619) 744-1943

RF PARTS
435 SOUTH PACIFIC STREET
SAN MARCOS, CA 92069

REMOTE CONTROL A/B SWITCH

$20 each (3+)
plus shipping
MONEY BACK GUARANTEE
A/B/C SWITCH $25 each (3+)

CONTROLLED BY ANY REMOTE!

Now you can switch between two TV signal sources without getting up or even reaching for a different remote control! Simply press any button on any remote control and hold it down for two seconds. QuikSwitch contains a patented sensor that causes it to switch sources each time it receives an uninterrupted infrared signal for two seconds. And you won't need a spare AC oulet, because QuikSwitch operates a full year on 2 "AA" alkalines, 3 years on lithiums!

HIGH ISOLATION **100% SOLID STATE** **MADE IN U.S.A.**

VISA®

MILESTONE PRODUCTS
5698 WESTBOURNE AVE - COLUMBUS, OH 43213
1-800-535-7827

MasterCard

Licensed Under U.S. Patents 4,935,733 and 5,047,765 Other Patents Pending

BLOWOUT! TIMELINE INC. BLOWOUT!

Over 10 years and 27,000 customers and still growing

LIQUID CRYSTAL DISPLAYS

240x64 dot LCDs with built-in controller.

AND 4021ST-EO. *Unit is EL back-lit.* **$79.00 or 2 for $149.00**

OPTREX. DMF5005 **$69.00 or 2 for $129.00**

160 x 128 dot LCD with built-in controller (T6963C)

20 character x 16 line **$79.00 or 2 for $149.00**

Mfr.: Toshiba TLX-1013-EO. *Unit is EL back-lit. Dim: 5⅛"L x 4⅛"H. The built-in controller allows you to do text and graphics.*

Alphanumeric—parallel interface

16x1 .....3 for $25.00	20x2.....$12.00	40x1.....$8.00
16x1 (lg. char.)....$12.00	20x4.....$25.00	40x2 .....2 for $25.00
16x2.....$8.00	20x4 (lg. char.)....$25.00	40x4.....$25.00
16x2 (lg. char.)....$12.00	24x2.....$12.00	4x2.....$5.00
16x4.....$15.00	32x4.....$10.00	

5V power required • Built-in C-MOS LCD driver & controller • Easy "microprocessor" interface • 98 ASCII character generator • *Certain models are backlit, call for more info.*

Graphics and alphanumeric—serial interface

size	Mfr.	price	size	Mfr.	price
640x480 (backlit)	Epson	$35.00	480x128	Hitachi	$15.00
640x400 (backlit)	Panasonic	$25.00	256x128	Epson	$20.00
640x200	Toshiba	$15.00	240x128 (backlit)	Optrex	$20.00
480x128 (backlit)	ALPS	$15.00	240x64	Epson	$20.00
			160x128	Optrex	$15.00

LASER PRODUCTS

HeNe Laser Head (10Mw max. output) TEMOO, 15.5" long MFG: NEC **$99.00**

Laser Power Supply (for HeNe tube) **$89.00**

LASER SCANNER ASSEMBLY $29.00

Assembly intended for a laser printer. Includes laser diode, polygon motor (6 sided) and misc. optics and lenses.

LASER DIODE (5mW) with collimator **$20.00**

VISIBLE LASER DIODE: 5mw at 670nm **$15.00**

Index guided. Threshold current 40 ma typical.

POLYGON MOTOR UNIT & DRIVER $79.00

Ten-sided first surface mirror mounted on an armature that spins at 125 revolutions per second yielding a beam sweep rate of 1250 sweeps per second. The driver for the polygon unit requires 24 volts and plus and minus 12 volts to operate. There is also an f-theta lens in front of the polygon scanning mechanism with a three inch diameter. Great for optical experiments, etc. Very high quality units. **(MFR: JAPAN ELECTRONICS)**

NETWORK

Proteon ProNet-4 Model p1347 Token Ring Board $49.00

16 bit • 4 Mbps • IEEE 802.2 and 802.5 compatible • twisted pair • interoperable with IBM Token Ring network

POS & BAR CODE

MAGNETIC CARD READER *$25.00*

Includes: • 20 character dot matrix display with full alpha-numeric capability • keypanel with full alpha-numeric entry • separate 7.5 VDC/0.5 Amp power supply • standard telephone interface extension cord • lithium battery and flat-cone speaker.

HP bar code wand (HBCS 2300).....$25.00

POWER SUPPLYS

SWITCHING POWER SUPPLYS $12.00 or 2 for $20.00 115/230 Volts

73 WATT (2) 4 pin power connectors attached • Dim: 8.5" L x 4.5" W x 2" H
Output: +5V @ 2-9.75, A, +12V @ 0-1.5 A, -5V @ 0-0.4 A, -12V @ 0-0.5 A

68 WATT Dim: 5.5" L x 3.2" W x 1.7" H • Output: 5V @ 4 A, 12V @ 4A

60 WATT Dim: 8¾ x 4¼ x 3 • Output:5V @ 6A + 12V @ 1A - 5V @ 1A - 12V @ 1A

CHARGE COUPLED DEVICES

"The Spy In The Sky" $29.00

MATRIX TYPE

Sony CCD Imager - designed for black and white composite video cameras. Picture elements: 384 (H) x 491 (V)

Chip size 10.7 (H) x 9.3 (V) mm² • Unit cell size 23.0 (H) x 13.4 (V) um². Ceramic 24 pin DIP package • Mfr: Sony, Part# 016AL

4096 element CCD $19.00
1024 element CCD $15.00
2048 element CCD $15.00 • 1728 element CCD $15.00

LINEAR TYPE

MONITORS

Non-Enclosed TTL

Comes with pinout. 12V at 1.4 Amp input • Horizontal frequency 15Khz. • Ability to do 40 and 80 column.

5 inch Amber $29.00 • 7 inch Amber $39.00
9 inch Amber or Green $29.95

5" COLOR MONITOR $49.00

• Flat Faceplate • 320 x 200 Dot Resolution • CGA & Hercules Compatible
• 12 VDC Operation • 15.75 KHz Horiz. Freq. • 60 Hz Vert. Sync. Freq.
• Open Frame Construction • Standard Interface Connector • Degaussing Coil included • *Mfr. Samtron*

MISCELLANEOUS

ADAPTEC 4070A (RLL) OR 4000A (MFM), SCSI Controller, your choice $25.00

IBM 370 option XT and AT emulation boards $35.00

HACKER CORNER

POINT OF SALE BANK TERMINAL $69.00 or 2 for $129.00

• LCD Display 20 Char. x 4 Line • Printer 16 Column Dot Matrix - Epson • 24 Key Domed Membrane Keypad • Intel 80C32 Processor • 2 PCMCIA Sockets (ICC Slots) • Dallas DS1287 Realtime Clock • 2 Solid State Buzzers (Piezo Electric) • 4 Crystals • Rockwell Modem Chip • Telephone Line Interface (4 Pin "RJ" Connector) • RS-232 Interface (8 Pin "RJ" Connector) • NI-CAD Battery Pack Inside
Note: We have not been able to bypass an access code in the software. Thus, while time of day and other introductory things are displayed on LCD, the full original capabilities of this unit cannot be guaranteed. Also, we do not have a source for the smart cards that were to go in the PCM CIA sockets. Requires 12 volt adapter for power. (Not included) Dimensions: 9-1/2L x 6-1/4W x 2-1/2 D • Original cost over $450.00

CAMERA BLOCK $149.00

FOR ROBOTICS AND EVERYTHING ELSE

Unit is for Hi Band 8mm CamCorders, includes 8X zoom lenses, D/D converters, built-in CCD 2/3 in, 420 thousand picture elements, complementary mosaic filters. Excellent performance. High resolution, high sensitivity, low lag, low smear, good color reproduction, no distortion, 1/60-1/10000sec variable speed digital shutters, TTL auto focus, auto white balance, one-push auto white balance, auto/manual iris and gain up switch. Can be controlled by a 4bit micro computer. Remote controlling is possible for zoom and focusing. **NOTE:** These are PAL (European Standard) Units. **SONY PART #EVI-101 (PAL)**

CELL SITE TRANSCEIVER $79.00 2 for $149.00

These transceivers were designed for operation in an AMPS (Advanced Mobile Phone Service) cell site. The 20 MHz bandwidth of the transceiver allows it to operate on all 666 channels allocated. The transmit channels are 870.030-889.980 MHz with the receive channels 45 HMz below those frequencies. A digital synthesizer is utilized to generate the selected frequency. Each unit contains two independent receivers to demodulate voice and data with a Receive Signal Strength Indicator (RSSI) circuit to select the one with the best signal strength. The transmitter provides a 1.5 watt modulated signal to drive an external power amplifier. channel selection is accomplished with a 10 bit binary input via a connector on the back panel. Other interface requirements for operation are 26 VDC (unregulated) and an 18.990 MHz reference frequency for the digital synthesizer. The units contain independent boards for receivers, exciter, synthesizer, tunable front end, and interface assembly (which includes power supplies and voltage-controlled oscillator). Service manual, schematics and circuit descriptions included.

Encased Black & White Composite CCD Camera with Adapter

IR viewing to 1000 nm 7 ½ L x 2 ¾ W x 1 ¾ H

Comes complete with CCD camera, mounting nut on bottom of casing, 12VDC power supply. Excellent low light capability, standard RCA NTSC video out. **$89.00**

Great for: entryway security/remote monitoring, video conferencing/desktop video conferencing **2 for $159.00**

This miniature camera is perfect for multimedia computer applications as well as security and surveillance. NTSC output allows use with all popular video digitizing boards for Apple Macintosh and Microsoft video for Windows. Connects directly to any composite monitor or VCR with "video" input. Its razor-sharp wide-angle lens focuses from two inches to infinity and its state-of-the-art CCD technology accurately captures 16 level grayscale images for Quick Time movies and still pictures. Records at 30 frames per second and 260 lines resolution with excellent low light capability. Uses 12VDC (adapter supplied) and standard RCA cable.

Portable Micro Terminal $99.00 or 2 for $149.00

Flip up LCD display (9-16 VDC) • Can communicate with any computer having RS 232 port • Can communicate with another Microterminal • Ideal toy for the electronic hobbyist • Onboard microprocessor, data RAM (32K) and Video RAM (64K) • Contains built-in diagnostics and set up capabilities. • Original intention for POS applications. • display size 40x16 (256 x 128 pixels.) Dimensions: 6.3" W, 11"L, 2"H. (With LCD up height is 7.1")

BAREBONES 286-12 COMPUTER $49.00 (2 FOR $79.00)

Slimline desktop case, 100 watt supply, math co-processor support. On board IDE, & Floppy controllers. 2 COM ports and 1 parallel port with software setup. Supports up to 8 Megs using standard 30 PIN SIMMs. Internal room for (1) 3 1/2 inch IDE hard drive and (2) 3 1/2 inch floppies. Four 16 BIT ISA slots, accepts full length AT size cards. Keyboard can be set to no test at boot. Case size is 15.5"W x 16"D x 4"H.
(Motherboard can be purchased separately: $29.00 or 2 for $49.00)

.6" COMPOSITE MINIATURE COLOR DISPLAY $149.00

Fully encased. Dim: 1.3" x 1.3" x 4". 12 Volts DC power. NTSC signal. 250 H x 300 V resolution. Focus adjustable eyepiece. Applications include camcorder viewfinder, helmet mounted display, etc... Original cost over $600.00

23605 Telo Ave., Torrance, CA 90505
Order desk only: **USA: (800) 872-8878 CA: (800) 223-9977**
L.A. & Technical Info: **(310) 784-5488** Fax: **(310) 784-7590**
OEM INQUIRIES WELCOME

Minimum Order: $20.00. Minimum shipping and handling charge $5.00. We accept cashiers checks, MC or VISA. No personal checks or COD's. CA residents add 8.25% sales tax. We are not responsible for typographical errors. All merchandise subject to prior sale. Phone orders welcome. Foreign orders require special handling. Prices subject to change without notice. 20% restocking fee for returned orders.

CIRCLE 275 ON FREE INFORMATION CARD

DO-IT-YOURSELF AUDIO AMPLIFIER KITS

Mark V Electronics, Inc.
8019 E. Slauson Ave.,
Montebello, CA 90640
In business since 1985

Enclosures at Unbeatable prices !

Free Catalog 213/888-8988 Fax 213/888-6868

Order 1-800-521-MARK / 1-800-423-FIVE

Kit skill levels are specified as ▲ beginner ▲▲ intermediate or ▲▲▲ advanced!

Metal Cabinets with Aluminum Front Panel

Best Buy

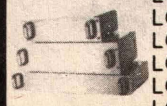

LG-1273	3x12x7"	$ 26.50
LG-1684	4x16x8"	32.50
LG-1924	4x19x11½"	38.25
LG-1925	5x19x11½"	42.00
LG-1983	2¼x19x8"	35.25
LG-1923	3x19x11½"	36.50
LG-1927	7x19x11½"	50.50

LG- Black anodized rack cabinet

New

*LL-1923B	2¾x19x12"	69.50
*LL-1925A	5x19x12"	79.50

*LL- High quality full Aluminum Cabinet
*LL- Front panel .157" & other panels .078"
*LL- Gold plated cap screw for front panel

- **Dimensions in inches ±.05**
- **Custom-made for other dimensions if over 100 pcs for single model !**

Modular Desktop Consoles

	L x W x H	
LE-453	4x4¾x3"	$ 7.50
LE-653	6x4¾x3"	9.75
LE-853	8x4¾x3"	11.75

LE- Black finished aluminum panel 1mm thick.

Camera Housing

*LD-1244	2¾x10¾x4"	$55.00
**LD-1516	3¾x13¾x4"	29.50
**LD-1565	4x13¾x5¼"	31.75

*LD- Stainless Steel 0.7mm
**LD- Sheet Metal 1mm

Alarm Box with Lock

Mejor Compra !

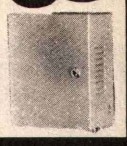

LB-1085	8¼x10¼x5"	$18.75
LB-1395	9¼x13¼x5"	25.50
LB-1525	12¼x15¼x5"	35.25
*LB-1494	9¼x14¼x4¼"	21.50
LB-1383A	8½x13¼x4"	23.25

*No lock & LB- Sheet Metal 0.8mm

Power Transformers &**Toroidal Transformer

001	28/30V x 2	6A	$ 30.00
002	36V x 2	3A	25.00
003	40V x 2	6A	32.00
**008	28/30V x 2	6A	40.00
**009	48/53V x 2	8A	66.00
**012	33/40/42Vx2	6A	48.00

TA-800MK2 ▲▲ 120+120W Pre & Main Stereo Amp. (4 lbs.)

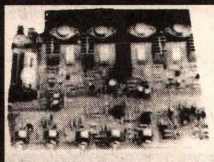

Kit:$ 67.92
Asmb.$ 86.95

Power Output:120W into 4 ohms RMS. 72W into 8 ohms RMS. Frequency Response:10-20KHZ. THD: <0.01%. Tone Control: Bass ±12dB, Mid & Treble ±8dB. Sensitivity: Phono Input, 3mV into 47K. Line, 0.3V into 47K. Signal to Noise Ratio: 86dB. Power Requirement: 40VDC @ 6A. Suggested Mark V model 001 or 008 transformer. Recommended Metal Cabinet LG-1924.

AF-3 ▲▲▲ 300W MOSFET High Power Mono Amp. (7 lbs.)

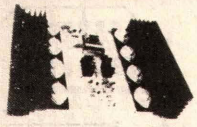

Kit:$ 165.00 Asmb.$ 195.00

Power Output: 300W into 4 ohms RMS. 200W into 8 ohms RMS. Frequency Response: 10HZ-20KHZ. THD: <0.03%. Signal to noise ratio: 91dB. Input Sensitivity & Impedance at 1KHZ, 1V 47K. Load Impedance 4-16 ohms. Power Requirement: ±55 to ±65VDC 8A. Suggested Mark V model 009 Transformer. Capacitor 10,000uf 80-100V model 016 or 019. Recommended Metal Cabinet LG-1925 for each channel.

TA-388 ▲▲▲ Class A FET Dynamic Buffer Stereo Pre-Amp (1 lb.)

Best Pre-Amp

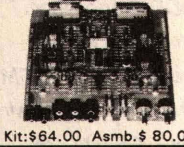

Kit:$64.00 Asmb.$ 80.00

Frequency Response (at rated output): Overall 10HZ-100KHZ +0.5dB-1dB. THD: Overall <0.007% at or below rated output level. Channel Separation (at rated output 1KHZ): Overall better than 70dB. Hum & Noise: Overall better than 90dB. Input Sensitivity (1KHZ for rated output): 300-600mV. Maximum Output Level: Pre-Amp output 1.8V (0.1% THD). Power Requirement: 30V X 2 AC 500mA.

SM-100 ▲▲▲ 150 MHZ 8 Digit Frequency Counter (2 lbs.)

Best Buy

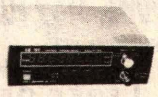

Kit:$ 79.00
Asmb.$ 99.00

Frequency Range: 10HZ-150MHZ. Gate Time: 0.01s, 0.1s, 1s, 10s. Input Sensitivity: KHZ range 10HZ-10MHZ 20mV(min.). MHZ range 1MHZ-120MHZ 20mV(min.), 120MHZ-150MHZ 35mV (min.), 150MHZ-200MHZ 40mV(typical). Time Base: 10MHZ crystal, ±10 ppm. Input Impedance: 1M ohm. Response Time: 0.2s. Resolution: 0.1 HZ: 10s gate time, 1HZ: 1s gate time, 10HZ: 0.1s gate time, 100 HZ: 0.01s gate time. Hold the last input signal. Reset counter to 0. DC 9V power adapter not included.

TY-35 ▲ FM Wireless Microphone

Clearance Sale

Kit:$ 12.50 $ 6.99

This is a low power real FM transmitter. Transmit frequency within 88 to 108 megahertz. Transmit range about 200 ft. It has high sensitivity sound pickup by a capacitance microphone. May be used strictly for series purposes such as remote wireless monitering.

TY-2 ▲ Fluorescent Light Driver

Kit:$ 14.75 Asmb.$ 20.50

This unit drives 6-40W fluorescent light for portable and emergency use. Works from a 7.2-16V DC battery. Includes a "Hi-Efficiency Switching Mode IC Driving Circuit" suitable for use with different lights.

School Project Kits Source ...

SM-36	Dynamic Noise Reduction	▲	$ 26.00
TA-006	6W Mini-Amplifier	▲	9.50
TA-28	Digital Voice Memo	▲▲	9.90
TA-120	36W Class A Power Amp.	▲▲	32.50
TA-201	Mircophone Mixer Mono Amp	▲	20.79
TY-45	20 Bar/Dot Level Display	▲▲	38.25
TR-503	Regulated DC Power Supply	▲	18.75
TA-50	Melody Generator	▲	13.85

SM-720 AC/DC Stereo Pre & Main Power Amp.

Kit:$ 77.00
Asmb.$ 102.00

AC or 12 volt DC power sources for home,portable or mobile operation. 110V or 220V AC power mains. It features dual channel bass & treble tone controls, phone input for magnetic cartridge, tape recorder input & output jacks, an auxiliary input for FM tuner or compact disc player & a microphone input jack for use as a public address or sing-along amplifier. Case & transformer included! (9 lbs.) ▲▲▲

See our catalog for more kits!

Minimum order $ 20. We accept Visa, MasterCard & Money Orders. Checks allow 2 weeks for clearance. We ship by UPS ground inside US (2 lbs min $ 5.00) and ship by US mail outside US. Please call for orders shipping & handling or fax (foreign) orders. PO Orders are welcome from schools. We are not responsible for typographical errors.

CIRCLE 333 ON FREE INFORMATION CARD

DIGITAL STORAGE

OSCILLOSCOPE

WITH SPECTRUM ANALYZER, DVM, FREQ. COUNTER, AND DATA LOGGER.

from **$189.**

O-SCOPE MODULES CONVERT PC'S INTO MULTIPURPOSE TEST AND MEASURING INSTRUMENTS.

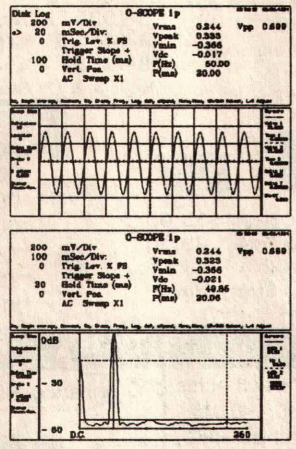

MasterCard VISA

No room on the bench? Too much to carry? Why lug a scope around? Just toss an O-SCOPE into laptop case or tool kit. When you need a Digital Storage Scope, Spectrum Analyzer, Data Logger, or DVM, plug the O-SCOPE into a PC printer port and see it all on the monitor. Continous, delayed, or triggered sweeps can be frozen on the screen, printed out , or saved to disk. Frequency spectrums DC to 500KHz.

Both single and dual channel models accept standard scope probes and works on 286 or faster desktop and laptops.

FEATURES:
- SMALL & PORTABLE
- USES PRINTER PORT
- USES STD. PROBES
- DC TO 500 KHz (OScope II)
- 10v/div. TO 50 mv/div.
- X-Y DISPLAY (OScope II)

OPTIONS:
- PROBE SETS
- EXTERNAL TRIGGER
- DUAL TRACE
- AUTOMOTIVE PROBES
- BATTERY PACK
- SOFT & HARD CASES

MADE IN U.S.A. **SAME DAY SHIPPING**

INCLUDES CABLE, SOFTWARE & MANUALS

O-SCOPE Ip (DC-50KHz, single trace) ♦♦♦♦♦♦♦♦♦♦♦♦♦ $189.
O-SCOPE II (DC-500KHz, dual trace) ♦♦♦♦♦♦♦♦♦♦♦♦♦ $349.
SHIPPING: $7.50 (2ND DAY $11.50)

SEND CREDIT CARD INFO., M.O., or CHECK,OR CALL

1-800-980-9806

Allison Technology Corporation

8343 CARVEL, HOUSTON, TX. 77036 U.S.A.
PHONE: 713-777-0401 FAX: 713-777-4746 BBS: 713-777-4753

http://www.atcweb.com

Motion Control System

$299.95

INCLUDES NEW! (3) Slot Motherboard, Dual Stepper Controller Card, 12VCT 3 Amp Transformer, (2) Stepper Motors, Easy to use I.B.M Software!

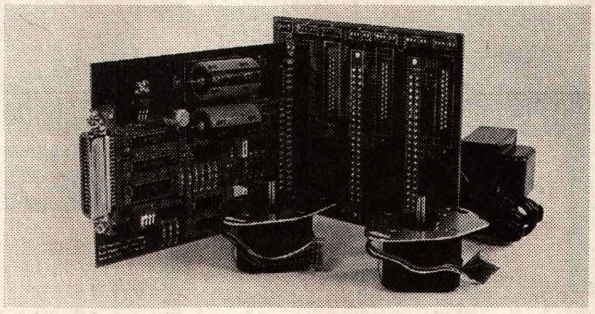

Complete System "Nothing more to Buy!" Unit# SCK-2000

- Design Robots, Plotters, Laser Systems, CNC Machines!
- Drives (2), 100 step, 3.6 degree, 4 Phase Stepping Motors!
- Unipolar 12v motors full step control. Torque is 8oz inches!
- Bi-Directional 8 Bit Read and Write Port!
- Board Addressable, 16 Possible Choices!
- Fits in Standard 19" inch Card Rack!
- Connects to any compatiable I.B.M. LPT Port (1,2,3)..
- With Additional Cards Control 32 Motors on 1 LPT Printer Port!
- Features Include: Variable Speed, Step, Range, Direction, and On\Off Control!
- System is expandable, Add I/O cards, Slave cards, and Amplifier cards.
- **Free** QBasic & Gwbasic Source Code $ 59.95 value! *

Send Check or M.O. to:

CYBERMATION
"Intelligent Controllers"

1943 Sunny Crest Dr., Suite 288, Fullerton. CA 92635

Call Us Today!
Tel (714) 879-2000
Fax (714) 992-2082
Visa\Master\Amex Charge Accepted

Units are in stock and ready to be shipped!
** Add $12.00 S&H: CA residents please add sales tax **

CADPAK for Windows

PROFESSIONAL SCHEMATIC CAPTURE AND PCB SOFTWARE

NEW PRICE FOR WINDOWS!! $199

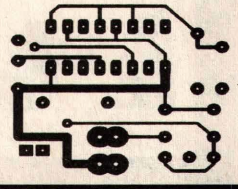

ISIS Schematic

ISIS is an Easy To Use Schematic Drawing Tool.

- Automatic wire routing & dot placement.
- Exports diagrams to other applications.
- Full control of drawing appearance.
- Libraries with thousands of components.

ARES PCB Software

Powerfull CAD Software for PCB Generation

- *Advanced routing*
- *Libraries, including SMT*
- *Includes Gerber Viewing*
- *Fast & Easy to use.*
- Exports diagrams to DTP.
- *30" x 30" board*

LOW PRICES!

STARTS AS LOW AS $199 FOR WINDOWS, $159 FOR DOS

PRICES IS IN US FUNDS - PLEASE INCLUDE $15 S/H

R4 SYSTEMS INC.
1100 GORHAM ST. SUITE 118-332
NEWMARKET ONTARIO
CANADA L3Y 7V1

FREE DEMO
WRITE OR CALL
TODAY

905 898-0665 FAX 905 898-0683 BBS 905 898-0508

Internet r4system@astral.magic.ca

PROFESSIONAL DESOLDERING with the

Lane Norman - Normans Electronics Inc. Atlanta GA 404-451-5057
A cost effective solution to desoldering equipment at less than half the price of most equipment. It's performance is ASTOUNDING.

Harold Smedberg - Smedberg Electronics - Custer MI
The SC7000 has reduced my damage to PC boards by 90%. It has also decreased my desoldering time by 50%. The best priced tool on the market.

Mike Murphy - Service Center -Van Nuys CA 818-785-7805
The single best investment of repair equipment we've made. It outperforms all other desoldering tools we've used. Easier to use and least expensive.

DEN-ON SC7000

Bob Monroe - M.A.R.C. Electronics - Virginia Beach VA 804-468-3932
Best investment we've made. Saves time, especially with multi-sided PCB's. Extremely pleased with warranty. Failed within 6 months and replaced by DEN-ON overnight.

Dick Manning - Dicks Electronics - Hartland WI 414-367-8339
The ease & speed of component removal greatly increases productive time. The SMD kit makes SMD removal a breeze, even for inexperienced Techs.

Dave Hayes - E-H Engineering Ltd - Lincoln NE 402-466-6720
Has been a durable & reliable desoldering unit. Our use has been both lab & field application over the last 2 yrs. with positive results.

Bob Sorrels CET/CSM Polytronics Microcomputer - Shreveport LA
We've used our SC7000 almost every day for about three years with virtually no problems. Just clean it before you turn it off for the day.

George Hefner - Hefner Electronics - Coleridge NE 402-283-4333
Being a one-men service center, I hesitated to spend the money on a desoldering tool , however all that changed when I nearly ruined a $400 computer logic board. It has cut my desoldering time by 50 to 75%.

Steven Gray - Electronic Wizards - Wichita KS 316-686-8324
By far the best desoldering tool we've ever used. Much more suction than other similar types we've tried. No trouble with postage stamp IC's or anything else.

Dennis McMannis - Thorn Services International - Mabelton GA
The SC7000 has decreased my use of wick by 75% and at $25 a roll, it pays for itself within months. My total bench time is reduced by approx. 20%.

Don Cressin - Certified Electronics Serv ice - Ellicott City MD 301-461-8008
We have obtained excellent results with the SC7000 including repairing high density U/V tuners. It is one of the best purchases we have made.

Doug Pettit - LuRay Electronics - LuRay VA 703-743-5400
We found that the SC7000 not only saves money vs. wick, but saves valuable time in troubleshooting. It allows you to be more accurate in removing SMD's.

Paul Horvat - Service Excellence Inc. - Bergenfield NJ 201-387-7776 It has made a almost impossible job (desoldering a 64 pin CPU) a piece of cake.

Tom Mullett - JC Penny TD&S - Wausato se WI 414-259-2486 The SC7000 is a very easy to use, self-contained desoldering tool. We had a 70% increase in production after the purchase of the SC7000. I highly recommend it.

Randy Whitehead - Service West - Salt Lake City UT 801-262-4069
My techs thought it would be a waste. I bought one anyway after a demo. My techs then fought over it. Now we have three. It is the Best desoldering tool we have ever used.

Timothy Kraft - Monikraft, Inc. - Cherry Hill NJ 609-751-3252
We replaced all our existing desoldering stations with the SC7000. Our technicians are very pleased with the improved performance, portability, and reliability over our previous higher priced equipment.

Alan P. Dunasky - Al's TV, VCR, & Computor Service -Cleaveland, OH 216-631-8132 One of my most valuable tools in the shop. I would be lost without it.

Bill Warren CET/CSM - Warrens Audio & Video - Knoxville TN - 423-546-1128 We have been extremely satisfied with the quality and durability of the DEN-ON SC7000 as well as with after the sale support.

Keith Sahs - J & M Electronics - Omaha NE 402-291-7100 It's a must tool for my bench. I can desolder multiple pin IC's quickly and clean. It will even take up large solder amounts on tuner and case grounds.

Ray Wurmnest - Ray's Electronics, Inc.-Bloomington IL 309-829-3238
The SC7000 saves time when changing out parts in the home or in the Service Center — Worth every penny we spent.

Specifications

- Totally Self Contained diaphragm vacuum pump and AC motor for high vacuum suction or reversible hot air blow for SMD removal.
- 100Watt Ceramic heater with zero-crossover switching heater control circuit which prevents spikes and leakage currents.
- Unique patented long lasting filter cartridge design. Solder builds up on easily cleaned baffle, while air flows around the outside of baffle.
- Totally ESD Safe. The housing contains carbon and the tip is at ground potential for complete ESD Protection.
- Maximum vacuum of 600mmHg is attained in 0.2 seconds.
- Temperature adjustable from 300°C - 450°C or 572°F - 842°F

FREE TRIAL
Available on Request

Industrial User Price $550.00
Our Regular Price $445.00

Sale Price $395.00

Limited Supply at Sale Price

Price includes Stand, two extra filter cartridges, tip wrench and tip cleaner.

Visa - M/C - Discover - American Express - Terms to Qualifying Companys
30 Day Money Back Total Satisfaction Guarantee - One Year Parts and Labor Warranty

HOWARD ELECTRONIC INSTRUMENTS INC
6222 N. Oliver Wichita, KS 67220

Toll Free U.S. and Canada
1-800-394-1984

Web Site www.heinc.com
E-Mail Jerihoward@aol.com
International (316) 744-1993
or Fax (316) 744-1994

CIRCLE 323 ON FREE INFORMATION CARD

EARN MORE MONEY!

Be an FCC LICENSED ELECTRONIC TECHNICIAN!

No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radiotelephone License." This valuable license is your professional "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Maritime, Radar, Avionics and more...even start your own business! You don't need a college degree to qualify, but you do need an FCC License.

No Need to Quit Your Job or Go To School

This proven course is easy, fast and low cost! GUARANTEED PASS—You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

Or, Call 1-800-932-4268 Ext. 210

COMMAND PRODUCTIONS
FCC LICENSE TRAINING, Dept. 210
P.O. Box 2824, San Francisco, CA 94126
Please rush FREE details immediately!

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

ONLY COOL-AMP SILVERPLATES ON THE JOB.

From a customer testimonial:

"Ok, your edge connectors don't connect. Or you want to plate your own PC creations, but you don't want to bother with electro-plate solutions. The plating on the socket...has worn off and no longer makes reliable contact...what are you going to do now?

"Give the people at Cool-Amp a call. They have a silver plating compound I have used for the past couple of years that solves all of the above problems and more. This white powder has an infinite shelf life...and is easy to use.

"It will actually put a permanent silver plate on copper, brass or bronze...There are no messy or dangerous chemicals. Application could not be easier. Use a clean rag and a little bit of water and just rub it on a clean surface. In minutes you can permanently silver plate a circuit board or replate a power amp tube or socket.

"It has saved me time, money and my sanity."

Cool amp has even outperformed electroplating in recent tests. It is time-proven since 1944.

COOL-AMP

AND CONDUCTO-LUBE. *THE* SILVER-BASED CONDUCTIVE LUBRICANT.

The upstart, since 1952. Developed for switches, uses continue to expand to all applications needing a conductive lubricant.

Conducto-Lube

ORDER FACTORY DIRECT:
503-624-6426 or FAX 503-624-6436

CIRCLE 228 ON FREE INFORMATION CARD

ATTENTION DEALERS

BUY DIRECT FROM THE WHOLESALER

GET THE BEST PRICES AND SERVICE

ALL UNITS ARE IN STOCK FOR IMMEDIATE SHIPMENT

ADD-ONS

	QTY 5	QTY 10	QTY 20	QTY 50+
STEALTH-1000-P	$55	$48	$45	CALL
TVT-3 GOLD	$48	$41	$38	CALL
TNT-3	$52	$45	$42	CALL
STEALTH 80-P	$61	$54	$49	CALL
M-80	$70	$64	$58	CALL
PIO+	$75	$68	$58	CALL

NEW CONVERTERS

CENTURY CT-3000	$68	$64	$60	CALL
SA-8511	$75	$70	$65	CALL

NOVAVISIONS

NV-5600	$205	$195	$185	CALL
NV-5700	$195	$185	$175	CALL
NV-5800	$195	$185	$175	CALL
NV-5750	$305	$295	$285	CALL

BOSS COMBOS

BOSS 1	$210	$195	$185	CALL
BOSS 2	$210	$195	$185	CALL
BOSS 3	$210	$195	$185	CALL

ZENITHS

ST-1600	$210	$195	$185	CALL

REFURBISHED CONVERTERS

REGAL • SA • PANASONIC *CALL FOR THIS MONTH'S SPECIALS*

1-800-800-0766

KIMTRONICS INC

30 day money back guarantee. All shipping and handling at customers expense. Anyone implying theft of cable service will be denied sale. NO FLORIDA SALES.

KIM-1

CIRCLE 331 ON FREE INFORMATION CARD

SEE US NOW AT http://www.cir.com

CIRCUIT SPECIALISTS INC.

Check Out What We Have To Offer:

Fantastic DMM Offer!!!

Don't let the price fool you. This meter is a digital multimeter designed for engineers and hobbyists. Equipped with 5 functions and 19 ranges. Each test position is quickly and easily selected with a simple turn of the FUNCTION/RANGE selector rotary switch.

Rubber Boot Included

Our Best Offer Ever on a High Quality Full Sized DMM

General

Display: 3-1/2 Digit LCD, 21mm Figure Height with Automatic Polarity
Overrange Indication: 3 Least Significant Digits Blank
Temperature for Guaranteed Accuracy: 23°C±5°C RH<75%
Temperature Ranges:
Operating: 0°C to 40°C (32°F to 104°F)
Storage: -10°C to 50°C (14°F to 122°F)
Power: 9V Alkaline or Carbon-Zinc Battery(NEDA1604)
Low Battery Indication: BAT on Left of LCD Display
Dimensions: 188mm long x 87mm wide x 33mm thick
Net Weight: 400g

DC Voltage (DCV)

Range:	Resolution:	Accuracy:
200mV	100µV	
2000mV	1mV	
20V	10mV	±(1%rdg+2dgts)
200V	100mV	
1000V	1V	

Maximum Allowable Input: 1000V DC or Peak AC.

DC Current (DCA)

Range:	Resolution:	Accuracy:
200µA	100nA	
2000µA	1µA	
20mA	10µA	±(1.2%rdg+2dgts)
200mA	100µA	
10A	10mA	±(1.2%rdg+2dgts)

Overload Protection: mA Input. 2A/250V fuse.

AC Voltage (ACV)

Range:	Resolution:	Accuracy:
200V	100mV	±(1.2%rdg+10dgts)
750V	1V	

Frequency Range: 45Hz-450Hz
Maximum Allowable Input: 750V rms
Response: Average Responding. Calibrated in rms of a Sine Wave.

Resistance (Ω)

Range:	Resolution:	Accuracy:
200Ω	100mΩ	
2000Ω	1Ω	
20KΩ	10Ω	±(1.2%rdg+2dgts)
200KΩ	100Ω	
2000KΩ	1KΩ	
20MΩ	10KΩ	±(2%rdg+10dgts)

Maximum Open Circuit Voltage: 2.8V

Diode Test
Measures forward voltage drop of a semiconductor junction in mV test current of 1.5mA Max.

hFE Test
Measures transistor hFE.

$19.00 any qty

CAT NO	DESCRIPTION	PRICE
9300G	Rugged High Quality DMM with Rubber Boot	$19.00

Switchable Scope Probe Sets

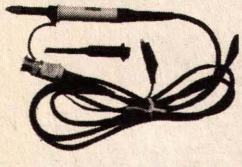

(Selectable X1/Ref/X10) These high quality scope probe sets are for oscilloscopes up to 60MHz (model HP 9060) or 150MHz (model HP9150). Both sets include a handy storage pouch and include an IC test-hook adapter for the probe. The BNC connector rotates to avoid cable tangle or kink. Cable length is 1.4 meters.

CAT NO	DESCRIPTION	PRICE EACH 1	10	100
HP-9060	Scope Probe Set DC~60MHz	$16.49	$14.49	$11.58
HP-9150	Scope Probe Set DC~150MHz	24.95	21.95	18.62

Positive Photo Resist Pre-Sensitized Printed Circuit Boards

These pre-sensitized printed circuit boards are ideal for small production runs. They provide high resolution and excellent line width control. High sensitive positive resist coated on 1oz. copper foil allows you to go direct from your computer plot or art work layout. No need to reverse art.

Single-Sided, 1oz. Copper Foil on Paper Phenolic Substrate

CAT NO	DESCRIPTION	PRICE EACH 1	10	50
PP101	100mm x 150mm/3.91" x 5.91"	$2.55	$1.90	$1.70
PP114	114mm x 185mm/4.6" x 6.6"	2.98	2.45	1.98
PP152	150mm x 250mm/5.91" x 9.84"	5.40	3.98	3.60
PP153	150mm x 300mm/5.91" x 11.81"	6.15	4.48	4.10

Single-Sided, 1oz. Copper Foil on Fiberglass Substrate

CAT NO	DESCRIPTION	PRICE EACH 1	10	50
GS101	100mm x 150mm/3.91" x 5.91"	$ 3.90	$2.98	$2.60
GS114	114mm x 185mm/4.6" x 6.6"	4.80	3.49	3.20
GS152	150mm x 250mm/5.91" x 9.84"	8.69	5.98	5.78
GS153	150mm x 300mm/5.91" x 11.81"	10.20	7.20	6.80

Double-Sided, 1oz. Copper Foil on Fiberglass Substrate

CAT NO	DESCRIPTION	PRICE EACH 1	10	50
GD101	100mm x 150mm/3.91" x 5.91"	$ 5.07	$3.68	$3.38
GD114	114mm x 185mm/4.6" x 6.6"	5.95	4.29	3.99
GD152	150mm x 250mm/5.91" x 9.84"	10.47	7.39	6.98
GD153	150mm x 300mm/5.91" x 11.81"	11.95	8.69	8.30

Etching Chemicals/Ferric Chloride

A dry concentrate that mixes with water to make 1 pint of etchant, enough to etch 400 sq. inches of 1oz board.

CAT NO	DESCRIPTION	PRICE EACH 1	5
ER-3	Makes 1 pint	$3.50	$2.75

Developer This product is used as the developer on our positive photo-resist printed circuit boards. Includes instructions. 50 gram package, mixes with water,

CAT NO	DESCRIPTION	PRICE EACH 1	10	25
POSDEV	Positive Developer	$ .95	$ .80	$ .50

Etching Tank This handy etching system will handle PC boards up to 8"x9", two at a time. Ideal for etching your PCB's! System includes an air pump for etchant agitation, a thermostatically controlled heater for keeping etchant at optimum temperature and a tank that holds 1.35 gallons of etchant. A tight fitting lid is also supplied to prevent evaporation when system is not being used. Typical etching time is reduced to 4 minutes on 1oz. copper board!

REDUCES ETCHING TIME!

CAT NO	DESCRIPTION	PRICE
12-700	Etch Tank System	$37.95

Desoldering Pumps

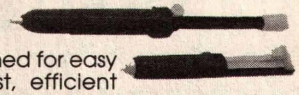

These powerful plastic body desoldering pumps are designed for easy one hand operation for fast, efficient desoldering. Double O-ring piston seals for maximum suction.

CAT NO	DESCRIPTION	PRICE EACH 1	5	10
08-366S	Large Desoldering Pump	$15.89	$13.49	$11.95
08-366E	Regular Desoldering Pump	10.89	8.59	7.39
08-366TIP	Replacement Tip	1.95	1.95	1.95

!!!!!!! SEE OUR ON-LINE CATALOG AT http://www.cir.com !!!!!!!

CIRCLE 321 ON FREE INFORMATION CARD

Electronic Soldering System

Here's the ideal solution when **Temperature Control** is required. Easy to use slide control allows user to set system from 300°F to 840°F. Voltage to iron from control unit is 24V Iron heating power is 48W. Replaceable 5.3mm tip is standard. Replacement irons and tips are available.

AS LOW AS $50.00

CAT NO	DESCRIPTION	PRICE EACH 1	5
SL10	Temp Controlled Soldering Iron	$56.00	$50.00
SL24V	Spare 24V Soldering Iron	10.50	7.50

Electronic Soldering System with LED Display

Deluxe temperature controlled system with LED display for maximum accuracy. Temperature is adjustable from 160°-480°C (320°-900°F). Iron heating power is 48 Watts. Runs on 24V from controller unit. Replacement irons and tips are available. Tip size is 5.3mm.

AS LOW AS $75

CAT NO	DESCRIPTION	PRICE EACH 1	5
SL30	Deluxe Soldering System w/LED	$86.00	$75.00
SL24V	Spare 24V Soldering Iron for SL10 or SL30	10.50	7.50

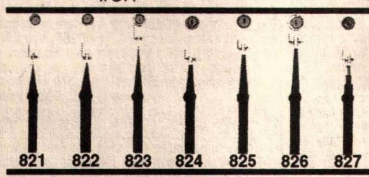

Replacement Tips for SL10/SL30

We now offer a variety of replacement tips for the SL10/SL30 soldering stations.

CAT NO	DESCRIPTION	PRICE EACH 1	5
821	1/32" Pencil Tip	$1.39	$1.19
822	1/32" Pencil Tip	1.39	1.19
823	1/64" Pencil Tip	1.39	1.19
824	1/16" Chisel Tip	1.49	1.29
825	1/8" Chisel Tip	$1.49	$1.29
826	3/64" Chisel Tip	1.49	1.29
827	3/64" Pencil Tip	1.59	1.39

Ball Bearing 12V DC Fans

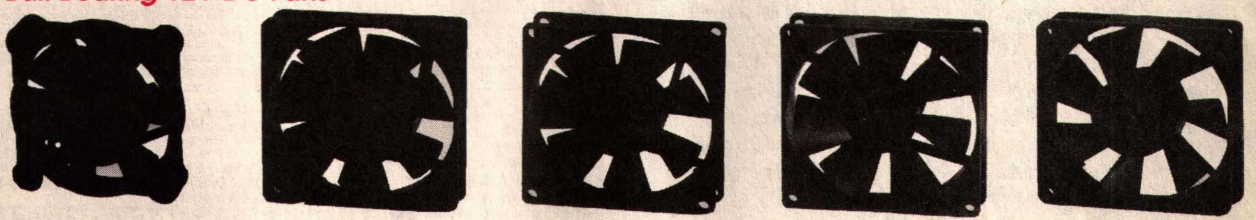

These High Quality Fans feature Ball Bearings and Brushless DC Motors. All of them are designed to meet UL, CSA & VDE Standards. Design these fans into power supplies, computers or other equipment requiring additional air flows for heat removal. These fans are regular Circuit Specialists stock items — they are not surplus.

INDUSTRY BEST PRICING!

CAT NO	PRICE EACH 1	10	25	100
CSD 4010-12	$ 9.88	$ 6.38	$5.48	$4.87
CSD 6025-12	9.38	5.91	5.41	4.71
CSD 8025-12	8.88	5.85	5.19	4.49
CSD 9225-12	8.95	6.14	5.29	4.59
CSD 1225-12	11.45	8.96	7.82	6.85

Specifications

CAT NO	DIMENSIONS (MM)	RATED VOLTAGE (V)	START VOLTAGE (V)	INPUT CURRENT (A)	AIR FLOW (CFM)	STATIC PRESSURE (INCH-H_2O)	SPEED (RPM)	NOISE LEVEL (dB)	WEIGHT (g)
CSD 4010-12	40x40x10mm	12	7	0.06	5.1	0.19	5,500	26	20
CSD 6025-12	60x60x25mm	12	5	0.13	13.7	0.165	4,500	28	65
CSD 8025-12	80x80x25mm	12	5	0.16	37.8	0.177	3,000	31	80
CSD 9225-12	92x92x25mm	12	5	0.32	42	0.18	2,800	37	95
CSD 1225-12	120x120x25mm	12	5	0.35	62	0.180	2,500	42	135

• SOLDER • SOLDER • SOLDER • SOLDER • SOLDER • SOLDER •

We stock high quality 60/40(Sn%/Pb%), .031" and 63/37, .031" diameter. This is prime JIS certified solder that we maintain as a regular stock item (It is not "Left-overs, Rejects or Surplus") and you can buy it from us at a fraction of the price that you are used to.

Tired of Paying Inflated Prices for Solder?

CAT NO	DESCRIPTION	PRICE EACH 1	10	25
RH60-1	1-lb. Spool, .031", 60/40	$ 6.90	$ 5.96	$ 5.30
RH63-1	1-lb. Spool, .031", 63/37	6.95	6.10	5.41
RH60-4	4.4-lb. Spool, .031", 60/40	24.00	21.90	17.92
RH60-TUBE	6-oz. Tube, .031", 60/40	.99	.89	.79

CCD Camera - IR Responsive

As Low As $109!!

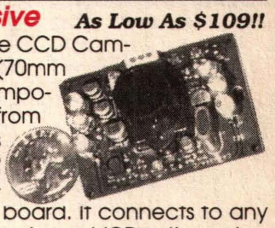

This black and white monochrome CCD Camera is totally contained on a PCB (70mm x 46mm). The lens is the tallest component on the board (27mm high from the back of the PCB) and it works with light as low as 0.1 lux. It is IR Responsive for use in total darkness. It comes with six IR LED's on board. It connects to any standard monitor, AUX or video input on a VCR or through a video modulator to a TV. Works with a REGULATED 12V power supply (11V-13V). Hooks up by connectiong three wires: red to 12V, black to ground (power & video) and brown to video signal output.

CAT NO	DESCRIPTION	PRICE EACH 1	5
CA-H34A	PCB Mounted IRCCD Camera	$125.00	$109.00

!!!!!!! SEE OUR ON-LINE CATALOG AT http://www.cir.com !!!!!!!

CIRCUIT SPECIALISTS, INC.

SINCE 1971

800-811-5203
602-464-2485
602-464-5824(FAX)

WE ACCEPT: VISA MasterCard DISCOVER

RECEIVE OUR LATEST 132 PAGE CATALOG!

It's chock full of all types of electronic equipment and supplies. We've got I.C.'s. capacitors, resistors, pots, inductors, test equipment, breadboarding supplies, PC supplies, industrial computers, data acquisition products, personal computers and computer parts, plus much, much more. FAX us your name and address or call **800-811-5203, ext. 5,** to leave a message on our catalog request line.

CIRCLE 321 ON FREE INFORMATION CARD

The **Smallest**, Most **Secure**, Best **Range**, **3 Channel** Remote Receiver.

Security Receiver for... Home Automation, Garage Doors, Home Security Add On, Auto Convenience Package (Door Locks, Trunk Pop, Windows-Up/Down, Car Start), N/O or N/C Contacts.

Security - 70 billion hopping codes with anti-scan processing. Unbreachable security; never repeats the same code twice. Double EEPROM memory.
Incredible Range - No cross talk or blockage. Range up to 1000 feet.
3 Channel - Our universal receiver controls up to 3 items with only one receiver (optional relay needed). Push both buttons together for third channel output.
Interfaces with most home and auto security systems for easy remote integration.
Comes with (1) three channel receiver, (1) long range three channel remote, (1) universal 120 VAC transformer.

ALL FOR ONLY $99.95 + shipping & sales tax.

Street Smart Security
619) 462-1167
7147 University Avenue • La Mesa, CA 91941
Send, Fax or Call Order In - Use Credit Card or Check. Fax (619) 462-0652

Low Cost CAD Software
Now In Windows™95

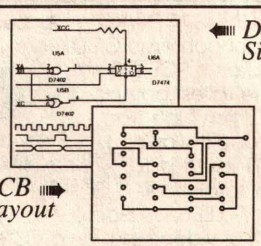

Design & Simulation

PCB Layout

- Easy to use schematic entry program **(SuperCAD)** for circuit diagrams, only $149. Includes netlisting, bill of materials, extensive parts libraries.
- Digital simulator **(SuperSIM)** allows you to check logic circuitry quickly before actually wiring it up. Works directly within SuperCAD and displays results in "logic analyzer" display window. Starting at $149 this is the lowest cost simulator on the market. Library parts include TTL, and CMOS devices.
- Analog simulator **(mentalSPICE)** for $149. Allows AC, DC and transient circuit analysis. Includes models of transistors, discretes, and op amps.
- Circuit board artwork editor and autorouter program **(SuperPCB)**, starting at $149. Produce high quality artwork directly on dot matrix or laser printers. You can do boards up to 16 layers including surface mount. Includes Gerber and Excellon file output. Autorouter accepts netlists and placement data directly from the SuperCAD schematic editor.
- **New!**--Complete electronic design package **(SuperMAX)** including schematic editor, analog and digital circuit simulation, and printed circuit board layout with autorouter for only $549!.

Write or call for free demo disks:
MENTAL AUTOMATION, INC.
5415 - 136th Place S.E.
Bellevue, WA 98006
(206) 641-2141
Internet: http://www.mentala.com

TOP SECRET

CONSUMERTRONICS
2011 Crescent Dr., P.O. Drawer 537
Alamogordo, NM 88310
--- Please order by Mail or Fax only ---
Fax: (505)434-0234, 439-1776 (orders only; if you get voice, enter *#11#11 any time), 24-hr
Customer Service & Tech Support: (505)439-8551 (8AM-6PM MST, Mon-Sat) Relates directly to your order or prospective order.
Web Site: Visit our popular site (tell your friends) at: http://users.aol.com/wizguru/hi-tech.html
10% Off on orders $100+ 15% Off over $200+ Add $5 total S/H (US, Canada). All items in stock. Postal M.O. is fastest. VISA, MC CC OK. COD ($49-$999), add $8. New Catalog (200+ offers) $2 w/ order, $5 w/o (no CC), $24/foreign. NO dealers.
Since 1971. As seen on CBS *60 Minutes,* Forbes, etc. By John Williams - former Lockheed Senior Engineer, NMSU CS Professor, DOD Electronic Weapons Engineer, NIH Health Physicist. Sold for educational purposes only.
Wanted: 5 MAC IIfx, PC486 (or better), peripherals, new surplus electronic parts, test equipment - buy, trade. ***All software supports all IBM-PC systems**

Off-the-Shelf HARDWARE

Van Eck Systems★Data Card Reader/Writers★ATM3★Security/Surveillance★RF/EM/μWave/Radar/Ultrasonic/IR/Light/Sound Detectors/Receivers/Xmitters/Jammers/Blasters★Neurophone/Rife/Hieronymus/Resonant Crystal Radionics★ EM Lab/Weaponry/Countermeasures★ESS Infinity Devices★Voice Disguisers★Lineman's Hand-sets★Bug/Tap Detector/Blaster★Phone Color Boxes★DTMF Decoders★Carjack/Kidnap Foiler★Bumper Beeper/Child Finder★Panic Button★Shriek Module★TENS★Subliminal Mixer/Amp (Ultrasound & Infrasound)★Electronic Dowsers★Hidden Presence Detectors★Hearing Assistor★Vortex Generator★6th Sense Communicator★Noise Cancel. System★Levitator - many more! See our New Catalog!

SPECIAL PROJECTS

We design/build/obtain/repair/modify/maintain/consult on any device/system/process/project - electronic/computer/mechanical/optical (ex: phone/auto/security/radionic/lab/energy/HV/EM/RF/radar/ultrasonic/IR/UV/commo/consumer) for business/personal/invention needs. Describe & include $30 pre-engineering fee (no obligation). Time & cost estimates 7-10 days. Confidentiality guaranteed.

CELLPHONE MODS

See our **Catalog** for our infamous cellphone modification guide **($69)** - detailed, comprehensive, covers all makes - 10 times more info than competitor's "guide"). (Do **Special Projects** above to get up-to-date hardware/software).
Free Data Search: As a special **FREE** service to our C&CP customers, we will perform one **FREE** search of our massive cellphone database if requested within 30 days of your purchase of C&CP. Data now on cellphones is so great, we can fit in C&CP only that in greatest demand. Search results not guaranteed. Request by mail (don't fax); include a #10 SASE.

PAGER (Beeper) MANUAL

Describes in detail how Pagers work, different types and uses, frequencies, advantages over and uses with cellphones, and tips and tricks. And how Pagers are hacked and countermeasures. Includes the plans for your own **Personal Pocket Paging System** (transmitter and receiver). **$49.**

HACKING FAX MACHINES

Describes in detail how Fax machines are hacked and countermeasures (hacking Faxes is much more complex than just connecting a third Fax to the phone line). Includes Fax protocols, commo parameters, and 2:1 and 4:1 compression. And insights into designing Fax interception devices and modifying existing Faxes into Stealth Faxes do the job. **$49.**

VOICE MAIL HACKING

How **Voice Mail Box (VMB)** systems are used and the specific ways they are hacked. Includes **ASPEN, MESSAGE CENTER, BIX, GENESIS, EZ, SYDNEY, PHONE MAIL, AUDIX, CINDY, CENTAGRAM, SPERRY LINK, RSVP,** etc. Absolutely required for all users, sysops and security personnel! **$29.**

PBX HACKING

1,000s of PBXs are hacked to the tune of $ Billions/yr! While **"VOICE MAIL HACKING"** details how VMSs are hacked for "phun" and profit - including VMS methods for hacking PBXs themselves - **"PBX HACKING"** addresses ALL issues relating to PBX hacking, including countermeasures! Can your business or agency afford a $90,000 phone fraud loss (the average loss due to hacked PBXs)? As described in **Forbes Magazine. $29**

PHREAKING CALLER ID & ANI

Details on how they work and dozens of effective ways of defeating **Caller ID, ANI, *69, *57,** and **Call Blocking** and ***67.** Also describes **Caller ID, Orange, Beige, Cheese** and **CF Boxes, ESS, SS7, E-911,** various **CLASS** services, **CNA, NON PUB DA, CAMA, DNR, 800-ECR, Diverters, Extenders, Centrex** - more. **$29.**

COMPUTER PHREAKING

Describes in detail how computers penetrate each other, and how **VIRUSES, TROJAN HORSES, WORMS,** etc are implemented. Dozens of computer crime and abuse methods and countermeasures. Includes disk filled with hacker text files and utilities, and the legendary **FLUSHOT+** protection system **(Ed. Choice, PC Magazine).** BBS advice, password defeats, glossary - much more! **Manual + Disks* $39.**

Beyond PHONE COLOR BOXES

Dozens phone color boxes described - many circuits. Plus **Call Forwarding, Conferencing, Phreak History, Glossary, Diverters, Extenders, Loops, REMOBS, Bridging Heads & Cans, Optocom, 3rd Party** and many other non-box methods - more. **$39.**

HACKING ANSWERING MACHINES

How answering machines are hacked to listen to - even erase - messages, and to convert them into mini-VMBs. And countermeasures - **protect yourself from snoops, stalkers, burglars and pranksters! $29.**

CREDIT CARD SCAMS

Cardholders, merchants, banks suffer $ Billions in losses annually because of credit card fraud. Describes every known means of credit card fraud and scams. **Protect yourself! $29.**

AUTOMATIC TELLER MACHINES

ATM crimes, abuses, vulnerabilities and defeats exposed! 100+ methods detailed, include: Physical, Reg. E, cipher, PIN compromise, card counterfeiting, magnetic stripe, false front, TEMPEST, Van Eck, tapping, spoofing, inside job, super-cool, vibration, pulse, high voltage - others. Case histories, law, countermeasures, detailed security checklist, labeled internal photos, figures. ATMs contain up to $250,000 in cash! Recent $350,000 ATM crime spree still unsolved! **$39.**

CONS, SCAMS & SWINDLES

Cons & scams and related swindles fleece Americans of $100+ Billion per year! The most comprehensive survival manual on cons & scams of all kinds - from the classic to hi-tech. Details on 100s and many variations. And countermeasures. **Protect yourself! $39.**

INTERNET CONS & SCAMS

Internet cons, scams and related frauds now rake in $2+Billion annually! Most are done anonymously and with little fear of prosecution (difficult to prove and to find the perpetrators). Described in detail, includes countermeasures. **$29.**

Beyond VAN ECK PHREAKING

Eavesdropping on TV and computer video signals using an ordinary TV described in detail. Includes security industry reports. Range up to 1 KM. Plans include both the **Consumertronics** and the original **Top Secret Van Eck designs! $29.**

The HACKER FILES

Compilation of 100s of the best articles written (in ASCII) by top hackers & phreakers. Covers every major topic in hackerdom! **3 HD Disks* $59.**

STOPPING POWER METERS

As reported on **CBS "60 Minutes": How certain devices can slow down - even stop - watthour meters - while loads draw full power!** Device simply plugs into one outlet and normal loads into other outlets. Also describes meter creep, overload droop, etc. Plans **$29.**
I.Q. MANUAL: External magnetic ways (applied to the meter itself) to slow down and stop watthour meters while drawing full loads. Plans. **$25.** **KW-HR METERS:** How watthour meters work, calibration, error modes (many), ANSI Standards, etc. **Demand** and **Polyphase Meters.** Experimental results to slow and stop meters by others. **$25. Any 2, $47. All 3, $69.**

UNDER ATTACK!

Electromagnetic Interference and **Electronic Weapon Attacks** cause: Cancer, birth defects, and profound psychological, neurological, cardiovascular and immune system disorders! Destructive to people, animals, plants, equipment! Includes **ACTUAL CASES OF EM ATTACKS** (we investigated)! Includes how to verify and pinpoint EMI and electronic attack sources, and effective countermeasures. **$29.** **EM BRAINBLASTER:** Tutorial and plans for powerful **ELECTROMAGNETIC WEAPONS** and **LAB DEVICES.** Optimum circuits, freqs, waveforms, duty cycles, intensities. Thorough. **$29.** Both **$49.**

MIND CONTROL

Concern and fear increases over EM and ultrasonic mind (and body) control technologies - especially implants! Unfortunately, there is much more misinformation and disinformation published than facts. Some victims are controlled and exploited by arm-chair "experts" and so-called victims' assistance groups - **one even demands the policing of the Internet to prevent and remove postings it doesn't approve of! $39.** Visit our site at: http://users.aol.com/wizguru/mindcontrol.html

RADIONICS MANUAL

Exciting electrical, electronic, electromagnetic therapeutic, diagnostic & preventive devices (mostly experimental). History, descriptions, plans (dozens), availabilities of **Radionics Devices** from early to modern. While drugs cost $100s, electricity costs pennies! **$29.** **HEAL THYSELF:** Plans for 3 major electronic therapeutic devices of types approved by **FDA. $19.** Both **$39.**

HIGH VOLTAGE DEVICES

HV devices plans: **Stun Gun, Taser, Prod, Cane, Blaster, Flasher, Zapper, Audio/RF/Radar Jammer, Fence Charger, Plasma & Van de Graaff Gens., Jacob's Ladder, Geiger Counter, Ozone Gen., Fish Stunner, Plant Stim., Kirlian,** more! All plans for only **$29.**

STEALTH TECHNOLOGY

Police radar is fascinating! It also has error rates of 10-20%! Every known error mode - stealth method and material used to minimize radar reflections - tactic and strategy to fight unjust radar tickets (that cost you $100s in insurance and risk cancellation) - methods to detect and jam signals - fully described! **$29.**

SECRET & SURVIVAL RADIO

Optimum survival and security radio equipment, methods, freq allocations and voice/data scrambling/encoding. Includes small receivers/transmitters, telemetry, antenna optimizations, remote monitoring and control, security, surveillance, and ultrasonic, fiber-optic and infrared commo. 70+ circuit plans, tables. **$29.**

CRYPTANALYSIS TECHNIQUES

Five powerful menu-driven crypto programs (in .COM and .BAS source code) to analyze, decrypt "secure" ciphertexts. Worked-out examples. Recommended by prestigious **"Computers & Security." Manual+Disk* $29.**

CIRCLE 226 ON FREE INFORMATION CARD

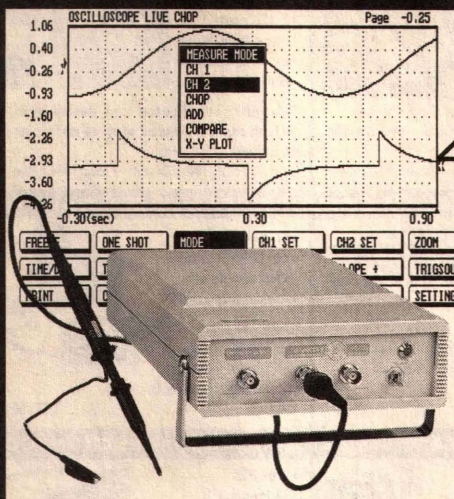

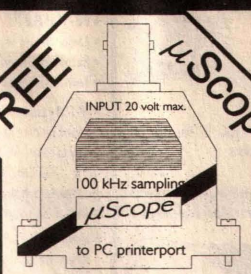

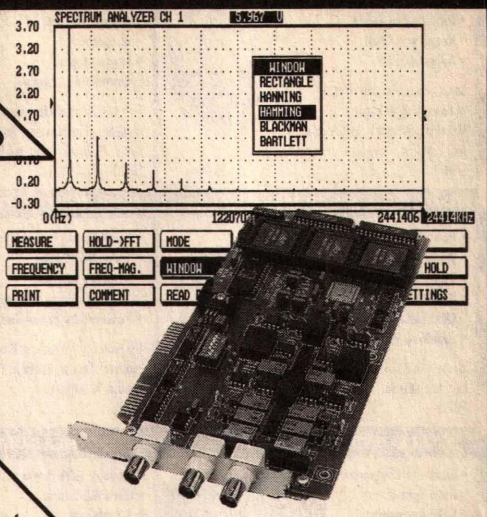

You get a free *µScope*
when you buy a TP508 or a HS508
until september 1st 1996

resolution 8 bits
sampling speed 100 kSamples/sec
input range 2.5V, 5V, 10V and 20V
connects to PC parallel printer port

Software for the PC-based instruments

contains an Oscilloscope, a Spectrum analyzer, a Voltmeter, and a Transient recorder. All instruments are controlled in the same intuitive way and provide for saving and recalling waveforms and settings, cursor measurements, hard-copy on matrix / laser printer and online help. Minimum requirements: a 80286-based PC with 2MByte and running MSDOS 3.3 or higher.

Call toll-free 1-800-626-6929 for a free demo disk and our catalog

Easy installation: just plug in and measure

TiePieSCOPE HS508

- *interface PC parallel printer port*
- *sampling speed 50 Msamples/sec*
- *resolution 8 bits*
- *input range 50 mV/div - 20V/div*
- *record length 32KByte/channel*
- *price US$1054 incl. software, user manual and 2 probes (1:1/1:10 switchable)*

TP508

- *interface PC-XT/AT ISA slot*
- *sampling speed 50 Msamples/sec*
- *resolution 8 bits*
- *input range 5 mV/div - 20 V/div*
- *record length 32 KByte/channel*
- *price US$1098 incl. software, user manual and 2 probes (1:1/1:10 switchable)*

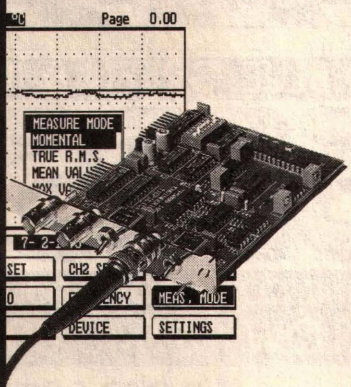

Digital Voltmeter
CHANNEL 1 input range: 80 mV AC
CHANNEL 2 input range: 30.0 V AC
1.3254
PASS
MEASURING : TRUE RMS (V)
DISPLAY : CH1 (REL. ON!)
MEASURING : TRUE RMS (V)
DISPLAY : X(COMP
SETTINGS

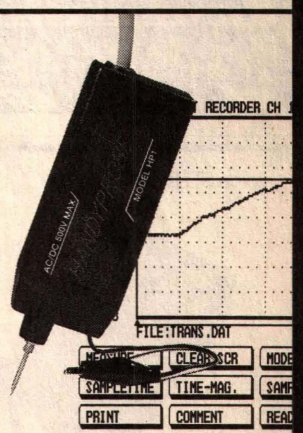

TP5008

- *interface PC-XT-AT ISA slot*
- *sampling speed 200ksamples/sec*
- *resolution 8 bits*
- *input range 125 mV/div - 5 V/div*
- *programmable analog output channel*
- *price US$307 incl. software, user manual*

HANDYSCOPE

- *interface PC parallel printer port*
- *sampling speed 100ksamples/sec*
- *resolution 12 bits*
- *input range 125 mV/div - 5 V/div*
- *no external power required*
- *price US$499 incl. software, user manual and 2 probes (1:1/1:10 switchable)*

HANDYPROBE

- *interface PC parallel printer port*
- *sampling speed 100ksamples/sec*
- *resolution 8 bits*
- *input range 125 mV/div - 100 V/div*
- *no external power required*
- *price US$169 incl. software, user manual*

CONWAY Engineering, Inc.
8393 Capwell Drive, Oakland, California USA 94621-2113
Tel: (510) 568-4028 Fax: (510) 568-1397
BBS: (510) 568-6533 Internet: http://www.crl.com/~conway/

Call toll-free 1-800-626-6929 for a FREE demo disk and a catalog of all our instrments!

TiePie engineering

CIRCLE 320 ON FREE INFORMATION CARD

SOLAR POWERED HAT FAN

- Solar Powered
- Durable Fan in bill
- Keeps you Cool!
- Adjustable Fit

Keeps you cool on hot days, while working or playing. Makes a great gift.! Specify color: red, light blue, navy blue, white, and yellow.

SPHF-1 ..... $15.00ea.

STEPPER MOTOR CONTROLLER KIT

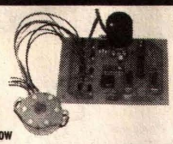

- Adjust speed
- Change direction of rotation.
- Single step or Continuous stepping

Easy to assemble! LED's show sequence of motor steps. Runs on 12VDC. Includes Stepper Motor, PC Board, Parts, and Instructions.

SMK-1 ..... $25.00

CAMCORDER VIDEO TAPE

- HI-8
- P6-120 HMPX
- Major Brand Name
- Excellent Condition
- Jewel Box Included

HI-8 120 minute video cassette tape (used). They were recorded on once and played a few times. Then bulk erased. Ready to record on again.

CCT-1 . .$3.00ea/10+ 2.80ea/50+ 2.65ea/100+ 2.50ea

SUPER VHS VIDEO TAPES (USED)

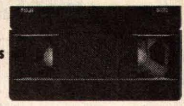

- Super VHS Tapes
- T-120Minute
- Major Brand Names
- Excellent Condition
- Great Price!

These tapes were used for a brief period, then bulk erased. The record tabs have broken out, so you will need to cover the notch with a piece of tape.

S-VHS . .$3.00ea/10+ 2.80ea/50+ 2.65ea/100+ 2.50ea

MINIATURE FM TRANSMITTER KIT

- Powerful 2 stage Audio Amplifier
- Tunes 100-108Mhz
- Requires 9V Battery (Not Included)
- Sensitive mike picks up Whispers

Works with any FM radio or broadcast receiver. Easy to assemble.

FM-32 ..... $10.95

MINI PHONE TRANSMITTER KIT

- Small Phone Transmitter
- Tunes 90-95Mhz
- Attaches to phone line any where in home.
- Powered by phone line.

Use with any FM radio or broadcast receiver. Easy to assemble. Just lift the handset to activate.

FM-16 ..... $9.95

AMAZING EMERGENCY FLASHLIGHT

- Hand Powered!
- Never needs batteries
- Operates even underwater!

Never be caught without a flashlight again due to dead batteries. Dynamo produces power to provide light. Great for the car, boat, and house.

EL-1 ..... $9.95

DC MOTOR SPEED CONTROLLER KIT

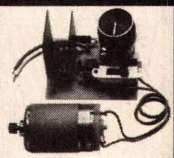

- Control speed
- Clockwise or Counter Clockwise Rotation
- Runs on 6 to 12VDC

Easy to build. Control speed and direction of small DC motors. Includes PC Board, Motor, Parts, and Instructions.

MSC-1 ..... $15.00

VIDEO CLARIFIER

- Eliminate Copyguards!
- Auto Sync Boost
- Fully Automatic
- State-of-the Art Circuitry

Allows for flawless viewing of all prerecorded tapes. Restores tapes to broadcast quality. Eliminates annoying interference. Compatible with all VCR's and T.V.'s. Operates on 4 AA batteries. (Not Included)

VC-3 ..... $49.95

B/W PINHOLE CAMERA WITH AUDIO

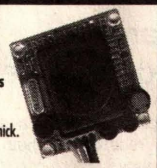

- Pinhole with Audio
- Ultra Miniature!
- 3.7mm lens
- Prewired with RCA plugs

Ultra mini camera measures 1 3/16" x 1 3/16" x 9/16" thick. 420 Horizontal lines. .1 Lux Runs on 9-12VDC@100ma

PHC-1 ..... $159.95

MINI B/W CAMERA W/STAND

- B/W CCD CAMERA
- Prewired with RCA Plugs
- Metal Housing • Stand w/Hardware
- Adapter Included

Measures 3 7/8" Long (Including Lens) x 1 1/4"W x 1"H Small enough to fit in your hand! Has 0.2 Lux, 400 TV lines, operates on 12VDC@1.5W. Includes stand & power adapter, & prewired with RCA plugs.

CCD-2 ..... $159.95

ULTRA PLIER 14 FUNCTION TOOL

- Ultra Plier
- 14 Functions
- Ultimate Handy Tool!
- Fits in the Palm of your Hand!

You have every type tool in one implement. Includes Pry Bar, Wire Cutter, 2 Wire Strippers, Phillips Screwdriver, 2 Flathead Screwdriver, File, Small Blade and Bottle Opener. Comes with Nylon Pouch.

Plier $12.95

CALL TOLL FREE

1-800-526-3717

SATISFACTION GUARANTEED

645 Temple 7E ▲ Long Beach ▲ California 90814

▲ (310) 434-5641 ▲ FAX (310) 434-9142 ▲

1. California residents must include sales tax.
2. Visa, MC, & money orders accepted
3. Quanties limited – prices subject to change.
4. Shipping $5.^{00}$ & up.

Black Feather ELECTRONICS

CIRCLE 311 ON FREE INFORMATION CARD

price SET: US$ 299.00

new! new! new! new!

VIDEO - LINK

2,4 GHz

wireless

VIDEO / AUDIO transmission

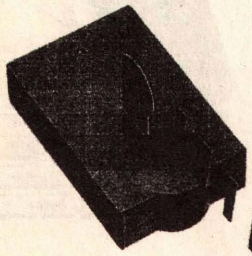

up to 1/4 mile open area

power supply not incl.
A/V cable incl.

works with all TV-SYSTEMS NTSC/SECAM/PAL

techn. data:
RF power output: 10mW
DC power : 11.....16V/DC-0.5A
dimension: 130x80x35mm
AUDIO: in / out
VIDEO: in / out
frequency: 2.4 GHz / pll stab.
modulation : A/V FM

shipping charge air parcel US$ 45.00

PICOTRONIC
Zollamtstr.48, 67663 Kaiserslautern GERMANY
FAX++49-631-29579 BBS++ 49-631-21048
phone 0631 29187

WE SELL RED, BLUE-GREEN & IR

LASERS

HUNDREDS OF UNITS TO CHOOSE FROM!

PRICES AS LOW AS $40.00!

- Experiments
- Laser Light Shows
- Cutting & Burning
- Communications

We also carry books and plans about LASERS.

CALL FOR FREE CATALOG!

TEL (909) 278-0563

FAX (909) 278-4887

MWK INDUSTRIES

1269 W. Pomona, Corona, California 91720

See our catalog on the internet.

HTTP://WWW.PWEB.COM/MWK/MAIN.HTM

EMAIL: MKENNY1989@AOL.COM

Learn About Computers Hands-On With This Pentium Computer Kit

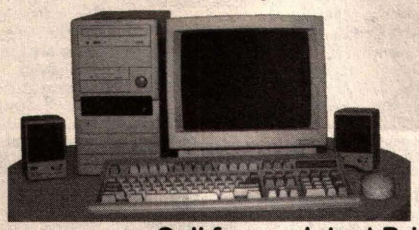

ONLY $1399

Call for our latest Pricing

Kit Includes all the parts, tools and instructions you need to build a Pentium multimedia computer in your own home. The manual includes over 100 pages of illustrations, instructions and explanations written especially for this kit.

Call Innova Technologies now to order!

1-800-290-9066

A free brochure is also available.

IN STOCK

service \'sər - vəs\ *noun*
- The occupation of performing work or functions that benefit and contribute to the welfare of others.
syn. see **Mouser Electronics**

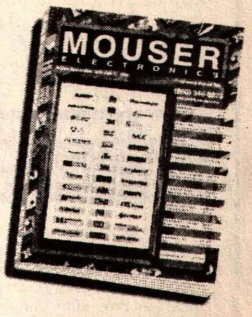

Call for your ***FREE*** *324 page catalog TODAY!*

65,280 Products
126 Manufacturers
All Orders Ship Same Day

- Passive Components
- Semiconductors
- Electromechanical
- Connectors/Cable
- Surface Mount and Through Hole

MOUSER® ELECTRONICS

800-992-9943
FAX: 817-483-0931
http://www.mouser.com
sales@mouser.com

958 North Main St., Mansfield, TX 76063

CIRCLE 306 ON FREE INFORMATION CARD

CAPITAL ELECTRONICS INC.

"QUALITY IS OUR CAPITAL CONCERN."

Complete On Site Electrical Engineering Lab

- Product Engineering
- Firmware Development
- Reverse Engineering
- RF Circuit Design & Manufacturing
- Micro Controller & EPROM Hardware & Software Development

From Auto-Routing to CNC Routing to Electronic Assemblies. . .
Capital Electronics is Your Best Route For Printed Circuit Boards.

Design/Layout
- CAD Layout Services
- Compatible With Almost All CAD Systems
- From Schematics or Sample PCB's
- Photoplotting Services
- 28,800 Baude Modem

Printed Circuit Boards
- Single & Double Sided
- Multi-Layer & Flexible PCB's
- From Quick Turn Prototypes to Scheduled Production Runs
- Fine Lines, SMT
- Electrical Testing
- Precious Metal Plating

Assembly Services
- Fast Turn Board Stuffing
- Wire Harnesses
- Wave Soldering
- Acquisition of Parts
- Final Testing
- Turnkey Services
- Custom Enclosures

For Quick & Competitive Pricing or More Information, Please Call Us Today!
852 Foster Avenue • Bensenville, IL 60106
(708) 350-9510
Fax (708) 350-9760 • Modem (708) 350-9761

Internet Access:
For Automated Info Response: INFO@capital-elec.com
E-Mail: Quote@capital-elec.com
Web Access: http://www.capital-elec.com

CIRCLE 332 ON FREE INFORMATION CARD

Learn MICROCONTROLLERS EMBEDDED SYSTEMS and PROGRAMMING...

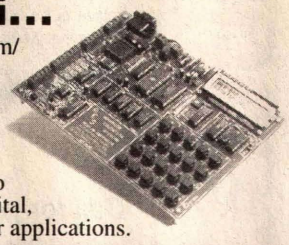

...with the AES learning system/ embedded control system. Extensive manuals guide you through your development project. All programming and hardware details explained. Complete schematics. Learn to program the LCD, keypad digital, analog, and serial I/O. for your applications.

THREE MODELS AVAILABLE. Choose from an Intel 8051, Intel 8088, or Motorola 68HC11 based system. All models come with:

•32K Byte ROM, 32K Byte RAM • 2 by 16 Liquid Crystal Display • 4 by 5 Keypad • Digital, Analog, and Serial I/O • Interrupts,timers, chip-selects • 26 pin expansion connector • Built-in Logic Probe • Power Supply (can also be battery operated) • Powerful ROM MONITOR to help you program • Connects to your PC for programming or data logging (cable included) • Assembly,BASIC, and C programming(varies with model) • Program disks with Cross Assembler and many, well documented, program examples • User's Manuals: cover all details(over 500 pages) • Completely assembled and ready to use • Source code for all drivers and MONITOR • Optional Text Book

Everything you need. From $279.
Money Back Guarantee

Call for Free Info Pack, or see WEB at http://www.aesmicro.com
714-550-8094,FAX 714-550-9941

AES Advanced Educational Systems

Call 1-800 -730-3232

AES 970 W. 17TH STREET, SANTA ANA, CA 92706, USA

CONTROL
RELAYS • LIGHTS • MOTORS

MEASURE
TEMPERATURE • PRESSURE • LIGHT LEVELS • HUMIDITY

INPUT
SWITCH POSITIONS • THERMOSTATS • LIQUID LEVELS

MODEL 30 ..... $79

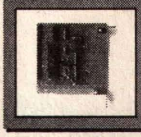

- PLUGS INTO PC BUS
- 24 LINES DIGITAL I/O
- 8 CHANNEL- 8 BIT A/D/ IN
- 12 BIT COUNTER
- UP TO 14K SMP/SEC

MODEL 45 ..... $189

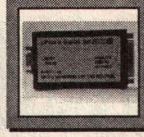

- RS-232 INTERFACE
- 8 DIGITAL I/O
- 8 ANALOG INPUTS
- 2 ANALOG OUTPUTS
- 2 COUNTERS-24 BIT

MODEL 100 ..... $279

- 12 BIT 100 KHZ A/D
- 4 ANALOG OUTPUTS
- 3 TIMER COUNTERS
- 24 DIGITAL I/O

MODEL 60 ..... $179

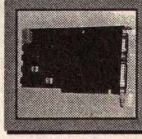

- 8 2-AMP RELAYS
- 16 DIGITAL I/O
- 1 8-BIT ANALOG INPUT

MODEL 40 ..... $99

- RS-232 INTERFACE
- 20 LINES DIGITAL I/O
- 8 ANALOG INPUTS
- PWM OUTPUT
- OPTIONAL 12 BIT A/D

MODEL 70 ..... $239

- RS-232 INTERFACE
- 16 BIT A/D
- 5.5 DIGIT
- UP TO 60 SMP/SEC

NEED A CUSTOM PCB? TRY US.

PRAIRIE DIGITAL, INC.

PHONE 608-643-8599 • FAX 608-643-6754

546 SEVENTEENTH STREET • PRAIRIE DU SAC, WISCONSIN 53578

CIRCLE 326 ON FREE INFORMATION CARD

FREE

Monthly Special! Free window clip antenna with these radios!

TRIDENT | Bearcat

TR2400 $499
100KHz to 2.06 GHz

BC230 $229
Turbo Scan with 800MHz

BC3000 $369
25MHz to 1.3 GHz

Trident Spectrum Analyzer

1-1300MHz in two bands with a Span that's variable from 500 MHz to 10 MHz. 80db on Screen Range, marker generator, 200K/10K selectable bandwidth, -117dBm Sensitivity, outputs to any x/y o'scope.
$699.00

These are a few of our products and price values. For more information dial toll free or see our web site, or get instant specs & info. from our fax back service.

Toll Free, 24 Hours! For orders. 317 543 9771 for tech support. For Fax Facts Instant catalog sheet service, dial 317 849 8683. ACECOMMS@aol.com Email

ACE COMMUNICATIONS

Web: www.aceomms.com. Mastercard, Visa, Checks, Approved P.O.'s & COD (add $5.50) & AMEX, Discover. Prices, specs and availability subject to change. Ground shipping and handling charge $7.95

10707 E. 106th St. Fishers, IN 46038

CIRCLE 212 ON FREE INFORMATION CARD

NOW MAKE AN EXTRA $600 PART TIME WEEKENDS -- UP TO $2,000 A WEEK FULL TIME IN *Explosive* SATELLITE DISH TV/ELECTRONICS FIELD!

Hottest Career Opportunity Since Invention of the VCR!

See How Fast The Money Rolls In!

Part time: *Here's what you can earn over a typical weekend:*

Install 2 Satellite dish systems at $200	= $400
Repair 4 TV's at $50 each	= $200
Total Weekend Income	**= $600**

Full time: *Working just five days a week you could easily earn:*

Install 5 Satellite dish systems at $200	= $1,000
Repair 10 TV's, average $50 each	= $500
Clean and adjust 10 CD players, average $35 each	= $350
Service 2 Home entertainment centers at $75	= $150
Total Weekly Income	**= $2,000**

In addition you can make big extra profits on other supplies you furnish!

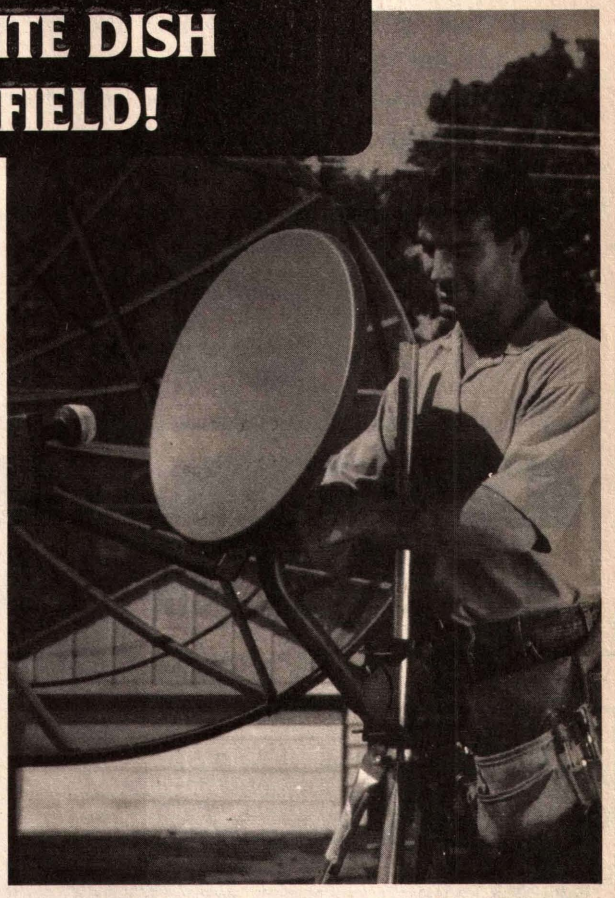

Get in *THE FAST LANE* on the NEW "INFORMATION SUPERHIGHWAY" Everyone's Talking About!

It's exciting! It's gigantic! The technology of tomorrow is here today! You've been reading and hearing about the amazing Information Superhighway. It's so new that few technicians are equipped to service this fast emerging field! Foley-Belsaw gives you Satellite dish technology (including new mini-dish) along with the electronic expertise you need to make big money servicing TVs and other electronic equipment.

Be your own boss! It's quick and easy to become an expert at home in your spare time. Earn really BIG money adjusting, installing and repairing · ***Satellite dish systems*** · ***TVs*** · ***Amplifiers*** · ***CD players*** · ***AM/FM tuners*** · ***Home entertainment centers.*** Every home, every business, every office in your area desperately needs your expertise!

Your timing just couldn't be better! Never before and probably never again will you have a ground-floor opportunity like this to get into a booming business of your own, make really big money starting right away, be your own boss and enjoy financial freedom and security. The fact you're reading this message shows you're smart enough to realize this!

Satellite dish/TV/Electronics is easy to learn in your spare time at home. This modern, practical hands-on course combines simple step-by-step lessons with easy-to-follow video cassette guidance. No special experience or electronics background is necessary. Just average mechanical aptitude and the ability to follow simple A-B-C repair procedures that are clearly outlined for you.

And when you complete the course you will receive Foley-Belsaw's official diploma attesting to your expertise.

30-DAY NO RISK TRIAL
Send for details

Send coupon today for FREE Fact Kit. No obligation.

Don't miss out on this once-in-a-lifetime opportunity. Send in the coupon NOW. Get all the facts and study them in the privacy of your own home. There's absolutely no obligation and no salesman will call on you. So don't delay. Mail the coupon today!

MAIL TODAY FOR FREE INFORMATION PACKAGE

Foley-Belsaw Institute
6301 Equitable Road
Kansas City, MO 64120-1395

FOLEY BELSAW *Since 1926*

- ☐ **YES!** Without obligation send free information kit so I can learn how to become a professional **Satellite Dish/TV/Electronics Specialist,** in order to earn high extra income. Dept. 31310
- ☐ **VCR Repair-**Unlimited profits in this growing field. Dept. 62530
- ☐ Interested in an exciting, money making career in **Computer Repair, Maintenance and Upgrade?** Dept. 64435
- ☐ **Personal Computer Programming-**Learn fast at low cost for big earnings. Dept. 35258

Name _____

Address _____

City _____ State _____ Zip _____

Call toll-free *1-800-487-2100*

CIRCLE 330 ON FREE INFORMATION CARD

Before You Blow Thousands of Dollars on Tango, Or-Cad or Protel Try

MS DOS

EZ-ROUTE™

The Most Complete Schematic-PCB Layout-Auto-Router System

The EZ-ROUTE™ system from AMS for IBM PC, PS/2 and compatibles is an integrated system and includes Schematic Capture, PCB Layout, Automatic Router, Design Rule Checker, Gerber Plot View and Gerber file import capability. The EZ-ROUTE™ system is complete, totally intuitive and easy to use.

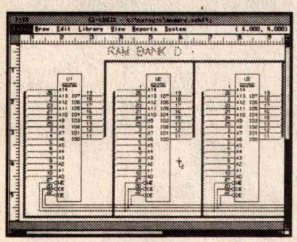

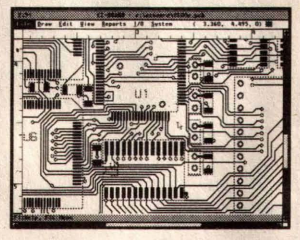

For a FREE Evaluation call:

1-800-972-3733

30 DAY NO-HASSLE MONEY BACK

- 20,000+ parts library
- A through E sheet sizes
- On-Line Design Rule Checker
- 256 board layers
- Imports files from Gerber, Protel and Or-Cad and 8 other formats
- SMD on both sides of board
- Netlist output compatible to: Futurenet, Pcad, Edif and 16 other formats
- Output to penplotter, Gerber photoplotter, dot-matrix and laser printers

EZ-ROUTE Pro™ $695 EZ-ROUTE Std™ $249

ams **Advanced Microcomputer Systems, Inc.**
1460 SW 3rd Street • Pompano Beach, FL 33069
Phone (954) 784-0900 • Fax (954) 784-0904

CIRCLE 309 ON FREE INFORMATION CARD

Learn by Example!

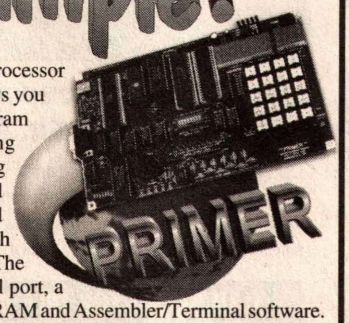

The PRIMER 8085 Based Microprocessor Training and Control System shows you how to program by example. Program examples take you from writing simple programs to controlling motors. This trainer can be used stand alone via the keypad and display or connected to a PC with the optional upgrade ($49.95). The Upgrade includes: an RS232 serial port, a serial cable, 32K of battery backed RAM and Assembler/Terminal software.

EXPERIMENTS USING THE PRIMER INCLUDE:

- Measuring Temperature
- Using a Photocell to Detect Light Levels
- Making a Waveform Generator
- Constructing a Capacitance Meter
- Motor Speed Control Using Back EMF
- Interfacing and Controlling Stepper Motors
- Scanning Keypads and Writing to LCD/LED Displays
- Using the Primer as an EPROM Programmer

The PRIMER is only $119.95 in kit form. The PRIMER Assembled & Tested is $169.95. Please add $5.00 for shipping within the U.S. Picture shown with upgrade option and optional heavy-duty keypad ($29.95) installed.

EMAC, inc.
P.O. BOX 2042, CARBONDALE, IL 62902
618-529-4525 Fax 457-0110 BBS 529-5708

1985 - 1996 OVER 10 YEARS OF SERVICE

The Hacker's Companion CD-ROM

Want a war-dialer program or something to crack a password? Do you want to learn how the phone company gets ripped off, or learn how to build a red box, or modify a cellular phone? Want to see what the security holes in a VAX are? Or how to compromise a Unix machine or a BBS? Want to learn how to use the system in ways you never imagined possible? This CD is the place to look! It contains all kinds of computer, telephone and general hacking information. Even a video of dutch hackers breaking into a classified US military computer! In all, 552 megabytes of fascinating information that's hard to get anywhere else!

PC-Compatible CD-ROM $49.95
Shipping $3

Call (800)719-4957 now!

to order (Visa/MC/COD) or call or write for **FREE CATALOG** of hard-to-get information about *computer viruses, computer hacking, security and cryptography*!!

American Eagle Publications, Inc.
P. O Box 1507
Show Low, AZ 85901

CIRCLE 282 ON FREE INFORMATION CARD

Quality Reconditioned Test Equipment from Danbar

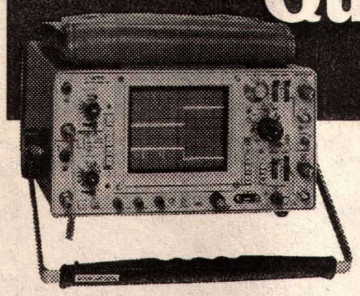

Tektronix 475 Oscilloscope

Portable Scope, 200 MHz bw, dual channel, 2 mV/ div sensitivity, 1 ns/ div sweep rate, delaying timebase, trigger view, beam finder. Includes 2 probes.

Special $925.00

Tektronix 485 Oscilloscope

Portable Scope, 350 MHz bw, dual trace, 5 mV/ div sensitivity, 1 ns/ div sweep rate, 3.0 div/ ns writing speed. Includes 2 probes.

Special $850.00

Tektronix 2213 Oscilloscope

Dc to 60 MHz bw, 2 mV sensitivity, 5 nS/ div sweep speed, advanced trigger system, with 2 probes.

Special $650.00

Tektronix 7844 Oscilloscope

Dc to 400 MHz mainframe, dual beam, 0.9 ns risetime, 1 ns/ div max sweep rate, 8 x 10 cm display. Includes the following plug-ins: (1) 7A19, (1) 7A26, (1) 7B85, & (1) 7B80.

$1250.00

Tektronix 7904 Oscilloscope

Dc to 500 MHz Oscilloscope mainframe .8 ns risetime, 500 ps max sweep rate, includes the following plug-ins: (1) 7A24, (1) 7A26, (1) 7B80 & (1) 7B85.

$1100.00

Hewlett-Packard 54100D

Digitizing Oscilloscope, 1 GHz, 350 ps rise time, 10 ps resolution, 40 ms/sec max. digitizing rate, pre-trigger viewing, logic triggering, digital storage.

Special $4000.00

Hewlett-Packard 54110D

Digitizing Oscilloscope, 1 GHz,2 channel,40 ms/s max. digitizing rate, 4 MHz single-shot bw, color display, pre-trigger viewing, digital storage, logic triggering capability, HP-IB programmable.

$5500.00

Tektronix P6201 Active Probe

Dc to 900 MHz, 1X with readout.

Special $200.00

WANTED USED TEST EQUIPMENT

Hewlett-Packard 8569B

10 MHz to 22 GHz, input preselection, 1.7 to 22 GHz, resolution 100 Hz to 3 MHz.

Special $7500.00

Hewlett-Packard 214B

Pulse Generator, high power 100 V, 2 A output into 50 Ω, 10 MHz repetition rate, constant duty cycle.

New boxed $1995.00

Hewlett-Packard 141T Spectrum Analyzer System

141T with 8552B and 8553B. The mainframe provides variable persistence and storage. Covers 1 kHz to 110 MHz, 10 Hz resolution bw, high sensitivity -140 dBm.

$1750.00

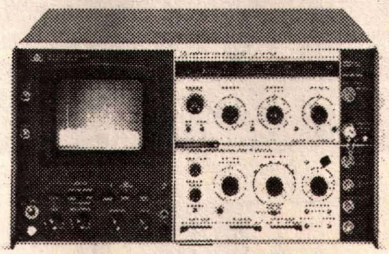

Hewlett-Packard 5314A

Universal Counter, 100 MHz, 100 ns time interval, portable.

Special $275.00

Racal Dana 9303

True RMS RF Level Meter, 10 kHz to 2 GHz frequency range, level range of 30 uV to 3 V, basic accuracy of 1%.

Special $500.00

Wandel & Goltermann SPM-16

Selective Level Meter, 10 kHz to 160 MHz, high frequency accuracy, uncertainty less than 1 X 10 -7, digital and analog display.

$1000.00

California Instruments 1201WF

Frequency Changer, output voltage is adjustable from 0 to 260 volts at frequencies of 47 to 500 Hz. Digital display allows monitoring of RMS output voltage, frequency and RMS load current.

New $1950.00

Fluke 1900A

Multifunction Counter, frequency, period, period averaging and totalize measurements, 6-digit display.

$189.00

Wavetek SAM-1-450

Signal Level Meter, simple hum and carrier-to-noise measurement, built-in-calibrator, frequency range 4 MHz to 450 MHz, extremely portable.

$695.00

Hewlett-Packard 8901A

Modulation Analyzer, 150 kHz to 1300 MHz, measures AM/FM to 1% accuracy, Measures RF frequency and RF power, completely automatic. Options available.

Special $4500.00

Hewlett-Packard 1725A

Portable Oscilloscope, 275 MHz, 10 mV/ div to 5V/ div vertical deflection factor, 10 nS max sweep rate. Has opt 034 is DMM, includes 2 probes.

$695.00

Hewlett-Packard 1740A

100 MHz bw, 5 mV/ div deflection, 50 nS/ div max sweep rate expandable to 5 nS/ div, with 2 probes.

$495.00

Hewlett-Packard 6263B

0 to 20 V, 0 to 10 A, built in overvoltage protection.

New $450.00

Wavetek 2001

1 to 1400 MHz, 10 mS to 100 S sweep. ext AM/FM modulation, start/ stop, △F, CW modes, markers available.

$795.00

Wavetek 3002

Signal Generator, 1 kHz to 520 MHz, .001% accuracy, 6 digit readout and 1 kHz resolution, -137 to +13 dBm.

$795.00

Please call for our Free 1996 Catalog

14455 NORTH 79TH STREET • UNIT C • SCOTTSDALE • ARIZONA 85260
(602) 483-6202 • FAX (602) 483-6403

DANBAR SALES COMPANY

CIRCLE 235 ON FREE INFORMATION CARD

❖ ATTENTION CABLE VIEWERS ❖

CABLE VIEWERS. . .get back to your BASIC Cable Needs

Call 800-577-8775

For information regarding all of your BASIC cable needs.

5 GOOD REASONS TO BUY OUR FAR SUPERIOR PRODUCT

- ❖ PRICE
- ❖ EFFICIENT SALES AND SERVICE
- ❖ WE SPECIALIZE IN 5, 10 LOT PRICING
- ❖ ALL FUNCTIONS (COMPATIBLE WITH ALL MAJOR BRANDS)
- ❖ **ANY SIZE** ORDER FILLED WITH SAME DAY SHIPPING

BASIC ELECTRICAL SUPPLY & WAREHOUSING CORPORATION

We handle NEW equipment ONLY - Don't trust last year's OBSOLETE and UNSOLD stock!
COMPETITIVE PRICING—DEALERS WELCOME

HOURS: Monday-Saturday 9-5 C.S.T.

It is not the intent of B.E.S.W. to defraud any pay television operator an we will not assist any company or individual in doing the same
*Refer to sales personnel for specifications.

P.O. Box 8180 ■ Bartlett, IL 60103 ■ 800-577-8775

CIRCLE 334 ON FREE INFORMATION CARD

NEW!!!

MONITOR REPAIR SOFTWARE

LEARN COMPONENT LEVEL ELECTRONIC REPAIR

- * USER FRIENDLY WINDOWS FORMAT
- * STEP-BY-STEP TROUBLESHOOTING ASSISTANCE
- * EXPANDABLE "REAL WORLD" REPAIR DATABASE
- * PRE-LOADED WITH OVER 200 PROVEN REPAIRS
- * SUPPLIERS, PARTS AND MANUFACTURERS LISTINGS

DISTRIBUTORS WANTED
CALL TODAY

IVS, INC.
13311 STARK RD.
LIVONIA, MI 48150
(800) 886-2201

TURN YOUR PC INTO A
DIGITAL STORAGE OSCILLOSCOPE!

mission technology, Inc.'s PC-MultiScope now sold by Amaze Electronics

As reviewed in the May 1996 issue of *Electronics Now!*

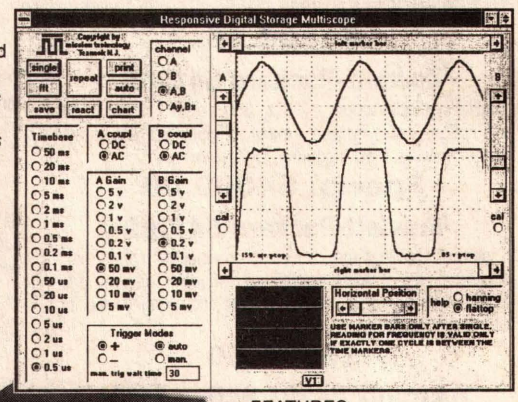

At right: Actual scope screen as seen on your PC monitor.

For industrial, hobbyist, educational, automotive, audio, and medical uses

$399 + S/H. Visa/MC/Check OK.
Add $99 for source code option

FEATURES:

1. Dual channel; external triggered
2. Digital storage; Windows based
3. Connects to PC parallel port
4. 20Mhz max. digital bandwidth; 2Mhz max. analog bandwidth
5. Programmable gain from 5v/div to 5mv/div
6. Frequency analyzer function
7. Strip chart recorder function
6. Integrated 16 bit output
7. Visual Basic source code avail.

AMAZE ELECTRONICS CORPORATION
amaze@hooked.net www.hooked.net/users/amaze
Phone: 800-996-2008 Fax: 408-996-0366

Unbeatable Discount Prices

1 YEAR WARRANTY
15 DAY MONEY BACK GUARANTEE

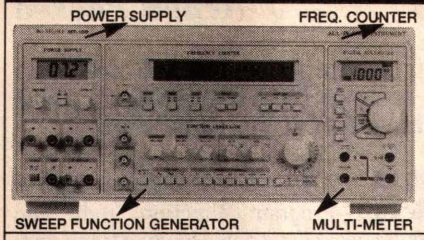

MT-100

Reg. $599.

$419.00

Four Instruments in One Instrument

1 Function Generator
- Sine, Square, Triangle, Pulse, Skewed Sine, Ramp, TTL
- 0.2 Hz ~ 2MHz

2 Frequency Counter
- 8 Digit LED
- 1 Hz ~ 100MHz
- ± (1 Hz + 1 dgt. + Time Base Error)

3 Power Supply
- 3-1/2 Digit LCD
- Triple output: #1. 0~50V, 0.5A MAX #2, 15V, 1A #3. 5V, 2A

4 Digital Multimeter
- 3-1/2 Digit LCD
- DCV, ACV, Ω, DCA, ACA
- ± (0.5% + 2 dgts)

FG-140 2MHz Function Generator

Reg. $249. **$149.00**

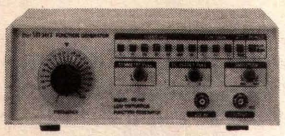

- 0.2 Hz ~ 2.0 MHz, 7 Decades
- Sine, Square, Triangle, Pulse, Ramp, Skewed Sine
- VCF, Symmetry
- Variable DC Offset Control

2MHz Sweep Function Gen. w/Freq. Counter

FG-150

Reg. $399. **$229.00**

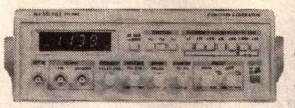

- 4 Digit LED Display
- Sine, Square, Triangle, TTL, Pulse, Ramp, Skewed Sine
- Linear/Logarithmic Sweep
- 10 MHz Freq. Counter

1.0GHz Frequency Counter, High Resolution

FC-200

Reg. $399. **$219.00**

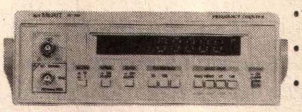

- 1.0 Hz ~ 1.0 GHz
- 8 Digit LED Display
- Auto & Manual Range
- 4 Selectable Gate Times
- 1MΩ & 50Ω Input Impedance

Oscilloscope Probe Set

Switch Selectable X1/X10

HP-9060, 60MHz Reg. $29. **$17.00**
HP-9150, 150MHz Reg. $49. **$27.00**
HP-9250, 250MHz Reg. $59. **$37.00**

PS-500 DC Power Supply

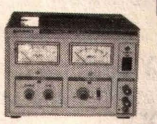

Reg. $249. **$159.00**

- 0 - 30 VDC
- 0.1 ~ 3A
- Short & Overload Protection

PS-540 DC Power Supply

Reg. $399. **$249.00**

- 0 - 16 VDC
- 0.1 ~ 10A
- Short & Overload Protection

Deluxe O'scopes w/Phillips CRT. "BEST BUY!"

OS-3304 Reg. $499. $349.00

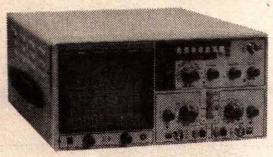

OS-3324 Reg. $599. $429.00

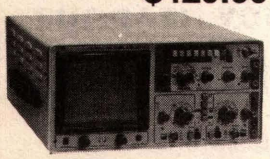

OS-3344 Reg. $899. $649.00

OS-3304 25MHz, Dual Trace

1 • DC to 25 MHz. Dual Channel
- 6" Rectangular CRT with Internal Graticule 10x8cm (Phillips P31)
- Uncalibration LED.
- High Sensitivity 1 mV/div to 2mV/div X-Y modes, Z Axis (intensity modulation)
- Rise time 14n Sec. or less.
- Full TV Trigger for TV-V & TV-H
- Acceleration Potential 2kV
- 60MHz (X1.X10) Probe Kit: 2 sets
- Power: 115/230V AC

OS-3324, 3 Function

1 • OS-3304

2 • Dual Component Tester/Comparator

3 • Triple DC Power Supply 5VDC, +12 VDC, -12VDC

OS-3344, 5 Function

1 + 2 + 3 • OS-3324

4 • Frequency Counter 100MHz, 7 Digit LED Display

5 • Function Generator 0.02 Hz to 2.0 MHz

OS-3315 40MHz, Dual Trace Sweep Delayed

Reg. $799. **$549.00**

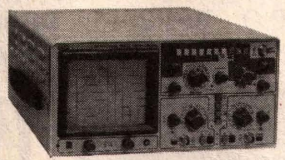

- DC to 40 MHz. Dual Channel
- Delayed Sweep 100nS to 1.0S 7 decade
- 6" Rectangular CRT with Internal Graticule 10x8cm (Phillips P31)
- Uncalibration LED.
- High Sensitivity 1 mV/div to 2mV/div X-Y modes, Z Axis (intensity modulation)
- Rise time 8.5nS or less.
- Full TV Trigger for TV-V & TV-H
- Acceleration Potential 12kV
- Variable Hold Off
- 16ns ~ 1.0s Time Base
- 60MHz (X1.X10) Probe Kit: 2 sets
- Power: 115/230V AC

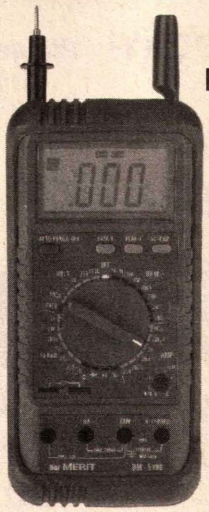

Bel MERIT

DM5050C
DM5100

Reg. $149.

$89.00

Including Deluxe Holster

Features (DM5050C/DM5100)

- Basic DCV Accuracy: ± 0.25%
- AC/DC Volt & Amp, Ohm
- Diode, Continuity Beeper
- Alligator Clip Test-Leads
- Lead Holders/Velcro Strap Holster

DM5050C, DMM + Capacitance

- 9 Function / 42 Range
- Multimeter
  Ohm: Up to **2000MΩ**
  Amp: AC/DC 2 Amp
- Extended Capacitance Meter (9 Range)
  0.1pF - 20,000µF
  Zero Adjust Knob
- Trig Lamp

DM5100, Wide Range w/Logic

- 11 Function / 45 Range
- Auto Power Off
- Data Hold & Peak Hold
- Freq: Up to **20MHz**
- Amp: Up to **20A AC/DC**
- Ohm: Up to **200MΩ**
- Capacitance: **1p - 200µF**
- Logic: TTL, TR hFE

Digital Engine Analyzer

Reg. $119. **$69.00**

DM230
- 3 1/2 Digit LCD
- **Engine Analyzer** Taco, Dwell, Duty Cycle
- **DMM** DCV, DCA, Ω
- **Temperature** 0 ~ 1.999°F
- Diode
- Continuity
- Holster, Temp. Probe, Clip Leads

Capacitance Meter

Reg. $79. **$49.00**

CM210
- 3 1/2 Digit LCD
- 0.1p-20,000µF 9 Ranges
- 0.5% basic Accu.
- Zero Adjust Knob
- Test Leads & Built in Socket

Pen-Type DMM w/Logic

Reg. $79. **$59.00**

DM150
- 3 1/2 Digit
- Dual Display
- Auto & Manual
- DCV, ACV, ACA, DCA, Ω
- Logic CMOS/TTL
- Data Hold
- Diode
- Continuity

Multifunction DMM

Reg. $99. **$64.00**

DM4050
- 3 1/2 Digit
- Basic Accuracy: 0.25%
- Heavy Duty, 20A AC/DC Resistance 20MΩ
- Capacitance
- Freq. up to 20MHz
- TR-hFE
- Diode
- Continuity
- Deluxe Holster

BMC *Your Best Source for High Standard Electronics*

P.O. Box 744, Lake Forest, CA 92630-0744

Order & Free Catalog

800-532-3221

(714) 586-2310 Fax (714) 586-3399

VISA MasterCard

CIRCLE 297 ON FREE INFORMATION CARD

Robot Kits

✓ *Academic-Level Books*
✓ *Build it Yourself*
✓ *Action Packed*

EASY TO BUILD You do ALL electronic & mechanical assembly using 2-color Instruction Books with step-by-step, well-illustrated directions for assembly, experiments and testing. Each Robot Kit applies different electronic & robotic principles. Learn how Robots work and have fun at the same time!

606A *"Scrambler"* **All Terrain Robot** This 6-legged Robot walks over rough terrain. Uses high-tech infrared beam to sense and avoid avoid objects in its path. 32 page Book. **$37.95**

603A *"Copycat"* **Programmable Robot** Program direction, light and sound using detachable keypad (included) or optional PC. Learn digital logic basics. 44 page Book. **$57.35**

602A *"Blinky"* **Pathfinder Robot** Follows path made with a marker pen or tape. Red/green LEDs react to steering changes, adding fun and interest. 28 page Book. Infrared emitter/detectors. **$36.95**

601A *"Scooter"* **Sound Controlled Robot** Backs up, changes direction, goes forward when it hears loud noise or hits an object. Florescent red. 24 page Book. Fast-paced excitement! **$18.95**

DEPENDABLE PRODUCTS Since 1963, Graymark's ONLY business has been producing educational electronic kits. We do one thing and we do it right. That's why Graymark has the largest selection of electronic kits. And, our ***"It works or we fix it"*** policy guarantees success for YOU!

ORDER TODAY! ***Phone:*** *VISA/MasterCard*
Mail: *Check/Money Order, VISA/MasterCard*
Add: *$4.00 Shipping*

CALL FOR ***FREE*** 40 PAGE CATALOG

Graymark P.O. Box 2015, Tustin, CA 92681 **800-854-7393**

CIRCLE 317 ON FREE INFORMATION CARD

Radiotelephone - Radiotelegraph

FCC Commercial License

Why Take Chances?

Discover how easy it is to pass the exams. Study with the most current materials available. Our **Homestudy** Guides, Audio, Video or PC "Q&A" disks make it so fast, easy and inexpensive. No college or experience needed. The new commercial FCC exams have been revised, covering updated Aviation, Marine, Radar, Microwave, New Rules & Regs, Digital Circuitry & more.We feature the Popular "Complete Electronic Career Guide". 1000's of satisfied customers **Guarantee** to pass or money back. Newest Q&A pools.

Send for **FREE DETAILS** or call

1-800-800-7588

WPT Publications
4701 N.E. 47th St.
Vancouver, WA 98661

Name_____

Address_____

City_____ St.___ Zip_____

1-800-800-7588

DIRECT FREQUENCY READOUT

SCPC AUDIO RECEIVER

FULL COMMERCIAL FEATURES

UNIVERSAL SCPC-200 AUDIO RECEIVER

SERVICES ON SCPC RADIO

All Sports • News Networks • AP - UPI • Radio Nets • Talk Shows • Hometown Sports • Music - Classical, Jazz, Rock • Major Radio Stations • Financial News • Over 430 Channels and Growing.

FEATURES OF THE SCPC-200

Easy Direct Frequency and Transponder Tuning - 50 TO 90 MHz (LCD) • 50 Channel Memory Bank • C and Ku Band Agile - 950 - 1450 MHz • Automatic LNB Drift Compensation (ADC) • Automatic Companding • Digital Frequency Lock-On (DFL) • High Quality Audio • Commercial Digital Synthesizer • Full LCD Display • Built in U.S.A. by the Leading SCPC Receiver Manufacturer

INTRODUCTORY PRICE $399 plus S & H - CALL: 1-614-866-4605

UNIVERSAL ELECTRONICS, INC. *Communications Specialists*
4555 GROVES RD., SUITE 12, COLUMBUS, OH 43232
(614) 866-4605 FAX (614) 866-1201

MONDO•TRONICS'

Robot Store

Robot Kits Kits Kits!!!

New Low Price!

Hyper Peppy Robot #3-296 $29.95

Bright red, white & blue, and clear dome. Runs forward until it bumps object or hears loud noise, reverses & turns 90°, then resumes. With complete instructions. 14 cm W x 13 L x 9 H. No soldering required. *A fun & frantic first robot!* Two AA NiCads INCLUDED!

Sonic Rover Robot #3-174 $27.95

A great, low-priced kit. "Bump & run" operation like Hyper Peppy above. Molded body, red/green LED, great 48 pg manual. 14 cm L x 12 W x 7 H. Requires soldering. *A fast moving first robot!* Two AA NiCads INCLUDED!

New Low Price!

Spider Walking IR Avoider Robot #3-186 $79.95

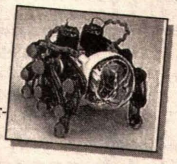

Futuristic & maneuverable 6-legged walker with IR for object avoidance. Complete instructions, requires soldering. 13 cm L x 13 W x 10 H. Two AA & one 9V NiCad INCLUDED!

Line Tracker Robot #3-188 $69.95

Easy-to-assemble. Front mounted sensors follow black line on white paper. Stylish molded gray & green, with complete instructions. 16 cm L x 14 W x 10 H. Needs no soldering! Two AA and one 9V NiCad INCLUDED!

Light Sensing Robot #3-216 $68.95

Clever sensors system lets this robot avoid objects & solve walled mazes! Dual motors, rubber tires, preassembled gear box & circuit board. 7 cm W x 16 H x 23 L. No Soldering! Three AA NiCads INCLUDED!

New Low Price!

S-Cargo Sound Controlled Robot #3-295 $34.95

You control the action by clap or whistle. Rotate left, go forward or stop. Top mounted microphone & smooth design to glide through the environment. 11 cm dia. Requires soldering. Ideal for Robot Golf. Two AA & one 9V NiCad INCLUDED!

Advanced Robots

New Low Price!

WAO II Programmable Robot #3-280 $74.95

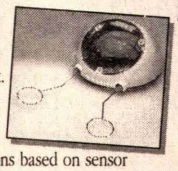

A sophisticated, full function robot kit. 2 motors, programmable 4-bit micro, 26 button keypad, sensor arms for collision or edge detection. Moves in all directions, performs if-then decisions based on sensor input, even do-loops! Requires soldering. Great intro to robot programming. Three AA & one 9V NiCad INCLUDED!

PC Interface for WAO II #3-195 $29.95

Parallel cable & 5.25" DOS disk for easy program handling.

A Top Selling Kit!

Mobile Robots Brains & Brawn Kit #3-148 $489.00

A complete, serious research robot platform from MIT. With all hardware, C software, 68HC11 CPU, memory, sensors, wheels, motors, chassis, instructions & more. 18 cm dia. The ideal companion kit to the Mobile Robots book (#3-098). *NOTE: Indicate PC or Mac version.*

Best seller!

Robot Builder's Bonanza #3-114 $18.95

Practical, ready-to-use circuits, devices, mechanisms, sources, tools, vision, grippers, navigation & more! 336 pgs, illust.

Gadgeteer's Goldmine #3-129 $21.95

Unique high-tech projects & hard-to-find info. Robots, high voltage Tesla & Van de Graaff generators, Kirlian photos, lasers & much more! 400+ pgs, illust.

Mobile Robots #3-098 $39.95

From MIT, a complete guide to designing & building robots: hardware, software, sensors, motors, "subsumption" software. 336 pages, illust. A must for all roboticists.

Sensors for Mobile Robots #3-145 $59.95

Whoa! Everything about sensors: tactile, proximity, range, acoustic, laser, radar, microwave, path following, dead reckoning, compasses, gyros & more. 550 pgs. Fun & intelligent!

507 Mechanical Movements #3-173 $9.95

Reprinted from 1893 – when steam was king! Discover 100's of cams, clutches, linkages, latches, ratchets & more! Don't reinvent the past - use it! 120 pg, illust. High powered!

The Robot Zoo #3-149 $19.95

A big, imaginative & fun book about animals that work like robots – or are they robots that work like animals??? 50 full color pages. For kids of all ages.

IC Hobbyist's Handbook #3-164 $19.95

Toss those old IC data books! This practical collection has 80 common ICs to make 100s of circuits! Amps, linear, logic, CMOS – with specs, pinouts, sample circuits – even component values (gasp!). 120 pgs. A basic resource!

Controlling the World With Your PC #3-165 $35.00

Convert ordinary serial & parallel ports into object-detecting, motor-spinning monsters! 42 circuits AND software in BASIC, C and Pascal! 256 pages, illustrated, with DOS disk.

Forrest Mims Engineer's Notebook #3-166 $19.95

A classic from THE circuit master himself, 100s of circuits, 156 pgs, 350 illust. Great starting point for the beginner – an ideal reference for the advanced!

Basic Stamps

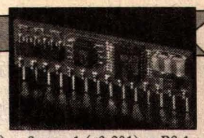

Stamp One Starter Pack #3-294 $149.95

A complete starter set: Stamp Programming Package (#3-199), a Stamp 1 (#3-201), a BS-1 Carrier Board, & a 9V NiCad. $161.85 value. *Upgradeable – add a Stamp 2 & Carrier Board 2 for full Stamp 2 power!*

Stamp Two Starter Pack #3-279 $169.95

Everything needed to move with the Stamp 2: Programming Package (#3-199), one Stamp 2 module (#3-198), one BS-2 Carrier Board, a 9V NiCad. $180.90 value. Monstrous power!

BASIC Stamp Programing Pkg #3-199 $99.00

With cables, manuals, app notes & Stamp DOS program to edit, file, download & debug both type 1 & 2 Stamps.

BASIC Stamp 1 #3-201 $34.95

8 input/output lines, EEPROM for 100 instructions, 4 MHz.

BASIC Stamp 2 #3-198 $49.00

16 input/output lines, EEPROM for 600 instructions, 20 MHz clock (up to 38,400 baud), touch tones, X-10, more!

Carrier Board, BS1 #1-105 $19.95

Carrier Board, BS2 #1-106 $24.95

Solar Powered Robots

BEAM Manual & Buttons #3-286 $19.95

Learn the philosophy, practice & history of solar powered BEAM robotics. Shows robots, creators, events, winners from past games, tech references, more. 114 pages, illust. Informative & fun!

BEAM Videotape, VHS #3-287 $14.95

Dave's exclusive "insider look" at the the world of BEAM robotics. Solar-powered gizmos fighting for survival, time-lapse footage, 1995 BEAM Games, more! 60 min, VHS.

Dave's BEAM Solar Engine Kit #3-119 $29.95

Harness fusion power today! Circuit uses a tiny (11 x 55 mm) solar cell to drive a motor up to 3 RPM! A complete power plant with all parts & instructions. Just add solder & sun!

Mechanicals

Dump Truck Kit #3-212 $49.95

Great full function wheeled base – rugged rubber tires, 3 motors: steer left-right, drive forward-reverse, dump up-down. 22 cm L x 14 H x 12 W. Includes two D NiCads!

Power Shovel/Dozer Kit #3-211 $39.95

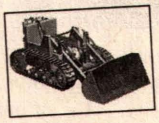

An excellent full function tank base. Wire controlled left, right, forward, reverse, plus scoop up & down. 10 cm W x 28 L x 10 H. Has extra track & wheels. Two D NiCads INCLUDED!

Tracked Vehicle Parts Kit #3-293 $22.95

Get on track! Track, wheels, sprockets, axles, hardware, as in Dozer above, plus fwd/rev only gearbox, 3V DC motor & battery holder. 10 cm W x 18 L. Tech Tip: Replace gearbox with 2 R/C Servos for full fwd-rev-left-right action!

R/C Servo #3-278 $19.95 or Servo 6-Pack #3-263 $89.95

Quality RCD HS-300 servo, 42 oz/in, 0/19 sec. With app notes.

Muscle Wires®

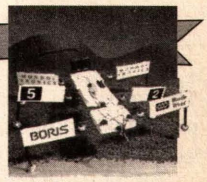

Muscle Wires Project Book & Deluxe Kit #3-168 $59.95

Create direct linear action with Muscle Wires. They contract up to 5% when powered! Use them in robots, models and anything needing strong all-electric *motion*. 128 page book, full plans for BORIS, a motorless walking robot & 14 others. Includes one meter each 50, 100 & 150 µm dia Muscle Wires. *Get moving today!*

Order Toll Free! 24-hour Voice Order Line – **VISA MasterCard**

800-374-5764

Request our FREE Robot Store Catalog!

Mondo-tronics

524 San Anselmo Ave. #107-107
San Anselmo, CA 94960

Questions: 415-455-9330
Fax: 415-455-9333
Email: info@mondo.com
Web: www.RobotStore.com

To Order: Send check, MO or credit card info. All orders add $5.00 P & H. Calif. orders also add sales tax.

International Orders Welcome! First Class P&H: $12.00

Tel: (954) 974-6864
Fax: (954) 974-6818

Gateway Products Corp.

Please mail orders to:
P. O. Box: 93-6397
Margate, FL 33093

Popular I.C.s
LM324 ... 45¢
LM339 ... 45¢
LM358 ... 45¢
NE555 ... 40¢
LM556 ... 50¢
LM741 ... 40¢
Deal U3: 12 pcs total, (2pcs of each)....$5.00

Popular CMOS
CD4001B.... 30¢
CD4011B.... 30¢
CD4013B.... 40¢
CD4017B.... 50¢
CD4028B.... 40¢
CD4050B.... 40¢
CD4066B.... 40¢
CD4069B.... 40¢
Deal V8: 16 pcs total, (2pcs of each)....$5.00

DEAL M3....$5.00
7805 7812
7905 7912
12 pcs total (3pcs of each)

DEAL J1.....$3.50
78L05
78L12
10 pcs total (5pcs of each)

5mm (T1 3/4) Diffused LEDs
Red..... 8¢
Green.... 10¢
Yellow... 12¢
Deal L3: 30 pcs total, (10pcs of ea.).....$2.50

Transistors
PN2222A .... 8¢
PN2907A .... 8¢
2N3904 ..... 7¢
2N3906 ..... 7¢
2N4401 ..... 8¢
2N4403 ..... 8¢
Deal N8: 60 pcs total, (10pcs of ea.).....$4.00

More Transistors
MPSA05.... 13¢
MPSA13.... 13¢
MPSA27.... 13¢
MPSA42.... 13¢
MPSA56.... 13¢
MPSA92.... 13¢
Deal Q2: 30 pcs total, (5 pcs of ea.).....$4.00

More Transistors
2N2222A ... 30¢
2N4124 ..... 11¢
2N4126 ..... 11¢
2N5401 ..... 14¢
MPSH10 ... 13¢
2N3055 ..... 69¢
TIP31C ..... 55¢
TIP32C ..... 55¢
TIP117 ..... 55¢
TIP120 ..... 60¢
TIP125 ..... 65¢

3mm (T1) Diff. LEDs
Red..... 8¢
Green.... 10¢
Yellow... 12¢
Deal L6: 30 pcs total, (10pcs of ea.).....$2.50

Semiconductors
74LS174 ... 40¢
74LS244 ... 45¢
74LS245 ... 45¢
74LS374 ... 45¢
LM386N .... 45¢
MC1488 .... 45¢
MC1489 .... 45¢

V. Regulators
LM317T..... 69¢
7805..... 49¢
7808..... 49¢
7812..... 49¢
7815..... 49¢
7818..... 49¢
7824..... 49¢
7905..... 49¢
7908..... 49¢
7912..... 49¢
7915..... 49¢
78L05..... 39¢
79L05..... 39¢
78L12..... 39¢

CRYSTALS
3.5795MHz ..... 99¢
4.0000MHz ..... 99¢
11.000MHz ..... 99¢
11.0592MHz ..... 99¢

Computer Stuff
6ft printer cable..... $4
6ft VGA extension.... $4
3-b serial mouse..... $9
101 key keyboard .. $19
1.44Mb 3.5" drive... $29
1Gb hard drive $230

DIODES
1N914 ..... 3¢
1N4148 ..... 3¢
1N4001 ...1A/50V .... 3¢
1N4004 ..1A/400V .... 4¢
1N4007 ...1A/1kV..... 5¢
Deal P7: 50 pcs total, (10pcs of ea.).....$2.00

Power Diodes
1N5401 ..3A/100V ... 8¢
1N5404 ..3A/400V ... 9¢
1N5408 ...3A/1kV... 10¢
6A10 ..... 6A/100V.. 24¢
6A100 .....6A/1kV... 32¢
Deal H8: 25 pcs total, (5pcs of ea.).....$3.00

1W Zener Diodes
1N4728A.... 3.3V ... 10¢
1N4733A.... 5.1V ... 10¢
1N4739A.... 9.1V ... 10¢
1N4742A.....12V ... 10¢
1N4744A.....15V ... 10¢
1N4746A.....18V ... 10¢
Deal Z5: 30 pcs total, (5pcs of ea.).....$2.50

Germanium Diodes
1N34A..... 15¢
1N60..... 15¢
1N270..... 30¢
Deal G5: 18 pcs total, (6pcs of ea.).....$2.50

RADIAL LYTICS
1uF/50V..... 6¢
2.2uF/50V.... 6¢
3.3uF/50V.... 6¢
4.7uF/50V.... 6¢
10uF/50V..... 7¢
22uF/50V..... 8¢
33uF/50V..... 9¢
47uF/50V.... 10¢
Deal A2: 40 pcs total, (5pcs of each)....$3.00

RADIAL LYTICS
10uF/25V..... 6¢
22uF/25V..... 6¢
33uF/25V..... 6¢
47uF/25V..... 7¢
100uF/25V.... 8¢
220uF/25V.... 9¢
330uF/25V.. 14¢
470uF/25V.. 17¢
Deal A7: 40 pcs total, (5pcs of each)....$4.00

1A SCHOTTKY
1N5817 ...1A/20V .. 20¢
1N5818 ...1A/30V .. 23¢
1N5819 ...1A/40V .. 24¢
Deal Y6: 9 pcs total, (3pcs of each)....$2.00

3A SCHOTTKY
1N5820 ...3A/20V .. 32¢
1N5821 ...3A/30V .. 36¢
1N5822 ...3A/40V .. 40¢
Deal Y9: 9 pcs total, (3pcs of each)....$3.00

Ceramic Disc
(All caps rated 50V)
10pF ..... 6¢
22pF ..... 6¢
27pF ..... 6¢
33pF ..... 6¢
47pF ..... 6¢
100pF ..... 6¢
150pF ..... 6¢
220pF ..... 6¢
Deal R4: 40 pcs total, (5pcs of each)....$2.50

Ceramic Disc
(All caps rated 50V)
270pF ..... 6¢
330pF ..... 6¢
470pF ..... 6¢
.001uF ..... 6¢
.01uF ..... 6¢
.022uF ..... 6¢
.047uF ..... 8¢
.1uF ..... 8¢
Deal R7: 40 pcs total, (5pcs of each)....$2.50

Mono Caps....8¢ea
.01uF/50V .047uF/50V
.022uF/50V .1uF/50V
Deal B5: 40 pcs total, (10pcs of ea.).....$2.50

Tantalum Caps
1uF/35V ..... 18¢
2.2uF/35V .... 22¢
10uF/35V .... 45¢
Deal T6: 15 pcs total, (5pcs of each)....$3.50

Toggle Switches
Miniature size 1/4" Panel hole
on-on.....SPDT.... 50¢
on-off-on ...SPDT.... 60¢
on-on.....DPDT.... 70¢
on-off-on ...DPDT.... 80¢
Deal S3: 8 pcs total, (2pcs of each)....$5.00

DEAL W2...$2.50
120 pcs total (20 pcs of each: 10, 47, 100, 470, 1k, 4.7k. All 1/4W 5%.

DEAL W5....$2.50
100 pcs total (20 pcs of each: 10K, 47K, 100K, 470K, 1M. All 1/4W 5%.

400V BRIDGES
1Amp
1.5Amp
4Amp
DF04M.....DIP ..... 40¢
W04M..... Round ... 35¢
KBL04.....In-line ... 90¢
Deal X8: 6pcs total, (2pcs of each)....$3.00

SOLDER ROLL
SN63/37
.031" dia
1 Lb Roll
$7.80

VISA MasterCard

$10.00 minimum order. We accept VISA, MC, MO, Check, No-CODs. Please add $5.00 for shipping & handling (foreign addresses: $8.50). Florida addresses add your applicable county sales tax. Hours: Mon-Fri: 9AM to 5PM (EST). All new premium parts. Send for free Catalog.

CIRCLE 316 ON FREE INFORMATION CARD

Video Camera Blowout Sale!

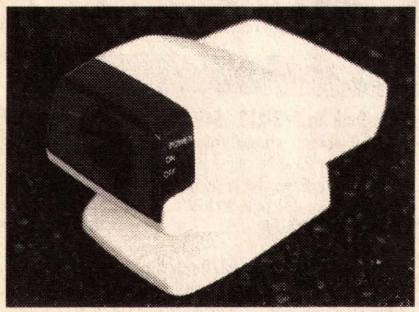

When a major multimedia company closed a division, they surplused a limited quantity of quality **COLOR** CCD video cameras. These cameras were part of a high end video conferencing system.

Manufactured by a division of Panasonic, these units are designed to sit on top of a computer monitor and can be used for video conferencing, security, ATV, or multimedia purposes.

- 330 line **COLOR** CCD imager
- 3 lux sensitivity for low light applications
- Standard 1V p-p NTSC output
- Built-in microphone with preamp
- Standard RCA video and audio jacks
- Includes 12v wall mount transformer
- Auto iris with sensitivity adjust
- 5mm fixed focus lens from 10" to infinity
- 5" long x 3" wide x 3" high- 7.5oz.

Call Today! Limited Quantity!

This OEM paid over $400.00 each. **Your price is only $179.00 plus $5.00 shipping/handling** (continental US only).

Sycard Technology
1180-F Miraloma Way
Sunnyvale, CA 94086

MasterCard and Visa accepted
CA orders add Sales Tax
Sorry, No CODs

(408) 749-0130 or (408) 749-1323 Fax

EPROM+
PROGRAMMING SYSTEM USES PARALLEL PORT

SUPPORTS OVER 600 CHIPS

EPROMS (24, 28, 32 & 40* PIN PLUS 27CXXX)
1702, 2708,16,32,32A,64,64A,128,128A,256,512
513,011,010,101,301,1000,1001,1024,210,020
2000,2001,220,240,2048,4001,4002,040,080,8001
2516,32,64,68764, **TMS2716**

FLASH EPROMS
28F256, 512, 010, 020 PLUS 29CXXX, 29FXXX

EEPROMS & NVRAMS (PLUS CXXX)
2804,16,16A,17, 2864, 64A, 65, 28256, 28C010
X2210,X2212,DS1220,1225,1230

SERIAL EEPROMS*** (8 PIN PLUS CXX)
2401,02,04,08,16,32,65,2444,59C11,8572,82,92
9306,46,56,66,16811,911,80011A, **ER1400/58657**

BIPOLAR PROMS*** (16 THROUGH 24 PIN)
74SXXX AND 82SXXX FAMILY

MICROCONTROLLERS*** (UV,EE AND FLASH)
8741,42,48,49,8751,87C51,8752,C52,87C5XXX
87C75X,89C51,52,68705,68HC705,68HC711E9
PIC16C5X,PIC16C6X,PIC16C7X,PIC16C8X

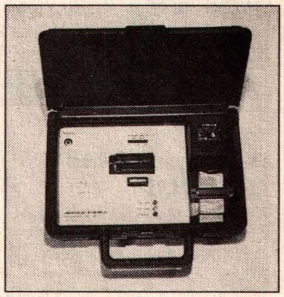

*ADAPTER REQUIRED - ASSEMBLED ADAPTERS AVAILABLE / DETAILED DIAGRAMS INCLUDED

- **SOFTWARE - READ, VERIFY, PROGRAM, COPY, DISK FILE LOAD & SAVE, CHECKSUM, PLUS A FULL SCREEN BUFFER EDITOR WITH 20 COMMANDS**
- **READS INTEL HEX , MOTOROLA S-RECORD AND BINARY FILES**
- **FAST! - MANY DEVICES PROGRAM IN UNDER 10 SECONDS**
- **RUGGED (9"X 6"X 3"), PORTABLE ENCLOSURE WITH CARRY HANDLE DESIGNED FOR BENCH AND FIELD SERVICE.**
- **ACCESSORY CONNECTOR FOR FUTURE EXPANSION**
- **LED INDICATORS SHOW POWER, PROGRAMMING & SYSTEM STATUS**
- **MADE IN THE USA - 30 DAY MONEY BACK GUARANTEE - 1 YR WARRANTY**
- **SYSTEM INCLUDES: PROGRAMMING UNIT, POWER PACK, CABLE PRINTED MANUAL AND SOFTWARE**

ANDROMEDA RESEARCH
P.O. BOX 222
MILFORD, OHIO 45150
(513) 831-9708
FAX (513) 831-7562

$289

VISA MasterCard

ADD $5.00 SHIPPING - $5.00 C.O.D.

NEW!!! 1996 PRINT Catalog!

PRINT™ 1996

We Make Ordering Simple!

Products International
EQUIPMENT, TOOLS & SUPPLIES
FOR ELECTRONIC PRODUCTION
MAINTENANCE & SERVICE

TOLL FREE 800-638-2020
FAX 800-545-0058
IN MARYLAND
CALL 301-587-7824
FAX 301-585-5402

KENWOOD

LEADER

HITACHI

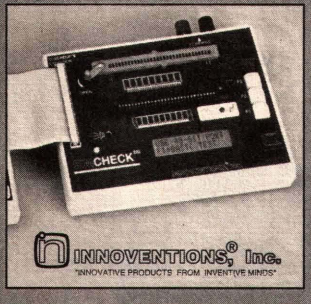
INNOVENTIONS, Inc.
"INNOVATIVE PRODUCTS FROM INVENTIVE MINDS"

BK PRECISION
MAXTEC INTERNATIONAL CORP.

PACE

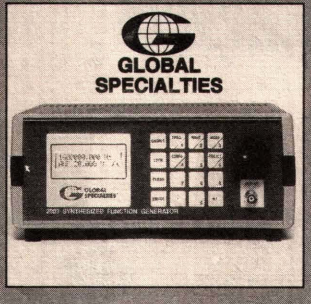
GLOBAL SPECIALTIES

SRS
STANFORD RESEARCH SYSTEMS

AVCOM

PRINT™ Products International

*8931 Brookville Road * Silver Spring, Maryland 20910 * 800-638-2020 * Fax 800-545-0058*

Call 800-638-2020 today for your free copy of the NEW 84 page 1996 catalog, jam packed with the best values in test and measurement instruments available today!!!

CIRCLE 264 ON FREE INFORMATION CARD

VOICE CHANGERS!
ELECTRONIC KITS AND MORE!

ELECTRONIC KITS!

WE ACCEPT VISA, MC, MO, COD
SHIPPING & HANDLING EXTRA

BUY WITH CONFIDENCE FROM XANDI
• 30-DAY REFUND POLICY
• TECH SUPPORT NUMBER (602-894-0992)

- Powerful 2 stage audio amplifier.
- Tunes 88-108 MHz.
- Up to 1 mile range.
- Requires 9V battery. (Not incl.)
- Sensitive, picks up sounds at the level of a whisper.

SUPER-MINIATURE FM TRANSMITTER
Super small FM transmitter. Use with any FM broadcast receiver. Easy to assemble, all chip (SMT) parts are pre-assembled to the circuit board.
XST500 E-Z Kit $49.95

- Sensitive audio amplifier, picks up sounds at the level of a whisper.
- Tunes 88-108 MHz.
- Up to 1/2 mile range.
- Miniature photo battery mounts right on circuit board. (Included)

MICRO-MINIATURE FM TRANSMITTER
Including the battery, this is the Worlds smallest FM transmitter. Use with any FM broadcast receiver. Easy to assemble, uses pre-assembled circuit board.
XWB1000 E-Z KIT $46.95

- Up to 1/2 mile range.
- Miniature photo battery mounts right on circuit board.
- Transmits at 143 MHz.
- Amazing audio sensitivity, picks up sounds at the level of a whisper.

CRYSTAL CONTROLLED FM TRANSMITTER
Including the battery, this is the Worlds smallest crystal controlled FM transmitter. Transmits to any scanner type receiver. Easy to assemble, uses pre-assembled circuit board.
XTL1000 E-Z KIT $69.95

- Transmits a continuous beeping tone.
- Transmits at 143 MHz.
- Up to 1 mile range.
- Works with most any scanner type receiver.

TRACKING TRANSMITTER
Only 0.75 by 1.8 inches including the battery, the XTR300 is ideal for use in locating lost model rockets, bicycles, automobiles, games of hide and seek, and contests.
XTR300 E-Z Kit $79.95

- Dial your phone from anywhere and listen to the sounds inside your home.
- Two digit Touch Tone code for secure operation.

TELEPHONE SNOOP
The latest in home or office security. Call home from anywhere, enter a two digit security code, and hear the sounds in your home . Automatically turns on without ringing the phone, verifies code, then activates for one and a half minutes.
XPS-CASE KIT $13.95
XPS1000 C KIT $55.95

- Smallest Phone transmitter anywhere!
- Tunes 88-108 MHz.
- Up to 1/4 mile range.
- Attach to phone line anywhere in house.
- No batterie required, powered by phone line.

SUPER-MINIATURE PHONE TRANSMITTER
Worlds smallest FM phone transmitter. Use with any FM broadcast receiver. Easy to assemble, all chip components are pre-assembled to the circuit board.
XSP250 E-Z Kit $34.95

- **Professional quality.**
- Uses new Microwave Integrated Circuit amplifier.
- **Not a kit**, ready to use.
- Covers 1 to 2,000MHz.
- Adjustable sensitivity.
- Audio jack for privacy ear phone.

SUPER SENSITIVE BUG DETECTOR
Any intercepted signal causes an audio tone that increases from a low pitched growl to a high pitched squeal as you get closer to the source of the signal.
XBD500 ..... $149.95

- Use with any FM broadcast receiver.
- Hear every sound in an entire house!
- Up to 1 mile range.
- Powerful 2 stage audio amplifier.

MINIATURE FM TRANSMITTER
The XFM100 has a super sensitive microphone and is capable of picking up sounds at the level of a whisper and transmitting them to any FM broadcast receiver.
XFM100 C Kit $21.95

- Digital voice changing: male to female, female to male, adult to child, child to adult.
- Anonymity on any call.
- Button for normal operation.
- 16 levels of voice masking.

VOICE CHANGING TELEPHONE
STOP THOSE ANNOYING TELEPHONE CALLS!
Sound older and tougher when you want to. Not a kit. Fully assembled. Single phone operation only.
TRANSITION 2000 ..... $99.95

- Digital voice changing: male to female, female to male, adult to child, child to adult.
- Use with any modular phone.
- 16 levels of voice masking.
- Connects between handset and phone.

VOICE CHANGING ACCESSORY
STOP THOSE ANNOYING TELEPHONE CALLS!
Sound older and tougher when you want to. Not a kit. Fully assembled. Use with single or multi-line phones.
TRANSITION 2001 ..... $69.95

- Uninterrupted coverage of 800 to 950 MHz.
- Works with any scanner that can receive 400 to 550 MHz.

800-950 MHz SCANNER CONVERTER KIT
If your scanner can receive 400-550 MHz, just add the XLC900 for ***uninterrupted*** 800-950 MHz coverage. It converts all 800-950 MHz signals down to 400-550 MHz so your scanner can receive them! Add our custom case kit for that "Professional" look.
XLC-CASE KIT $13.95
XLC900 C KIT $49.95

- Transmit high quality stereo to any FM stereo receiver.
- Built-in output level monitor for quick and easy tuning.
- Ideal for use with personal CD player.

FM STEREO TRANSMITTER
Transmit full-bodied Hi Fi stereo to any FM stereo receiver. Separate left and right inputs and gain controls. Includes an output booster stage for greater range.
XFS-CASE KIT $13.95
XFS108 C KIT $39.95

XANDI ELECTRONICS, INC. Serving the public since 1981
1270 E Broadway Rd. # 113, Tempe AZ 85282

TOLL FREE ORDER LINE: 1-800-336-7389
FAX LINE: 1-602-731-4748
ASK FOR A CATALOG OF ALL OF OUR PRODUCTS

SEND MAIL ORDERS TO: XANDI ELECTRONICS BOX 25647 TEMPE, AZ 85285-5647

CIRCLE 281 ON FREE INFORMATION CARD

AT LAST! DC-20 MHz SYNTHESIZED PERFORMANCE FOR ONLY $795!

- DC-20 MHz, .1 Hz resolution, DC offset
- Linear/Log Sweep
- Dualtone Generation
- Internal/External AM
- Internal/External FSK
- Internal/External FM
- Burst
- Internal/External PM
- DTMF Generation
- Internal/External SSB
- DTMF Detection
- Internal/External BPSK
- Power Level Measmt

$795 Quantity 1 Made in U.S.A.

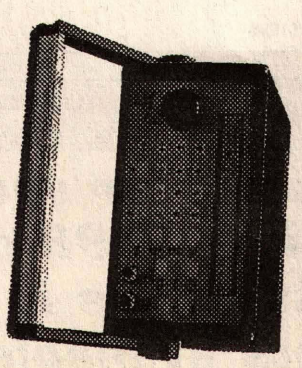

The SG-100 gives you .1 Hz synthesized precision and a wide diversity of modulation functions all of which can be performed using an internally generated or externally applied signal. You also get signal analysis functions that are just not offered on any other signal source such as DTMF Detection and Power Level Measurement. And because you can download new instrument functions to Flash memory, you can ensure that your SG-100 will never become obsolete.

The SG-100 is available NOW and is ready to turn your engineering bench into a real powerhouse!

C.O.D. P.O.

Telulex Inc.
2455 Old Middlefield Way S, Mountain View, Ca. 94043 (415) 938-0240
Fax: (415) 938-0241 http://www.telulex.com email:sales@telulex.com

CIRCLE 328 ON FREE INFORMATION CARD

386 SBC $83

OEM (1K) PRICE
INCLUDES:
- 5 SER (8250 USART)
- 3 PAR (32 BITS MAX)
- 32K RAM, EXP 64M
- STANDARD PC BUS
- LCD, KBD PORT
- BATT. BACK. RTC
- IRQ0-15 (8259 X2)
- 8237 DMA 8253 TMR
- BUILT-IN LED DISP.
- UP TO 8 MEG ROM
- CMOS NVRAM

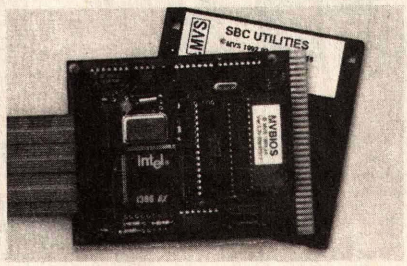

USE TURBO C, BASIC, MASM RUNS DOS AND WINDOWS
EVAL KIT $295

$95 SINGLE PIECE PRICE
UNIVERSAL PROGRAMMER
- DOES 8 MEG EPROMS
- CMOS, EE, FLASH, NVRAM
- EASIER TO USE THAN MOST
- POWERFUL SCRIPT ABILITY
- MICROCONT. ADAPTERS
- PLCC, MINI-DIP ADAPTERS
- SUPER FAST ALGORITHMS

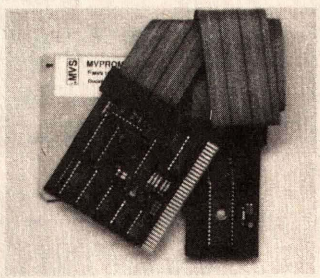

OTHER PRODUCTS:

8088 SINGLE BOARD COMPUTER	OEM $27	*95
PC FLASH/ROM DISKS (128K-16M)	21	75
16 BIT 16 CHAN ADC-DAC CARD	55	195
WATCHDOG (REBOOTS PC ON HANGUP)	27	95

*EVAL KITS INCLUDE MANUAL BRACKET AND SOFTWARE.
5 YR LIMITED WARRANTY
FREE SHIPPING
HRS: MON-FRI 10AM-6PM EST

MVS MVS BOX 850 MERRIMACK,NH (508) 792 9507

ALL ELECTRONICS CORPORATION

QUALITY PARTS

FAST SHIPPING

DISCOUNT PRICING

CALL, WRITE, FAX or E-MAIL For A Free 64 Page CATALOG. Outside the U.S.A. send $2.00 postage.

"HI-8" VIDEO CASSETTE (USED)

ATTENTION CAMCORDER USERS!

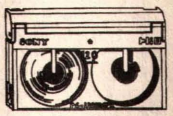

SONY Hi-8
Top quality, metal particle 120 minute video cassettes. Used for a short time, then bulk-erased. Each cassette has its own plastic storage box. Satisfaction Guaranteed.

$3.00 each

CAT # VCU-8

10 for $28.00 • 100 for $250.00

RANGE 20 METERS (65.6 FEET) INDOOR/OUTDOOR PHOTOELECTRIC SWITCH

SICK Optex # WS/WE260-M230
Invisible infrared beam and switch is useful for a variety of security, safety and sensing applications such as perimeter alarms, electric gate or garage door controls or conveyor line sensing. Modulated beam covers a 20 meter distance even with poor visibility. IP-66 enclosure rating makes it dust proof and splash resistant, suitable for most outdoor conditions. Light/dark switching selector. Sensitivity adjustment control. LED power and sense indicators. Two position cable entry gland (90 deg. apart) accepts 1/2" threaded conduit and a variety of wire sizes. Glass fiber-reinforced plastic housings are 3.05" x 2.5" x 1". Supply voltage: 22-240 Vac. Solid State Output: 0.5 amp (must have load to operate). Includes mounting brackets and hardware. UL and CSA listed.

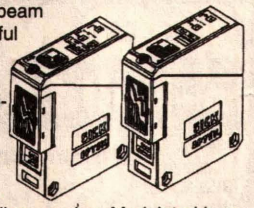

CAT # PES-4 ***NEW LOWER PRICE!*** **$35.00 each**

MAGNETIC CARD READER

Magtek# 21045002
Credit card or ID card magnetic strip reader consists of break-resistant plastic card guide with decoder pc board and head. Head is mounted on spring steel strip which keeps it pressed against the card surface. Terminated with a socket connector at the end of 5 color-coded leads.
3.57" X 0.9" X0.95"

CAT# MCR-2 **$6.00 each**

FLASH ASSEMBLY

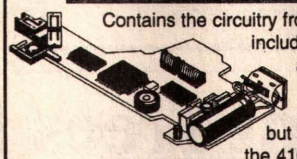

Contains the circuitry from a camera including the flash assembly. We have no hook-up information, but we're sure that the 410 uf, 300 volt photo-flash capacitor, flash tube and trigger transformer are worth the price. 4.5" X 2.7" X 0.8" h.

$2.00 each **CAT# FSH-4**

10 for $15.00

ULTRA-BRIGHT LED

Rohm # SLA-580MT-E49 T-1 3/4
GREEN, water clear in off state. 500+ mcd @ 2.1 v, 16ma.
CAT# LED-33 **2 for $1.00**

100 for $40.00 • 1000 for $300.00

FAX/MODEM LINE PROTECTOR

Ora Electronics # MP700
Protects against data interruptions and eavesdropping of private conversations when fax machine, modem or phone shares a line with other similar devices. Easy to install. Plugs inline between wall jack and telephone line. Requires one for each instrument sharing the same line.

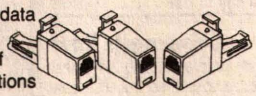

$3.00 per package of 3 devices **CAT # MP-700**

THERMOELECTRIC COOLER PELTIER JUNCTIONS

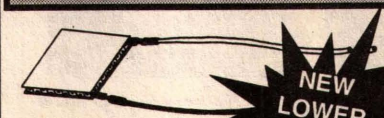

NEW LOWER PRICING

These incredible miniature solid state heat pumps raise or lower temperature in a small area almost instantly. Utilizing the Peltier effect these modules perform the same cooling or heating functions as freon based refrigerators but they do it with no moving parts, and are very reliable. Current applied to the device will produce heat on one side and cold on the other side, up to 68° C difference between the two sides. Modules can be mounted in parallel to increase the heat transfer effect or can be stacked to achieve high differential temperatures. 127 thermocouples per device. Operates on 3-12 Vdc. Requires a heatsink to prevent overheating.

Two sizes available.

1.18" (30 mm) square
X 0.15" (3.8 mm) thick.

$17.00 each **CAT# PJT-1**
5 for $75.00

1.57" (40 mm) square
X 0.15" (3.8 mm) thick.

$26.00 each **CAT# PJT-2**
5 for $110.00

Quantity Pricing Available!

SPECIAL SALE! METAL OXIDE VARISTOR

Harris / GE # V130LA20B or equivalent
130 Vac nom. 70 Joules .
Peak pulse current: 6,500 amps.

$1.00 each **CAT# MOV-130-20**

100 for $75.00

ORDER TOLL FREE 1-800-826-5432

MAIL ORDERS TO:
ALL ELECTRONICS CORP.
P.O. BOX 567
VAN NUYS, CA 91408-0567

FAX (818) 781-2653 • INFO (818) 904-0524
http://www.allcorp.com/
E-MAIL allcorp@allcorp.com

NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D • Shipping and Handling $5.00 for the 48 Continental United States - ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.

CIRCLE 214 ON FREE INFORMATION CARD

SHOW TIME CABLE

The Best in Cable
CONVERTERS & DESCRAMBLERS

Take a LOOK at the exciting new *Prelude!*

Just $339!

We work hard to be the Low Cost Leader! Shop the rest, then call us to compare. We guarantee you, no other reputable firm can beat our prices!

COD • Master Card • Visa • Amex • Discover

Show Time Cable • 643 N. 98th Street, Ste. 260 • Omaha, NE 68114

Your Low Price Leader!
Order By Phone, Fax, or Mail
800-643-4258

ABC ELECTRONICS 315 7TH AVE N. MPLS. MN. 55401
(612)332-2378 FAX (612)332-8481 30 DAY WARRANTY
WE BUY TEST EQUIPMENT AND COMPONENTS.

TEK 453 50 MHZ OSCILLOSCOPE	$200.00	TEK 7844 400MHZ O-SCOPE FRAME	$400.00
TEK 475 200 MHZ OSCILLOSCOPE	$500.00	TEK 485 350 MHZ OSCILLOSCOPE	$600.00
TEK 7633 100MHZ STORAGE O-SCOPE FRAME	$300.00	TEK 7623 100MHZ STORAGE O-SCOPE FRAME	$300.00
TEK 7104 1GHZ O-SCOPE	$2750.00	TEK 7403 60 MHZ O-SCOPE FRAME	$150.00
(7104 INCLUDES 7A29,7A29,7B10,7B15)		TEK 7603 100 MHZ O-SCOPE FRAME	$150.00
TEK 7704A 250 MHZ O-SCOPE FRAME	$200.00	AVEX SCOPE PROBE 100MHZ X1/X10 NEW	$35.00
TEK 465B 100MHZ O-SCOPE	$450.00	HP 8601 110MHZ SWEEP/SIGNAL GENERATOR	$350.00
FLUKE 37 3.5 DIG DMM	$100.00	FLUKE 5205A POWER AMPLIFIER	$2500.00
BECKMAN PPS-100 30VDC 3.5 AMP P-SUPPLY	$350.00	HP 8012A PULSE GENERATOR	$400.00
RACAL-DANA 1991 160MHZ COUNTER IEEE	$500.00	TEK J16/J6503 LIGHT METER	$300.00
TEK 2235 100MHZ O-SCOPE	$650.00	TEK 2246 100MHZ 4CH. O-SCOPE	$1500.00
TEK 465B 100MHZ 0-SCOPE	$450.00	TEK DAS 9100 W/PROBES	$750.00
TEK 475A 250MHZ O-SCOPE	$600.00	HP 1651A LOGIC ANALYZER	$1500.00
LEADER LBO516 100MHZ O-SCOPE	$300.00	HP 3453A 3.5 DIGIT MULTIMETER	$100.00
HP 141T/8553B/8552B SPEC.ANLZ.	$1500.00	HP 141T/8554B/8552B SPEC.ANLZ.	$1500.00
GENRAD 1657 RLC BRIDGE	$750.00	HP 8016A WORD GENERATOR	$300.00
GENRAD 1658 RLC BRIDGE	$900.00	TEK 7B53 100 MHZ TIME BASE	$75.00
TEK 7A26 200 MHZ DUAL TRACE PLUG IN	$75.00	TEK 7B80 400 MHZ TIME BASE	$100.00
TEK 7A24 400 MHZ DUAL TRACE PLUG IN	$200.00	TEK 7B85 400 MHZ TIME BASE	$125.00
TEK 7B92 500 MHZ TIME BASE	$125.00	TEK 608 MONITOR	$650.00
WAVETEK 175 WAVEFORM GEN.	$300.00	WAVETEK 157 PROG.WAVEFORM SYN.	$300.00
FLUKE 540B TRANSFER STANDARD	$1000.00	FLUKE 8010A DMM	$100.00
HP 3581A WAVE ANALYZER	$300.00	HP 5359A TIME SYNTHESIZER	$1000.00
GENRAD 1396B TONE BURST GEN.	$200.00	SENCORE LC53 CAP-IND.METER	$400.00
AVCOM PSA-35A SPEC. ANALYZER	$1000.00	BOONTON 9200	$400.00
PHILLIPS PM5519G PAL TV GENERATOR	$1000.00	TEK 7D20 PROGRAMABLE DIGITIZER	$400.00
DRANETZ 626 DISTURBANCE ANALYZER	$1500.00	TEK 577 D1 /177 CURVE TRACER	$1500.00
FLUKE 8505A 6.5 DIG. DMM	$250.00	KRONE-HITE 3202 FILTER	$300.00
SYSTRON-DONNER HR60-8C	$300.00	EMI SCR300-3 POWER SUPPLY	$300.00
NJE S-325 2500VDC-10MA POWER SUPPLY	$300.00	HP432A/478A POWER METER	$300.00
PTT 5100 TELEPHONE SIMULATOR	$500.00	PTT 5151 IMPAIRMENTS SIMULATOR	$500.00
PTT 5000 MODEM TEST SET	$500.00	HP 6286A 0-20VDC/10APOWER SUPPLY	$500.00

Plant Trees for America™

TACTICAL ELECTRONICS

Plans • Ready-to-Use • Easy-to-Build Kits

3 Mi Voice Transmitter
• Ultra-Sensitive Mike
• Crystal Clear
• Tunes 80-130 MHz.
FMV1K Kit/Plans $39.50

3 Mi Telephone Xmitter
• Tune-able 80-130 Mhz • Undetectable
• Only transmits when phone is used
VWPM7K Kit/Plans $39.50

Extended Play Telephone Taping System
• Tapes Phone Conversation • Extends Tape X4 • Check Local Laws before using!
TAP30X Ready to Use $84.50

3 Mi Tracker Transmitter
• Tunable Output
• Uses FM Radio
• Excellent Signal Beacon
HOD1K Kit/Plans $39.50

Window Bounce Laser Listener
Aim at window and listen to sounds from reflected light. CAUTION - Not for illegal use. LWB3 Plans $10.00
LWB30 Ready to Use (req's vid tripod) $199.50

Telephone Line Grabber Infinity Transmitter
Use any Tone phone to monitor a premises, access other calls or control up to 8 devices! TELCON1 Plans/Kit .. $99.50
TELCON10 Ready to Use $149.50

Cybernetic Ear!
Enhances normal hearing 3-4 times! Adjustable volume control, fits easily into either ear. Many, many uses.
CYBEREAR Ready to Use $19.95

Invisible Pain Field Intruder Deterrent
System detects intrusions and turns on a sonic field of pain, causing disorientation, acute paranoia, nausea and more. The perpetrator - man or animal - soon vacates! Protects 4 individual areas up to 5000 sq ft. Non hazardous when used as instructed.
PPG4K Kit/Plans $129.50
PPG40 Ready to Use $199.50

Control Their Minds!
Programmable audible and visual stimuli induces hypnotic trances.
HYP2K Kit/Plans $29.95
#EH2 Book of Hypnosis $14.95

Long Range Microphone
24" dish focuses signals to an ultra-high gain amplifier. Parabolic dish to BUG Mother Nature and more!
PM5K Kit/Plans $149.50
• Optional wireless module transmits captured sounds to an FM radio.
WM5K Kit for Wireless Option $29.50

FireBall Gun
Shoots flaming ball - two shot capacity. Great for special effects and remote fire starting. *CAUTION REQUIRED!*
FIREBALL Plans (dangerous product) . $10.00

See In Total Darkness!
• High Quality IR Night Vision Scope with IR illuminator. SD10 Ready to Use ... $199.50

FANTASTIC BRIGHTNESS!
High Quality Laser Pointer
LAPN67 15mw equv, 1500' $39.50
LAPN63 30mw equv, 3000' Price on Req

1000' Potato Cannon
Not a Toy! Uses electronic or piezo ignition. CAUTION REQUIRED!
POT1 Plans (dangerous product) ... $10.00

Phasor Sonic Blast Pistol
Rids areas of unwanted pests. Trains and conditions wild and domestic animals. Great for barns, attics, cellars, gardens.
PPP10 Ready to Use ..... $ 69.50

Shocker Force Field /Vehicle Electrifier
Make hand and shock balls, shock wands and electrify objects. Great payback for those wiseguys!
SHK1K Easy to Assemble Kit $19.50

Electric Charge Gun
Life is Precious - PROTECT IT! Stuns/immobilizes attackers 15 feet away! Check your state laws for legality. More knockdown power than most handguns. No permanent injury. ID coded.
ECG1 Data (Creditable to purch) $10.00
ECG10 Charge Gun, Ready to Use, *includes FREE Stun Gun!* $249.50

STUN GUNS - sold separately:
STUN100 100,000 Volts $34.50
STUN200 200,000 Volts $49.50

VISIT US ON THE WEB!
http://www.amazing1.com

INFORMATION UNLIMITED
Dept ENS-2, Box 716, Amherst, NH 03031
Phone: 603-673-4730 FAX: 603-672-5406
MC, VISA, COD, Checks accepted Please add $5.00 S & H

CATALOG! FREE with Order or send $1 P&H

24 Hour Phone **800-221-1705** *Orders Only Please!*

LASERS

Pen & Pointer in One

- Four Times Brighter
- Mont Blanc™ Style Pen

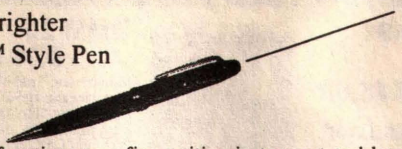

This laser pointer functions as a fine writing instrument and laser pointer all in one. The 650nm laser appeares four times brighter than standard laser pointers. Output power: 3.5 to 4.5 milliwatts. Includes batteries and gift box. One year warranty.

Cat. #: LPPEN **$57.00**

FREE CATALOG

- Helium-Neon
- Argon
- Semiconductor
- Ruby
- Scanners
- Lightshow Equipment

30 Day Satisfaction Guarantee.

Midwest Laser Products
P.O. Box 262, Frankfort, IL 60423
Phone: (815) 464-0085 FAX: (815) 464-0767
Email: mlp@nlenx.com
VISA / MC Accepted
Please include $7.50 S&H within US. IL res. add 7.75% sales tax.

ACTIVE MICRO — We Want Your Excess Inventory

- INTEGRATED CIRCUITS
- MEMORY (NEW OR USED)
- EPROMS (NEW OR USED)
- CIRCUIT BOARDS
- DIODES
- TRANSISTORS
- LED'S

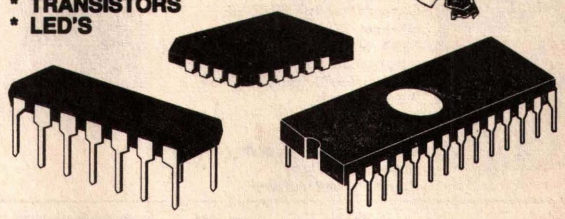

Tel 310-494-4851 Fax 310-494-4913
1891 Obispo Ave Signal Hill, CA 90804

CABLE TV NEW DESCRAMBLER PRODUCTS

Baseband Technology

SONIC-1 Replace ALL J*****, PIO, and S/A, Including Baseband
SONIC-TOC Replace ALL TOC. Including Fibre Optics and Baseband
SONIC-ZEN Replace Zen. Model ST 1600-2000

Limited Time Only! **$319.95**

Features

- VOLUME CONTROL
- Channel 2 or 3
- Last Channel Recall
- Parental Lockout
- Favorite Channel Memory
- New fiber Optic Technology

CALL **1-800-472-5632**
RJM Electronics
No Florida Sales!

It is not our intent to defraud any pay TV operator. Customers are required to limit the use of product to comply with State and federal laws regarding Cable TV.

Satellite TV 'BIBLE"

4th 'DIGITAL' edition

The aclaimed "bible" of satellite TV – ALL theTECHNICAL DETAILS –

- Operation, installation & troubleshooting of analog and digital satellite systems
- The transition from analog to digital TVRO

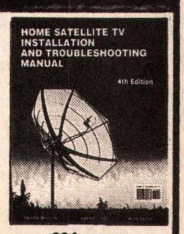

1-800-483-2423
TO ORDER
or for a FREE books/software/video CATALOG

324 pages
8-1/2" x 11"
$30 plus $4 s/h

BAYLIN publications
1905 Mariposa, Boulder, Colorado 80302, USA
Telephone: 303-449-4551 FAX: 303-939-8720

HOME AUTOMATION

Largest Selection of Home Automation in The World!

Computer Control of Your Home!

- Lighting
- Audio/Video
- Security Systems
- Video Surveilliance
- Phone Systems
- Heating/Cooling
- Pet Care Automation

Widest Range of X-10 Devices

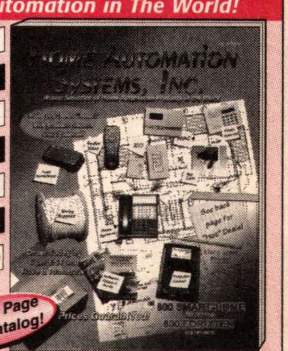

FREE 72 Page Color Catalog!

HOME AUTOMATION SYSTEMS, INC.
151 Kalmus Dr., Ste. L4
Costa Mesa, CA 92626
Questions: 714-708-0610
FAX: 714-708-0614

Call 800-SMART-HOME
24 Hours 800-762-7846
E-mail: catalog@smarthome.com
http://www.smarthome.com/smarthome

Don't lose sight of Glaucoma.

NATIONAL EYE HEALTH EDUCATION PROGRAM

ALFA ELECTRONICS

HIGH QUALITY TEST EQUIPMENT
BEST PRICE

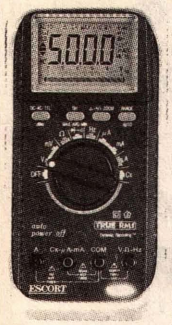

DMM 89 $179.00

Most Advanced DMM

All Purpose & Communication

-80.7 to 81.4 dBm with 4Ω–1200Ω
20 reference impedances
True RMS
Frequency counter: 0.01Hz-10MHz
Capacitance: 1pF-50,000µF
Measure AC volt to 20kHz
5000 counts, 0.1% accuracy
Auto/manual range, fast bar graph
Min/Max/Ave/DH/Relative/Zoom
Auto power off
Input warning
Splash proof
Volt, amp, ohm, logic, diode, continuity
Ruggedized case
Rubber holster included

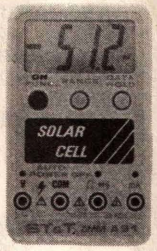

DMM A91

~~$49.95~~

NOW $45.00

Plus Free Case

Solar Cell Powered
Large Display

Diode, Continuity
Volt, Amp, Ohm
Data Hold
Auto power off
7 functions, 19 ranges
3.5 Digit, 0.6% accuracy
Auto/Manual ranging
Energy saver
Student & hobbyist's favor

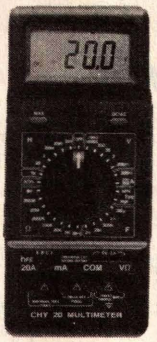

DMM 20 $74.95

Inductance: 1µH-40H
Capacitance: 1pF-200µF
Frequency: 1Hz-20MHz
Volt, amp, ohm, diode,
20 Amp AC/DC current
Transistor HFE
Continuity, duty %
Peak hold/Max
Ruggedized case
Rubber holster $8.00

Full line of DMMs, economy, compact, ruggedized, solar cell, automotive, heavy duty, industrial, starts from $19.95

Fluke Multimeter	
Fluke 12	$84.95
Holster C-10	$10
Fluke 70 II	$75.95
Fluke 73 II	$97.50
Fluke 75 II	$129
Holster C-70	$16
Fluke 77 II	$155
Fluke 79 II	$175
Fluke 29 II	$175
Fluke 76	$175
Fluke 87	$287
Fluke 867	$1199
Fluke 97 Scope Meter	$1785
Fluke 105 Scope Meter	$2799

LCR Meter 131D $229.95

Most Advanced LCR

Dual display:L/Q or C/D
Inductance: 0.1µH-1000H
Capacitance:0.1pF-10,000µF
Impedance:1mΩ-10MΩ
0.7% basic accuracy
Auto/manual range
Dissipation factor & Q factor
Serial & parallel mode
Relative mode for comparison and to remove parasitics
Statistics, tolerance,
Best for design, incoming testing & production
SMD and chip component test probe $25.00

LCR Meter 814 $189.95

Best Resolution LCR

Inductance: 0.1µH-200H
Capacitance: 0.1pF-20,000µF
Resistance: 1mΩ-20MΩ
1% basic accuracy
Dissipation factor indicates leakage in capacitor and Q factor in inductor
Zero adjustment to reduce parasitics
Best for high frequency RF
SMD and chip component test probe $25.00

LIMITED QUANTITY SPECIAL
DIGITAL LCR 680 $74.95
0.1pF, 1µH, 10mΩ resolution

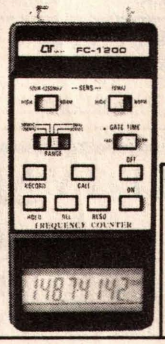

Frequency Counter FC-1200 $129.95

Frequency:0.1Hz-1.25GHz
Display: 8 digit LCD
Period: 0.1µs-0.1s
Records Max/Min/Average
Data hold, relative mode
Telescoping antenna $8.00
Deluxe case $5.00

Also Available:
AC/DC clamp meter,Light meter, Thermometer, pH meter, High voltage probe, Digital caliper, Anemometer, Electronic scale, Force gauge,Tachometer, Stroboscope, Humidity & EMF adapter, Sound level meter, Frequency counter, SWR/field strength/power meter, Dip meter

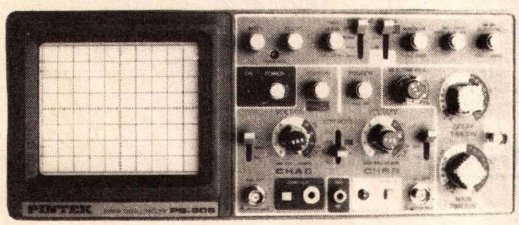

20 MHz Oscilloscope with Delay Sweep PS-205 $429.95

Dual Trace, Component test, 6" CRT, X-Y Operation, TV Sync, Z-Modulation, CH2 Output, Graticule Illum, 2 probes each has x1,x10 switch. Best price with delay sweep.

PS-200	20 MHz DUAL TRACE	$339.95
PS-400	40 MHz DUAL TRACE	$494.95
PS-405	40 MHz DELAY SWEEP	$569.95
PS-605	60 MHz DELAY SWEEP	$769.95
PS-1000	100 MHz DUAL TRACE	$999.95

Scope Probe: 60MHz x1, x10 $15, 100MHz x1, x10 $22
250MHz x1, x10 $29, 250MHz x100 $39

Digital Storage Scope

DS-303 30MHz, 20M Sample/sec $849.95

DS-303P with RS-232 interface $1,049.95

Switchable between digital and analog modes
2 K word per channel storage
8 bit vertical resolution (25 Lerel/div)
Expanded Timebase 10ms/div - 0.5 s/div
Refresh, Roll, Save all , Save CH2, Pre-Trig
Plotter control

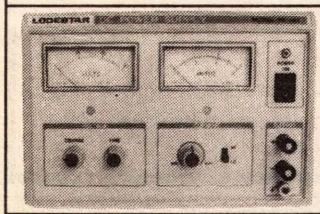

DC Power Supply PS-303 $159.00

0-30 VDC , 0-3A output

Constant voltage & constant current mode
0.02% + 2mV line regulation
0.02% + 3mV load regulation
1 mVrms noise and ripple
Short circuit and overload protected
PS-8200 with digital voltmeter $179.00
Also available: 30V/5A, 60V/3A, 60V/5A 16V/10A, 30V/10A

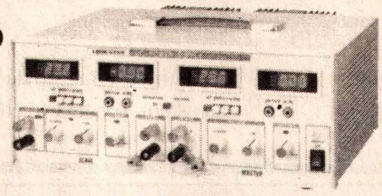

DC Power Supply Triple Output PS-8202 $499.95

Two 0-30 VDC , 0-3A outputs
One fixed 5VDC, 3A output
Capable of independent or tracking operation
Constant voltage and constant current mode
Four digital meters for volt and current display
Excellent regulation and low ripple
Short circuit and overload protected
Also available: 30V/5A triple output $549.95
Dual tracking 30V/3A, 30V/5A, 60V/3A, 60V/5A

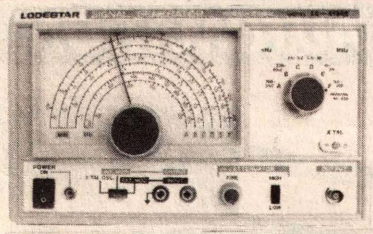

RF SIGNAL GENERATOR SG-4160B $124.95

100 kHz-150MHz sinewave in 6 ranges
RF Output 100mVrms to 35 MHz
Internal 1kHz, External 50Hz-20kHz AM modulation
Audio output 1 kHz, 1 Vrms

RF SIGNAL GEN./COUNTER SG-4162 AD $229.95

Generates RF signal same as SG-4160B
6 digit frequency counter 1Hz - 150 MHz for internal and external source Sensitivity <50mV

AUDIO GENERATOR AG-2601A $124.95

10Hz - 1MHz in 5 ranges
Output: 0-8Vrms sinewave
0-10Vp-p squarewave
Synchronization: ±3% of oscillation frequency per Vrms
Output distortion:
0.05% 500Hz - 50kHz
0.5 % 50Hz - 500kHz
Output impedance: 600 ohm

AUDIO GEN./COUNTER AG-2603AD $229.95

Generates audio signal same as AG-2601A
6 digit frequency counter 1Hz-150MHz for internal and external sources Sensitivity <50mV

FUNCTION GENERATOR FG-2100A $169.95

0.2 Hz -2 MHz in 7 ranges
Sine, square, triangle, pulse and ramp
Output: 5mV-20Vp-p
1% distortion, DC offset ± 10V
VCF: 0-10V control frequency to 1000:1

FUNCTION GEN/ COUNTER FG-2102AD $229.95

Generates signal same as FG-2100A
Frequency counter 4 digits
Feature TTL and CMOS output

SWEEP FUNCTION GEN./COUNTER $329.95

0.5Hz to 5 MHz in 7 ranges
Sweep: Linear 10:1/Log 10:1 20ms to 2s
AM Modulation
Gated Burst, Voltage Control Generator
Generator Control Voltage & 6 digit counter
1Hz-10MHz for internal & external sources

ALFA ELECTRONICS
741 Alexander Rd., Princeton, NJ 08540

(800) 526-2532/(609) 520-2002
FAX:(609) 520-2007
Visa, Master Card, American Express, COD, Purchase Order Welcome

15 DAY MONEY BACK GUARANTEE. 1 YEAR WARRANTY
CALL OR WRITE FOR FREE CATALOG

CIRCLE 213 ON FREE INFORMATION CARD

INSTEK®

Test & Measuring Instruments

ISO 9002 CERT. #934163

100 MHz Cursor Readout Scope
4 ch, 8 traces OS-6101 $1,499.95

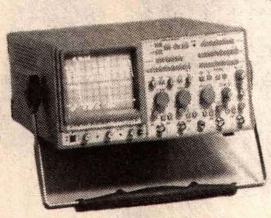

* 4 independent channels, 8 traces
* Time /Voltage cursor measurement
* ALT triggering function for 4 ch.
* Sweeps to 2ns/div, Delayed Sweep
* TV Sync., Ch. 1 output, Z-axis input
* 2 probes(x1, x10)

100 MHz Scope, 4ch. 8 traces
Best value all purpose scope
OS-6100B $1,329.95

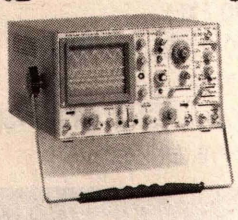

* 4 channels, 8 traces
* High sensitivity 500μV/div
* Sweeps to 2ns/div, Delayed sweep
* 20 kV accelerating voltage
* TV sync., Z-axis input
* A and B gate output
* Best price 100 MHz scope
* 2 probes(x1, x10)

50 MHz Triggering Oscilloscope
OS-653 $699.95

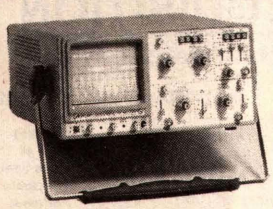

* Dual Channel
* Hold Off Function
* Delayed Sweep
* Built-in Delay Line
* TV Sync
* ALT Triggering
* High sensitivity 1 mV/div
* Trigger level lock function
* Z-axis input, CH1 output
* 2 probes(x1, x10)

20 MHz Oscilloscope
OS-622B $344.95

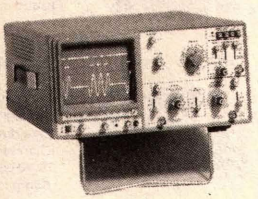

* Dual trace, X-Y operation
* TV Sync., Z-axis input,CH 1 output
* High sensitivity 1 mV/div
* Trigger level lock
* 2 probes (x1, x10)

OS-623B - 20 MHz w/Delayed Sweep.....$ 449.95
OS-935 - 5 MHz One channel.....$ 209.95

DC Linear Power Supplies
Single Output

* Constant voltage and constant current mode
* Voltage regulation ≤0.01%
* Current regulation ≤0.2%
* Low ripple and noise
* Overload and reverse polarity protection
* Features 2 analog or 1 digital meter(PS series)
  2 analog or 2 digital meters(PR series)

PS-1830 : (0-18V, 0-3A).....$209.95
PS-1830D : Digital Display.....$219.95
PS-1850 : (0-18V, 0-5A).....$219.95
PS-1850D : Digital Display.....$244.95
PS-3030 : (0-30V, 0-3A).....$224.95
PS-3030D : Digital display.....$254.95
PS-6010 : (0-60V, 0-1A).....$209.95

PR-1810H : (0-18V, 0-10A).....$349.95
PR-3060 : (0-30V, 0-6A).....$314.95
PR-6030 : (0-60V, 0-3A).....$314.95
PR-6030D : Digital Display.....$399.95

Triple Output DC Power Supplies

* Two variable 0-30VDC, 0-3A outputs
* One fixed 5VDC, 3A output
* Auto tracking
* Auto serial and parallel operation
* Constant voltage and constant current mode
* Continuous/dynamic load can be selected
* Features 4 analog or 2 digital displays

PC-3030 : (0-30V, 0-3Ax2).....$499.95
PC-3030D : Digital display.....$549.95

Programmable DC Power Supplies

* High stability , low drift, 4 digit display
* Front/rear output-sense switch selectable
* Auto step running w/timer settings
* 100 point programmability (PPS series)
* 50 point programmability (PPT series)
* Auto serial and parallel operation (PPT series)
* Auto tracking (PPT series), IEEE-488.2 and SCPI compatible command set (optional)

PPS-1860G: (0-18V, 0-6A).....$1099.95
PPS-3635G: (0-36V, 0-3.5A).....$1099.95
PPS-6020G: (0-60V, 0-2A).....$1099.95
PPT-1830G: (0-18V, 0-3Ax2, 0-6V, 0-5A).....$1399.95
PPT-3615G: (0-36V, 0-1.5Ax2, 0-6V, 0-3A).....$1399.95

Digital Display Function Generator
FG-8016G $239.95

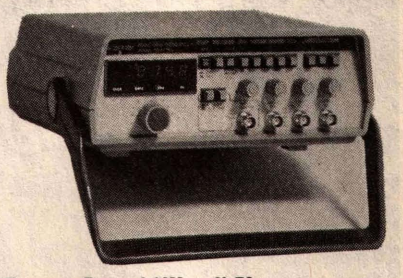

* Frequency Range: 0.02Hz to 2MHz
* Three Instruments in one: Function generator, Pulse generator & Frequency counter.
* Sine, Triangle, Square, TTL Pulse and CMOS output
* Built-in 6 digit counter with INT/EXT function
* 1000:1 tuning range
* Variable DC offset control

FG-8015 Function Generator
* 0.02Hz-2MHz (No Counter).....$189.95
FC-8131 Intelligent Counter 1.3GHz.....$469.95
FC-8270 Intelligent Counter 2.7GHz.....$629.95
UC-2010G Universal Counter.....$294.95

Digital Multimeter & C Meter
DM-8034(3½ digits) $179.95

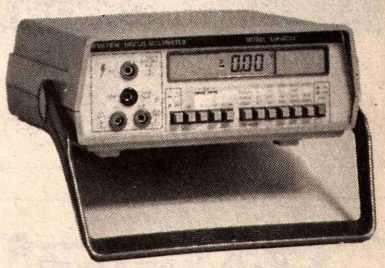

* 8 Function, AC/DC voltage, AC/DC current, resistance
* Built-in C meter, diode test and audible continuity check
* High voltage 1000V and 20A range
* 0.5% basic accuracy

DM-8040 (3¾ Digits, True RMS)
* Measures ACV to 50 kHz.....$339.95
DM-8055 (5½ Digits).....$649.95
* 0.006% basic accuracy
* 1μV, 1mΩ, 1nA resolution
* dBm measurement
* Auto range, relative mode, Max/Min
DM-8055G(5½ Digits, GPIB).....$889.95

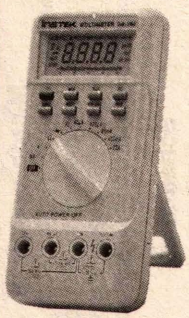

Model DM-392
(3¾ digits) $109.95

* Auto/Manual ranging(38 ranges)
* 42 Segment analog bar graph
* Data Hold/Min-Max memory /Relative mode
* Auto power off
* Overload protection
* Audible continuity check /diode test
* Capacitance: 1pF-40μF
* Frequency: 0.1Hz-1MHz
* 20 Amp range
* Double high energy fused (1A, 20A)
* 0.3% DCV accuracy

DM-351 : 3½ Digits w/Continuity, Auto Off.....$54.95
DM-352 : 3½ Digits, Cap. Freq. hFE, 20 Amp.....$79.95
DM-353 : 3½ Digits, Cap. Freq. Temp. hFE.....$84.95
DM-391 : 3¾ Digits, Auto, Cap. Freq. Min/Max....$99.95
DM-392 : 3¾ Digits, Hold, Min/Max 20Amp.....$109.95
DM-393 : 3¾ Digits, Peak, Logic, hFE, Freq.....$119.95

ALFA ELECTRONICS
741 Alexander Rd., Princeton, NJ 08540

(800) 526-2532/(609) 520-2002
FAX:(609) 520-2007

15 DAY MONEY BACK GUARANTEE. 2 YEAR WARRANTY
CALL OR WRITE FOR FREE CATALOG AND QUANTITY DISCOUNT.
Visa, Master Card, American Express, COD, Purchase Order Welcome

CIRCLE 213 ON FREE INFORMATION CARD

$449.95 **Device Programmers** $139.95

$9^{1/2}$ x $5^{3/4}$ x $1^{1/4}$ **EMP-20**

- Easy to use software, on-line help, full sceen editor
- **Fast Programming** (EMP-20)
  27C010A, 23 seconds
  28C020, 34 seconds
  27C040, 95 seconds
- **Made in USA**
- 1 Year Warranty
- Technical Support by phone
- 30 day Money Back Guarantee
- FREE software upgrades available via BBS
- Demo SW via **BBS (EM20DEMO.EXE) (PB10DEMO.EXE)**
- **E(e)proms** 2716 - 8 megabit, 16 bit 27210-27240, 27C400 & 27C800,
- **Flash** 28F256–28F020, (29C256–29C010 (EMP-20 only))
- **Micros** 8741A, 42A, 42AH, 48, 49, 48H, 49H, 55, 87C51, 87C51FX, 87C751,752
- **GAL, PLD** from NS, Lattice, AMD-**16V8, 20V8, 22V10** (EMP-20 only)

PB-10 Internal Card for PC

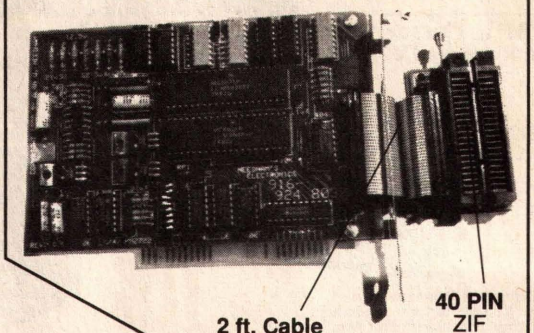

FOR MORE INFORMATION CALL

4630 Beloit Drive, Suite 20
Sacramento, CA 95838
(Monday-Friday, 8 am-5 pm PST)

NEEDHAM'S ELECTRONICS, INC.

MasterCard C.O.D. VISA

(916) 924-8037
BBS 916-924-8094
FAX 916-924-8065

CIRCLE 257 ON FREE INFORMATION CARD

Advanced Circuit Designs will...

PALs
Test all functions and write code to perform the same task.

GALs
Extract out the exact same fuse map, depending on the manufacturer and type.

Microprocessors
Extract out the exact same code for PIC, 16C54, 16C55, 16C56, 16C57, and 16C84.
Extract out the exact same code for Motorola 68705 series (U3, U5, R3, R5, P3, P5), 80993, and 68HC705C8.
ACD also works with Intel, AMD, and other microcontrollers not listed.

Schematics
Design/layout schematics, and generate printed circuit board gerber files for projects.

Call about our secure integrated circuit readers!
ACD can also provide additional resources for populating your circuit boards.

Disclaimer: ACD works with copywritten secured devices only when the copyright holder is the customer. ACD also works with secured devices that have not been copywritten.

Call TODAY for a price quote!
(703) 764-5361
please leave a message

ACD Advanced Circuit Designs, Inc wwwww

5765-F Burke Centre Parkway, Suite 317, Burke, Virginia 22015 (703) 764-5361

DATA ACQUISITION
and Control Hardware for PC's

ANA100 Analog I/O ..... $ 99

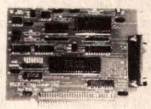

* 8 Channel 8-Bit
* 0 to 5 Volt Input
* 14 TTL I/O lines
* Analog Output
* 400KHz Sampling

DIG100 Digital I/O ..... $ 39

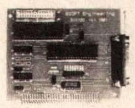

* 8255 PPI
* 24 or 48 TTL I/O Lines option
* Selectable Base Address

ANA150 Analog/Counter... $ 89

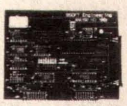

* 8 Channel 8-Bit 0 to 5 Volt input
* 3 16-Bit Counters
* 400KHz Sampling

DIG200 Counter I/O ..... $ 79

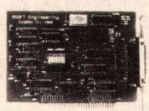

* 3 16-Bit Counters
* 8 TTL Input lines
* 8 TTL Output lines
* Selectable Clock Frequency input

ANA200 Analog I/O ..... $ 79

* 1 Channel 12-Bit 0 to 5 Volt input optional bi-polar
* 100KHz / 300KHz Sampling rate
* 24 TTL I/O lines

ANA201 Analog ..... $ 129

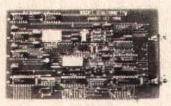

* 8 Channel 12-Bit
* x1, x5, x10, x50 Programmable Channel gain
* 100KHz/300KHz Sampling rate

Engineering Software - PC/MSDOS

Easy-PC Professional XM - Integrated Electronics cad system, Schematic Capture, Circuit Analysis, and PCB Design in one software package ..... $ 399.00

PC-SCOPE - Digital Storage Oscilloscope, 1, 2, 4, or 8 Channel Capture and Data Display. Works with ANA100, ANA150, and ANA201 Boards .....$ 39.00

MasterCard/Visa orders accepted
More hardware and software items available, Call for information or
See our catalog on the internet: http://www.bsof.com
E-mail: sales@bsof.com

BSOFT Software, Inc.

Phone 614-491-0832 * Fax 614-497-9971
444 Colton Road * Columbus, OH * 43207

Miniature Transmitters and Receivers

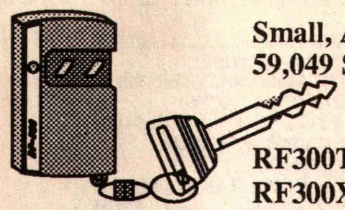

Small, Attractive, High End Quality, 2 Channel 318 MHz Transmitter
59,049 Settable Codes, 120'–300' Range, 1–1/4" x 2" x 9/16", Assembled

		Qty 1	5	10
RF300T	150' Range Transmitter	24.95	19.95	15.95
RF300XT	300' Range Transmitter	29.95	24.95	19.95

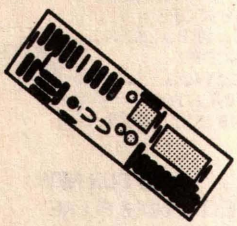

Small, High End Quality, 2 Channel Receiver for the RF300 Transmitters
1–1/4" x 3–3/4" x 9/16" PCB w/ .1" spaced pads for standard connectors
Input: 8–24 vdc Output: Gated CMOS Momentary and Latching Lines

		Qty 1	5	10
RF300R	Receiver, Fully Assembled	24.95	20.95	16.95
RF300RK	Receiver, Complete Parts Kit	19.95	15.95	12.95
RF300PA	Pre–Amplifier. Doubles Range	14.95	11.95	9.95

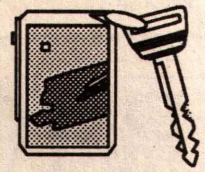

Small, Economical, Single Channel Transmitter and Receiver Set
Set Code, 60' Range, 1–7/8"x2–3/8"x7/16" (T), 2"x2–3/4"x9/16" (R)
Receiver Input: 5 vdc Output: Gated TTL Momentary Line

		Qty 1	5	10
RF60	Transmitter and Receiver Set	24.95	19.95	14.95

Add $ 4 shipping for first item + $ 1 for each additional item. Ca. residents add 8.25% tax
Visa, Mastercard, Money Orders Personal Checks and Cash C.O.D.s

Visitect Inc.

P.O. Box 14156 Fremont, CA. 94539 (510) 651–1425 Fax (510) 651–8454

CIRCLE 322 ON FREE INFORMATION CARD

New and Pre-Owned Test Equipment

Goldstar

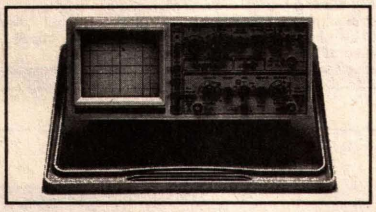

Model OS-9100P ⟶ $899.00

Full 100 MHz Bandwidth!

- Dual-Channel, High Sensitivity
- TV Synchronization Trigger
- Calibrated Delayed Sweep
- Includes Two Probes, 2 Year Warranty

FREE SHIPPING! ON GOLDSTAR EQUIPMENT ANYWHERE IN THE U.S. Excluding AK & HI

BK PRECISION MAXTEC INTERNATIONAL CORP. **Model 4040 $499.00**

20 MHz Sweep/Function Generator

- 0.2 Hz to 20 MHz, 5 digit LED Display
- AM & FM Internal or External Modulation
- Sine, Square, Triangle, TTL, CMOS Outputs
- Burst Operation
- External 30 MHz Frequency Counter

NEW!

Pre-Owned Oscilloscope Specials

B+K Precision 1476 10 MHz $229.00
Great Starter Scope!

Tektronix 465	100 MHz	$629.00
Tektronix 465B	100 MHz	$749.00
Tektronix 475	200 MHz	$849.00
Tektronix 475A	250 MHz	$929.00

- The Industry Standard of Oscilloscopes
- Dual Channel, Calibrated Delayed Sweep
- Professionally Refurbished
- Aligned & Calibrated to Original Specifications
- 6 Month Warranty - The Longest Available!

LOWEST PRICES EVER!

NEW FLUKE MULTIMETERS & TEKTRONIX OSCILLOSCOPES

The Industry Standard in Multimeters
Model 79 II ..$172.00 Model 87 ..$285.00

NEW!
TEKTRONIX TDS SERIES ON SALE!

Test Equipment Depot

A FOTRONIC CORPORATION COMPANY

1-800-996-3837

P.O. BOX 708 Medford, MA 02155

VISA MasterCard AMEX C.O.D. **TOLL FREE 1-800-99-METER** (617) 665-1400 • FAX (617) 665-0780

CIRCLE 318 ON FREE INFORMATION CARD

TEST EQUIPMENT SALES

customer satisfaction #1 priority !

WE BUY SURPLUS EQUIPMENT

ANRITSU MS96A...OPTICAL SPEC.ANALYZER...$5995

HP 3776B-001-004....PCM TERMINAL TEST SET...$1295
(UNUSED IN HP BOX)

TEK 2465.....300 MHz 4 CH. SCOPE.....$2950

TEK 2445.....150 MHz 4CH. SCOPE.....$1950

TEK 2465B.....400 MHz 4 CH. SCOPE.....$6695

TEK 2252....100 MHz PROGRAMMABLE SCOPE...$2795

HP 8112A.....50 MHz PULSE GENERATOR.....$4495

HP 3325A.....SYNTH./FUNC. GENERATOR.....$1995

TEK 7L5.....SPECTRUM ANALYZER P/I.....$1495
(INCLUDES L3 MODULE)

TEK 7104.....1 GHz SCOPE MAINFRAME.....$2695

TEK 577 D2.....CURVE TRACER.....$1295
(WITH 177 TEST FIXTURE)

TTC FIREBERD 2000 COMM. ANALYZER..$2995
(W/ CASE AND 5 INTERFACES)

TEK 2235.....100 MHz 2 CH. SCOPE.....$1095

NEW TEKTRONIX SCOPES W/ 3 YEAR MFG. WARRANTY !!

TEK THS 720...100 MHz 500MS/s HANDHELD SCOPE & DMM.....$2195

TEK TDS 340.....100 MHz 500 MS/s SCOPE W/DIGITAL REAL TIME & FFT $2695

TEK TDS 420A.....200 MHz 4 CH. SCOPE W/ DRT, FFT & DISK DRIVE.....$6295

FLUKE 45.....DUAL DISPLAY BENCHTOP DIGITAL MULTIMETER.....$679

MC & VISA ACCEPTED

NEW SCOPES IN STOCK

P.O. BOX 986
LONDONDERRY, NH 03053

PHONE (800) 684-4651
FAX (603) 425-2945

ASK ABOUT OUR NEW TEKTRONIX & FLUKE PRODUCTS

Weeder Technologies

Electronic KITS!

Call for FREE CATALOG!

From $29 to $55

Pro-Kit™

PO Box 421, Batavia, OH 45103

513-752-0279

Home Automation

Connects between a TW523 and an RS-232 serial port. Use your PC or Mac to receive and transmit all X-10 commands. Create your own program to control your home automation system, turning on/off any device plugged into an electrical outlet with responce to time/date, other X-10 transmissions or any other computer input stimuli.

Caller ID / RS-232

Connects between a telephone wall jack and an RS-232 serial port. Decodes the caller ID data sent over the phone line and sends it to your PC or Mac, in a pre-formatted ASCII character string. Create your own program to log the name, number, date, and time of all incoming calls.

Telephone Call Restrictor

Connects to telephone wall jack. Disables all phones on the line if attempting to either: dial a number that has been stored in memory "Block" mode or, dial a number that has not been stored in memory "Allow" mode. Use touch-tone phone to enter telephone numbers into memory, and choose mode. Program from any phone on the line using your password.

50 MHz Frequency Counter

Reads frequency from 1Hz to 50MHz and displays up to 7 digits on a 16x1 character LCD display. Auto-range feature provides floating decimal point and automatically affixes the correct suffix (Hz, KHz, or MHz). Microcontroller based provides for very small parts count, only 2" x 3" big.

Telephone Scrambler

Scrambles your voice before sending it over the telephone line. Prevent eavesdropping from an extension or tap. Connects between your telephone and wall jack. No modifications are required to your telephone. Full duplex operation.

IR Remote Control Receiver

Learns and records the data patterns emitted by standard infrared remote controls used by TVs, VCRs, Stereos, etc. Lets you control all your electronic projects with your TV remote. Seven individual I/O pins can be assigned to any button on your remote, and can be configured for either "toggle" or "momentary" action.

Vocal Filter

An audio device which can be used with a home component stereo system to filter out the main vocal sound track from standard stereo recordings (CD, tape, record or FM), leaving the background music to sing along with. Produce your own karaoke tapes from your personal library.

DTMF Decoder/Logger

Keep track of all numbers dialed or entered from any phone on your line. Connects to your telephone wall jack. Decodes all 16 touch-tones and displays them on an LCD display. Holds the last 240 digits in a nonvolitile memory. Scroll through and view all telephone numbers dialed, credit card numbers entered, etc.

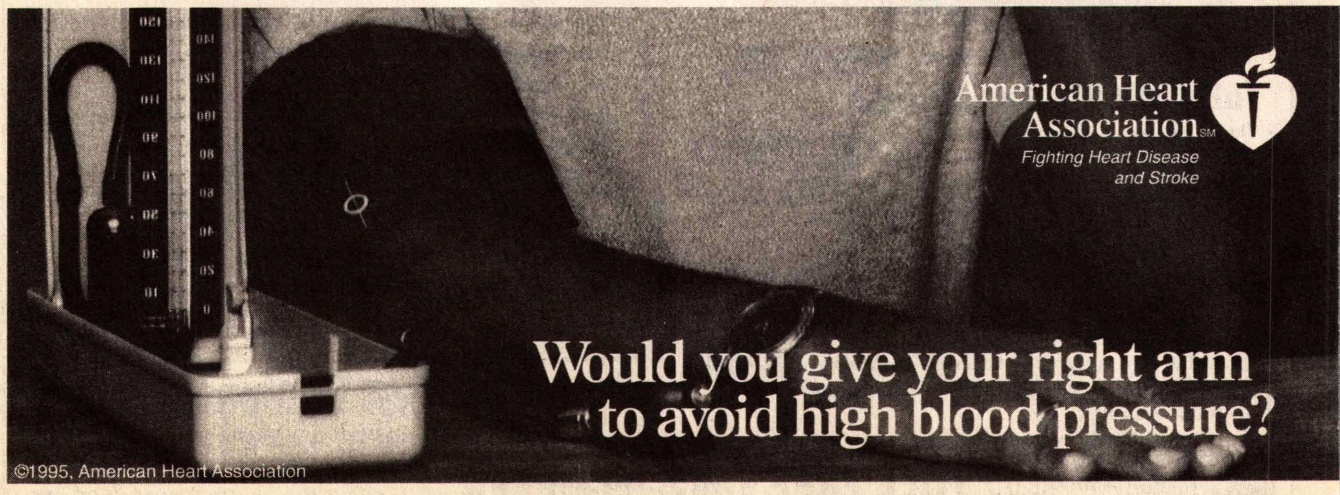
American Heart Association℠
Fighting Heart Disease and Stroke
Would you give your right arm to avoid high blood pressure?
©1995, American Heart Association

Cellular Extensions

from

"THE CELLULAR EXPERTS"

Motorola 3 Watt Bag from $225.
Nec P120 12oz. Portable $299.
Motorola PT 550 10oz. "Flip" Phone $399.

Others available, buy new from us, or send us your phone.
Get a second or third phone with no additional monthly charges!
Motorola, NEC, Panasonic, Audiovox and many others!

Fax Back Hotline, For 24hr. info. call from your FAX (714) 581-7460 or call

(800) 457-4556

Nationwide paging available. C.G.C. Dealer inquires welcome.

Move Up to the Ultimate in Robotic Kits.

OWIKIT™

OWI's "Next Generation" of affordable, rugged Robot Kits challenge the enthusiast to solder circuit boards and mechanically assemble.

Each OWIKIT also incorporates the basic principles of robotic experiments, sensing and locomotion, guaranteeing an exciting, hands-on adventure of knowledge and fun!

Visit our homepage @ http://www.owirobot.com

But remember! OWI is the recognized founder and leader in Educational Robot Kits. ACCEPT NO IMITATIONS.

EDUCATORS • HOBBYISTS • ENGINEERS

EK ELEKIT

1160 Mahalo Place, Suite B
Rancho Dominguez, CA
90220-5443

(310) 638-7970
Fax: (310) 638-8347

NEW ROBOT.TECH.CURR.	**MV-RTC**	**Teacher's Manual**	**158 Pg. Book**	**74.95**
S-CARGO	**OWI-936K**	**Sound Sensor**	**47 Pg. Book**	**29.95**
WAO II	**OWI-961K**	**Programmable - Graphic**	**59 Pg. Book**	**69.95**
SPIDER	**OWI-962K**	**Infrared Sensor**	**49 Pg. Book**	**49.95**
LINE TRACKER	**OWI-963K**	**Infrared Sensor**	**48 Pg. Book**	**49.95**
MANTA	**OWI-966K**	**Sound / Touch Sensor**	**44 Pg. Book**	**29.95**
MOON WALKER	**OWI-989K**	**Solar Sensor**	**10 Pg. Book**	**34.95**

MasterCard VISA

Order M - F: 8a.m. - 4p.m. PST

CIRCLE 327 ON FREE INFORMATION CARD

Throbbing Modems

by **Joshua Bagby, of *Penthouse* fame!**

The reviews tell it all: this is the #1 book on cyber-intimacy! 290 pages, November 1995, $17.95 ***NEW!***

ULTIMATE Scanner

Bill Cheek's 3rd book on scanner mods is just terrific! Enter the 21st century with the mad modmaster. 242 pages, highly illustrated, large format, 1995, $29.95

EMERGENCY RADIO!

Scanning the news *as it happens*

by Norm Schrein, "Mr. Scanner," President of the Bearcat Radio Club
214 pages, $14.95

TravelScan

Good Frequencies Across America

Henry Eisenson **(FINALLY!)**
150 pages, 1/96, $9.95

NEW (1/96)
Great reviews!

Smart Casino Gambling
Olaf Vancura, PhD
364 pages, $24.95

Cheating at Blackjack, **SQUARED**
Dustin D. Marks
208 pages, $24.95

S/h $4 1st book, then $2 ea.
CA add tax.

✔ our WWW site!

INDEX Publishing Group, Inc.
3368 Governor Dr., Suite 273S
San Diego, CA 92122
Fax orders: (619) 552-9050
Toll free orders: 800-5466707
www.electriciti.com/~ipgbooks
e-mail: ipgbooks@indexbooks.com

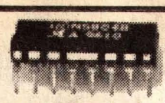

STEPPER MOTOR DRIVER IC

UCN5804. Drives a unipolar stepper in one of three operating modes: single phase, two phase or half step. Up to 1.25 Amps per phase. Step and direction input. Drive with a 555 oscillator, parallel port, etc. Build your own robot turntable for model trains, anything that requires precision positioning.

931002 **$4.50 each**

• Above, packaged with 5V stepper motor (92M010) and schematics.

931003 **$9.95 each**

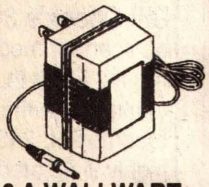

9 VDC 1.0 A WALLWART

Center positive coaxial connector.

96E009 **$5.95 each**

Send $2.00 for our Latest Catalog!

$4.00 Foreign. Refundable on First Order.

ALLTRONICS

2300-D Zanker Road • San Jose, CA 95131

Voice (408) 943-9773 • Fax (408) 943-9776

World Wide Web: http://www.alltronics.com

On-Line Ordering: (408) 943-0622

030996 14400-N-8-1-24 Hrs.

It's Here!!!

PBASIC* Compiler

Put BASIC Stamp I programs directly into your PIC - no BASIC Stamp necessary!

Creates editable assembler source and hex files for use with any PIC programmer.

Introductory price $99.95

❖ Pocket PIC Programmers from $34.95

❖ PICProto prototyping boards $9.95-$19.95

*BASIC Stamp and PBASIC are trademarks of Parallax, Inc.

microEngineering Labs

Box 7532 Colorado Springs CO 80933

(719) 520-5323 FAX 520-1867

PROGRAMMERS OVER 50 MODELS

ADVANTECH EETOOLS NEEDHAMS DATA I/O ICE TECHNOLOGY HILO SYSTEM GENERAL CHROMA MODULAR CIRCUIT TECHNOLOGY XELTEK

PROMAX EMP-20 MEGAMAX MEGAMAX4 SIMM/SIP TESTER EMUPA

CALL ADVANTECH LABTOOL	629 EETOOLS SIMMAX
689 ICE TECH MICROLV	795 CHROMA SIMM/SIP
669 EETOOLS ALLMAX +	350 MOD-MCT-EMUPA/R
429 EETOOLS PROMAX	279 MOD-MCT-EMUP/R
439 EETOOLS MEGAMAX	49 EPROM 1G TO 512K
539 EETOOLS MEGAMAX4	79 EPROM 1G TO 1MEG
429 XELTEK SUPERPRO II	99 EPROM 4G TO 1MEG
529 XELTEK SUPERPRO II P	199 EPROM 16G TO 1 MEG
269 XELTEX SUPERPRO L	99 EPROM 1G TO 8MEG
179 XELTEK ROMMASTER II	129 EPROM 4G TO 8MEG
479 MOD-MCT-EMUPA	250 EPROM 8G TO 8MEG

LABTOOL48 MICROMASTER SUPERPRO ALLMAX PLUS ROMMASTER2

General Device Instruments

Sales 408-241-7376 Fax 241-6375 BBS 983-1234

Web www.generaldevice.com E-Mail icdevice@best.com

BUGGED??

EAVESDROPPING is unbelievably widespread! Electronic Devices with amazing capabilities can be monitoring your telephone and room conversations RIGHT NOW! Are you sure you're safe? **FREE CATALOG tells you fast!** Includes Free Bonus details on fantastic opportunities now open in Counter-Surveillance field. Exciting, immensely interesting and EXTREMELY profitable (up to $250 hr) full/part-time income. Call Now! 1-800-732-5000

Prototype it..... FAST!

with ProtoQuick 8051 or Z8

- Complete single board computers
- Up to 32K EPROM and 8K RAM
- 12 sq. in. plated-through proto area
- RS232 C serial port w/ DB25 conn.
- Op. sys. in EPROM w/ source code
- Assembled, ready to run - 5v. only
- MS-DOS cross-assembler included

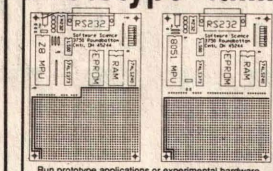

ProtoQuick Z8 and 8051

$99.00 each

Run prototype applications or experimental hardware from the serial port - **WITHOUT PROGRAMMING!**

Software Science

Software Sciences 3750 Roundbottom Road Cincinnati, OH 45244 USA

(513) 561-2060

"6-WAY COPY CAT $1495.00*"

ASK ABOUT EE3!

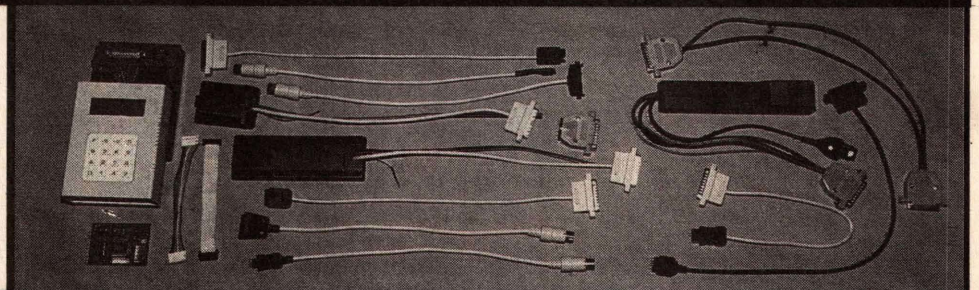

MENU#	PROGRAMS THE FOLLOWING PHONES	PRICE
1	MOTOROLA ONLY w/elite & 951C !!!	$1495
2	Above PLUS NEC P100-200-300-400-600-700	FREE
3	All of above PLUS SONY	FREE
4	All of above PLUS GE /Ericsson (newest mode)	FREE
5	All of above PLUS AUDIOVOX (does new 800!)	FREE
6	All of above PLUS MITSUBISHI/DiamondTel	FREE

Not a Kit! Full 5 year warranty! *Cables optional

All units are sold for EXPERIMENTAL AND EDUCATIONAL PURPOSES ONLY!

CALL US TODAY AT 770.973.8474 ..web page @ www.celltec.com

CIRCLE 305 ON FREE INFORMATION CARD

LASERS & ACCESSORIES

WE SPECIALIZE IN
Laser and Laser Related Surplus Inventory

HENE LASERS

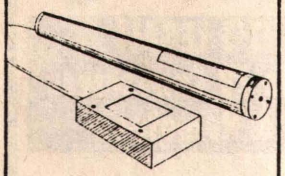

- Complete Systems
- Plasma Tubes
- Power Supplies

DIODE LASERS

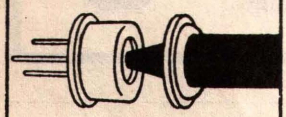

- Visible I/R
- Complete Modules
- Collimating Optics
- Drive Circuits

ACCESSORIES

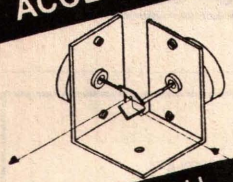

- Books
- Optics
- Electro-Optics

CALL FOR A FREE CATALOG!

We want your Laser related surplus items. Call or Fax us today for a quote!

MEREDITH INSTRUMENTS

P O Box 1724
5035 N. 55th Ave. #5
Glendale, AZ 85301

Phone: 602-934-9387
Fax: 602-934-9482

HTTP://WWW.MI-LASERS.COM

ACTUAL SIZE B&W CCD BOARD CAMERA
3.6mm Adjustable manual focus or 5.5mm pin hole lens
LATEST SONY HYPERHAD IMAGE SENSOR

PIN HOLE LENS ONLY NEEDS 1/16" HOLE TO SEE THROUGH
RESOLUTION: MORE THAN 380 LINES
MIN. ILLUMINATION: 0.4 LUX
SENSETIVE TO IR LIGHT
S/N RATIO: BETTER THAN 50DB (AGC OFF)
POWER: 9 - 13 VDC LESS THAN 150 MA
WILL RUN ON 9 VOLT BATTERY
BUILT-IN ELECTRONIC AUTO IRIS
SHUTTER SPEED : 1/60 - 1/50,000 SEC
VIDEO OUTPUT: 75 OHM, 2/1 INTERLACE
1.0 VOLT P/P COMPOSITE
CONNECTS TO ANY MONITOR OR VCR

1.5" SQ.
HIDE THIS CAMERA IN
PICTURES
SMOKE DETECTORS
THERMOSTATS
LAMPS
CLOCKS
RADIOS

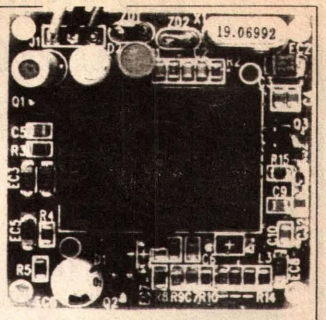

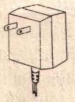

Plug in power supply $ 6.95

QTY	3.6mm	PIN HOLE
1-3	$ 115.00	$ 130.00
4-9	$ 110.00	$ 125.00

BC ELECTRONICS
1508 LEXINGTON • BEDFORD, TEXAS 76022
PHONE (817) 267-7792 FAX (817) 283-7797

REMEMBER, ONLY YOU CAN PREVENT FOREST FIRES.

A Public Service of the USDA Forest Service and Your State Forester.

Ad Council

The best replacement for all name-brand
CONVERTERS & DESCRAMBLERS

STARGATE INFINITY 3000!
A Revolution In Technology!

FREE DECODER UPGRADE!

The most advanced converter/descrambler available - offers what no other company can!

- 125 Channels (800 Mhz)
- Replaces all Major Cable Company Equipment
- 30-day Money-back, no questions asked Guarantee
- 1-Year Warranty
- Ask about our Extended Warranty Program
- Moved? Cable System Changed? No problem!
  We'll upgrade your Decoder for FREE

Visit our new Web Site - http://www.earthlink.net/~mdelectronics

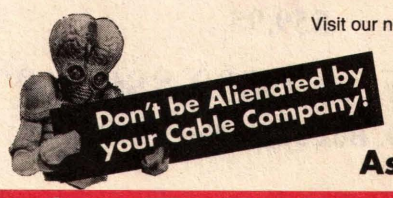

MD Electronics
5723 F Street • Omaha, NE 68117

Ask for your FREE Catalog TODAY!

1 800 624-1150

CIRCLE 304 ON FREE INFORMATION CARD

H-P AUDIO OSCILLATOR

HEWLETT-PACKARD 200CD OSCILLATOR, popular tube-type audio generator covers 5 Hz to 600 KHz in five bands; output 10 volts into 600 ohms or 20 V open circuit. Requires 115/230 VAC 50-400 Hz. 7"Wx10.8"Hx12.5"D, 20 lbs sh.
USED-CHECKED w/book **$125.00**

RADIATION DETECTOR

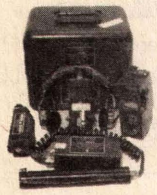

AN/PDR-63 RADIAC SET, military modular unit uses IM-226 module for 0-10-100-1000 rad/hour gamma detection, DT-507 low-range detector indicates 0-1-10-100-1000 mrad/hr and DT-508 0-500-5000 rad/hr plus simulates radiation absorption by human skin. Requires four AA batteries (not supplied). Set also includes ni-cad battery charger, headset, case, and manual; 15 lbs sh. **Used** **$185.00**

SCR & DIODES

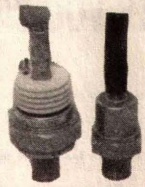

HIGH CURRENT COMPONENTS with pigtails but no mount hardware; Westinghouse/Power X mfg. Removed from equipment:
#SCR-135048Y, 1300 PIV 500 amp; 7" tail, 1lb. **$14.95**
#D-R610-0230, 200 PIV 300 amp; 4" tail ... **$ 8.95**
#D-18937300, 100 PIV 150 amp; 4" tail ..... **$ 3.75**

FIELD DAY KIT

AB-155 MAST KIT with eight self-stacking 66"Lx1.6" dia aluminum MS-44 mast sections to make 40 ft mast. Also four each rope guy lengths 31, 40, & 50 ft with clips; five guy rings, swivel base, six 15" stakes, and 2 lb hammer. 70 lbs sh. **UNUSED** ..... ~~$125~~ ... **$99.50**

MS-44 MAST SECTION only, aluminum 66"Lx1.4" dia; usable also as flag, tent, or volleyball net poles. **USED** ..... **$8.00 ea**

Prices F.O.B. Lima, O.• VISA, MASTERCARD Accepted.
Allow for Shipping • Write for latest Catalog
Address Dept. ES • Phone 419/227-6573 • Fax 419/227-1313

FAIR RADIO SALES
1016 E. EUREKA • Box 1105 • LIMA, OHIO • 45802

Tired of Paying Rent To Your Cable Company?

WHY RENT WHEN YOU CAN OWN? TAKE CONTROL OF YOUR TV!!!

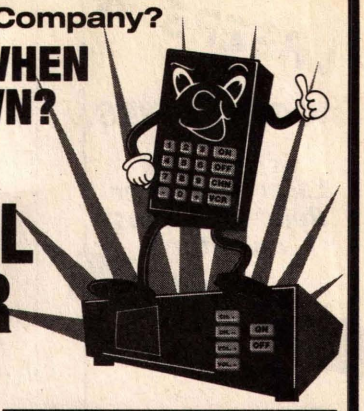

- **Over 5 Yrs. Experience**
- **Excellent Customer Service**
- **Prompt Delivery Anywhere**
- **Tell Your Friends About Us**
- **Call Today For Our LATEST SPECIALS!**

IT'S LEGAL! Cable TV Converters & Remotes

CALL TODAY!!!
1-800-228-2677
Mon. thru Fri. / 9 am-5 pm

VISA MasterCard

BOSS DISTRIBUTORS

The Electronic Experimenter's Journal
It's part catalog, part magazine and part data book with kits, parts, plans, articles, and application notes.
Call for your **FREE** copy today

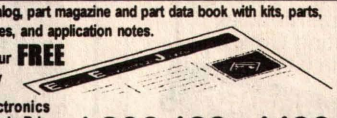

Debco Electronics
4025 Edwards Rd.
Cincinnati, OH 45209
1 800 423-4499

CABLE TV DESCRAMBLER KITS

Universal-New Product
This Product includes all the Parts, PC Board, Complete Schematic with Functional Guide. Generates Sync for most Video Applications.
$84.95

Tri-Mode Descrambler
This product includes all the parts PC Board and AC Adaptor. NO Enclosure included
$59.95

Universal 5000
Our fully assembled product is factory tested and GUARANTEED to work on your system.
$199.95

MasterCard

Call Toll Free 1-800-886-8699
M & G Electronics, P.O. Box 3310. No. Attleboro Mass. 02761

VISA

Anyone implying theft of Cable service will be denied assistance. NO MASSACHUSETTS SALES!

VIDEO SYNC GENERATOR

Restores Horizontal and Vertical Sync Lines from Distorted Analogue Video Formats

For Free Information Package on Completed Units and Pricing

• Call Toll Free •

1-800-236-5778

R.C. Distributing • PO Box 552 • South Bend, IN 46624

EZ-EP DEVICE PROGRAMMER - $169.95

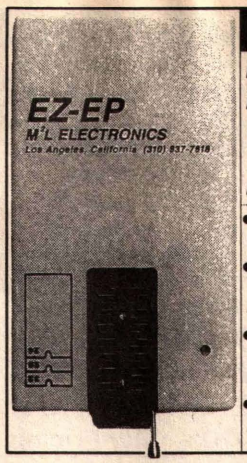

Fast - Programs 27C010 in 23 seconds.

Portable - Connects to PC Parallel Port.

Versatile - Programs 2716-080 plus EE and Flash (28F,29C) to 32 pins.

Inexpensive - Best for less than $200

- Correct implementation of manufacturer algorithms for fast, reliable programming.
- Easy to use menu based software has binary editor, read, verify, copy, etc. Free updates via bbs or web page.
- Full over current detection on all device power supplies protects against bad chips and reverse insertion.
- Broad support for additional devices using adapters.

Adapters Available

EP-51 (8751,C51)	$39.95
EP-11 (68HC11 E/A)	$59.95
EP-PIC (16C5x,61,62x,71,84)	$49.95
EP-PIC64 (16C62,63,64,65,73,74)	$39.95
EP-PEEL (iCT 22V10, 20G10, 18V8)	$59.95
EP-SEE (93x,24x,85x)	$34.95
EP-16 (16bit 40 Pin EPROMs)	$49.95
EP-49 (8742,48,49)	$49.95
EP-750 (87C750,751,752)	$59.95
EP-Z8 (Z86E03,04,05,06,07)	$39.95
EP-55 (8755)	$39.95
EP-51-PLCC (8751,C51)	$59.95
EP-PIC-SOIC(16C5x,61,62x,71,84)	$59.95
EP-PLCC (PLCC EPROMs)	$49.95
EP-SOIC (SOIC EPROMs)	$49.95
EP-LCC (LCC EPROMs)	$49.95

M²L Electronics

3526 Jasmine #4; Los Angeles, CA 90034

310/837-7818 Fax/BBS: 310/841-6050

http://www.cs.ucla.edu/csd-grads-gs3/loving/www/m2l.html

CA orders add 8.25% sales tax. Ground shipping - $5; 3 Day - $7; 2 Day $10; Overnight $17; COD $4.75.

ELECTRONIC SHOPPER

MEMBRANE SWITCH KITS!

FLAT PANEL KEYPADS ASSEMBLE IN MINUTES WITH YOUR LEGEND

AVAILABLE IN 4, 12, 16, 24 & 40 KEY TYPES

CONNECTOR AND BEZEL INCLUDED!

OPTIONAL "CLICKDOMES" AVAILABLE

DSK-4 $9.89

DSK-12 $14.29

INDUSTRIAL TYPES AVAILABLE

MORE THAN 30 LAYOUTS TO FIT MOST APPLICATIONS

CALL FOR FREE BROCHURE

SIL-WALKER

880 CALLE PLANO, UNIT N
CAMARILLO, CA 93012

PHONE: (805) 389-8100

FAX: (805) 484-3311

VISA / MASTERCARD

OCEAN STATE ELECTRONICS

MAKE CIRCUIT BOARDS THE NEW, EASY WAY WITH TEC-200 FILM

JUST 3 EASY STEPS:

- Copy Circuit pattern on TEC-200 film using any plain paper copier
- Iron film onto copper clad board
- Peel off film and etch

Convenient 8 1/2 x 11 size w/complete instructions

5 SHEETS	$6.25
10 SHEETS	10.75
20 SHEETS	16.25
50 SHEETS	33.50

DELUX CODE KEY

Adjustable, heavy duty brass base with ball bearing pivots. Designed for hard usage. 3/16" plated contacts.

$14.95

CODE PRACTICE OSCILLATOR & MONITOR

3" SPEAKER, HEADPHONE TERMINAL, VOLUME & TONE CONTROLS. USES 1 9V BATTERY.

Kit	$19.95
Wired	$24.95

VERNIER DIALS

1-1/2" Diameter 0-10 Marking	$10.95
1-1/2" Diameter 0-100 Marking	$14.95
2" Diameter 0-100 Marking	$15.95

REGULATED POWER SUPPLIES

13.8 VDC OUTPUT. 120 VAC INPUT. RATINGS ARE CONTINUOUS.

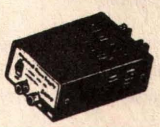

3 AMP	$29.50
5 AMP	39.50
6 AMP	46.50
10 AMP	59.50
20 AMP	129.50
30 AMP	139.50

SIGNAL INJECTOR/TRACER KIT

This handy tester is both a signal generator and receiver. As a generator use it to check out an amplifier, stage by stage. Also tests AM radio IF and RF stages. As a receiver you can pin point where a defective part exists. Will transmit and receive simultaneously.

$19.95

DIGITAL CAPACITANCE/ INDUCTANCE METER

DIGITAL LCR METER measures inductance, capacitance and resistance. At Last! An LCR meter that everyone can afford. Now you can measure coils, transformers, chokes from 1pH to 200H. Capacitors .1 pfd to 200 mfd and resistors from .1 ohms to 20 meg ohms. All in one handheld instrument.

LCR-1801 $119.95

LEARN COMPUTER THEORY BY BUILDING THIS KIT

DIGITAL TRAINER MODEL MM-8000

Starting from scratch you build a complete computer system. Our Micro-Master trainer teaches you how to write into RAMs, ROMs and run a 8085 microprocessor. You will write the initial instructions to tell the 8085 processor to get started and store these instructions in permanent memory in a 2816 E²PROM. Teaches you all about input and output ports, computer timers. Build your own keyboard and learn how to scan keyboard and display. No previous computer knowledge required. Simple easy to understand instruction teaches you to write in machine language. Upon completion of this course you will be proficient in computer technology.

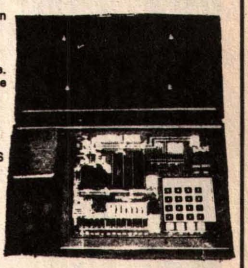

- Uses the 8085 Microprocessor
- Uses the 2816 E²PROM, electrically erasable programmable ROM
- Uses the 8156C, 2048 Bit static MOS RAM with I/O ports and timer
- Memory expandable option
- Built in 5V power supply
- 28 key keyboard
- Complete with lesson manual, instructions and experiments

$119.95

MAGNET WIRE

Enamel, coated solid copper. For winding coils, transformers and toroids. Prices for 1/4 lb. spools.

#14	$4.00	#20	$4.00	#28	$4.85	#36	$6.85
#16	4.00	#22	4.25	#30	4.85	#38	6.95
#18	4.00	#24	4.25	#32	4.85	#40	7.85
		#26	4.85	#34	6.25		

VARIABLE CAPACITORS

BROADCAST TYPE – 1/4" SHAFT

1 GANG 14-365 PF	$12.95
2 GANG 10-400/10-400 PF	$19.95

MANY MORE TYPES AVAILABLE FROM SMALL AIR TRIMMERS TO LARGE 4KV TUNER TYPE

SIGNETICS NE602AN $2.49
MINI-CIRCUITS SBL-1 $7.95

TOROIDS

IRON				FERRITE			
T-25-2	.35	T-50-6	.55	FT-37-43	.60	FT-82-43	1.00
T-25-6	.35	T-68-0	.75	FT-37-61	.60	FT-82-67	1.00
T-37-6	.45	T-68-2	.75	FT-37-77	.60	FT-82-75	1.00
T-37-12	.45	T-68-6	.75	FT-50-43	.75	FT-114-61	1.90
T-50-2	.55	T-80-2	.90	FT-50-61	.75	FT-140-43	3.15
T-50-3	.55	T-200-2	$5.00	FT-50-77	.75	FT-240-61	8.00

We stock a complete line of Toroids, Beads, and Ferrite Rods.

TO ORDER CALL 1-800-866-6626
OR
401-596-3080 FAX 401-596-3590

OR WRITE TO:
Ocean State Electronics
PO Box 1458
Westerly, RI 02891

Mail in orders please include $5 S/H
CANADA $12.00 – OVERSEAS $15.00
ALASKA & HAWAII $9.00
Minimum Order $10.00 (before shipping)
R.I. Customers Include 7% Sales Tax.

VISA MasterCard

CALL OR WRITE FOR FREE 120 PAGE CATALOG

CIRCLE 260 ON FREE INFORMATION CARD

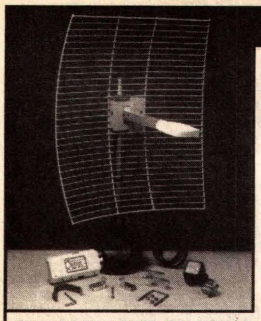

Quality Microwave TV Systems

WIRELESS CABLE - ITFS - MMDS
ATV - INTERNATIONAL - S-BAND
Amplifiers • Antennas • Books • Components
Filters • Systems • Video Products

- RF Frequency 1990 - 2700 MHz
- Cable Ready - VHF - UHF Outputs
- SASE For "FREE" Catalog or Send $1

PHILLIPS-TECH ELECTRONICS
PO Box 8533 • Scottsdale, AZ 85252

CHALLENGER SYSTEM
33-Channel 52dB+ Gain
Complete Grid $265
Five Year Warranty
FREE SHIPPING

ORDER LINE 800-880-MMDS
CATALOG / INFO 602-947-7700
FAX LINE 602-947-7799
Visa • M/C • Amx • Disc • COD's • Qty Pricing

CIRCLE 310 ON FREE INFORMATION CARD

NEW!! Checker 12 *E* Monitor tester

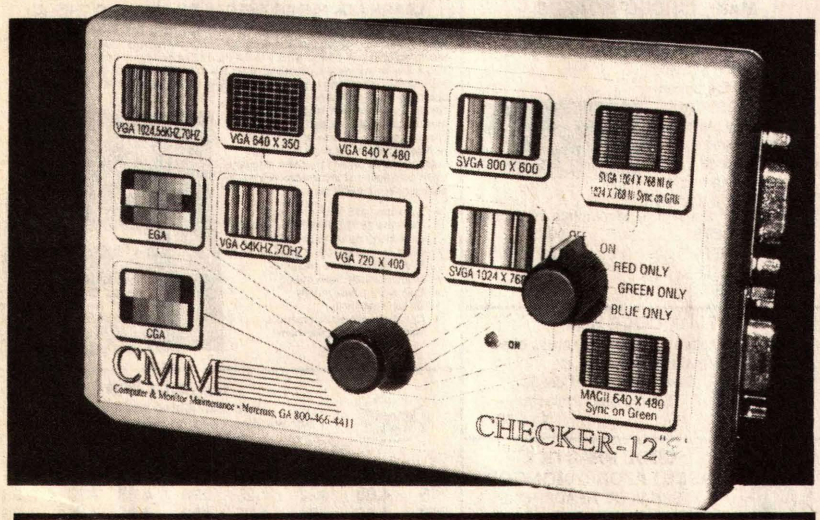

COLOR BARS, GRAY SCALE & SWEEPS TO 64 K hz!!!!!!

The "**Checker 12**" is an **easy to operate**, hand held , battery, or AC operated computer color monitor pattern generator. With its support of CGA(15.75khz), EGA(22khz), MACII(35khz), and VGA modes 1,2,3 (31.5khz), 800X600(35khz), **1024X768** interlaced. (35khz), **1024X768 non-interlaced**, & **1024X768NI *with sync on Green*** (48khz), **++ 2 NEW VGA MODES>>> 56 kHz x 70 Hz & 64 kHz x 70 Hz.** With its' single mode switch, you know exactly what type of monitor you are testing. Its' front panel color pictures, show just what you should be seeing on the monitor under test. You can quickly tell if the monitor is a VGA, SVGA, or a SVGA/NI. guessing. The "Checker 12" provides various test patterns for VGA monitors. X-hatch, for size and linearity and convergence set-up. White screen, for purity and CRT burn evaluation. Color bars and **8 step gray scale** for color tracking and balance. There is also a single color mode that allows for single color channel operation.

Price: $339.00 + $5.00 S&H.

Includes battery, AC adapter, Mac adapter and **1 year** warranty
(upgrade your Checker 12 to a 12 *E* for $49, call for details)
Please call about our other monitor test products, and offers,or vist our Webb site.

MasterCard VISA

CMM
Computer & Monitor Maintenance
6649 Peachtree Ind., Blvd., Suite N-1 • Norcross GA 30092
1-800-466-4411, 770-662-5633 (Voice), 770-840-8814 (Fax)
We're on the WEBB at http:/www.computermonitor.com

CIRCLE 336 ON FREE INFORMATION CARD

OUR LOWEST PRICES!

Global Specialties Is On The Move!

Affordable Spectrum Analyzer

Convert any oscilloscope to a full blown sprctrum analyzer.
• .4mHz to 1000 mHz high accuracy (1.5 dB
• -70 dBm to 0dBm dynamic range

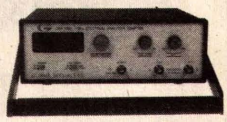

model #GSA1000.....869.95

1.3 GHz Hand Held Frequency Counter

• 5Hz-1300 mHz freq. & period measurements .0001 mHz resolution

model #5003.....219.95

Triple Power Supply (Lab Quality)

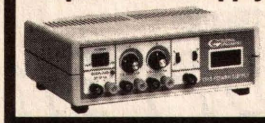

• +5VDC Plus two 1.2-20VDC @ 250MA

#1310 149.95

Call For Free! 40 Page Catalog

PinholeCamera

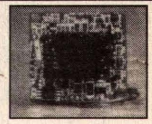

- Requires 1/16" opening size
- 1-1/2" x 1-1/2" x 7/8"
- Power 7.5-12VDC n • .8 lux
- 3.8mm lens included
- 380 lines resolution

12V DC Power Supply **9.95**

model #CVC50PH 139.95

Protek Test Equipment

20 MHz Oscilloscope
Dual Trace w/ Component Checker

#P3502C Dual Trace **375.95**
#P2510 100 MHz 3 Ch. 8 Trace **1195.00**

Protek Cutting Edge
The model 506 meter has a RS-232C serial interface. Measured values are transmitted to the computer via an interface cable and supplied software WINDOWS and MS-DOS. DCV 1000V ACV 1000V AC/DC Current 20A Res. 40 meg Ω freq. 10MHz
REG. ~~209.95~~
model #506.....169.95

Elenco Digital Capacitance Meter **Sale!**

- .1pF to 20,000 UF
- Banana jack and special insertion jack included

model #CM-1555
$49.95

ALL PHASE
VIDEO-SECURITY INC.
WHOLESALE VIDEO WAREHOUSE

Call For FREE
Catalog & Technical Assistance
Add $8.95 Shipping/Handling
NYS Add Tax
Visa/MC/Discover/Amex

MAIL ORDERS TO :
70 CAIN DR.
BRENTWOOD, NY 11717

1-800-945-0909
FAX: 516-435-7494

CABLE CONVERTERS/DESCRAMBLERS

★ ★ ★ ★ SUPER BUYS ★ ★ ★ ★
★ FULLY REFURBISHED UNITS ★

TOCOM™★ JERROLD™★ SCIENTIFIC ATLANTA™★ ZENITH™★ PIONEER™
"WE SERVICE MOST PRIVATELY OWNED CABLE CONVERTERS"

Phone **(219) 935-4128**

NCCA Member of National Consumer Cable Association

SORRY, NO INDIANA SALES

NATIONAL CABLE BROKERS

1801 W. JEFFERSON ST., PLYMOUTH, IN 46563

OUR POLICY: All products carry a two year warranty. Warranty covers parts and labor and return shipping.
WARNING: Theft of cable services is a crime. National Cable will not knowingly defraud any pay TV operator and we will not assist any individual or company in doing the same.

The Pocket Programmer
Only $129.95

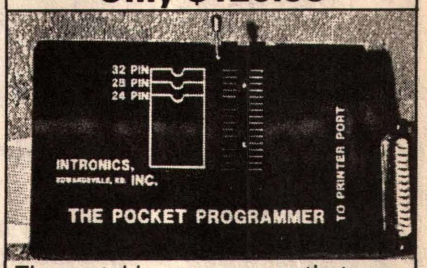

The portable programmer that uses the printer port of your PC instead of a internal card. Easy to use software that programs Eprom, EEprom, Flash & Dallas Ram. 27(C) / 28(C) / 28F / 29F / 29C & 25XX series from 16K to 8 Megabit with a 32 pin socket. Adapters available for Pic, PLCC, 5-Gang, 874X, 875X MCU's, 40-Pin X 16 & Serial Eprom's, and Eprom Emulator to 32K X 8.

Same Name, Address & Phone # for 13 Years... Isn't it Amazing ?

Intronics, Inc.
Box 13723 / 612 Newton St.
Edwardsville, KS 66113 Add $4.75 COD
Tel. (913) 422-2094 Add $4.00 Shipping
Fax (913) 441-1623 Visa / Master Charge

Cable TV Descramblers
Converters * Filters * Accessories

30 day Free Trial - *NO RISK!*
Unbeatable wholesale prices!
Affordable extended warranty
1 Year Warranty on *all* products
Call the cable professionals!

Free Catalog

Credit Cards Welcome!
1-800-379-3976
Orion Electronics
Prices starting as low as **$99!**

WE HAVE IT ALL!
Surveillance

Infinity Transmitters
FM Wireless Transmitter Kits
Vehicle Tracking Systems
Bug Detectors
Caller I.D.
Wired Mikes
Telephone Register with Printer
Long-play Recorders
Shotgun Mikes
Telephone Recording Adapters
Alcohol Testers
Telephone Scramblers
Hidden Video Cameras
Telephone Tap Detectors
Drug Testers
MUCH, MUCH, MUCH MORE.

Our 27th Year!
Small catalog FREE.
Larger catalog send $5.
Mail Order only.
Visa, MasterCard and C.O.D. accepted.
Inquire for dealers' prices.

A.M.C. SALES, INC.
193 Vaquero Dr. • Boulder, CO 80303
Mon.-Fri. 8 a.m.-5 p.m. Mtn. Time
800-926-2488
(303) 499-5405 • Fax (303) 494-4924

Pocket Cube™
Wireless cable box tester for authorized technicians.
Surface Mount Technology.
Works on J****** models D*5,D*V5,D*7,D*V7,D*BB, C*T,W*R.
Only $59.95 !
(plus $8 S&H)
30 Day Warranty
Pocket Cube with filter $69.95+S&H
Quantity discounts available.
Dealers Welcome!
NEW !
Pocket Cube Plus™
For testing of raw boxes.
CALL for current price !
Test chips available for J****** and SA8600.
Order 1-800-417-6689
Mon-Fri, 9AM-5PM EST.
If busy please keep trying.
VISA, MC, MO or CASHIERS CHECK
IEC, P O Box 52347,Knoxville, TN 37950-2347
Pocket Cube is a test generator ONLY.
Do not use these devices without authorization from your local cable company and local officials.
Prices subject to change. No TN sales.
This ad quotes cash discount pricing.
Returns are subject to a restocking fee.

BROADCAST TRANSMITTER

The **FMS2** studio quality transmitter is FULLY crystal controlled and programmable to any FM broadcast frequency.

Unit features: ALC, 2:1 compressor, audio buffer / amplifier, pre-emphasis, roll off filter, stereo generator, digital PLL tuning, 75 MHz-125MHz bandwidth, 500mW power output and a special introductory price of only $295.00 US.

Schematics for unit $27 *Catalog 800-504-1178*
Fax poll info 416-243-1067 *TEK Line 416-243-2260*
wavemach COMMUNICATIONS

CABLE TV CONVERTERS

Equipment & Accessories
Wholesalers Welcome
Call VISION TIME PRODUCTS
1-800-310-1153 M-F 8a-8p
NO TENN SALES

New Surveillance Devices !

Smoke Alarm and Table Clock Video Cameras Ultra miniature video cameras hidden in smoke alarm or alarm clock - your choice. Wide field of view and super .1 lux low light sensitivity! Undetectable!

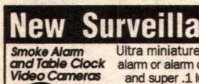

High quality B/W with 420 lines of resolution for ultra sharp images. Direct output of video and audio. $219.95 ea.

Best price on surveillance cameras anywhere!

Telephone Transmitter Kit hidden in dual modular adaptor Transmits both sides of conversation to any FM radio up to 1/4 mile. "SnapKit" technology. Uses phone line for power and antenna! Goes completely unnoticed. ***MA-100*** $25.95

High quality cassette deck plugs directly into telephone jack! Records up to 12 hours of conversations on a single cassette. Recording starts and stops automatically when phone is used! $99.95

Visa/MC (214)255-7490
Free shipping! Check/Money orders also accepted
Seymor-Radix Inc. Box 166055-N Irving,TX 75016
Now you can visit us on the internet at http://www.why.net/home/sr/

BEST BY MAIL
Rates: Write National, Box 5, Sarasota, FL 34230

READ "HOW TO Handle Tough Times." Excellent Booklet Reveals Astonishing Secrets! Mail $1.00: Creative Power, Dept.ELE, Post Office Box 1775, Mango, FL 33550.

MAKE YOUR BRAINSTORM BANKABLE! TWO HOUR VIDEO teaches patenting, development, marketing. Includes forms booklet! $19.95 + $3.00 P&H. Vocational Video, 1160 East Jericho, Huntington, NY 11743.

NEW CREDIT FILE. For FREE Information Package Call: 215-953-0222.

GET YOUR OWN FREE PAGER! Features voice-mail and multi-message delivery and much more! 1-800-956-2846 #987608039.

CALL TOLL FREE
(800) 292-7711
Se Habla Español

C&S SALES
EXCELLENCE IN SERVICE

WRITE FOR A FREE 60 PAGE CATALOG!

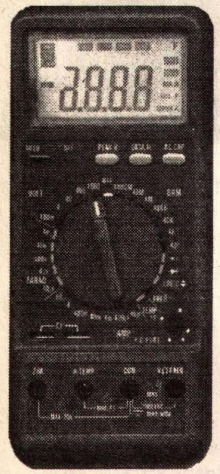

M-6100

Features:
- Computer Interface and Software with RS-232 Output
- Frequency to 4MHz
- Capacitance to 40nF
- Large 3 3/4 LCD display
- Temperature to 1999°F
- TTL logic
- Data/Peak hold
- Audible contiuity
- Auto power off
- Unit indicator
- Diode Test

NEW!

$125.00

TK-3000
$89.95

NEW!

Tools Included:
- SR-2 - Deluxe Soldering Iron
- SH-1 - Soldering Iron Stand
- ST-1 - Diagonal Pliers
- ST-2 - Long Nose Pliers
- ST-30 - Deluxe Wire Stripper
- SE-1 - Solder Ease Kit
- ND-3 - 3 pc. Nut Driver Set
- TL-8 - Precision Screw Drivers
- ST-5 - Screw Driver Slotted 3/16"
- ST-6 - Screw Driver #1 Phillips
- ET-10 - IC Puller
- SP-2 - Solder Pump
- ST-20 - Safety Goggles
- ST-9 - Pocket Screw Driver
- ST-4 - Solder Tube
- SW-3 - Solder Wick

A professional technician service tool kit in a metal reinforced tool case with heavy-duty handle and locks. A removable pallet handles most of the tools listed with more room for tools and parts in the lower half.

2MHz Function Generator
Model 4010

- Sine, Square, Triangle, Pulse and Ramp output
- Variable duty cycle

$195.95

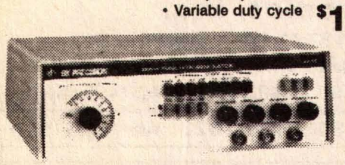

MX-9300 Four Functions in One

- One instrument with four test and measuring systems: 1.3GHz Frequency Counter • 2MHz Sweep Function Generator Digital Multimeter • Digital Triple Power Supply (0-30V @ 3A, 15V @ 1A, 5V @ 2A)

$479.95

NEW

Model XP-581

4 Fully Regulated DC Power Supplies in One Unit

4 DC voltages: 3 fixed - +5V @ 3A, +12V @ 1A, -12V @ 1A
1 Variable - 2.5 - 20V @ 2A

$85

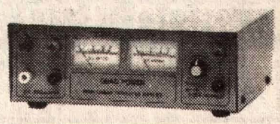

Digital Multimeter
Model EDM-83B

$169

18 Functions including freq to 20MHz, cap to 40µF, inductance to 40H, True RMS, Data Hold/min./max./avg., TTL logic.

Digital Multimeter
Model M-1700

$39.95

11 functions including freq to 20MHz, cap to 20µF. Meets UL-1244 safety specs.

Fluke Multimeters

70 Series
Model 70II . . . $69.95
Model 73II . . . $97.50
Model 75II . . . $135.00
Model 77II . . . $154.95
Model 79II . . . $175.00

80 Series
Model 83 . . . $235
Model 85 . . . $269
Model 87 . . . $289

B&K Precision Multimeters

Model 391 . . . $149
Model 390 . . . $139
Model 389 . . . $109
Model 388A . . . $99
Model 2707 . . . $79
Model 2860A . . $85

Kit Corner
over 100 kits available

PT-223K
$15.95
Phone kit with training course.

Fiber Optics Technology with training course
Model FO-30K
$19.95

Model AM/FM-108K
Transistor Radio Kit

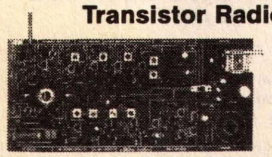

$29.95

M-1005K
Compact Multimeter Kit
$19.95
6 Functions & Transistor Test

XK-550 Digital / Analog Trainer

Elenco's advanced designed Digital / Analog Trainer is specially designed for school projects. It is built on a single PC board for maximum reliability. It includes 5 built-in power supplies, a function generator with continuously sine, triangular and square wave forms.
1560 tie point breadboard area.

XK-550
Assembled and Tested
$169.95

XK-550K - Kit
$139.95

Tools and meter shown optional

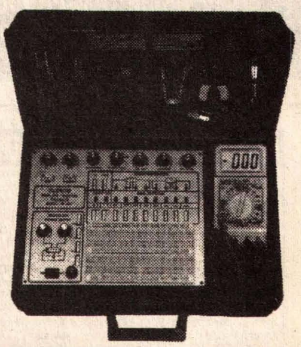

WE WILL NOT BE UNDERSOLD

UPS SHIPPING: 48 STATES 5%
OTHERS CALL ($5 min. / $15 max.)
IL RES. 8% TAX

C&S SALES, INC.

150 W. CARPENTER AVENUE
WHEELING, IL 60090
FAX: (847) 541-9904 (847) 541-0710

VISA MasterCard

15 DAY MONEY BACK GUARANTEE
FULL FACTORY WARRANTY
PRICES SUBJECT TO CHANGE WITHOUT NOTICE

CIRCLE 319 ON FREE INFORMATION CARD

FREE PROBES WITH ALL SCOPES

OSCILLOSCOPES

Lowest Prices of the Year!

WRITE FOR A FREE 60 PAGE CATALOG!

Japan Quality
But not Japan Prices!
Hitachi Laptop Color Digital Scopes

NEW! NEW!

150MHz 60MS/s VC-5460 $3695
50MHz 30MS/s VC-5430 $2695
20MHz 15MS/s VC-5410 $1795

100MHz

VC-6145 - Storage 4 Channel 100MS/s . . . **$4795**
VC-6155 - Storage 100MS/s $3995
VC-6545 - Storage 40MS/s $2995
V-1585 - 4 Channel $2095
V-1565 w/ Cursors $1795
V-1560 . . . . . $1595

50/60MHz

VC-6525 - Storage 20MS/s $2795
VC-6524 - Storage 20MS/s $2295
V-695 - 60MHz w/ Cursors $1549
V-555 - w/ Cursors $1095
V-552 . . . . . $949
V-509 - Battery Operated . $1795

20MHz

VC-5025A - 20MS/s DSO w/ DMM **$1160**
VC-5025 - 20MS/s DSO w/ DMM **$935**
VC-6523 - Storage 20MS/s $1995
V-252 . . . . . $449
V-209 - Battery Operated . $1425

Quality Scopes by Elenco

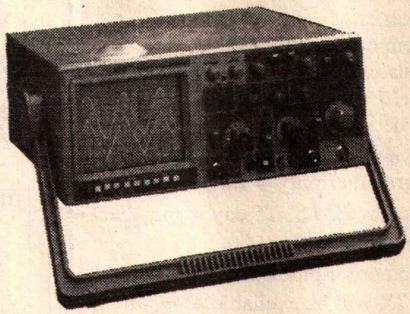

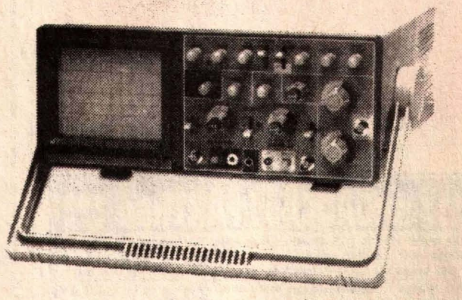

60MHz

DS-603 $1350
- Analog / Digital Storage
- 20MS/s Sampling Rate

S-1365 $795
- Analog w/ Cursors

S-1360 $759
- Analog with Delayed Sweep

40MHz

S-1345 $569
- Analog with Delayed Sweep

S-1340 $489
- Analog

2 Year Warranty

25/30MHz

DS-303 $1095
- Analog / Digital Storage

S-1330 $439
- 25MHz Analog
- Delayed Sweep

S-1325 $335
- 25MHz Analog

OSCILLOSCOPE SELECTION CHART

ANALOG

Model	Bandwidth MHz	Sensitivity (max)	No. of Channels	Sweep Rate Max ns/div	Delayed Sweep	Video Sync	Component Tester	Beam Find	Time Base
S-1365	60	1mV/div	2	10ns/div	Yes	Yes	Yes	Yes	2
S-1360	60	1mV/div	2	10ns/div	Yes	Yes	Yes	Yes	2
S-1345	40	1mV/div	2	10ns/div	Yes	Yes	Yes	Yes	2
S-1340	40	1mV/div	2	10ns/div	No	Yes	No	No	1
S-1330	25	1mV/div	2	10ns/div	Yes	Yes	Yes	Yes	2
S-1325	25	1mV/div	2	10ns/div	No	Yes	No	No	1

DIGITAL STORAGE

Model	Bandwidth MHz	Analog Sen (max)	No. of Channels	Sampling Rate	Memory Channel	Internally Backed Up	Pretrigger %	Output
DS-303	30	1mV/div	2	20MS/S	2K	Yes	0, 25, 50, 75	RS232
DS-603	60	1mV/div	2	20MS/S	2K	Yes	0, 25, 50, 75	RS232

B&K Precision at Discount Prices

20MHz Analog
2120 - $389.95
2125 - $539.95
Delayed Sweep

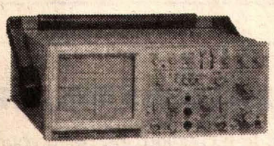

Model 1541C
40MHz
$695
Dual Trace

60MHz with Cursors readouts and Dual Time Base
Model 2260
$1225

Model 2160
60MHz Dual Trace
$949
Dual Time Base • Delayed Sweep

Model 2190A
100MHz 3 Channel
$1379
Dual Time Base • Delayed Sweep

Fluke Scopemeters

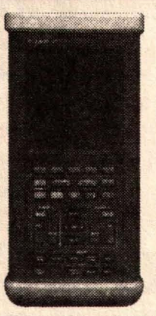

91 . . . . . **$1225**
92 . . . . . **$1525**
96 . . . . . **$1795**
97 . . . . . **$1795**
97A **$2945**
99 . . . . . **$2095**
Call or write for complete specs.

WE WILL NOT BE UNDERSOLD

UPS SHIPPING: 48 STATES 5%
OTHERS CALL ($5 min. / $15 max.)
IL RES. 8% TAX

C&S SALES, INC.

150 W. CARPENTER AVENUE
WHEELING, IL 60090
FAX: (847) 541-9904 (847) 541-0710

VISA MasterCard

15 DAY MONEY BACK GUARANTEE
FULL FACTORY WARRANTY
PRICES SUBJECT TO CHANGE WITHOUT NOTICE

CIRCLE 319 ON FREE INFORMATION CARD

CABLE T.V.
DESCRAMBLERS
Lowest prices, guaranteed!
CFS Electronics
(formerly C & C Electronics)
(800) 995-1749
VISA, MC, AMEX, C.O.D.

!!! BROADCAST FARTHER !!!
The model 1525 is a 75-110MHz RF amplifier that connects to mono or stereo FM transmitters and produces a *powerful* 15-20 watt signal which could broadcast up to 5 miles or more! Requires 75-250 mW drive.
Step by step plans complete with part source information and antenna designs . . . ONLY $14 PLUS $2 S&H NO C.O.D.'s
Progressive Concepts
BOX 586 STREAMWOOD, IL 60107
(708)736-9822 FAX: (708)736-0353
VISA MasterCard

CABLE TV CONVERTERS
Equipment & Accessories
Wholesalers Welcome
Call VISION TIME PRODUCTS
1-800-310-1153 M-F 8a-8p
NO TENN SALES

Robot Explorer Newsletter
Nano-ants, flying robots, Martian explorers. Explore an entire universe of exciting robots. 8 information-packed issues for only $14.95. Call now! MasterCard/Visa Accepted.
1-(800) GO-ROBOT or 1-(800)467-6268

Cable Aids Test
Orders Only 1-800-615-9221
Information 407-998-7883
Test Chips that fully activate Jerrold, Tocom, Zenith, SA, Pioneer and more. Quick-Board installation! Prices from $5 to $49.95 ea. **MC SPECIALTIES**
1 Year Warranty!
No FL Sales. Not for use in cable co. owned equipt. For test or repair only.

68HC11 and other
PLCC prototype adapters
that fit on a single breadboard strip!
PLCC sockets mounted on PCB with .25" leads
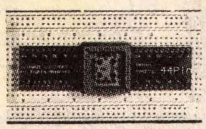
Patent-pending design for wire wrap, design prototyping & breadboarding
28 Pin-$ 6.95; 44 Pin-$ 9.49; 52 Pin-$ 13.49; 68 Pin - $ 14.95; 84 Pin -$ 18.95. All + S/H. Visa/MC/Check
AMAZE ELECTRONICS CORP.
Tel: 800-996-2008 Fax: 408-996-0366
amaze@hooked.net www.hooked.net/users/amaze

PIC Programmer
Development Tools
JM-PICE $245
- Programmer for PIC 16C5X, 16C6X, 16C7X, 16C84, and 17C4X in DIP packages.
- Assembler and Simulator.
- Emulates program memory, registers, and I/O for the PIC 16C5X.
- Instruction-level emulation for the PIC 16C71 and 16C84.
- Programmer only *$155*, Complete package *$245*. 15 day money-back guarantee.
- Adapters for emulating 16C6X and 16C7X will be available soon.

80C552
Development System
- *8051* core processor with 8 channel 10-bit *A/D* and *PWM*.
- 24 more I/O and RS-232 port.
- 32K ROM and 64K RAM.
- **$130** each SBC. High performance development system includes assembler, disassembler, real-time execution and debugging, monitor program, and examples (**$70** more).
- *80C31* Development System is also available.

ROMY-16
EPROM EMULATOR
Emulates ROM or RAM in 8- and 16-bit systems. **$195** (2716-27256) or **$245** (2716-27010). Window/menu driven interface. 15 day money-back guarantee. Optional assembler, disassembler, and ROM debugger **$100** each CPU.

68HC11
Development System
- Eight channel 8-bit A/D converter.
- 32K ROM and 32K RAM.
- $120 each SBC. 40x2 LCD $20.
- Add $70 for the real-time integrated development system.
- *Microprocessor Simulator/*Debugger *and Custom design are available.*

J&M *Microtek, Inc.*
83 Seaman Road, W Orange, NJ 07052
Tel: (201)325-1892 Fax:(201)736-4567

SURVEILLANCE
The Latest High Tech
Professional Electronic Devices
Our latest catalog offers a **HUGE** selection of surveillance, privacy devices including: hidden video equipment, electronic kits, telephone recording systems, touch tone decoders, scanners, telephone tap detectors, bug detectors, voice disguisers, telephone scramblers,locksmithing tools, and more. **Catalog $5.00.**
SPY OUTLET
P.O. Box 337, Buffalo, NY 14226
(716) 691-3476/(716) 695-8660

BUILD A 3 AXIS COMPUTER CONTROLLED
-CNC- MILLING MACHINE
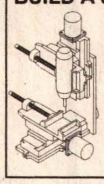
Or build your own NC router, Robot, Plotter, 3D. Digitizer etc., with MAXNC low cost kits. Machine parts or molds for your projects with computer precision. Works from CAD Dwgs. or from your own instructions. Software, Plans Instructions and materials list $ 65.00. Parts available. Phone or write for information.
MAXNC
6509 W. Frye Rd. suite 3 * Chandler, AZ 85224
Phone 1-602-940-9414

INTERFACE TO YOUR PC KEYBOARD INPUT !
Our KE-I8 Keyboard Encoder converts input from switches and keypads into PC compatible keyboard signals.
- Use with or without your own PC's keyboard
- Scans 9 x 9 matrix or 18 individual inputs
- PCXT, AT, PS/2 and Compatibles
- Looks like a Keyboard to your Computer

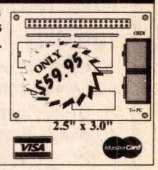

2.5" x 3.0"
Hagstrom Electronics
2 Green Lantern Boulevard
Endicott, NY 13760 (607) 786-7523
VISA MasterCard

Many Electronics inc
RFT,FTG,PIO-Supers,
Filters,FTG KIT's
800-716-3561 9-7est

CELLULAR PROGRAMMERS!
COPYCAT MOTOROLA CELLULAR PROGRAMMER: program any Motorola Phone up to 95IC. Complete Assembly: **$999**
COPYCAT KIT ONLY (unassembled complete with instructions): **$750**
ERICSON CLIP (program through the keypad): $350
OKI 900 modified (up to 5 numbers programmed in): **$400**
OKI CHIP only: **$75**
Also different programs available for all brands!
FOR DEALERS ONLY MASTER FILES AVAILABLE
DISCOUNT FOR QUANTITIES.
PH: 718-575-1474 718-768-4963
Fax: 718-369-3989
E MAIL: 104170.3043@COMPUSERVE.COM

"CATALOG KNOCKS SOCKS OFF"
For our free Catalog, just send your name and address to:
Consumer Information Center
Department KO
Pueblo, Colorado 81009

CLASSIFIED

CABLE TV

ATTN, cable box owners. Order your ID signal and bullet stopper before it's too late. Send $23.00 to **R.R. ENTERPRISE,** Box 3532, Easton, PA 18043.

SECRET Cable Descramblers Build your own descrambler for **Less** than $12.00 in **seven easy steps! Radio Shack** parts list and **Free** descrambling methods that **cost nothing** to try, included. Send $10.00 to: **INFORMATION FACTORY,** PO Box 669, Seabrook, TX 77586. For VISA/MC, COD's, (713) 922-3512 Anytime!

CABLE Descrambling New secret manual. Build your own descramblers for cable and subscription TV. Instructions, schematics for**SSAVI,** Gated Sync, Sinewave, (HBO, Cinemax, Showtime, UHF, Adult) $12.95, $2 postage. **CABLETRONICS,** Box 30502R, Bethesda, MD 20824.

CABLE TV Equipment & Accessories Wholesalers welcome! 30 day moneyback guarantee! Free catalog! **PROFORMANCE ELECTRONICS INC.,** 1 (800) 815-1512.

CABLE TV Test Chips for Jerrold, Tocom, Pioneer, Scientific Atlanta, etc...**Quick installation!** New Multi-Mode modules available. Prices from $5.00 each. **1 (800) 786-9025.**

CABLE-safe. Guarantee cable privacy. The one-way valve for your cable TV signal. Cable signals come in, but they don't go out! $29.95 + $3.00 S&H. VISA/MC/AMEX. **ELECTROMAN,** Box 24474, New Orleans, LA 70184. (504) 482-3017.

"CABLE Unscrambled. Everything you want to know about cable, but are afraid to ask. $10.00. **"Descrambler Schematics Revealed."** A powerful guide to descrambling schemes. $10.00. **"Baseband Video Explained."** Discover what a Baseband Signal is and how it's constructed. $10.00. Special offer. Get all three for only $25.00! VISA/MC/AMEX. **ELECTROMAN,** Box 24474, New Orleans, LA 70184. (504) 482-3017.

UNIVERSAL Descrambler. Unscramble signals using your VCR as the tuner. Works with virtually any system, this is the only one you need. Declare cable box independence! Fully assembled. $129.95 + $5.00 S&H. VISA/MC/AMEX. **ELECTROMAN,** Box 24474, New Orleans, LA 70184. (504) 482-3017.

"BULLET Buster". Protect your cable box against the infamous cable "bullet". The "Bullet" Buster acts as an electronic sheild. Installs in-line in seconds. Don't wait until it's too late! $19.95 + $3.00 S&H. VISA/MC/AMEX. **ELECTROMAN,** Box 24474, New Orleans, LA 70184. (504) 482-3017.

CABLE Descrambler! Anyone can build in seven steps with Radio Shack parts. Plans $5.00. 1 (800) 818-9103.

DESCRAMBLER Cable using simple circuit. E-Z to follow instructions $10.00. Complete kit with free bullet "Terminator". $20.00. 1 (800) 522-8053.

CABLE Bullet "Terminator/I.D. Blocker." Electronically shields yourself and your box. Factory direct. Lifetime Guarantee $14.95. 1 (800) 820-9024.

CABLE filter, build your own- plans, parts, PC board, case, $11.00. **VIDEO MEDIA,** Box 97-0408, Coconut Creek, FL 33097. 1 (954) 752-9202.

CABLE TV notch filters. Tunable from 50 to 300 Mhz (channels 0 thru 36). Eight different models available so specify frequency or channel number needed when ordering. $30.00 each plus $3.50 S/H per order. Huge quantity discounts. **STAR CIRCUITS** PO Box 94917, Las Vegas, NV 89193, 1 (800) 433-6319.

CABLE TV descramblers. Pioneer 6310's, Scientific Atlanta, Jerrold. Warranty. Lowest prices anywhere! Houston, TX (713) 691-4610.

"HACKERS Catalog". 40 pages and over 100 books, videos, software packages and test chips for hackers, crackers, phreakers, and experimenters. Free! 1 (520) 726-2833.

CABLE test modules/cubes. Pioneers, S/A, Tocoms, Jerrolds. Latest technology. Quantity discounts. Voice/Fax (718) 426-8515.

CABLE box testers & descramblers. Jerrold, Tocom. Scientific Atlanta, Pioneer. **REM VIDEO,** (602) 581-1496.

CARL'S Electronics - The Cable Hacker's Guide, stopping power meters, and electronic plans now available on-line. http://www.ultranet.com/~carlton.

SECURITY

SURVEILLANCE Privacy security protection. Catalog $5.00. **SPY EMPORIUM,** 6065 Hillcroft, Suite 413, Houston, TX 77081. (713) 774-1000.

SECURITY system equipment. Do it yourself and save. Covert camera's, control panel's, motion's, glassbreak detectors, siren's, contact switches, more. 1 (800) 335-2296. Fax 1 (519) 541-1277.

TEST EQUIPMENT

TEST Equipment pre-owned now at affordable prices. Signal generators from $50.00, oscilloscopes from $50.00. Other equipment including manuals available. Send $2.00 US for catalog. Refunded on first order. **J.B. Electronics,** 3446 Dempster, Skokie, IL 60076. (847) 982-1973.

QUALITY used test equipment for sale. Call, fax or write for list. **RIDGE EQUIPMENT,** PO Box 84, Mt. Airy, MD 21771. (301) 831-7671.

BUSINESS OPPORTUNITIES

EXCELLENT extra income! Assemble easy products at home. Program Guaranteed! 1 (800) 377-6000 Ext. 6870. Open Sunday.

EDUCATION & INSTRUCTION

ELECTRONIC engineering. 8 volumes complete. $109.95. No prior knowledge required. Free brochure. **BANNER TECHNICAL BOOKS,** 1203 Grant Avenue, Rockford, IL 61103.

CABLE TV TURN-ON CHIPS

SUPER Cable TV "Test Chips". Provides full service activation. Excellent; Instructions & illustrations.**Jerrold Starcom:** DP(V)5..DP(V)7.. DPBB7..CFT-2000..CFT-2200 Series. **Pioneer:** BA-5000 thru BA-6700.**Pioneer: Custom Programmer** (Clears E2 & rewrites new I.D. codes).**Scientific Atlanta:** 8500 thru 8600.**Tocom:** 5503-VIP..5507.**Zenith:** ST-1000 thru ST-5612.**Call Now!! MASTER COMPONENTS. 1 (800) 233-0570.**

THE CABLE TV SUPER CUBE

THE Mobilizer!! External **"Test Cube"** activator. Easy **plug-n-play** operation. Excellent instructions & illustrations. Supports all DP(V)7.. DPBB7..CFT-2000..CFT-2200 series converters. **New enhanced performance features:** Locked box revitalizer! Restore command! Plus much more!**Dealers wanted! Call Now!! MASTER COMPONENTS 1 (800) 233-0570.**

FREE
HOME AUTOMATION CATALOG!

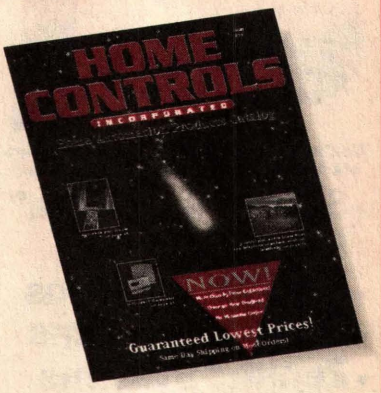

Home Controls' color catalog features truly affordable X-10 powerline controls, IR products, CCD cameras, wireless home control devices, security products, drapery controls, audio systems, and everything you can imagine for the remote and automated control of your home!

Call Toll Free
1-800-CONTROL

Contact us by E-Mail: homectrl@electriciti.com

Lowest Prices Guaranteed • Same Day Shipping • Superior Technical Support
No Minimum Order • Fabulous Freebies • Great Selection!

CIRCLE 335 ON FREE INFORMATION CARD

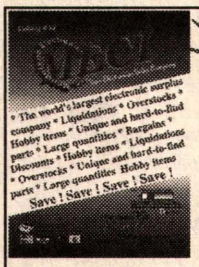
• The world's largest electronic surplus company • Liquidations • Overstocks • Hobby Items • Unique and hard-to-find parts • Large quantities • Bargains • Discounts • Hobby Items • Liquidations • Overstocks • Unique and hard-to-find parts • Large quantities Hobby Items
Save ! Save ! Save ! Save !

If you are not getting this catalog you are missing out on some of the best deals in electronics today! We have thousands of items ranging from unique, hard-to-find parts to standard production components. Call, write, or fax today to start your free subscription to the most unique catalog in the industry, filled with super values on surplus electronic and hobbyist type items. If you have a friend who would like to receive our catalog, send us their name and address and we will gladly forward them a complementary 100 page catalog.

Why pay more? Call today.

MECI

340 East First Street
Dayton, Ohio 45402

Fax Order Line
1-800-344-6324

Order Toll-Free
1-800-344-4465

CIRCLE 251 ON FREE INFORMATION CARD

CABLE TV DESCRAMBLERS

We Carry A Full Line Of Premium Converters And Descramblers Compatible With:

- Scientific Atlanta™ Systems
- Jerrold™ Systems
- Tocom™ Systems
- Zenith™ Systems
- Pioneer™ Systems

SATISFACTION GUARANTEED OR YOUR MONEY BACK!
BEST PRICES FREE CATALOG
Please have the MAKE & MODEL # of your full premium service cable box ready when you call!

ALLSTAR ELECTRONICS
800-782-7214
HOURS: 9-6 M-F 10-3 Sat EST

It is not the intent of Allstar Electronics to defraud any pay TV operator. Anyone implying theft of service will be denied assistance. All brand names are registered trademarks of their respective owners & are used for reference only. 110-64 Queens Blvd., #465, Forest Hills, NY 11375. NO NYS SALES!

BEST DEALER PRICING!

CABLE DIRECT
CONVERTERS • FILTERS
DESCRAMBLERS

IMPROVE YOUR IMAGE WITH VIDEO STABILIZERS

30 DAY FREE TRIAL!

FREE Cable TV Catalog.

VISA MasterCard DISCOVER

Now you can tune-in your favorite cable TV programming and SAVE $100'S - EVEN $1000'S on premium CABLE TV EQUIPMENT.

MODERN ELECTRONICS
1-800-906-6664
2125 S. 156TH CIRCLE • OMAHA, NE 68130

CLASSIFIED

SATELLITE EQUIPMENT

FREE Big dish catalog — Lowest prices, systems, upgrades, parts, tune-up kits, accessories, factory fresh and warranties, satisfaction guaranteed. **SKYVISION®,** 1012 Frontier Drive, Fergus Falls, MN 56537. 1 (800) 334-6455. Fax (218) 739-4879. See full page ad The Shopper Section.

NEW 18" Digital System — Save 30 - 60% on programming compared to other guys little dish. Introducing the new **DISH℠ Network** from **SKYVISION®,** 1018 Frontier Drive, Fergus Falls, MN 56537. 1(800) 500-9264. Fax (218) 739-4879. See full page ad The Shopper Section.

VIDEOCYPHER II descrambling manual. Schematics, video and audio. Explains DES, EPROM, CloneMaster, Pay-per-view (HBO, Cinemax, Showtime, Adult, etc.) $16.95, $2.00 postage. Schematics for Videocypher II Plus, $20.00. Schematics for Videocypher II 032, $15.00. Software to copy and alter EPROM codes, $25.00. VCII Plus EPROM, binary and source code, $30.00. **CABLETRONICS,** Box 30502R, Bethesda, MD 20824.

OBTAINING sound for your **VCII** and **VCII Plus** is **easy.** No codes needed. Details 1 (800) 211-5635.

MISCELLANEOUS ELECTRONICS FOR SALE

TUBES: "oldest", "latest". Parts and schematics. SASE for lists. **STEINMETZ,** 7519 Maplewood Ave., EN 46324, Hammond, IN 46324.

FIBER-Optic Projects — Swing into the new technology by assembling tried and true projects recently published. "Practical Fiber-Optic Projects" - BP374 is only $9.95. (price includes shipping) **ELECTRONIC TECHNOLOGY TODAY INC.,** PO Box 240, Massapequa Park, NY 11762-0240.

GREEN Thumb Alert— Electronics enters the Garden! New exciting book points out how gardeners can build simple gadgets to pomote sucess where the elements work against you. Some of the projects are: over/under temperature monitoring, dusk/dawn switching, automatic plant watering, warming cables, etc. "Electronic Projects for the Garden" only $9.95 (price includes shipping) **ELECTRONIC TECHNOLOGY TODAY INC.,** PO Box 240 Massapequa Park, NY 11762-0240.

CBers Order new CB Trick III CB book. Shows CB tune ups, amplifiers, and expert CB info! Send $19.95 to **MEDICINE MAN** CB, PO Box 37, Clarksville, AR 72830.

RESISTORS 20 for $1.00. LEDs 4 for $1.00. Catalog $1.00. **ZIPFAST,** Box 12238, Lexington, KY 40581-2238.

POOR reception on your A.M. radio? Our Signal Booster will help. Guaranteed! Send $2.00 for details (refundable with order). **FALA ELECTRONICS,** PO Box 1376, Dept. 4, Milwaukee, WI 53201.

ELECTRONIC surveillance and privacy assurance devices/wire, bug detectors, hidden camera's (Nanny Watch) cell/home, business phone, scramblers and other spy merchandise. Send $5.00 check/M.O. to: **I-SPY, INC.** P.O. Box 1707, Amherst, NY 14226. (716) 874-1707 for your catalog.

MEASURE-control: Physical conditions, machines, mechanical-electrical devices, processes, with your personal computer. Measurement data via modem if needed. **Eight channel system;** kit and assembled. Connects serial port. Includes: programs, comprehensive 50 page, **do-it-yourself training guide.** Easy! Affordable! Increase convenience, productivity! Request information: **TESTECH,** Box 53743, Lubbock, TX 79453. **(800) 299-6971.**

GOVERNMENT auctions in your area. Electronic equipment available at surplus prices! Call Now: 1 (800) 601-2212, ext. SP6870.

PLANS-KITS-SCHEMATICS

CRYSTAL set Handbook — Visit antiquity by building the radios your grandfather built. Assemble a "Quaker Oats" rig, wind coils that work and make it look like the 1920's! Only $10.95 plus $4.00 for shipping and handling. **CLAGGK INC.,** PO Box 4099, Farmingdale, NY 11735. US funds only! USA and Canada — no foreign orders.

FREE Catalog. 100 Leading-Edge kits. K1, PIC. Full instructions, source code. 1 (800) 875-3214. **SCIENCE FIRST,** 95 Botsford Place, Buffalo, NY 14216.

BUILD your own DC motor control. 1 to 480 amps w/surplus parts. **BEYOND ELECTRONICS,** 1 (800) 747-2861. Free catalog.

AWESOME kits: Voice changer, levitator, laser, gas sensor and more! Catalog $1.00. **LNS TECHNOLOGIES,** 20993 Foothill Blvd., Suite 307R, Hayward, CA 94541.

ELECTRONIC power angling rod plans. Retrofits to any new or existing mini-blind; Angles blinds automatically; day, night, temperature sensitive, remotely controlled; $5.00 to **DENNY'S DESIGNS,** P.O. Box 185, Oroville, CA 95965.

HOME automation via phone without expensive computers. Furnace, aircond., etc... on remotely. Components from local stores. Wiring required. Send for plans. Money orders only: $10.95. **AMR AUTOMATE CTR.,** PO Box 1176, Waltham, MA 02254-1176.

COMPUTER HARDWARE

INTEGRATED circuits designed to your specs and built. Almost any combinatorial/sequential circuit. 12-bit to 8-bit compression circuit was designed and built with max of 10nsec propagation delay. Send your specs/estimated quantity for price quote. **ELECTROMAG CO.,** PO Box 1463, Pacific Palisades, CA 90272. e-mail: electromag@aol.com.

COMPUTER SOFTWARE

SET your pc's clock from atomic source at NIST or USNO. Requires Windows95 and modem. $14.95. **NANOWARE,** PO Box 7468, Seminole, FL 34645.

Take Stock in America U.S. SAVINGS BONDS

NEW **MULTI PREQUENCY CUBES!**
WIRELESS CABLE BOX TESTER
EXTERNAL AND INTERNAL MULTI-FREQUENCY
WORKS ON ALL MODELS: J****,SA,PIONEER, ALSO FOR CFT 2200!
WORKS EVERYWHERE.
AUTOMATIC FREQUENCY FINDER!
60 DAYS WARRANTY
QUANTITY DISCOUNT AVAILABLE
DEALERS WELCOME!
PH: 718-575-1474 718-768-4963
Fax: 718-369-3989
E MAIL: 104170.3043@COMPUSERVE.COM
AMEX MO & COD
Pocket cube is a test generator only

Printed Circuits in Minutes Direct From LaserPrint!

8 1/2" x 11"
* Or Photocopy
**Use standard household iron or P-n-P Press.

1. LaserPrint*
2. Press On**
3. Peel Off
4. Etch

Press-n-Peel

Use Standard Copper Clad Board
20 Shts $30/ 40 Shts $50/ 100 Shts $100
Visa/MC/PO/Ck/MO $4 S&H
Techniks Inc.
P.O. Box 463
Ringoes NJ 08551
ph. 908.788.8249 fax 908.788.8837
http:\\chelsea.ios.com\~techniks
Retail Dealer Inquires Invited

NEW EASY PC

BRITISH DESIGN AWARD

SCHEMATIC and PCB C.A.D

ONLY **$145**

Includes

- MGA, CGA, EGA & VGA compatible.
- Design large multi layer boards.
- One level pull down menu and quick keys for fast layout.
- Dot matrix, laser, plotter, Gerber & N.C. drill output.
- 6 Month Free update Free Demo

OHIO AUTOMATION Inc.

7840 ANGEL RIDGE ROAD
ATHENS, OHIO 45701
(614) 592-1810
Visa & MasterCard Accepted

16 Bit Control

& Data Acquisition System

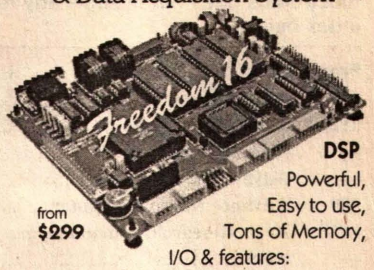

from **$299**

DSP
Powerful,
Easy to use,
Tons of Memory,
I/O & features:

16.8MHz 68HC16
RS-232 & RS-485
RT clock option

34 digital I/Os (7 IRQ)
+ LCD/Keypad port
+ 8 ch 10b fast A/D

Affordable "C" compiler/library
Multi-tasking kernel
Up to 256K ea. SRAM, FLASH memory

INTEC INOVENTURES INC.
Ph: (604) 721-5150 FAX: 721-4191

NEW! BAC552ES CONTROLLER

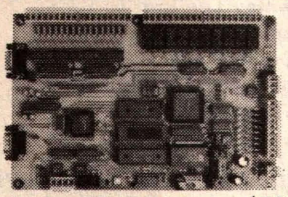

APPLICATION READY ONLY $319.95

The **BAC552ES** is a new enhanced backward compatible addition to the proven Basic Automation Controller BAC552.

NEW FEATURES: 3 serial ports (Console port, RS232 DTE with RTS/CTS and RS485) • 128K SRAM • 128K FLASH • secondary watchdog timer • serial EEPROM option • 60K for BASIC program • 64K SRAM / 64K FLASH for data storage • 64K FLASH for BASIC file backup

APPLICATIONS: *Industrial control • HVAC systems • security • home automation • data logging • remote control & monitoring*

SYLVA Control Systems a division of Sylva Energy Systems Inc.
519 Richard Street, Thunder Bay, Ontario, Canada P7A 1R2
Ph. 807-768-2487 Fax 807-683-6485 BBS 807-767-0587
WEB PAGE: http://www.sylvacontrol.baynet.net
Email: sylva@mail.baynet.net

UPGRADE YOUR COMPUTER!

VISA/MC Welcome!

TECHNOLOGY ASSOCIATES
959 W. 5th St. • Reno, NV 89503
(702) 322-6875 • Fax (702) 324-3900
www.techass.com • sales@hoopsware.com

Memory

1Mb (1x8-70 ns)	$10
4Mb (4x8-70 ns)	$30
4Mb (1x32-60 ns)	$29
8Mb (2x32-60 ns)	$58
16Mb (4x32-60 ns)	$104
32Mb (8x32-60ns)	$248

Hard Drives

R 350 Mb IDE	$139
WD 635Mb IDE	$179
WD 850Mb IDE	$200
WD 1.2Gb IDE	$229
WD 1.6Gb IDE	$285
Sea 2.1Gb IDE	$379

Motherboards

486xxx VLB, 256K	$76
486xxx PCI, 256K	$94
Pentium xxx, Intel Triton, 256K pipeline	$135
Pentium xxx, Intel Triton2, 512K pipeline	$174

CPU's

Cyrix 486DX2-80	$25
AMD 486DX4-100	$34
AMD 5x86-133	$45
Cyrix 5x86-120	$68
Intel Pentium 100	$150
Cyrix 686-100	$150
Intel Pentium 120	$199
Cyrix 686-120	$215
Intel Pentium 133	$290
Intel Pentium 150	$399
Cyrix 686-133	$440
Intel Pentium 166	$496

Video Cards

256K ISA SVGA	$23
Trident 8900 1Mb ISA SVGA	$48
Trident 9440 1Mb VLB SVGA	$39
Trident 9440 1Mb PCI SVGA	$59

Modems

14.4 Int Fax/Modem	$39
28.8 Int Supra PNP Fax/Modem	$115
28.8 Int Fax/Modem w/Voice	$125
28.8 Int USR Fax/Modem Windows/PNP	$165

Sound Cards

16-bit Sound Blaster Pro compatible	$39
16-bit SB ProPnP Sound Blaster AWE32 PNP	$85 $266

Miscellaneous

NEC 1.44Mb FDD	$31
TEAC 1.2Mb FDD	$56
4X CD-ROM IDE	$55
6X CD-ROM IDE	$65
Colorado Travan T1000 850Mb tape drive	$190
3-button serial mouse	$9
Spill-resist 101-key	$20

Controller Cards

ISA Multi I/O IDE, FDC, 2S/1P/1G	$14
VLB Multi I/O, EIDE FDC, 2S(16550), 1P(ECP, EPP)/1G	$18

NOTE: Prices are projections based on advertising lead times.

Prices and availability subject to change without notice.

CALL FOR DAILY LOW PRICES!

ADAPT-11

68HC11 Module for Solderless Breadboards

- miniature 2.0" by 2.8" module
- plugs vertically into solderless breadboard
- reset circuit, button, & mode select switch
- RS-232 int., 5V reg. & ext. pwr. conn.
- all I/O lines on dual row connector
- programs 68HC811E2 & 711E9 chips

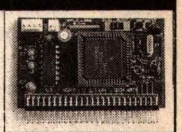

Starter Package comes with ADAPT-11 module, 68HC811E2 microcontroller with 2K EEPROM on-chip (re-programmable in circuit 1000s of times; no EPROM programmer or eraser required), PC serial cable for downloading code, Motorola Programming Reference Guide, ADAPT-11 User Manual, freely distributable 68HC11 software, and demo program. #AD11-SP $74.95 + $5 shipping & handling.

Use PLCCs in your Solderless Breadboard!
- Solderless breadboard socket adapters for all popular PLCC sizes.
- Vertical design saves space on breadboard.

Also available:
Solderless breadboard adapters for DB9 & DB25, and IDC (ribbon cable) connectors, from $5.

Visa, MasterCard, AmEx, Discover

TECHNOLOGICAL ARTS
309 Aragona Blvd., Suite 102, Box 418, Va. Beach, VA 23462
1644 Bayview Avenue, Box 1704, Toronto, ON M4G 3C2
voice/fax: (416) 963-8996 www.io.org/~techart

HIGH POWER AUDIO AMPLIFIER CONSTRUCTION

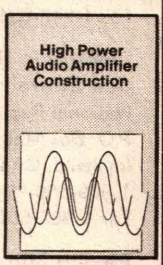

BP277—Here's background and practical design information on high power audio amplifiers capable of 300±400 watts r.m.s. You'll find MOSFET and bipolar output transistors in inverting and non-inverting circuits. To order your copy send **$6.25 plus $3.00** for shipping in the U.S. and Canada to **Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240.** U.S. and Canada only. Payment in U.S. funds by US bank check or International Money Order. Please allow 6-8 weeks for delivery. MA03

"NOW BUYING"

$$ BEST PRICES $$ AVAILABLE

SCIENTIFIC ATLANTA™ 8536 THRU 8600	**PIONEER™** 5135 THRU 6300
ZENITH™ 1086 THRU 1612	**JERROLD™** DPV7 DPBB7 DPV70 DPBB70 CFT
TOCOM™ 5503A VIP THRU 5507	

Midwest's Largest Brokers
(We buy quantities of one to one thousand units)

NATIONAL CABLE BROKERS
(219) 935-4128

GIANT! SPY ELECTRONICS CATALOG

ENTHUSIAST'S

Just Like In The Movies!
Fiber-optics• IR Detectors•UV Powder
Covert TV Cameras• Phone Transmitters
Laser/Parabolic Mic's•Nightvision• Wrist Watch Cameras•Time Lapse VCR's, Surveillance-Counter Surveillance•Homing Xmitters•Fiberscopes• Police Electronics•Micro-TV's• Phone Bug's• TV Xmitters Transmitters• Books/Video's and Much, Much More!

SECRET **EVIDENCE LOCATER**
Just whistle your secret code and it whistles back
$7.77+2.00 S&H

CATALOG *Rush!* $5.00 to CI ASSOCIATES
2801EN Shelterwood. Arlington, TX 76016

ADVERTISING INDEX

Electronics does not assume any responsibility for errors that may appear in the index below.

Free Information Number		Page
—	ABC Electronics	116
212	Ace Communications	104
—	Active Micro	117
—	Advance Circuit Design	120
309	Advance Micro Computer	106
—	Aegis Research, Canada	91
—	AES	104
213	Alfa Electronics	118
214	All Electronics	115
—	All Phase Video Security	128
—	Allison Technology	94
—	Allstar Electronics	134
—	Alltronics	124
—	Amaze Electronics	108
—	AMC Sales	129
282	American Eagle Publications	106
—	Andromeda	112
334	Basic Electrical Supply	108
—	Baylin Publications	126
—	BC Electronics	125
297	Bel-Merit	109
311	Black Feather	102
—	Boss Distributors	126
325	Brigar Electronics	90
—	Bsoft Software, Inc.	120
324	Butterworth Heinemann	86
319	C&S Sales, Inc.	130
332	Capital Electronics	103
—	CGC	123
305	CTG	124
321	Circuit Specialists	98
—	Cleveland Institute of Electronics	37
—	Command Productions	96
336	Computer Monitor Maintenance	128
226	Consumertronics	100
320	Conway Engineering Inc.	101
58	Cook's Institute of Elec. Eng.	13
228	Cool Amp Conducto Lube	96
—	Cybermation	91
234	Dalbani Electronics	85
235	Danbar Sales	107
331	Direct Cable Supply	97
312	EIA	88
—	Emac Inc.	106
—	Fair Radio	126
121	Fluke Corporation	CV2
330	Foley-Belsaw Co.	105
318	Fotronic	121
316	Gateway Products	112
—	General Device Instruments	124
122	Global Specialties	21
—	Grantham College of Engineering	4
317	Graymark International	110
—	Halcyon Group	117
129	Hameg	12
—	Home Automation	117
—	Home Controls	133
323	Howard Electronics	95
—	IEC	129
—	Index Publishing Group	123
—	Information Unlimited	116
—	Innova Technology	103
126	Interactive Image Technologies	CV4
—	Intronics, Inc.	129
315	IVS	108
—	J&M Microtek, Inc.	132
—	Learn Inc.	9
—	M&G Electronics	126
—	M-2-L Electronics	127
304	M.D. Electronics (Everquest)	125
333	Mark V Electronics	93
314	MCM Electronics	23
251	Mendelson Electronics Surplus	133
—	Mental Automation	100
—	Meredith Instruments	125
—	Merrimack Valley Systems	114
303	Micro 2000	87
128	Micro Code Engineering	5
—	Micro Engineering Labs	124
—	Midwest Laser Products	117
—	Milestone Products	91
—	Modern Electronics	134
—	Mondo-tronics	111
306	Mouser Electronics	103
—	MWK Industries	102
—	NRI Schools	17
—	National Cable Brokers	129
257	Needham Electronics	120
—	NESDA	15
258	New Sensor Corp.	82
260	Ocean State Electronics	127
327	OWI	123
262	Parts Express Inc.	83
310	Phillips Tech Electronics	128
—	Picotronic	102
—	Polaris Industries	81
326	Prairie Digital	104
264	Print (Pace)	113
—	R-4 Systems Inc.	94
78	Radio Shack	7
—	RC Distributing Co.	127
—	RF Parts	91
—	Show-Time	116
—	Sil Walker	127
270	Skyvision Inc.	28
—	Street Smart Security	100
308	Sun Equipment	84
—	Sycard Technology	112
—	Tab Books	1, 52
329	Tech Systems	89
—	Tektronix, Inc.	11
92	Tektronix, Inc.	CV2
328	Telulex	114
—	Test Equipment Sales	122
275	Timeline	92
—	U.S. Cyberlab	81
—	Universal Electronics, Inc.	110
322	Visitect Inc.	121
—	Visual Communications	13
—	Wavetek Corp.	19
—	Weeder Technologies	122
—	Windjammer Barefoot Cruises	12
—	World College	73
—	WPT Publications	110
281	Xandi Electronics	114

ADVERTISING SALES OFFICES

Gernsback Publications, Inc.
500 Bi-County Blvd.
Farmingdale, NY 11735-3931
1-(516) 293-3000
Fax 1-(516) 293-3115

Larry Steckler
publisher (ext. 201)

Christina Estrada
assistant to the publisher (ext. 209)

Arline Fishman
advertising director (ext. 206)

Michele Torrillo
advertising assistant (ext. 211)

Adria Coren
credit manager (ext. 208)

For Advertising ONLY

EAST/SOUTHEAST
Stanley Levitan
Eastern Advertising
1 Overlook Ave.
Great Neck, NY 11021-3750
1-516-487-9357
Fax 1-516-487-8402

MIDWEST/Texas/Arkansas/Okla.
Ralph Bergen
Midwest Advertising
One Northfield Plaza, Suite 300
Northfield, IL 60093-1214
1-847-559-0555
Fax 1-847-559-0562
bergenrj@aol.com

PACIFIC COAST
Janice Woods
Pacific Advertising
Hutch Looney & Associates, Inc.
6310 San Vicente Blvd.
Suite 360
Los Angeles, CA 90048-5426
1-213-931-3444 (ext. 228)
Fax 1-213-931-7309

Electronic Shopper
Joe Shere
National Representative
P.O. Box 169
Idyllwild, CA 92549-0169
1-909-659-9743
Fax 1-909-659-2469

Megan Mitchell
National Representative
1201 N. Rainbow Blvd., #50
Las Vegas, NV 89108
1-702-259-7043
Fax 1-702-259-7043

Customer Service
1-800-999-7139
7:00 AM - 6:00 PM M-F MST

Overpowered.

UP TO 2 GS/s SAMPLE RATE
The highest sample rates you can find in this class.

THE TEKTRONIX NAMEPLATE
From the world leader in oscilloscope technology, all the service and support you'd expect.

FAST FOURIER TRANSFORM (FFT)
Analyze waveforms faster. What others charge $500 or more for is built right in.

FLOPPY DISK DRIVE
Transfer data directly to your PC for documentation and analysis. A Tektronix exclusive at this price.

DIGITAL REAL TIME
Single-shot capture up to 400 MHz on each channel. The power to see reality, not some approximation of it.

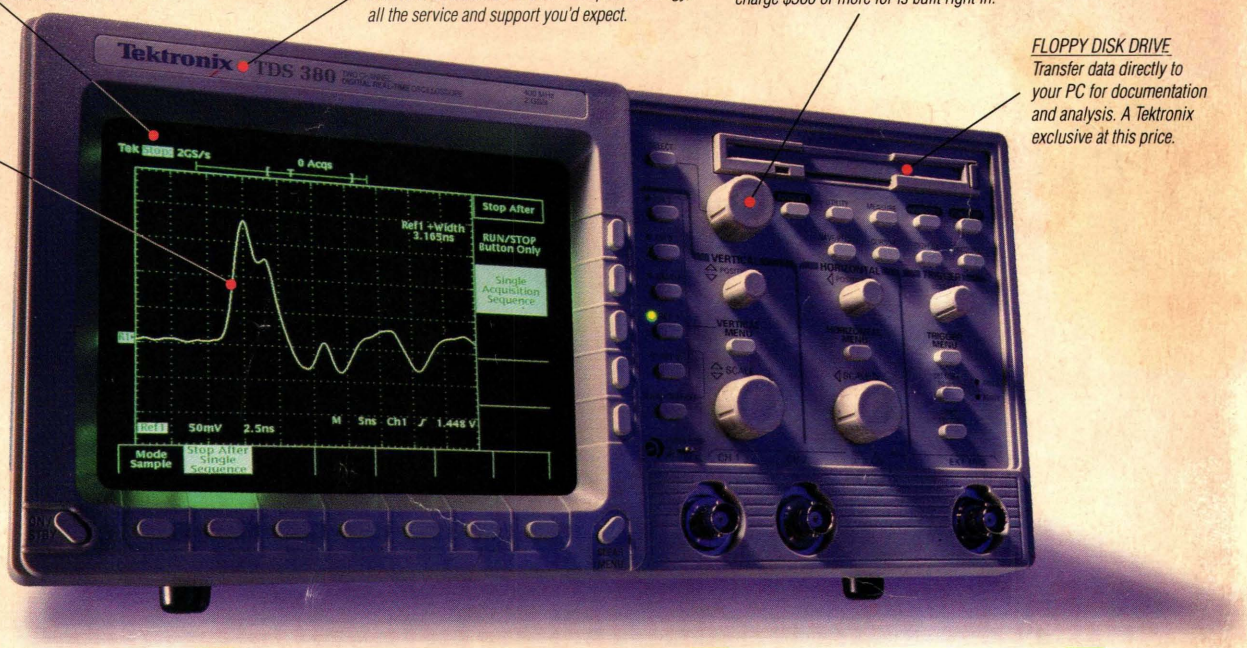

Underpriced.

With the breakthrough new TDS 300 Series, Tektronix redefines the price-performance benchmark in oscilloscopes. Numbers tell the story: A sample rate of up to 2 GS/s and a bandwidth of up to 400 MHz take you to the highest level of performance, Digital Real Time (DRT).

DRT is an exclusive oversampling technology that lets these scopes beat the real-world challenge of displaying infrequent, single-shot events.

You'll see things the other scopes can't even capture. The new TDS 300 Series also offers FFT and Disk Drives – features others charge hundreds of dollars more for, or don't even have.

Starting at $2,695

The biggest breakthrough, though, is in the number on the price tag. The TDS 300 Series starts at $2,695.* For this price, you get a level of performance you'd expect only in scopes twice as expensive. Contact your Tektronix Authorized Distributor for details, or call 1-800-479-4490, Action Code 471. Or find us on the World Wide Web at http//www.tek.com/mbd/w471. And prepare to be overwhelmed.

TDS 340, $2,695
100 MHz, 500 MS/s, DRT, FFT

TDS 360, $3,595
200 MHz, 1 GS/s, DRT, FFT, Disk Drive

TDS 380, $4,595
400 MHz, 2 GS/s, DRT, FFT, Disk Drive

Tektronix

ISO 9001 SEMA CERT. NR. 10001.01

*Manufacturer's suggested retail prices shown. ©1995 Tektronix, Inc. All rights reserved. Tektronix is a registered trademark of Tektronix, Inc. http://www.tek.com 40A-MU6220-1

CIRCLE 92 ON FREE INFORMATION CARD

Better Designs –Faster

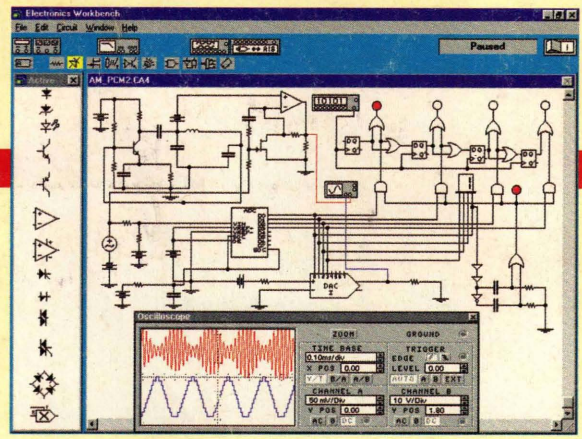

Guaranteed with Electronics Workbench!

Just click and drag to create and edit schematics. Mix analog and digital devices in any combination with full control over values, models and behavior. Try 'what if' scenarios and fine tune effortlessly. And on-screen waveforms always match actual circuit response. You'll create better designs faster—*Guaranteed!*

Guaranteed Satisfaction

Join over 70,000 customers and experience the power, flexibility and value that only Electronics Workbench offers. Receive unequaled service and free, unlimited technical support by phone, fax, e-mail, WWW, CompuServe and BBS. You'll be delighted. *We guarantee it.**

True Mixed-Mode Power

Connect any analog or digital device to any other device without limit. Only Electronics Workbench offers this professional power for under $2,000.

Real-World Digital

Real-world TTL and CMOS, complete with propagation delays and fanout. Unique at this price.

32-Bit Speed

Integrated SPICE analog and native-mode digital simulation in full 32-bit. Unique at this price.

Real-World Results

Unlimited supply of over 200 components and ICs and 350 real-world models—all perform as real devices.

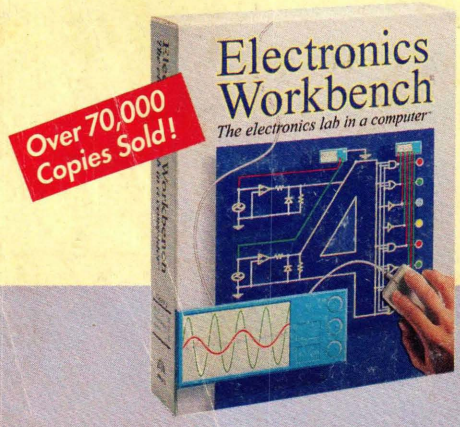

Electronics Workbench®

$299

***30-DAY MONEY-BACK GUARANTEE**

VERSION 4.1 FOR WINDOWS 95/NT/3.1, DOS AND MACINTOSH.

Ask about our Engineer's Pack with thousands of additional models and more. Version 4.0 users call for your free upgrade.

800-263-5552

INTERACTIVE

Fax: 416-977-1818 Internet: http://www.interactiv.com

CompuServe: 71333,3435/BBS: 416-977-3540/E-mail:ewb@interactiv.com

INTERACTIVE IMAGE TECHNOLOGIES LTD., 908 Niagara Falls Boulevard, #068, North Tonawanda, New York 14120-2060/Telephone 416-977-5550

TRADEMARKS ARE PROPERTY OF THEIR RESPECTIVE HOLDERS. OFFER IS IN U.S. DOLLARS AND VALID ONLY IN THE UNITED STATES AND CANADA. ALL ORDERS SUBJECT TO $15 SHIPPING AND HANDLING CHARGE

Australia: 2-519-3933 • Belgium: 2-384-73-09 • Brazil: 11-453-5588 • Canada: 416-977-5550 • Chile: 2-236-0300 • Cyprus: 9-641-801 • Czech Republic: 4-823-454 • Denmark: 33-25-0109 • Finland: 0-297-5033 France: 1-49-08-90-00 • Germany: 711-62-7740 • Greece: 1-524-9981 • Hungary: 1-215-0082 • India: 11-578-7055 • Indonesia: 21-470-0815 • Israel: 3-647-5613 • Italy: 11-437-5549 • Japan: 3-5395-2126 Malaysia: 3-774-2189 • Mexico: 5-593-5260 • Netherlands: 10-450-4949 • New Zealand: 9-267-1756 • Norway: 22-16-70-45 • Philippines: 973-27-0118 • Portugal: 1-814-6609 • Singapore: 777-2303 • Slovenia: 61-317-830 South Africa: 331-6-8309 • South Korea: 2-3452-9757 • Spain: 1-383-8335 • Sweden: 8-740-5500 • Taiwan: 2-366-0080 • Thailand: 2-398-6952 • UAE: 4-453505 • UK: 203-23-3216 • USA: 416-977-5550

CIRCLE 126 ON FREE INFORMATION CARD